

Prof. R. Chedid  
K. Kabalan  
F. Karamah  
I. El-Hajj

FACULTY OF ENGINEERING  
& ARCHITECTURE  
DEPARTMENT OF ELECTRICAL  
& COMPUTER ENGINEERING

FALL TERM 2007-08

## QUIZ #2

Name:.....  
ID:.....  
Professor:.....

Dec. 17, 2007

\*\*\*\*\*TEST ID UNKNOWN\*\*\*\*\*

(EECE 210) ELECTRIC CIRCUITS

CLOSED BOOK (1 ½ HRS)

1. Programmable Calculators are not allowed
2. Provide your answers on the computer's card only
3. Return the computer's card attached to the question sheet
4. Mark with a pencil your last name.
5. Mark your AUB ID NO.
6. The test ID No. is your exam version. Mark it in the box titled ' Test ID''.
7. Use pencil for marking your answers
8. When using eraser, be sure that you have erased well

Problems 1 and 2 below refer to the circuit shown in the figure below.

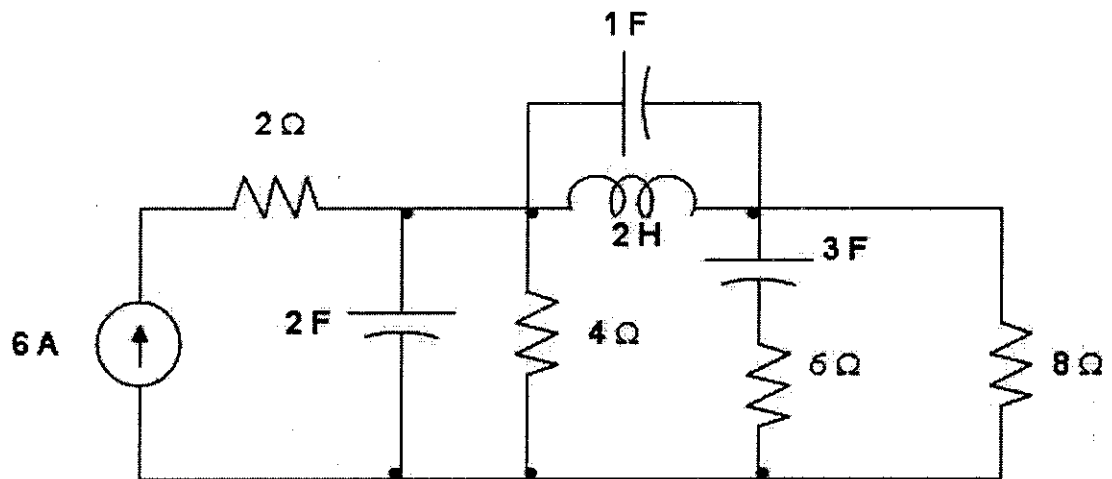


Figure Pb 1

**Problem 1**

The total energy stored in the inductor is

- (a) 16 J
- (b) 8 J
- (c) 4 J
- (d) 36 J
- (e) None of the above

**Problem 2**

The total energy stored in **all** the capacitors ( $C= 1$  Farad, 2 F and 3 F) is

- (a) 680 J
- (b) 384 J
- (c) 642 J
- (d) 640J
- (e) None of the above

Problems 3, 4 and 5 below refer to the circuit shown in the figure below. The switch was at position (a) for a long time. At time  $t=0$ , the switch is moved to position (b).

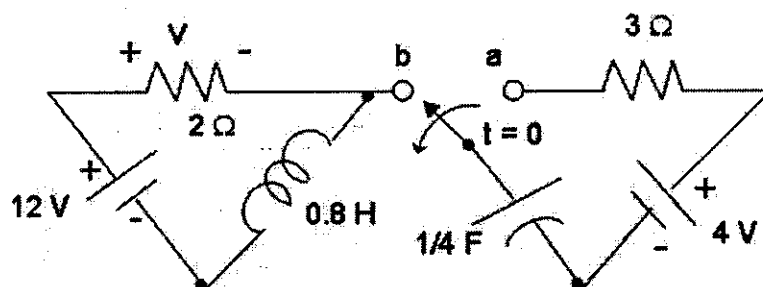


Figure Pb 2

**Problem 3**

The initial conditions, after the switch moves from *a* to *b*, on the capacitor, inductor and the voltage across the  $2\ \Omega$  resistor are:

- (a)  $i_L(0+) = 6\ \text{A}$ ;  $V_C(0+) = 4\ \text{V}$ ;  $V(0+) = 4\ \text{V}$
- (b)  $i_L(0+) = 6\ \text{A}$ ;  $V_C(0+) = 4\ \text{V}$ ;  $V(0+) = 8\ \text{V}$
- (c)  $i_L(0+) = 12/5\ \text{A}$ ;  $V_C(0+) = 4\ \text{V}$ ;  $V(0+) = 8\ \text{V}$
- (d)  $i_L(0+) = 6\ \text{A}$ ;  $V_C(0+) = 4\ \text{V}$ ;  $V(0+) = 0\ \text{V}$
- (e) None of the above

**Problem 4**

The differential equation governing the voltage across the  $2\ \Omega$  resistor is :

- (a)  $\frac{d^2V}{dt^2} + 8\frac{dV}{dt} + 5V = 60$
- (b)  $\frac{d^2V}{dt^2} + 2\frac{dV}{dt} + 5V = 60$
- (c)  $\frac{d^2V}{dt^2} + 2\frac{dV}{dt} + 5V = 12$
- (d)  $\frac{d^2V}{dt^2} + 3\frac{dV}{dt} + 5V = 60$
- (e) None of the above


**Problem 5**

The voltage across the  $2\ \Omega$  resistor after the switch moved from a to b is :

- (a)  $v(t) = 12 - 4e^{-t} \quad t \geq 0$
- (b)  $v(t) = 12 - 4e^{-t} \cos(2t) + e^{-t} \sin(2t) \quad t \geq 0$
- (c)  $v(t) = 12 - 4e^{-t} \cos(2t) + 2e^{-t} \sin(2t) \quad t \geq 0$
- (d)  $v(t) = 4e^{-t} \cos(2t) + 2e^{-t} \sin(2t) \quad t \geq 0$
- (e) none of the above.

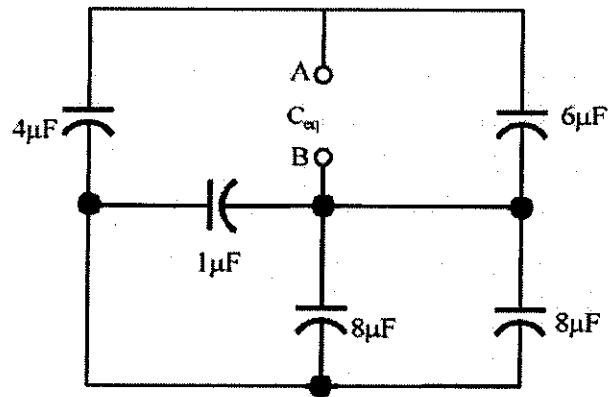**Problem 6**


Find  $C_{eq}$  the equivalent capacitance at terminals A-B.



- A)  $10.941\ \mu\text{F}$
- B)  $9.238\ \mu\text{F}$
- C)  $3.600\ \mu\text{F}$
- D)  $2.667\ \mu\text{F}$
- E) none of the above.

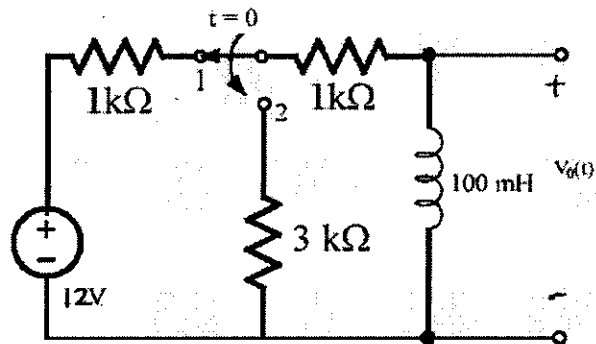**Problem 7**


The switch has been in position 1 for a long time before it moves to position 2 at  $t=0$ . Find  $V_o(t)$  for  $t > 0$



- A)  $-6 e^{-10000t}$  V
- B)  $18 e^{-40000t}$  V
- C)  $-24 e^{-40000t}$  V
- D)  $-24 e^{-10000t}$  V
- E) none of the above.

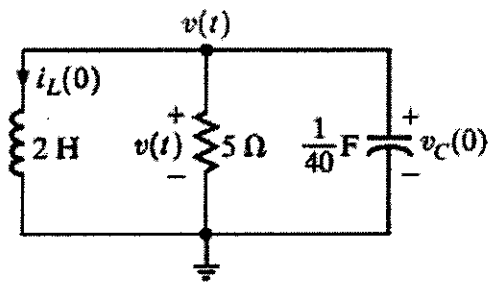
**Problem 8**

Determine the voltage  $v(t)$  if the initial conditions on the storage elements are  $i_L(0)=1A$  and  $V_c(0)=10V$ .



- A)  $e^{-4t}(10\cos 2t - 40\sin 2t)$  V
- B)  $e^{-4t}(10\cos 2t + 80\sin 2t)$  V
- C)  $e^{-4t}(-40\cos 2t + 10\sin 2t)$  V
- D)  $-80te^{-4t} + 10e^{-4t}$  V
- E) none of the above.

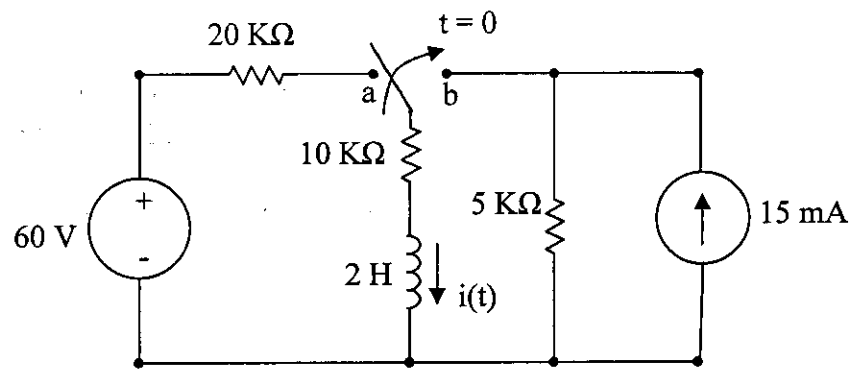Problems 9 to 12 depend on the circuit shown below



After being in the "a" position for a "long time", the switch in the circuit is moved to position b at  $t = 0$ .

**Problem 9**

Determine the initial condition for the current  $i(t)$ ;  $i(0^+)$

- a. 2 mA
- b. 3 mA
- c. 6 mA
- d. 0 mA
- e. None of the above

**Problem 10**

Determine the final value for the current  $i(t)$ .

- a. 15 mA
- b. 10 mA
- c. 5 mA
- d. 1.5 mA
- e. None of the above


**Problem 11**

Determine the Differential Equation for the current  $i(t)$  for  $t \geq 0$ .

- a.  $\frac{di(t)}{dt} + 15000i(t) = 75$
- b.  $\frac{di(t)}{dt} + 7500i(t) = 0$
- c.  $\frac{di(t)}{dt} + 15000i(t) = 0$
- d.  $\frac{di(t)}{dt} + 7500i(t) = 37.5$
- e. None of the above

**Problem 12**Solve for  $i(t)$  for  $t \geq 0$ .


- a.  $i(t) = -3e^{-7500t}$  mA
- b.  $i(t) = 2e^{-7500t}$  mA
- c.  $i(t) = (-3e^{-7500t} + 5)$  mA
- d.  $i(t) = (2e^{-7500t} + 3)$  mA
- e. None of the above

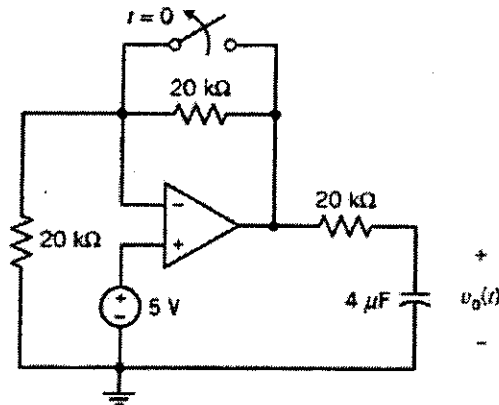**Problem 13**The switch in the circuit shown below opens at  $t=0$ . Determine  $v_0(t)$  for  $t > 0$ .

- a.  $v_0(t) = 5e^{-4000t}$  Volts
- b.  $v_0(t) = 5e^{-4000t} + 12$  Volts
- c.  $v_0(t) = 5e^{-2000t} + 12$  Volts
- d.  $v_0(t) = 5e^{-1000t} + 12$  Volts
- e. None of the above

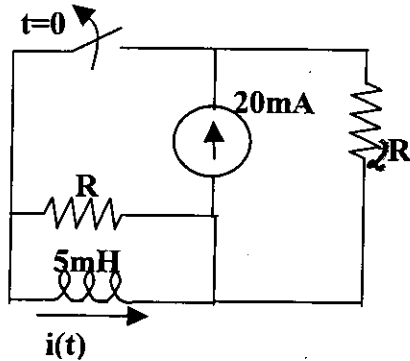**Problem 14**


Considering the circuit below, the switch was closed for a long time before it opens at  $t=0$ , find the current  $i(t)$  flowing through the inductance for  $t>0$ . ( $R=100\Omega$ ).



- a)  $10 \exp(-40000t)$  mA,  $t > 0$
- b)  $20 \exp(-40000t)$  mA,  $t > 0$
- c)  $10 \exp(-20000t)$  mA,  $t > 0$
- d)  $20 \exp(-20000t)$  mA,  $t > 0$
- e) None of the above

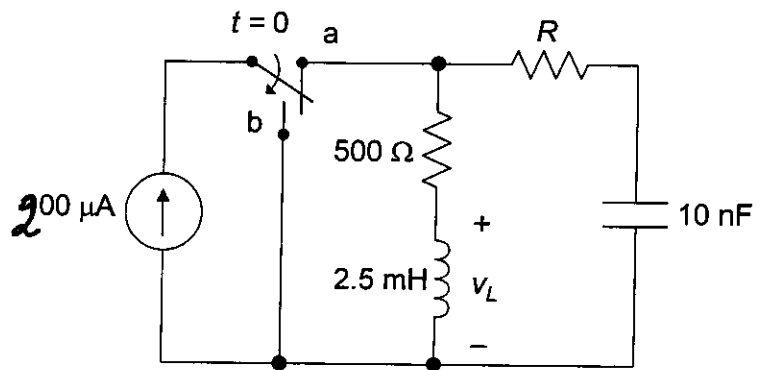**Problem 15.**

The switch in the figure is moved to position 'b' at  $t = 0$ , after being in position 'a' for a long time. Choose  $R$  so that the response is critically damped and determine the initial value of  $v_L$ .




- A. 50 mV
- B. -50 mV
- C. -100 mV
- D. -150 mV
- E. None on the above



# EECE 210 - Q.2

solution

#1.

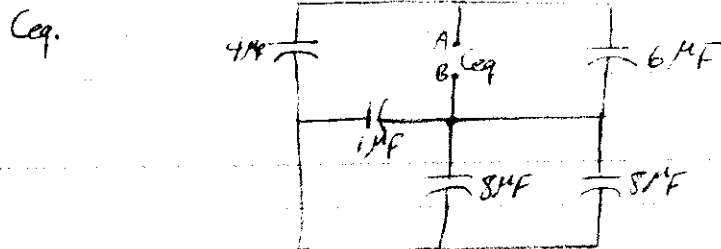

$$8\mu F \parallel 8\mu F = 16\mu F$$

$$16\mu F \parallel 1\mu F = 17\mu F$$


$$17\mu F \text{ series } 4\mu F = \frac{4 \times 17}{4 + 17} = 3.23809\mu F \parallel 6\mu F$$

$$\Rightarrow C_{eq} = 9.23809\mu F$$

- A) 9.238  $\mu F$
- B) 2.667  $\mu F$
- C) 3.600  $\mu F$
- D) 10.941  $\mu F$

#9

Volt) for  $t > 0$

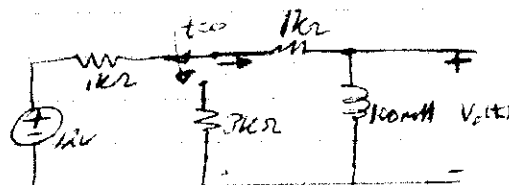

RL circuit:

$$V_L(t) = V_f + (V(0) - V_f) e^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}} = \frac{100\text{m}}{4\text{K}} = 25 \times 10^{-6} \text{ sec}$$

$$i(0) = i(0) = 6\text{mA} \Rightarrow V(0) = 6\text{mA} \times (\text{Voltage across } 1\text{k}\Omega \text{ \& } 3\text{k}\Omega)$$

$$= 24\text{V} e^{-4 \times 10^4 t}$$


$$V_f = 0 \Rightarrow V_L(t) = -24 e^{-4 \times 10^4 t}$$

- B)  $-24 e^{-10^4 t}$
- C)  $18 e^{-4 \times 10^4 t}$
- D)  $-6 e^{-10^4 t}$

✓

#15  $v(t)$  if  $i_L(0) = 1A$ ,  $v_C(0) = 10V$

RLC in parallel natural response

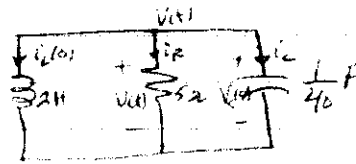

$$\omega_0 = \frac{1}{\sqrt{LC}} = 4.4721$$

$$\alpha = \frac{1}{2RC} = 4$$

$\omega_0^2 > \alpha^2 \Rightarrow$  underdamped

$$t=0 \quad L+R+i_C = 0$$

$$1 + \frac{v_C(0)}{R} + i_C = 0$$

$$i_C = -3$$

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 2$$

$$v(0) = B_1 = 10$$

$$\frac{dv(t)}{dt} = -\alpha B_1 + \omega_d B_2 = \frac{i_C(0^+)}{C} = \frac{-3}{40} = -120$$

$$-40 + 2B_2 = -120$$

$$B_2 = -40$$

$$v(t) = e^{-4t} (10 \cos 2t - 40 \sin 2t)$$

$$v(t) = e^{-4t} (10 \cos 2t + 80 \sin 2t)$$

$$v'(t) = -80t e^{-4t} + 10e^{-4t}$$

$$v'(t) = e^{-4t} (-40 \cos 2t + 16 \sin 2t)$$

Error:  $v_0 = D_2 = 10$


$$\frac{dv(0)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2$$

$$-120 = D_1 - 40$$

$$\Rightarrow D_1 = -80$$

2705

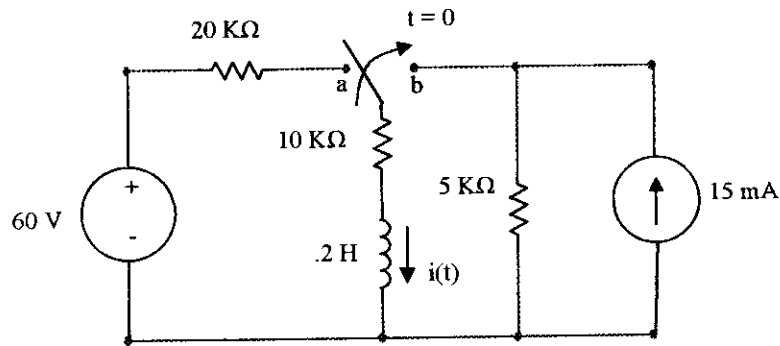Problems 1 to 3 depend on the circuit shown below



After being in the "a" position for a "long time", the switch in the circuit is moved to position b at  $t = 0$ .

**Problem # 2**

Determine the initial condition for the current  $i(t)$ ;  $i(0^+)$

- a. 2 mA
- b. 3 mA
- c. 6 mA
- d. 0 mA
- e. None of the above

Solution: When the switch is at position a for a long period of time, the inductor is a short circuit. The current is  $60/30000 = 2$  mA. As the current is continuous at all time  $t$ , then  $i(0^+) = i(0^-) = 2$  mA

**Problem # 3**

Determine the final value for the current  $i(t)$ .

- a. 5 mA
- b. 10 mA
- c. 15 mA
- d. 1.5 mA
- e. None of the above

Solution: When the switch is at position b for a long period of time, the inductor again acts as a short circuit. Using current divider rule, we obtain  $I(t) = 15 * 5 / 15 = 5$  mA

31

**Problem 4**

Determine the DE for the current  $i(t)$  for  $t \geq 0$ .

a.  $\frac{di(t)}{dt} + 7500i(t) = 37.5$

b.  $\frac{di(t)}{dt} + 15000i(t) = 75$

c.  $\frac{di(t)}{dt} + 7500i(t) = 0$

d.  $\frac{di(t)}{dt} + 15000i(t) = 0$

e. None of the above

Solution: Using source conversion, we obtain a voltage source of 75 Volts in series with a resistor of 15 K $\Omega$  and an inductor of 2H. Using KVL, we obtain

$$15 \cdot 10^3 i(t) + 2 \frac{di(t)}{dt} = 75 \quad \text{or} \quad \frac{di(t)}{dt} + 7500i(t) = 37.5$$

**Problem 5**

Solve for  $i(t)$  for  $t \geq 0$ .

a.  $i(t) = (-3e^{-7500t} + 5)\text{mA}$

b.  $i(t) = -3e^{-7500t}\text{mA}$

c.  $i(t) = 2e^{-7500t}\text{mA}$

d.  $i(t) = (2e^{-7500t} + 3)\text{mA}$

e. None of the above

Solution:  $i(t) = Ae^{-7500t} + B$


Using the initial and final conditions, we obtain:  $A+B=2$  and  $B=5$ .

Therefore,  $A=-3$ . The solution is:

$$i(t) = (-3e^{-7500t} + 5)\text{mA}$$
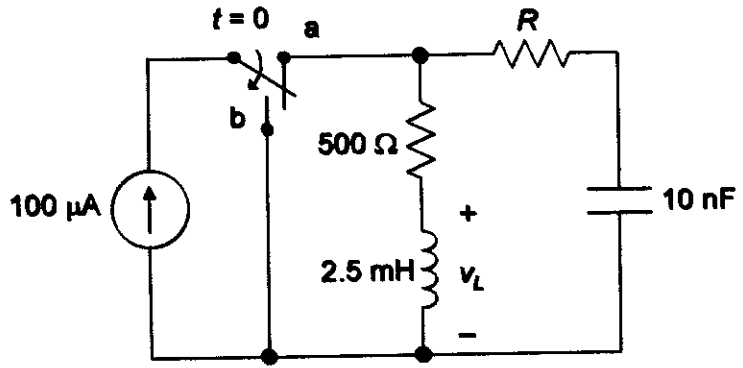
# 11.

The switch in the figure is moved to position 'b' at  $t = 0$ , after being in position 'a' for a long time. Choose  $R$  so that the response is critically damped and determine the initial value of  $v_L$ .




- A. 50 mV
- B. -50 mV
- C. -100 mV
- D. -150 mV
- E. None on the above

**Solution:** For critical damping,  $\frac{R_s}{2L} = \omega_0 = \frac{1}{\sqrt{10^{-8} \times 2.5 \times 10^{-3}}} = 2 \times 10^5 \text{ rad/s}$ , where  $R_s =$

$R + 500 \Omega$ ;  $R_s = 2 \times 2.5 \times 10^{-3} \times 2 \times 10^5 = 1000 \Omega$ . Hence,  $R = 500 \Omega$ . When the switch is in position a,  $i_L$  is  $100 \mu\text{A}$  and  $v_C$  is  $(100 \mu\text{A}) \times (500 \Omega) = 50 \text{ mV}$ . When the switch is moved to position b,  $i_L$  and  $v_C$  at  $t = 0^+$  remain the same. From KVL:  $50 = 0.1 \times 1000 + v_L$ , so that  $v_L = -50 \text{ mV}$ .

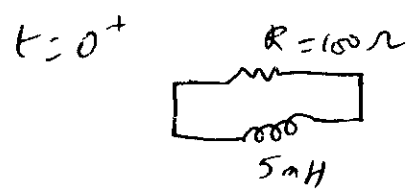
# 6.

$t = 0^-; i_L(0^-) = i_L(0^+) = 20 \text{ mA}$




$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{100}$$
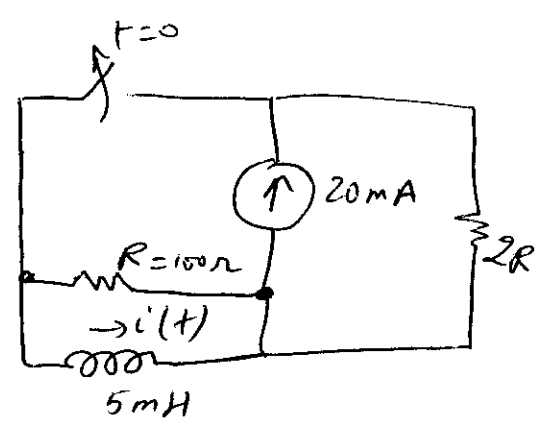
$$i(t) = I_0 e^{-\frac{t}{\tau}} = 20 e^{-\frac{100 \times 10^3}{5} t} \text{ mA} = 20 e^{-20000t} \text{ mA}, t > 0.$$




5)

**Problem 7**

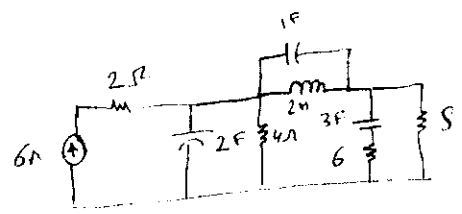

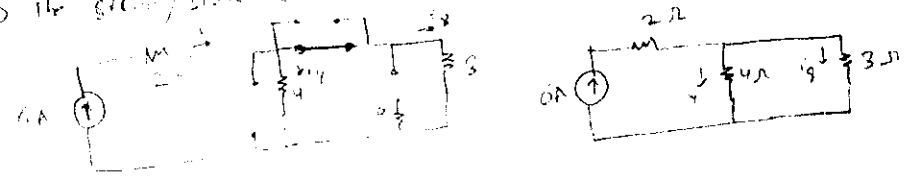Under steady state conditions, capacitor will act as an open circuit and inductor will act as a short circuit.  
 ⇒ If steady state circuit will look like.



The current through inductor is  $i_L$

$$\Rightarrow i_L = \frac{4}{4+3} \cdot 6 = \frac{24}{7} = 2 \text{ A}$$

∴ Energy stored in inductor ( $2 \text{ H}$ ) is  $W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2) (2)^2 = 4 \text{ J}$

**Problem 8**

The 1F capacitor is charged by the 6A current source.

$$Q_{1F} = 6 \Rightarrow W_{C,1F} = 0 \text{ J}$$

The 3F capacitor has the voltage as the 3Ω resistor.

$$V_{C,3F} = 16 \text{ Volts}$$

$$W_{C,3F} = \frac{1}{2} C V_{C,3F}^2 = \frac{1}{2} (3) (16)^2 = 384 \text{ J}$$

The 2F capacitor has the voltage as 6V DC source.


$$V_{C,2F} = 6 \text{ Volts}$$

$$W_{C,2F} = \frac{1}{2} C V_{C,2F}^2 = \frac{1}{2} (2) (6)^2 = 36 \text{ J}$$

$$\therefore W_C = W_{C,1F} + W_{C,2F} + W_{C,3F} = 36 + 384 = 420 \text{ J}$$

Answer is (D)

Problem 12

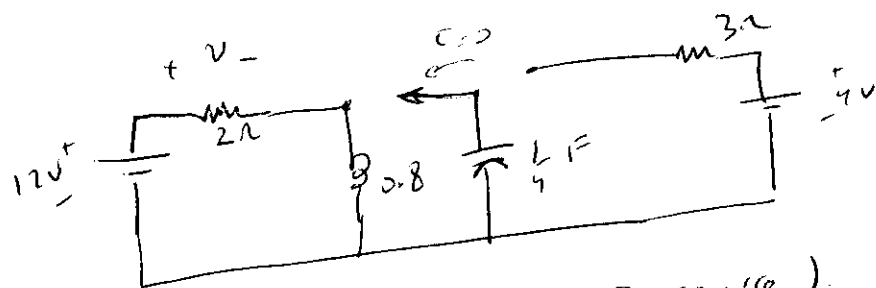


for  $t < 0$ ,  $v_c = 4V$  (fully charged to source)  
 $i_c = \frac{12}{2} = 6A$  (fully charged)

for  $t \geq 0$   
 $v_c(t^+) = v_c(t^-) = 4V$   
 $i_c(t^+) = i_c(t^-) = 6A$   
 $V(t^+) = 12 - v_c(t^+) = 12 - 4 = 8V$


∴ ANSWER is

Problem 13

circuit looks like

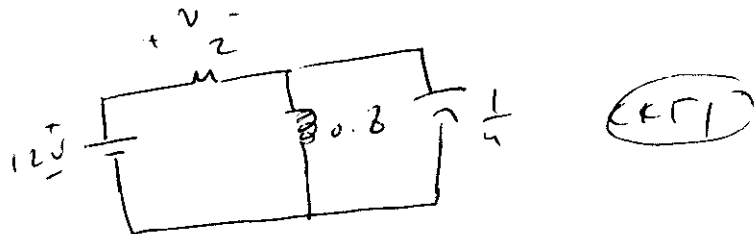

redraw to be parallel RLC

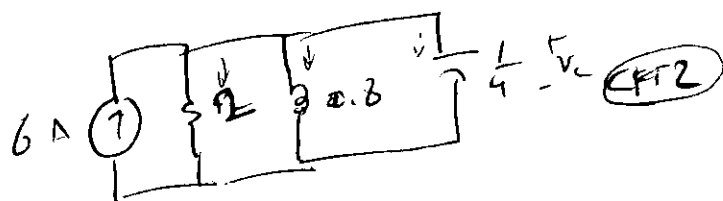

find  $v_c$  first, then  $v$  is simply  
 $v = 12 - v_c$   $t \geq 0$

in CFT2,  $v_c$  is governed by

$$\frac{d^2 v_c}{dt^2} + \frac{1}{R_c} \frac{dv_c}{dt} + \frac{1}{L_c} v_c = 0$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + \frac{1}{(2)(\frac{1}{4})} \frac{dv_c}{dt} + \frac{1}{(\frac{1}{4})(0.8)} v_c = 0$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + 2 \frac{dv_c}{dt} + 5 v_c = 0$$

replace  $v_c$  by  $12 - v$   $\Rightarrow \frac{d^2 (12 - v)}{dt^2} + 2 \frac{d(12 - v)}{dt} + 5(12 - v) = 0$

$$\ddot{v} + \frac{2dv}{dt} + 5v = 60 \Rightarrow \text{Answer is } (C)$$

### problem 14

Two ways to find  $v(t)$ : find  $v_L(t)$  then  $v(t) = 12 - v_L(t)$   
or find directly from O.P.E.

using  $v_L(t)$ :

$$v_L(0^-) = v_L(0^+) = 4V$$

$$i_L(0^-) = i_L(0^+) = 6A$$

$$\alpha = \frac{1}{2RC} = \frac{2}{2} = 1$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1/2)(0.8)}}$$

$\alpha < \omega_0 \Rightarrow$  underdamped.

$$\omega_d = \sqrt{-\alpha^2 + \omega_0^2} = \sqrt{-1 + (0.8)(1/2)} = \sqrt{4} = 2$$

$$\therefore v_L(t) = A e^{-t} \cos 2t + B e^{-t} \sin 2t \quad t \geq 0$$

$$\boxed{v_L(0) = 4 = A}$$

$$\begin{aligned} \frac{dv_L}{dt} \Big|_{t=0^+} &= \frac{1}{C} i_L(0^+) = \frac{1}{C} \left[ -i_L(0^+) - \frac{v_L(0^+)}{R} + 6 \right] \\ &= 4 \left[ -6 - \frac{4}{2} + 6 \right] = -8 \end{aligned}$$

$$\frac{dv_L}{dt} \Big|_{t=0^+} = -A + 2B = -8$$

$$= B = \frac{-8 + A}{2} = \frac{-8 + 4}{2} = -2$$

$$\therefore v_L(t) = 4e^{-t} \cos 2t - 2e^{-t} \sin 2t$$

$$v(t) = 12 - 4e^{-t} \cos 2t + 2e^{-t} \sin 2t \quad t \geq 0$$

answer is (C)