

7


Find V_x .

$V_p = V_n$

$V_p = \frac{10 \times 10k\Omega}{25k\Omega} = 4V.$



$V_n = 2k\Omega \times I$ So $2k\Omega \times I = 4V$ & $I = \frac{4}{2k\Omega} = 2mA.$

$V_x = 2mA \times 1k\Omega = 2V.$

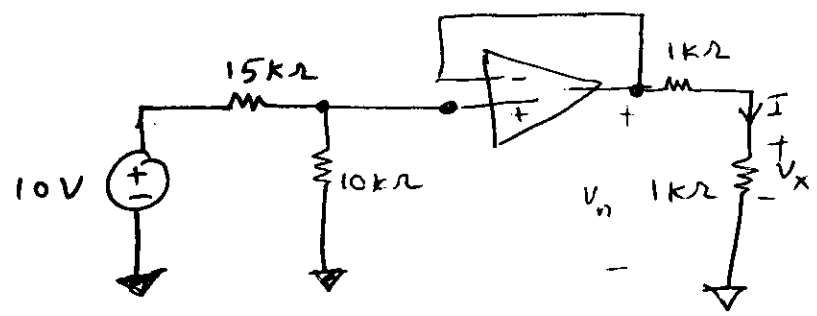


8

Find L_{eq} .

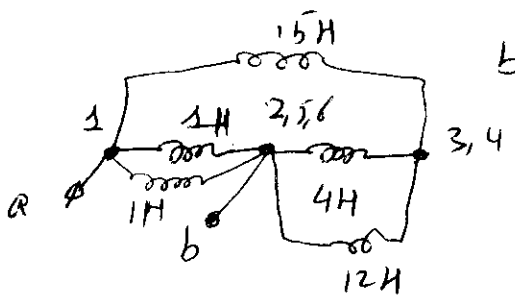
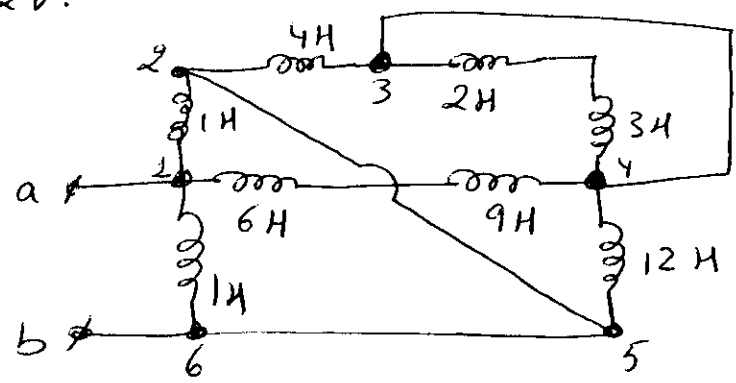


$L_{eq} = 0.486H$

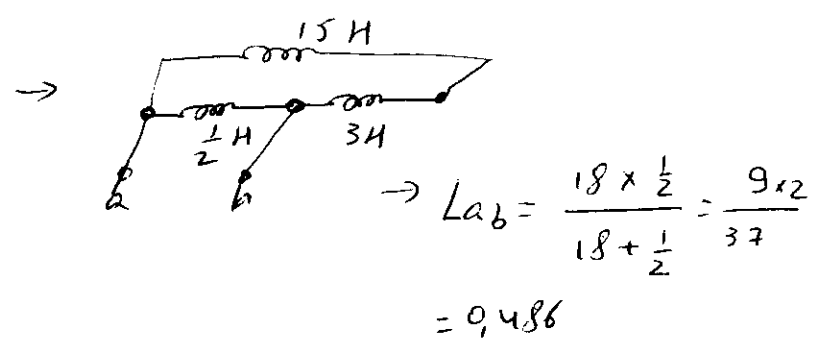


1

$C_{eq} = ?$

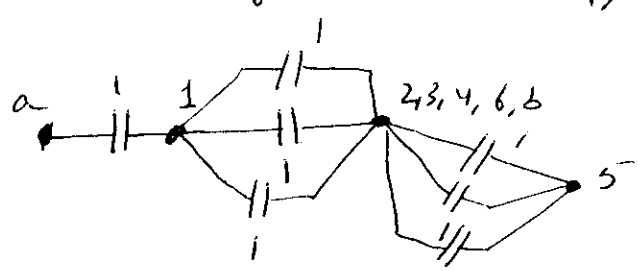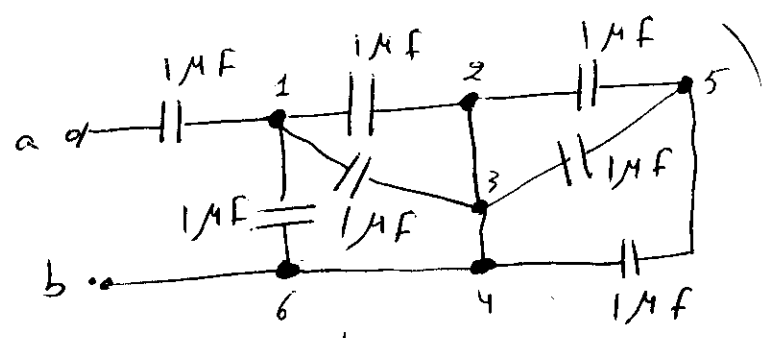

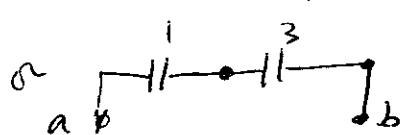$C_{eq} = \frac{1 \times 3}{4} = \frac{3}{4} \mu F.$




11-

find $i(0^+)$?

at $t=0^-$ ~~L~~ L was a S.C so

$$i(0^-) = 20 \text{ mA} = i(0^+)$$

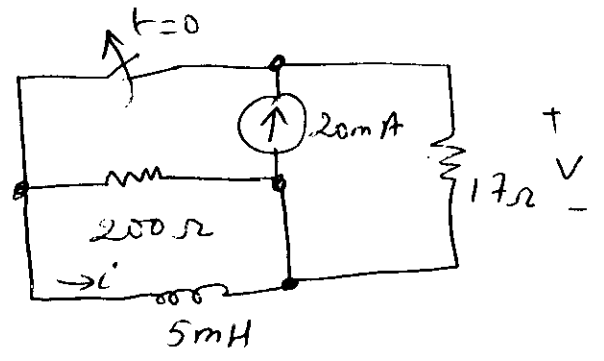

12-

find $V(0^+)$ in the above CKT.

at $t=0^+$ $i_L(0^+) = 20 \text{ mA}$ but circulates through the 200Ω .

the 20 mA current source circulates through the 17Ω .

$$\text{Hence } V(0^+) = 20 \text{ mA} \times 17 = 0.34 \text{ V.}$$

13-


find $V(0^+)$.

at $t=0^-$; C was O.C

$$V = V_{ab}$$

$$i = \frac{6 \text{ V}}{6 \text{ k}\Omega} = 1 \text{ mA.}$$
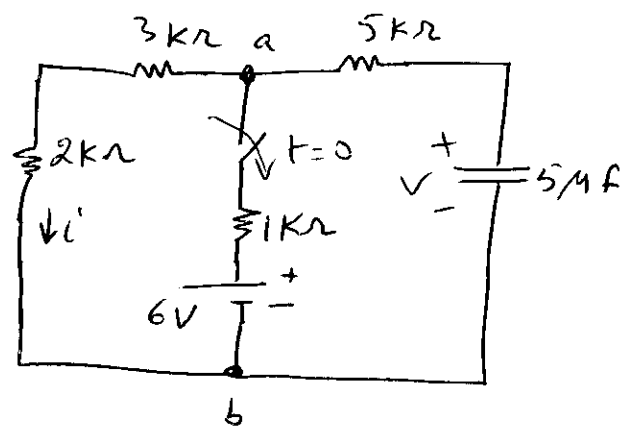
$$\& V_{ab} = 6 - 2 \text{ k}\Omega \times 1 \text{ mA} = 5 \text{ V.}$$



2-

find i_a .


$$\frac{V_n - V_a}{1 \text{ k}} + \frac{V_n - V_o}{1 \text{ k}} = 0$$

$$\text{or } 2V_n - V_a = V_o \quad (1)$$

$$\&: \frac{V_a}{5 \text{ k}} + \frac{V_a - V_n}{1 \text{ k}} + \frac{V_a - V_o}{1 \text{ k}} = 0$$

$$V_a \left[\frac{1}{5 \text{ k}} + \frac{2}{1 \text{ k}} \right] - \frac{V_n}{1 \text{ k}} = \frac{V_o}{1 \text{ k}}$$
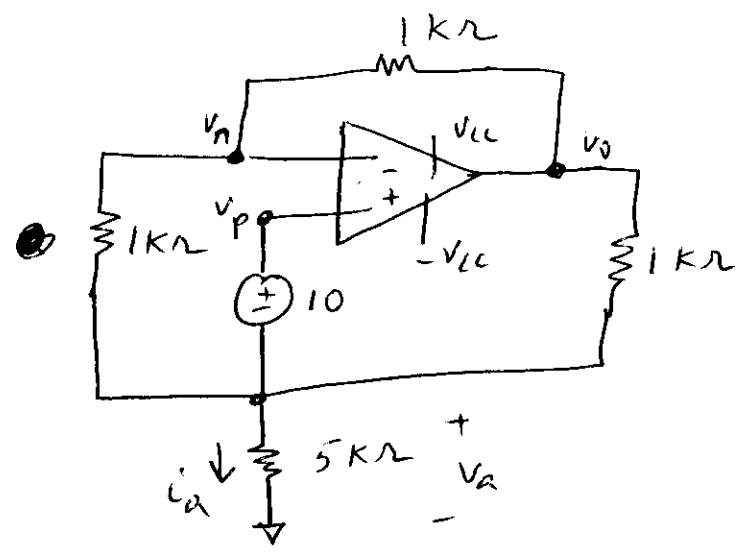
$$\text{or } \left[V_a \left(\frac{11}{5} \right) - V_n = V_o \right] (2)$$



(1) & (2) $\rightarrow 2V_n - V_A = V_A \frac{11}{5} - V_n$

$3V_n = \frac{16V_A}{5} \rightarrow V_n = \frac{16}{15} V_A$


Also: $V_n = V_p = V_A + V_g = V_A + 10$

Hence ~~30~~ $V_A + 10 = \frac{16}{15} V_A$

$\therefore \frac{V_A}{15} = 10 \rightarrow V_A = 150$


$i_A = \frac{150}{5} = 30 \text{ A}$

#3 $V_0(t)$? $t \geq 0$

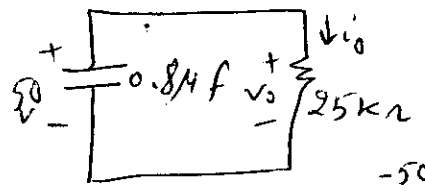

$\therefore V_0(t) = 50e^{-50t} \text{ V}, t \geq 0$

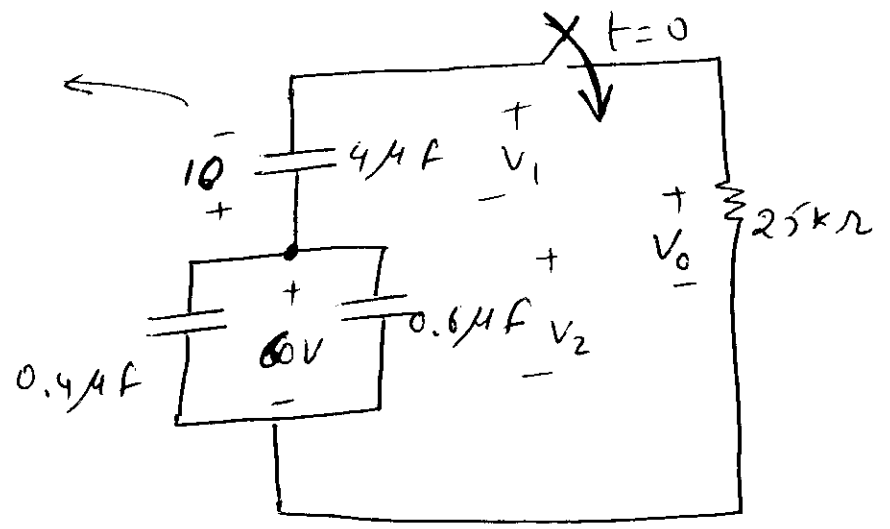$\tau = RC = 0.8 \times 10^{-6} \times 25 \times 10^3 = 50 \text{ s}$



#4 in problem 8, find $V_1(t) = ?$

$i_0 = \frac{V_0(t)}{25k} = \frac{50e^{-50t}}{25500} = 2e^{-50t} \text{ mA}$

$V_1(t) = -\frac{1}{C} \int_0^t i_0 dt - 10$


$= -\frac{1}{4 \times 10^{-6}} \int_0^t 2e^{-50t} dt - 10$

$= -\frac{1}{4 \times 10^{-6}} \times 2 \times \frac{1}{-50} e^{-50t} - 10$


$= \frac{+10^6 \times 10^{-3}}{2 \times 50} (e^{-50t}) - 10 = +10^4 \times 10^{-5} (e^{-50t} - 1) - 10$
 $= +10e^{-50t} - 20, t \geq 0$

4

9. $i_0(t) = ? \quad t \geq 0.$

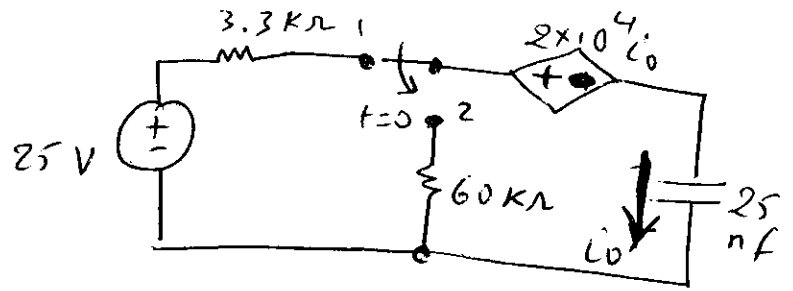


$t = 0^-$

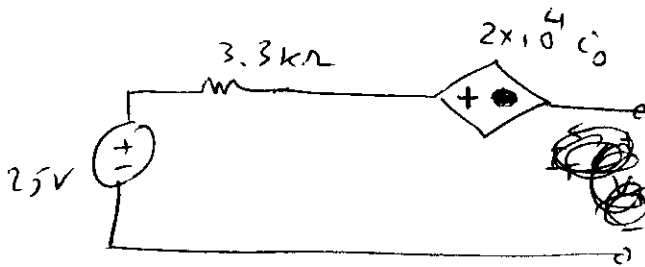

so $V_C(0^-) = 25V.$

by injection Method: $0 = V_T \cdot 2 \times 10^4 C_0 + 3.3k \cdot I_T + 25V = 0$
 after derivation $V_T = -2 \times 10^4 C_0$

at $t = 0^+$

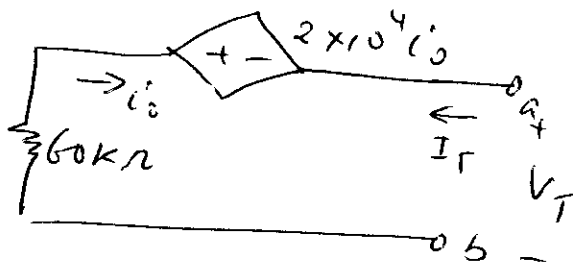


by injection Method:

$$V_T = -2 \times 10^4 C_0 + 60000 I_T$$

$$= 20000 C_0 + 60000 I_T = 80000 I_T$$

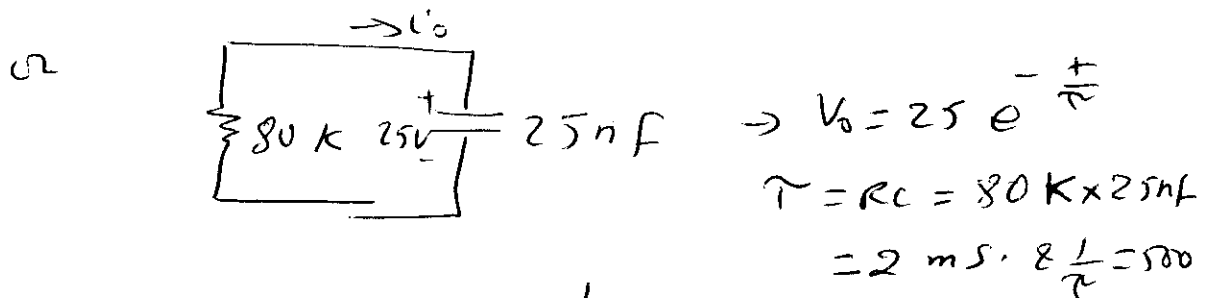so $\frac{V_T}{I_T} = R_{th} = 80000 = 80k.$



so $V_0 = 25 e^{-500t} V, \quad t \geq 0^+$

$i_0 = C \frac{dV}{dt} = 25 \times 10^{-9} \times 25 \times -500 e^{-500t}$
 $= -312.5 e^{-500t} \mu A, \quad t \geq 0^+$

10


#5 ~~dot~~ dot locations that is wrong

4 & 2 ✓

4 & 1 ✗

1 & 3 ✓

3 & 6 ✓

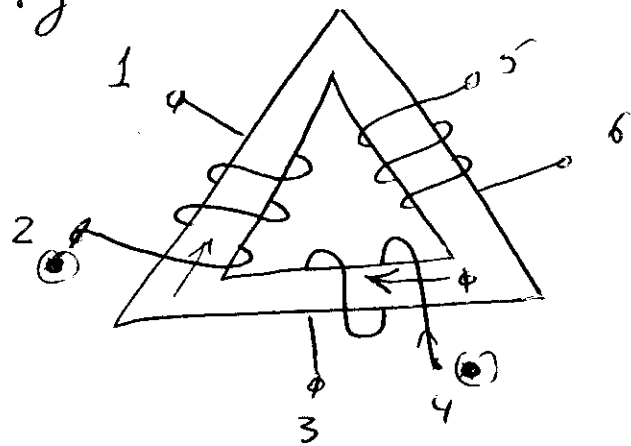

#6 ~~the~~ the current in a 2H inductor is:

$$i = 25 \text{ A} \quad \text{at } t \leq 0$$

$$i = (B_1 \cos 5t + B_2 \sin 5t) e^{-1t} \text{ A}, \quad t \geq 0$$

find ~~B_1 & B_2~~ B_1 & B_2 v across L is 100V at $t=0$

$$\text{so } v_L(0) = 100 \text{ V}$$

⊗

$$i(0^-) = i(0) = 25 = B_1 \cos 0 + 0 \rightarrow B_1 = 25$$

$$v_L = L \frac{di}{dt} = 2 (-5B_1 \sin 5t + 5B_2 \cos 5t) e^{-t} - (2B_1 \cos 5t + 2B_2 \sin 5t)$$

$$\text{at } t=0 \rightarrow v_L = 100 = 10B_2 - 2B_1$$

$$100 = 10B_2 - 50 \rightarrow$$

$$10B_2 = 150$$

$$B_2 = 15$$