

AMERICAN UNIVERSITY OF BEIRUT  
Department of Electrical and Computer Engineering  
**EECE210 Fall 2004**

**Quiz 1, November 5, 2004**

Prof Karamneh

---

**Directions:**

- You will have 1.5 hrs for this quiz.
- Write down your name *in ink* on all the pages. **DO IT NOW!**
- Answers must be explained or derived. **DO NOT** just write down an answer.
- It is a good idea to read the whole test before you begin. Some problems are divided into several parts with percentages indicated. You might be able to solve different parts independently.
- **DO NOT** talk to any of your colleagues under any circumstances. You will be penalized without warning.

---

**YOUR NAME HERE:**

---

**PROBLEM 1** (10%)

Consider the resistive network shown in figure 1. Find the voltage across the  $6\Omega$  resistor  $V_6$ .

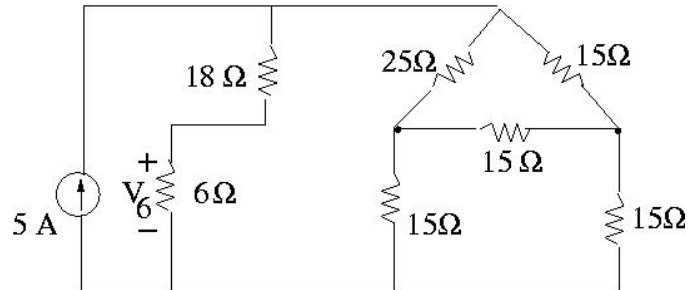


Figure 1: Problem 1

**PROBLEM 2** (20%)

Consider the network shown in figure 2,

a) If the dependent voltage source is such that

$$V_d = -2V_x,$$

find the amplification ratio  $A_v = V_2/V_1$  where  $V_2$  and  $V_1$  are as labelled.

b) If the dependent voltage source is  $V_d = aV_x$ , find the constant  $a$  such that the current  $i_o$  in the  $1/4\Omega$  resistor is zero.

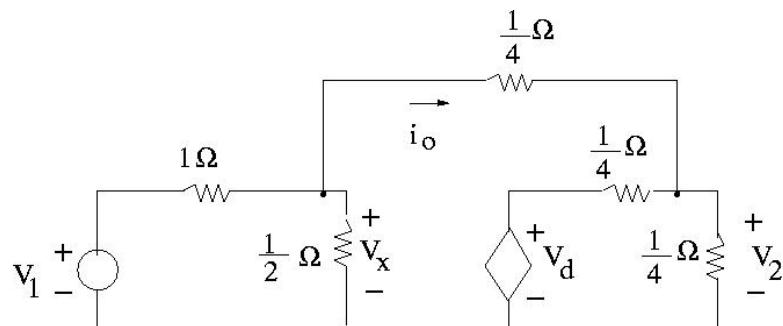


Figure 2: Problem 2

**PROBLEM 3** (20%)

Consider the resistive network shown in figure 3.

- (a) Find the voltage across the resistance termed  $R$  for any value of  $R$ .
- (b) Find the maximum power  $P_{max}$  that could be transferred to the load resistance  $R$ .

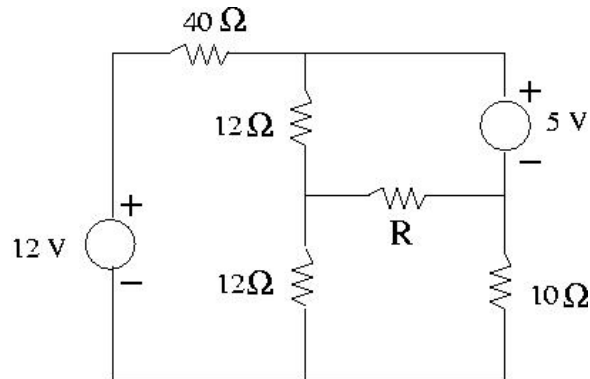


Figure 3: Problem 3

**Problem 4** (10%)

Find the power absorbed by the 10 Ohm resistor (termed with voltage  $v_{10}$ ) in the following circuit (figure 4) **using superposition**.

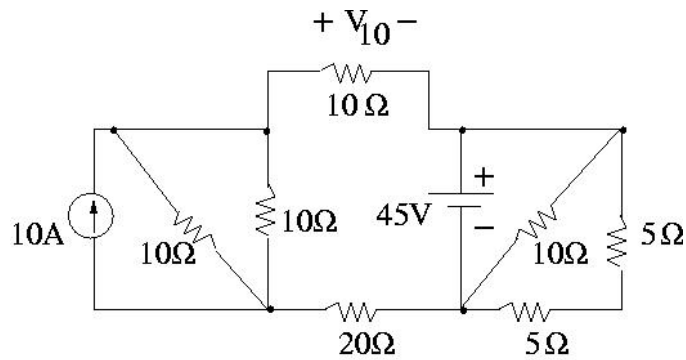


Figure 4: Problem 4

**PROBLEM 5** (20%)

Find the thevenin equivalent of the circuit shown to the *left* of a,b (inside the box).

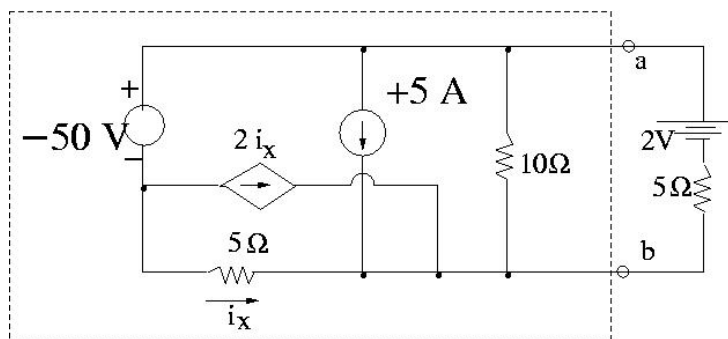


Figure 5: Problem 5

**PROBLEM 6** (10%)

Consider the circuit shown in figure 6 below.

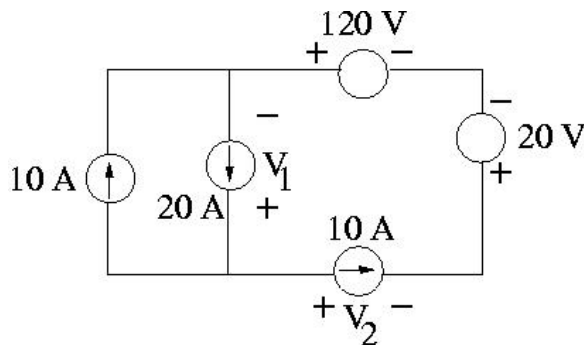


Figure 6: Problem 6

- (a) Is the interconnection valid? explain.
- (b) If you answered yes in part (a), find  $V_1$ ,  $V_2$  if the total power absorbed in this circuit is 2150 W.

**PROBLEM 7** (10%)

Consider the circuit shown in figure 7. Find the constant  $k$  such that  $v_y = 0$ .

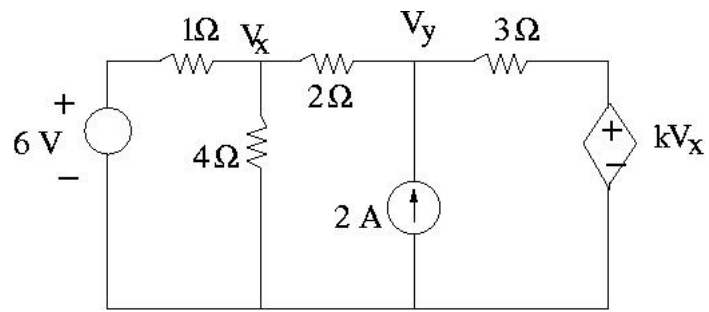


Figure 7: Problem 7