



**AMERICAN UNIVERSITY OF BEIRUT**  
**FACULTY OF ENGINEERING AND ARCH,**  
**EECE210- FALL 2005**  
**Quiz 1 Solutions**

Prof Karameh.

EECE 210 - FALL 05  
 QUIZ 1 SOLUTIONS

KARAMEH

PROBLEM 1  
 REDRAW :

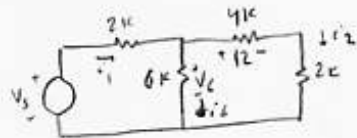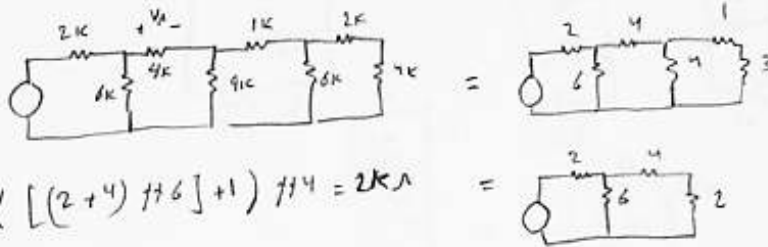


$$4i_2 = 12V \Rightarrow i_2 = 3mA \Rightarrow V_6 = 12 + 2000i_2 = 12 + 6 = 18V$$

$$\Rightarrow i_6 = \frac{18}{1k} = 3mA$$

$$\Rightarrow i_1 = i_6 + i_2 = 6mA$$

$$\Rightarrow V_s = 2000i_1 + V_6 = 2 + 6 + 18 = \underline{\underline{30V}}$$

PROBLEM 2

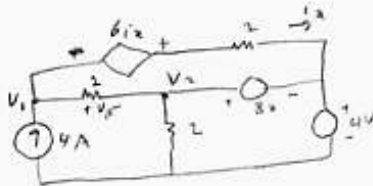

MANY WAYS TO SOLVE. TRY NODAL:

$$V_2 = 12V ; \quad \frac{V_1 - V_2}{2} + \frac{V_1 + 6i_x - 4}{2} - 4 = 0 \quad \text{--- (1)}$$

$$i_x = \frac{V_1 + 6i_x - 4}{2} \Rightarrow i_x = \frac{-V_1 + 4}{4}$$


$$\text{back into (1)} \Rightarrow \frac{V_1 - 12}{2} + 1 - \frac{V_1}{4} - 4 = 0 \Rightarrow \frac{V_1}{4} - 5 = 0 \Rightarrow V_1 = 36$$

$$\Rightarrow V_R = V_1 - V_2 = 36 - 12 = \underline{\underline{24V}}$$

1/A

### PROBLEM 3

a) Find  $V_{TH} = V_{oc} = ?$

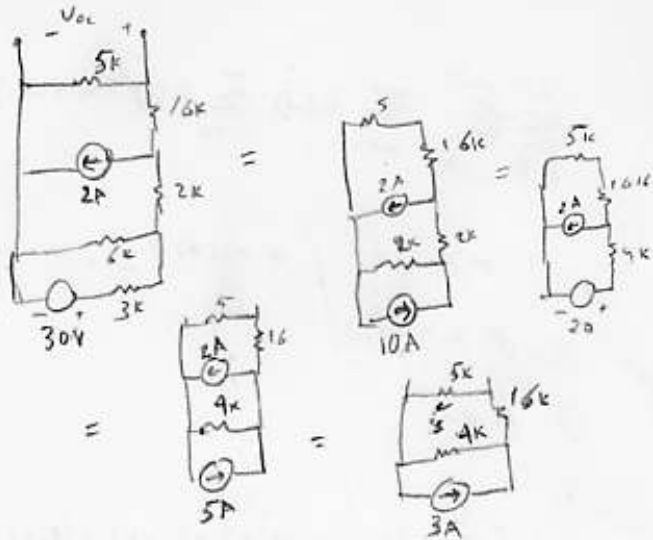

$$I_s = \frac{4+3}{4+5||6} = \frac{4+3}{25} = \frac{12}{25} A$$

$$\Rightarrow V_{oc} = \frac{12}{25} \times 5 = \frac{12}{5} = \underline{\underline{2.4 V}}$$

$$R_{th} = 5 || 20 = \frac{5 \cdot 20}{25} = 4 k\Omega$$



$$V_r = \left( \frac{2.4}{R+4000} \right) \cdot R$$




b)

$P_{max}$  when  $R = R_{th} = 4 k\Omega$


$$\Rightarrow V_r = \frac{2.4 \cdot 4}{8} = 1.2 V$$

$$d) P_{max} = \frac{(1.2)^2}{4k} = \underline{\underline{0.36 mW}}$$

PROBLEM 4

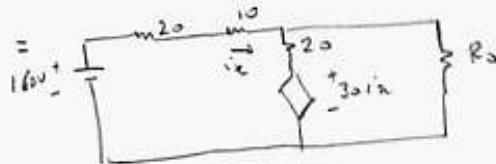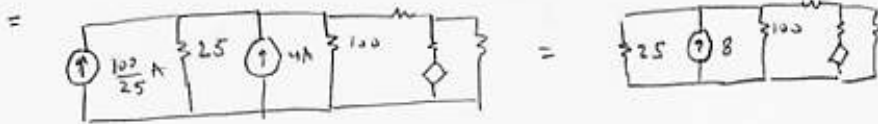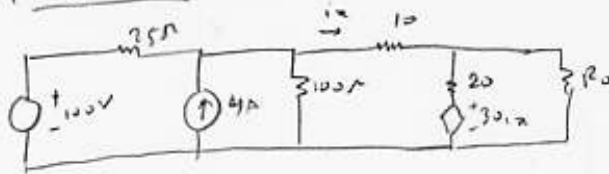

Let's find Thevenin equivalent.

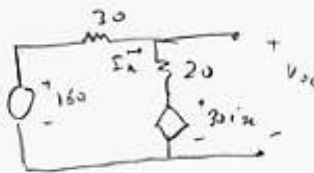


$$V_{oc} = 20 i_x + 30 i_x = 50 i_x$$

$$i_x = \frac{160 - 30 i_x}{50} \Rightarrow i_x = 2 \text{ A} \Rightarrow V_{oc} = V_{Th} = 100 \text{ V}$$

$$I_{sc} = I_1 + i_x$$

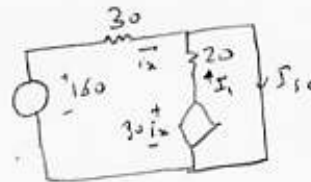
$$30 i_x = 20 I_1 \Rightarrow I_1 = \frac{3}{2} i_x$$



$$\Rightarrow I_{sc} = \frac{3}{2} i_x$$

$$i_x = \frac{160}{30} = \frac{16}{3} \text{ A} \Rightarrow I_{sc} = \frac{3}{2} i_x + i_x = \frac{5}{2} i_x = \frac{16 \cdot 5}{6} \text{ A}$$
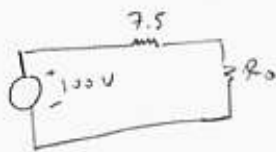
$$\therefore R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{100}{\frac{16 \cdot 5}{6}} = \frac{120}{16} = \underline{7.5 \Omega}$$






$$\text{Power in } R_o = \frac{V_{R_o}^2}{R_o} = \left( \frac{100}{R_o + 7.5} \right)^2 \cdot \frac{1}{R_o}$$

$$\Rightarrow 250 = R_o \left( \frac{100}{R_o + 7.5} \right)^2 \Rightarrow R_o^2 + 15 R_o + (7.5)^2 = 40 R_o$$

$$\Rightarrow R_o^2 - 25 R_o + (7.5)^2 = 0$$



$$\Rightarrow R_o = 2.5 \text{ or } R_o = 22.5 \Omega$$

PROBLEM 5

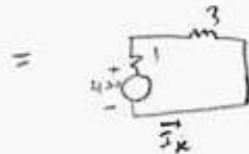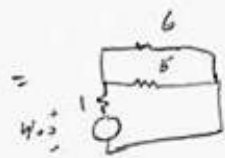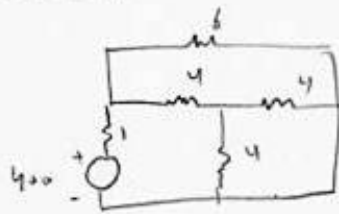


$\Rightarrow i_x = \frac{-400}{4} = -100 \text{ A}$

PROBLEM 6

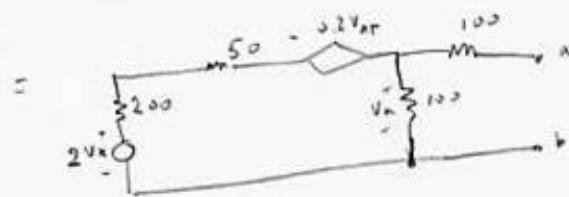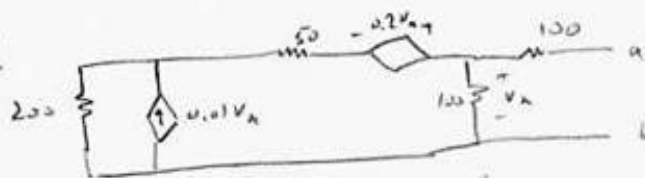

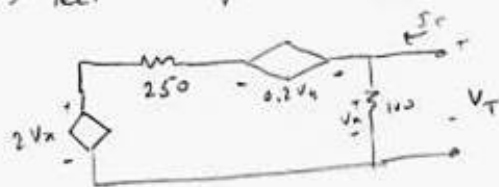Take out the 100Ω resistor a-b for the moment, add it later



find  $\frac{V_T}{I_T}$

NOTE:

$$\frac{V_T}{100} - I_T = \frac{V_T - 0.2V_T}{250} = 0 \Rightarrow 2.5V_T - 1.2V_T = 250I_T$$

$$\Rightarrow \frac{V_T}{I_T} = \frac{250}{1.3} = 192.3\Omega$$

$$\Rightarrow R_{Th} = \frac{V_T}{I_T} + 100 = \underline{\underline{292.3\Omega}}$$