

Name:.....
ID:.....
Major:.....

March 22, 2006

(EECE 210) ELECTRIC CIRCUITS & ELECTRONICS


CLOSED BOOK (1 ½ HRS)

Programmable Calculators are not allowed
Provide your answers on the computer's card only
Return the computer's card attached to the question sheet
Mark with a pencil your name and your ID-No
Use pencil for marking your answers
When using eraser, be sure that you have erased well


!!! PENALTY IS 6 TO 1 !!!

4. Determine V_o in the figure, assuming an ideal op amp.

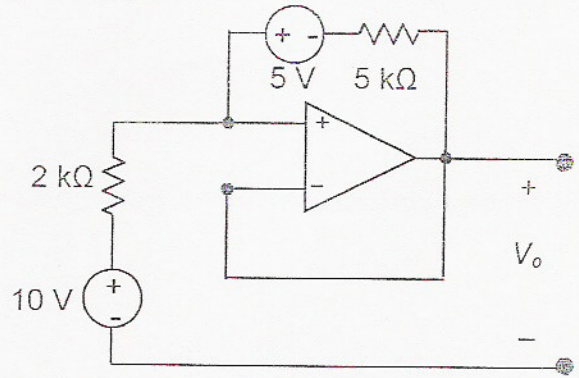- a) 15 V
- b) 5 V
- c) 6 V
- d) 8 V
- e) None of the above




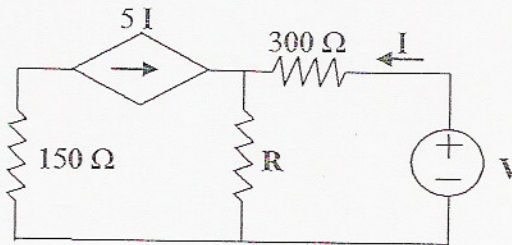5. In the circuit below R is a variable resistor. For what value of R the maximum power is transferred to it.




- a) 50Ω
- b) 100Ω
- c) 150Ω
- d) 250Ω
- e) None of the above

6. Find i in the circuit below.

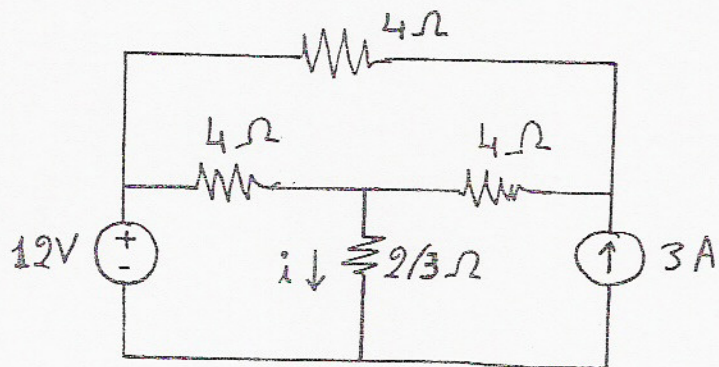


- a) 6.4 A
- b) 4.8 A
- c) 2.5 A
- d) 7.3 A
- e) None of the above

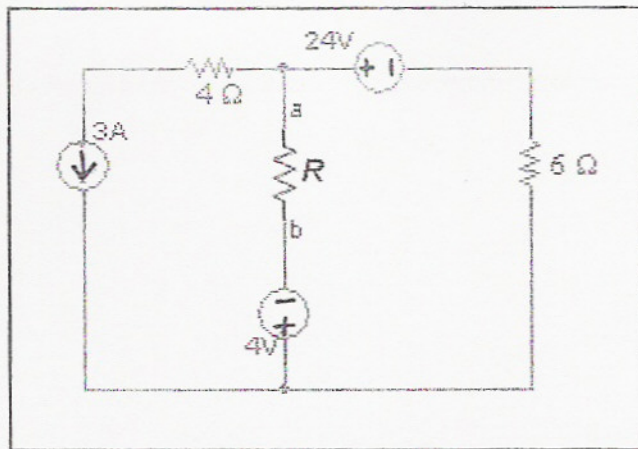7. A load resistance R in the range of $[1,8] \Omega$ is to be connected across the terminals a, b in such a way that maximum power is delivered to it. Determine the power dissipated by R .




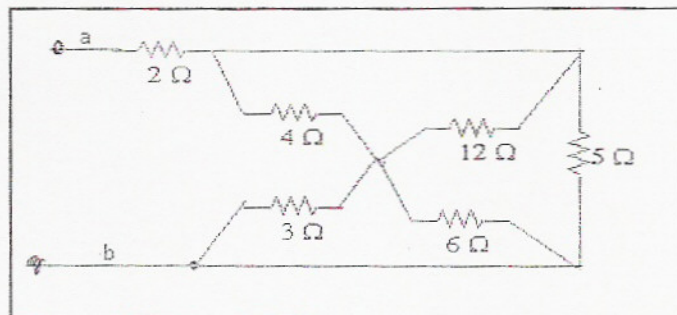- a) 10.58 W
 b) 4.17 W
 c) 5.95 W
 d) 8.26 W
 e) None of the above
8. Find the equivalent resistance between the terminals (a,b).




- a) 4.50 Ω
 b) 2.25 Ω
 c) 12.5 Ω
 d) 8.0 Ω
 e) None of the above

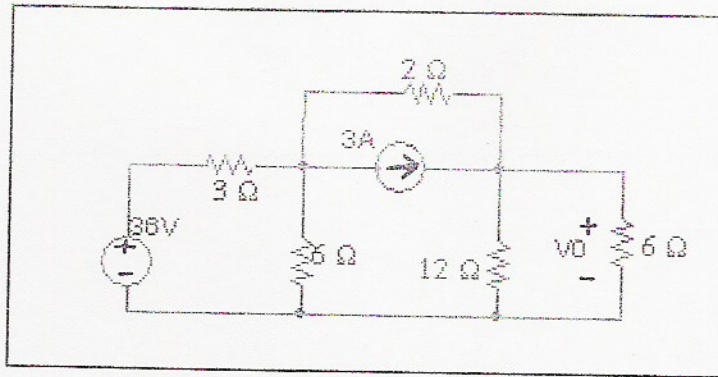9. Calculate the voltage V_o across the $6\ \Omega$ resistor due to the $36\ \text{V}$ source only.



- a) 15 V
- b) 12 V
- c) 18V
- d) 3 V
- e) None of the above

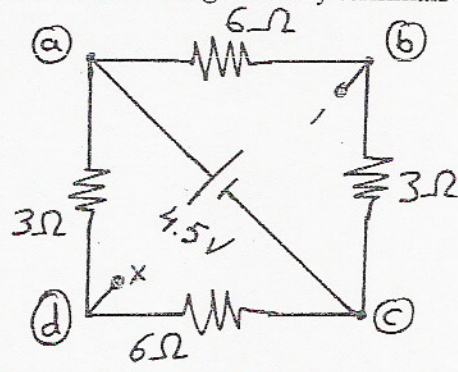10. For the circuit shown, find the Thevenin voltage seen by terminals b-d.




- a) 1V
- b) 1.5V
- c) 2V
- d) 2.5V
- e) None of the above

11. In problem 10, find the Thevenin resistance seen by terminals b-d:

- a) $2\ \Omega$
- b) $3\ \Omega$
- c) $4\ \Omega$
- d) $5\ \Omega$
- e) None of the above

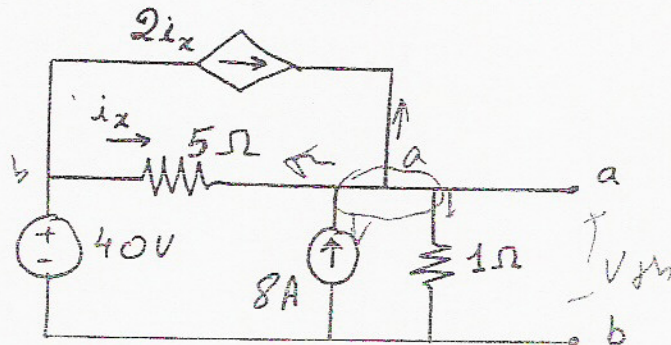12. For the circuit shown, find the Thevenin resistance seen by terminals a-b.



- a) $\sim 0.62\ \Omega$
- b) $\sim 1.6\ \Omega$
- c) $\sim 1.1\ \Omega$
- d) $\sim 0.93\ \Omega$
- e) None of the above

13. In problem 12, find the Thevenin voltage seen by terminals b-d.

- a) 10 V
- b) 20 V
- c) 30V
- d) 40 V
- e) None of the above