

Physics 211L Final exam

January 9, 2008

Name: _____

Section number: _____

Instructor's Name: _____

ID number: _____

DO NOT START THE EXAM BEFORE YOU ARE TOLD TO BEGIN

Grading

I	
II-1	
II-2	
II-3	
TOTAL	


The duration of this exam is 60 minutes.

No notes or books allowed.

Scientific calculators are allowed

All results should be given with the exact number of significant figures.

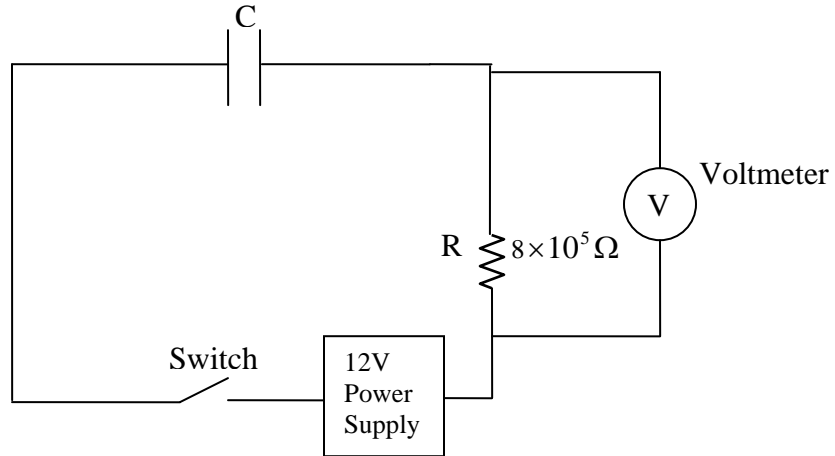- I. (55%) In order to measure the capacitance of an unknown capacitor, the following circuit is connected:



At $t=0$ the switch is closed, the readings of the voltmeter were recorded every 5 seconds with the following outcome:

t(seconds)	V(Volts)				
0	12.00				
5	3.210				
10	0.920				
15	0.273				
20	0.082				
25	0.019				

Note that the resistor has 4% tolerance.
 You may find the formulae on page 4 useful.

- a- Derive the relationship between V and t.
- b- Choose your variables such that you obtain a linear relationship between them.

c- Use linear regression to find the slope of your line along with its error.

d- Determine the capacitance C along with its error.

Linear Regression

The *method of least squares* is used to fit a curve (find a theoretical equation) to a set of experimental data. First assume that a linear relation exists between y and x

$$y = Ax + B \quad (1)$$

Substitution of $x = x_i$ will in general not give the value of y_i . The “errors” will be

$$e_i = y - y_i = Ax_i + B - y_i \quad (2)$$

To determine the best straight line that fits the N , sets of data, A and B have to be chosen so that the sum of the squares of the “errors” is minimized. This means that the simultaneous equations, obtained by equating the partial derivatives of $(y - y_i)^2$ with respect to A and B to zero, should be solved. This condition leads then to the following results

$$A = \frac{N \sum (x_i y_i) - \sum x_i \sum y_i}{\Delta} \quad (3)$$

and

$$B = \frac{\sum x_i^2 \sum y_i - \sum x_i \sum (x_i y_i)}{\Delta} \quad (4)$$

where

$$\Delta = N \sum x_i^2 - (\sum x_i)^2 \quad (5)$$

The *correlation coefficient* r provides an indicator of how good a fit the best straight line is. This coefficient is defined as

$$r = \frac{\sum (x_i - \bar{x})(y_i - \bar{y})}{\sqrt{\sum (x_i - \bar{x})^2 \sum (y_i - \bar{y})^2}} \quad (6)$$

For $r = 0$, the values of x and y are independent of one another and there is no linear correlation. The closer r is to $+1$ or to -1 , the better the linear correlation is.

Finally, the error in A is given by:

$$\sigma_A^2 = \frac{N}{N-2} \frac{\sum e_i^2}{\Delta}$$


II. Questions

1. In the “Electrical Circuits” experiment, how was the resistivity of a copper coil determined? Explain briefly the procedure and include necessary equations. (20%)

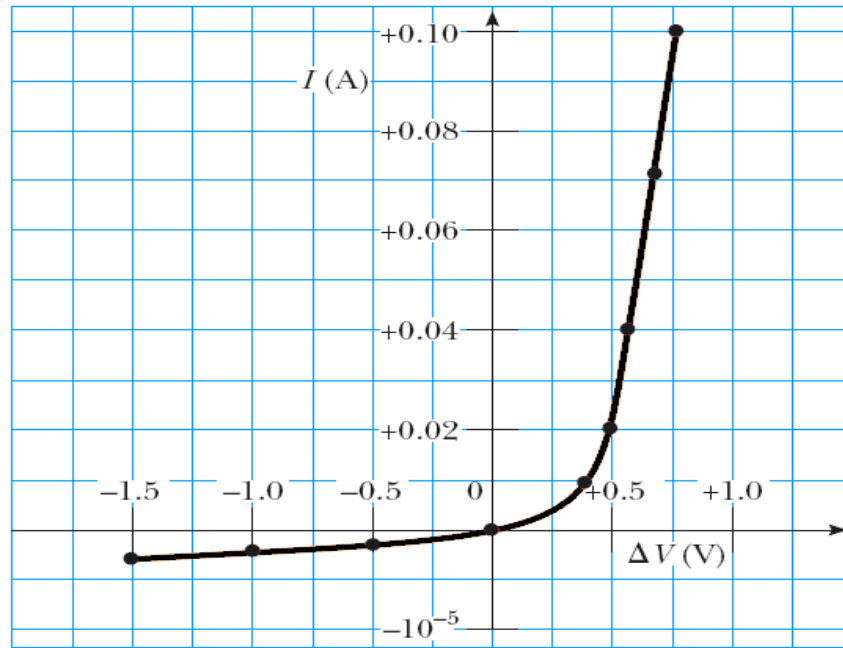2. (15%) The graph in the figure below shows the current I in a diode as a function of potential difference ΔV across the diode.

a- Determine the resistance of the diode for six different values of ΔV in the range from -1.5V to 1V . (5%)

- b- Based on your results, what electrical property does a diode possess? Does this classify the diode as an Ohmic device? Explain.(10%)



(a)

3. In the “Force between Two Parallel Conductors” experiment, how did we eliminate the effect of the earth magnetic field? (10%)