

1.7 Five coulombs of charge pass through the element in Fig. P1.7 from point A to point B. If the energy absorbed by the element is 150 J, determine the voltage across the element.


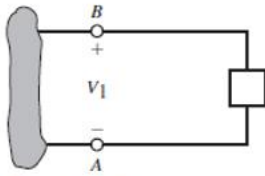


Figure P1.7

SOLUTION:

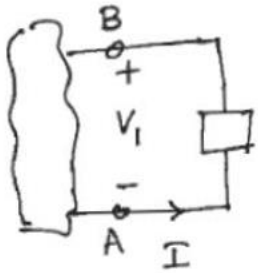

$$Q = 5 \text{ C}$$
$$W = 150 \text{ J}$$

For passive sign convention: $W = -V_1 Q$

$$V_1 = -\frac{W}{Q}$$

$$\boxed{V_1 = -30 \text{ V}}$$

- 1.8 The current that enters an element is shown in Fig. P1.8.
Find the charge that enters the element in the time interval
 $0 < t < 20$ s.

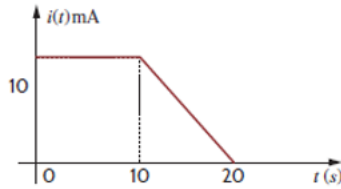


Figure P1.8

SOLUTION:

$$i(t) = m_1 t + b$$

$$m_1 = \frac{10 - 0}{10 - 20} = -1$$

$$i(t) = -t + b$$

$$10 = -10 + b$$

$$b = 20$$

$$i(t) = -t + 20 \text{ mA}$$

$$q(t) = \int_0^{20} i(t) dt$$

$$q(t) = \int_0^{10} 10 \times 10^{-3} dt + \int_{10}^{20} \frac{20-t}{1000} dt$$

$$q(t) = 10 \times 10^{-3} t \Big|_0^{10} + \frac{1}{1000} \left[20t - \frac{t^2}{2} \right]_{10}^{20}$$

$$q(t) = 0.1 + \frac{1}{1000} \left[20(20) - \frac{(20)^2}{2} - 20(10) + \frac{(10)^2}{2} \right]$$

$$q(t) = 0.1 + \frac{1}{1000} [200 - 200 + 50]$$

$$q(t) = 0.15 \text{ C}$$

1.16 The energy absorbed by the BOX in Fig. P1.16 is given below. Calculate and sketch the current flowing into the BOX. Also calculate the charge which enters the BOX between 0 and 12 seconds.

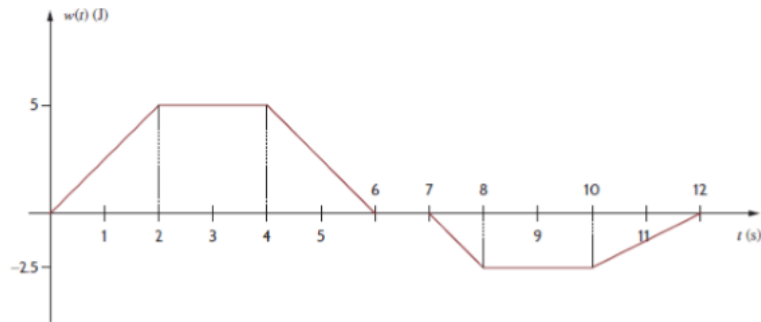
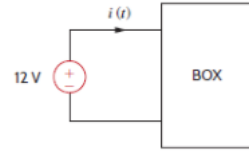


Figure P1.16

SOLUTION:

$$P = \frac{dW}{dt} \text{ (slope of the curve)}$$

$$P = v i \Rightarrow i = \frac{P}{v} = \frac{P}{12}$$

$$0 \leq t \leq 2 \text{ s} :$$

$$P = \frac{5 - 0}{2 - 0} = 2.5 \text{ W} , \quad i = \frac{2.5}{12} = 0.21 \text{ A}$$

$$\underline{2 \leq t \leq 4 \text{ s:}}$$

$$P = \frac{5-5}{4-2} = 0, \quad i = 0$$

$$\underline{4 \leq t \leq 6 \text{ s:}}$$

$$P = \frac{0-5}{6-4} = -2.5 \text{ W}, \quad i = \frac{-2.5}{12} = -0.21 \text{ A}$$

$$\underline{6 \leq t \leq 7 \text{ s:}}$$

$$P = \frac{0-0}{7-6} = 0, \quad i = 0$$


$$\underline{7 \leq t \leq 8 \text{ s:}}$$

$$P = \frac{-2.5-0}{8-7} = -2.5 \text{ W}, \quad i = \frac{-2.5}{12} = -0.21 \text{ A}$$

$$\underline{8 \leq t \leq 10 \text{ s:}}$$

$$P = \frac{-2.5 - (-2.5)}{10-8} = 0, \quad i = 0$$

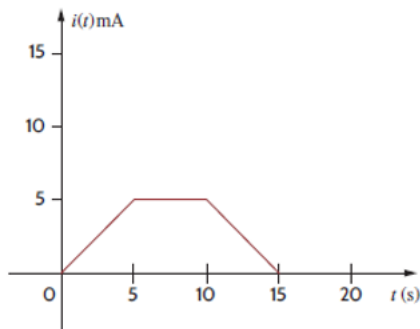1.17 The plot of current entering an element is shown in the figure.
Find the charge that enters the element from 5 to 15 seconds.



SOLUTION:

The charge through the element can be found by finding the area under the curve from 5 to 15 seconds.

$$\begin{aligned} \text{Thus charge flown} &= 5 \times (10-5) + \frac{1}{2} \times 5 \times (15-10) \\ &= 37.5 \text{ mC} \end{aligned}$$

1.37 Find I_x in the circuit in Fig. P1.37 using Tellegen's theorem.

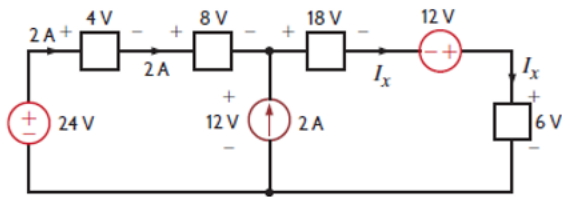


Figure P1.37

SOLUTION:

$$P_{24V} = (24)(-2) = -48W$$

$$P_{24V} = 48W \text{ supplied}$$

$$P_{4V} = (4)(2) = 8W \text{ absorbed}$$

$$P_{8V} = (8)(2) = 16W \text{ absorbed}$$

$$P_{2A} = 12(-2) = -24W$$

$$P_{2A} = 24W \text{ supplied}$$

$$P_{18V} = 18I_x \text{ absorbed}$$

$$P_{12V} = 12(-I_x) = -12I_x$$

$$P_{12V} = 12I_x \text{ supplied}$$

$$P_{6V} = 6I_x \text{ absorbed}$$

Power supplied = Power absorbed

$$P_{24V} + P_{2A} + P_{12V} = P_{4V} + P_{8V} + P_{18V} + P_{6V}$$

$$48 + 24 + 12I_x = 8 + 16 + 18I_x + 6I_x$$

$$12I_x = 48$$

$$I_x = 4A$$

2.20 In the network in Fig. P2.20, Find I_1 , I_2 and I_3 and show that KCL is satisfied at the boundary.

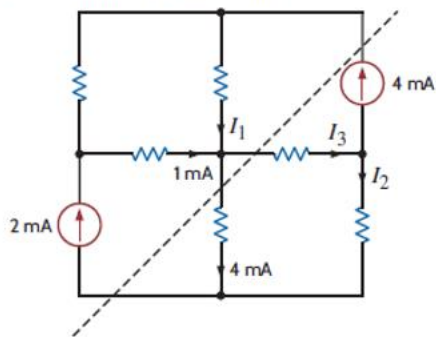


Figure P2.20

SOLUTION:

$$2\text{mA} - 1\text{mA} + 4\text{mA} = I_1$$

$$I_1 = 5\text{mA}$$

$$I_2 + 4\text{mA} = 2\text{mA}$$

$$I_2 = -2\text{mA}$$

$$I_3 = I_2 + 4\text{mA}$$

$$= 2\text{mA}$$

Across the Boundary (left-, Right +)

$$-2\text{mA} + 4\text{mA} + 2\text{mA} - 4\text{mA} = 0$$

2.30 The 10-V source absorbs 2.500 mW of power. Calculate (a) V_{ba} and (b) the power absorbed by the dependent voltage source in Fig. P2.30.


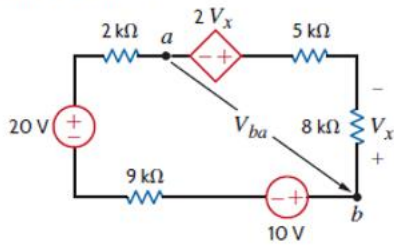


Figure P2.30

SOLUTION:

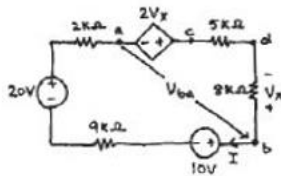

$$P_{10V} = 2.50 \text{ mW absorbed}$$

$$P_{10V} = 10I$$

$$\Rightarrow I = \frac{P_{10V}}{10} = 250 \mu\text{A}$$

$$\text{KVL for 'bacdb': } V_{ba} - V_{ca} - V_{dc} - V_{bd} = 0$$

$$\Rightarrow V_{ba} = V_{ca} + V_{dc} + V_{bd} \quad \text{--- (1)}$$

$$V_{bd} = -I(8 \times 10^3) = -(250 \times 10^{-6})(8 \times 10^3)$$

$$\Rightarrow V_{bd} = -2 \text{ V} \quad \text{--- (2)}$$

$$V_{dc} = -I(5 \times 10^3) \Rightarrow V_{dc} = -1.25 \text{ V} \quad \text{--- (3)}$$

$$V_x = V_{bd} = -2 \text{ V}$$

$$V_{ca} = 2V_x = -4 \text{ V} \quad \text{--- (4)}$$

$$\text{Substituting (2), (3), (4) in (1): } \boxed{V_{ba} = -7.25 \text{ V}}$$

$$P_{DS} = -2V_x I = -2(-2)(250 \times 10^{-6})$$

$$\Rightarrow \boxed{P_{DS} = 1 \text{ mW}}$$

2.57 Find R_{AB} in the network in Fig. P2.57.


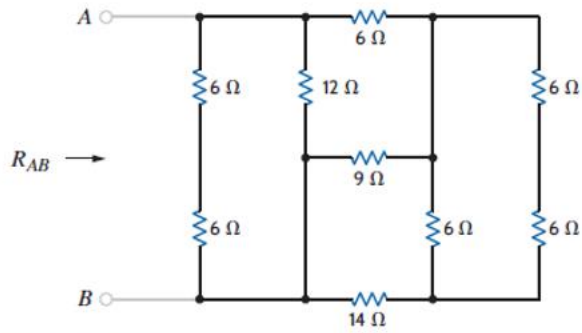


Figure P2.57

SOLUTION:

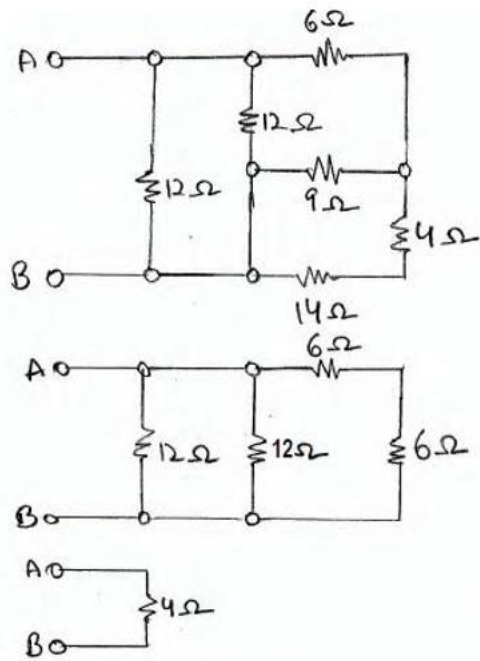

2.67 Determine I_o in the circuit in Fig. P2.67.


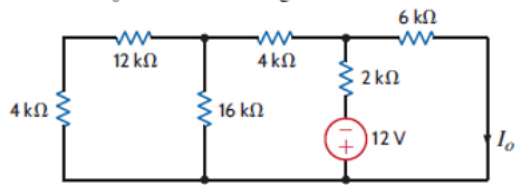



Figure P2.67

SOLUTION:

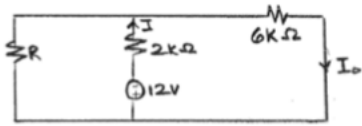

$$R = [(4k + 12k) \parallel 16k] + 4k$$

$$R = 8k + 4k = 12k \Omega$$

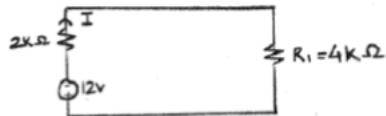

$$I = \frac{-12}{2k + 4k} = -2 \text{ mA}$$

$$R_1 = 12k \parallel 16k$$

$$R_1 = 4k \Omega$$

Current division:

$$I_o = \left(\frac{12k}{12k + 6k} \right) (-2 \text{ m})$$

$$I_o = -1.33 \text{ mA}$$

2.69 Calculate V_{AB} in Fig. P2.69.



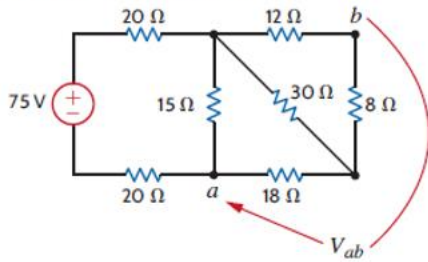
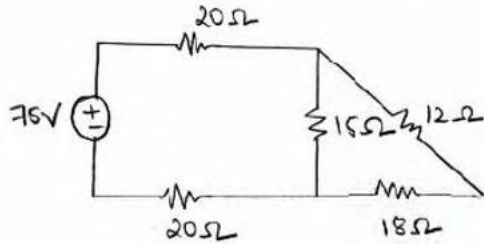
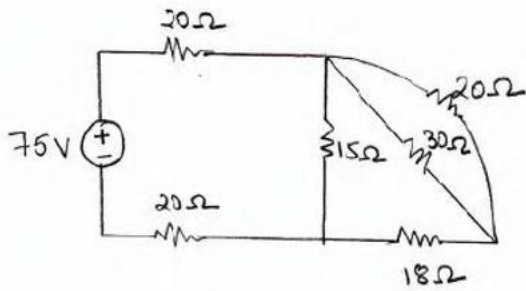



Figure P2.69

SOLUTION:

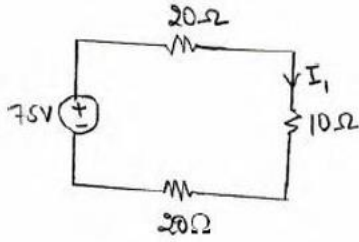

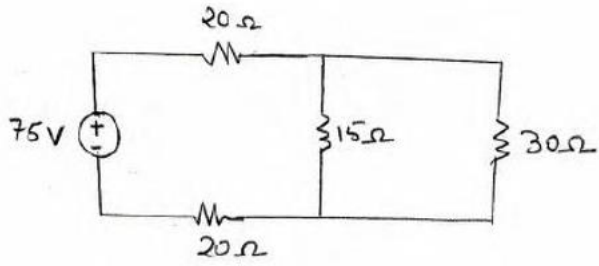


$$I_1 = \frac{75}{20 + 10 + 20} = 1.5A$$

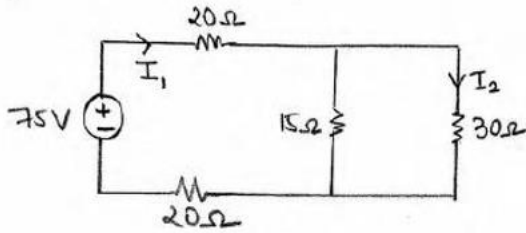


$$I_2 = 1.5 \left(\frac{15}{15 + 30} \right)$$

$$= 0.5A$$

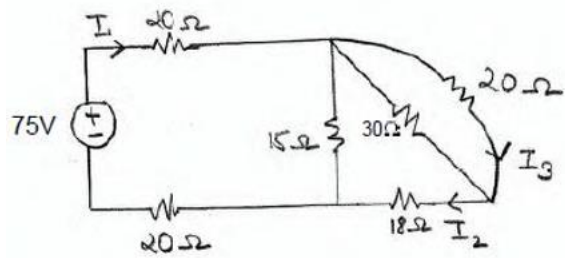
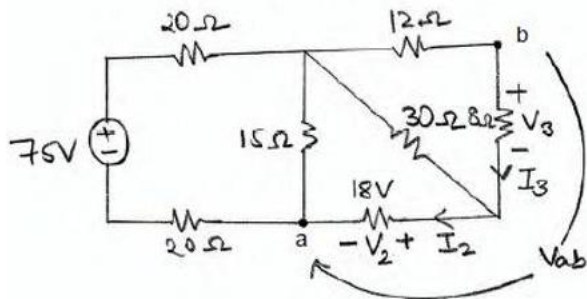
$$I_3 = 0.5 \left(\frac{30}{30+20} \right) = 0.3 \text{ A}$$



$$V_3 = 8 I_3 = 8(0.3) = 2.4 \text{ V}$$

$$V_2 = 18 I_2 = 18(0.5) = 9 \text{ V}$$

$$V_{ab} = -V_2 - V_3 = -9 - 2.4 = -11.4 \text{ V}$$

2.71 Calculate V_{ab} and V_1 in Fig. P2.71.



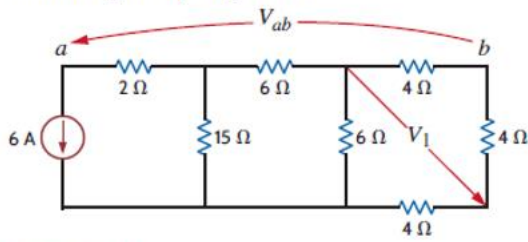
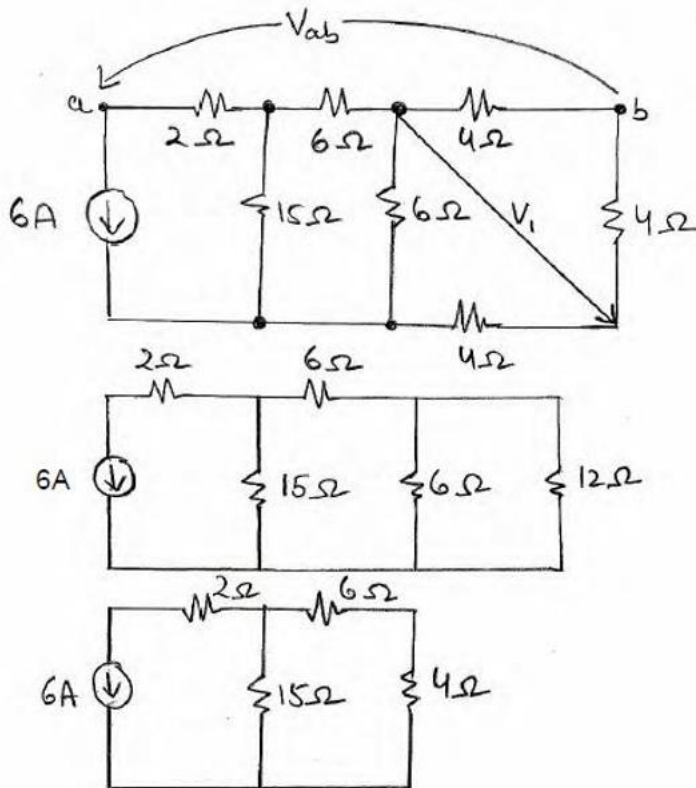


Figure P2.71


SOLUTION:

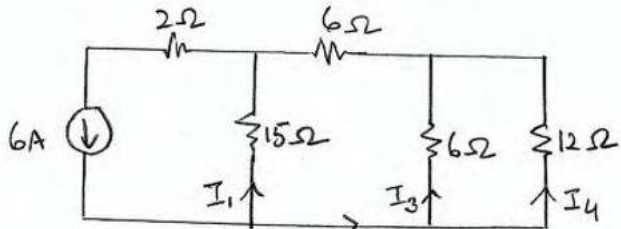

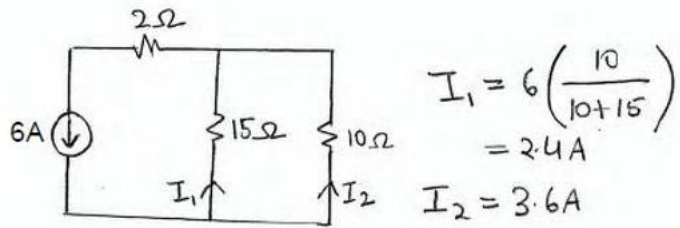

$$I_3 = 3.6 \left(\frac{12}{12+6} \right) = 2.4 \text{ A}$$

$$I_4 = 1.2 \text{ A}$$

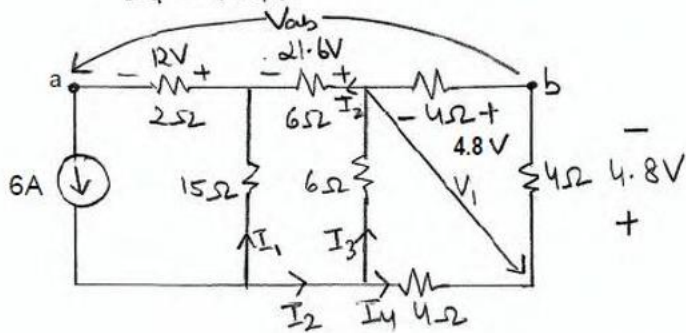

$$V_1 = 4.8 + 4.8 = \underline{9.6 \text{ V}}$$

$$V_{ab} = -12 - 21.6 - 4.8 = \underline{-38.4 \text{ V}}$$

2.83 In the circuit in Fig. P2.83.

- (a) Calculate V_y if $I_z = -3$ A
 (b) What voltage would need to replace the 5 V source to obtain $v_y = -6$ V if $I_z = 0.5$ A.

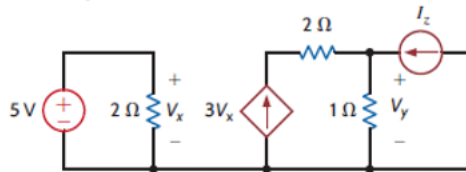


Figure P2.83

SOLUTION:

- a. $v_y = 1(3v_x + i_z)$
 $v_x = 5$ V and given that $i_z = -3$ A, we find that
 $v_y = 3(5) - 3 = 12$ V
- b. $v_y = 1(3v_x + i_z) = -6 = 3v_x + 0.5$
 Solving, we find that $v_x = (-6 - 0.5)/3 = -2.167$ V.

2.86 If $V_2 = 4\text{ V}$ in Fig. P2.86, calculate V_x .


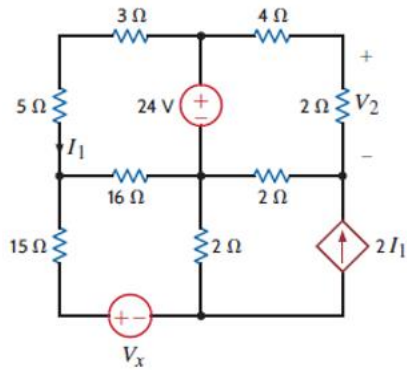


Figure P2.86

SOLUTION:

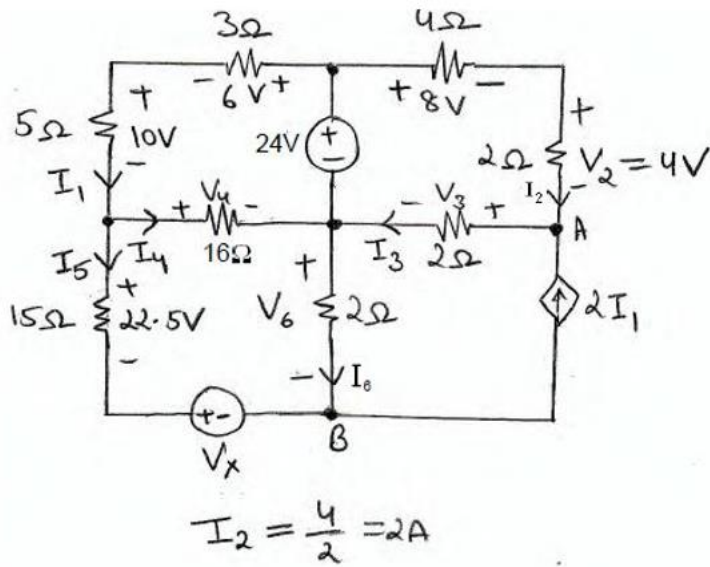

$$V_3 = -4 - 8 + 24 = 12V \quad I_3 = \frac{V_3}{2} = 6A$$

$$\text{KCL @ node A: } I_2 + 2I_1 = I_3$$

$$2 + 2I_1 = 6 \quad 2I_1 = 4 \quad I_1 = 2A$$

$$V_4 = -10 - 6 + 24 = 8V \quad I_4 = \frac{8}{16} = 0.5A$$

$$I_5 = I_1 - I_4 = 2 - 0.5 = 1.5A$$

$$\text{KCL @ node B: } I_6 + I_5 = 2I_1 = 4$$

$$I_6 = 4 - 1.5 = 2.5A \quad V_6 = 2I_6 = 5V$$

$$V_x = -2 \cdot 2.5 + 8 + 5 = \underline{\underline{-9.5V}}$$

2.92 The 5-A current source in Fig. P2.92 supplies 150 W. Calculate V_A .


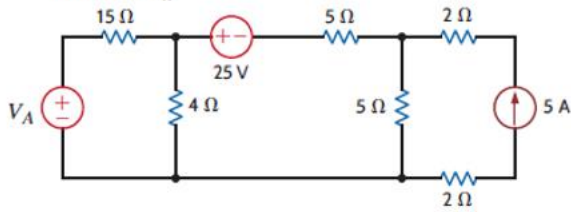


Figure P2.92

SOLUTION:

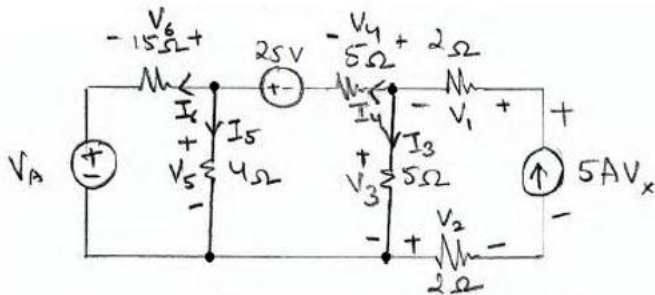

$$\begin{aligned}
 V_1 &= (5)(2) = 10V & V_x &= \frac{150}{5} = 30V \\
 V_2 &= (5)(2) = 10V \\
 V_3 &= -V_1 + V_x - V_2 = -10 + 30 - 10 = 10V \\
 I_3 &= \frac{V_3}{5} = \frac{10}{5} = 2A \\
 I_4 &= 5 - I_3 = 5 - 2 = 3A \\
 V_4 &= 5I_4 = (5)(3) = 15V \\
 V_5 &= 25 - V_4 + V_3 = 25 - 15 + 10 = 20V
 \end{aligned}$$

$$\begin{aligned}
 I_5 &= \frac{V_5}{4} = \frac{20}{4} = 5A \\
 I_6 &= I_4 - I_5 = 3 - 5 = -2A \\
 V_6 &= 15I_6 = 15(-2) = -30V \\
 V_A &= -V_6 + V_5 = -(-30) + 20 = \underline{\underline{50V}}
 \end{aligned}$$

3.4 Use nodal analysis to find V_1 in the circuit in Fig. P3.4.


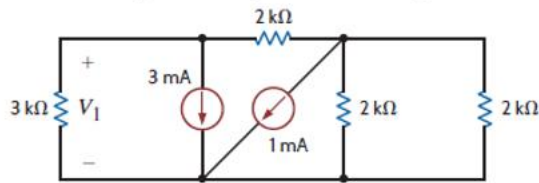


Figure P3.4

SOLUTION:

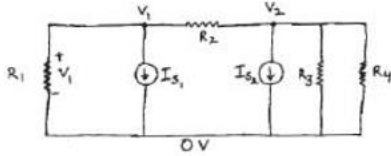

$$R_1 = 3 \text{ k}\Omega, R_2 = R_3 = R_4 = 2 \text{ k}\Omega, I_{S_1} = 3 \text{ mA}, I_{S_2} = 1 \text{ mA}$$

$$\text{KCL @ } V_1: \frac{V_1}{R_1} + I_{S_1} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1}{3 \times 10^3} + 3 \times 10^{-3} + \frac{V_1 - V_2}{2 \times 10^3} = 0$$

$$5V_1 - 3V_2 = -18 \quad \text{--- (1)}$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{R_2} + I_{S_2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} = 0$$

$$\frac{V_2 - V_1}{2 \times 10^3} + 1 \times 10^{-3} + \frac{V_2}{2 \times 10^3} + \frac{V_2}{2 \times 10^3} = 0$$

$$3V_2 - V_1 = -2 \quad \text{--- (2)}$$

Substituting equation (2) in (1), we get

$$V_2 = \frac{-2 - 18}{12}$$

$$V_1 = \frac{3V_2 - 18}{5} \Rightarrow \boxed{V_1 = -5 \text{ V}}$$

3.11 Find V_o in the network in Fig. P3.11 using nodal analysis.


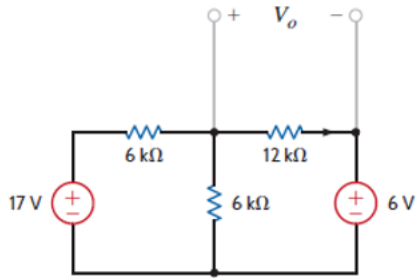


Figure P3.11

SOLUTION:

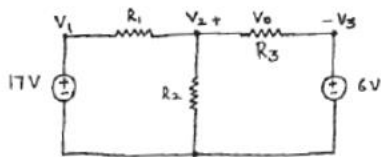

$$R_1 = R_2 = 6 \text{ k}\Omega, \quad R_3 = 12 \text{ k}\Omega$$

$$\text{@ } V_1: \quad V_1 = 17 \text{ V}$$

$$\text{KCL @ } V_2: \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0 \quad \text{--- (1)}$$

$$\text{@ } V_3: \quad V_3 = 6 \text{ V}$$

Substituting values of V_1 and V_3 in equation (1), we get

$$\frac{V_2}{R_1} - \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2}{R_3} - \frac{V_3}{R_3} = 0$$

$$V_2 \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{V_1}{R_1} - \frac{V_3}{R_3} = 0$$

$$V_2 \left[\frac{1}{6} + \frac{1}{6} + \frac{1}{12} \right] - \frac{17}{6} - \frac{6}{12} = 0$$

$$V_2 = 8 \text{ V}$$

$$V_o = V_2 - V_3$$

$$\boxed{V_o = 2 \text{ V}}$$

3.18 Find I_o in the circuit in Fig. P3.18 using nodal analysis.


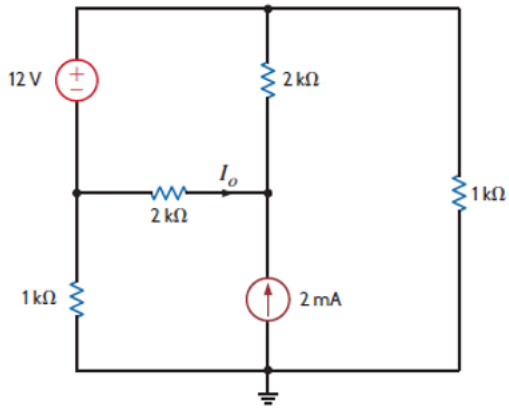


Figure P3.18

SOLUTION:

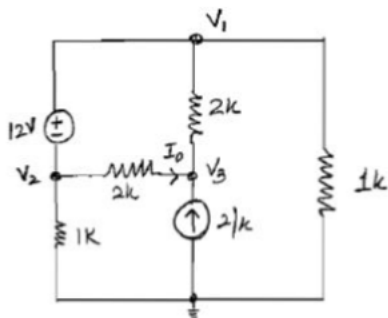

$$V_1 - V_2 = 12$$

$$\frac{V_1 - V_3}{2k} + \frac{V_1}{1k} + \frac{V_2}{1k} + \frac{V_2 - V_3}{2k} = 0$$

$$\frac{V_3 - V_1}{2k} + \frac{V_3 - V_2}{2k} = 2/k$$

$$\frac{V_1}{2k} - \frac{V_3}{2k} + \frac{V_1}{1k} + \frac{V_2}{1k} + \frac{V_2}{2k} - \frac{V_3}{2k} = 0$$

$$\frac{V_3}{2k} - \frac{V_1}{2k} + \frac{V_3}{2k} - \frac{V_2}{2k} = \frac{2}{k}$$

$$V_1 = V_2 + 12$$

$$\frac{V_2}{2k} + \frac{12}{2k} - \frac{V_3}{2k} + \frac{V_2}{2k} + \frac{12}{k} + \frac{V_2}{k} + \frac{V_2}{2k} - \frac{V_3}{2k} = 0$$

$$\frac{V_3}{2k} - \frac{V_2}{2k} - \frac{12}{2k} + \frac{V_3}{2k} - \frac{V_2}{2k} = \frac{2}{k}$$

$$V_2 \left(\frac{1}{2k} + \frac{1}{k} + \frac{1}{k} + \frac{1}{2k} \right) - V_3 \left(\frac{1}{2k} + \frac{1}{2k} \right) = -18/k$$

$$-V_2 \left(\frac{1}{2k} + \frac{1}{2k} \right) + V_3 \left(\frac{1}{2k} + \frac{1}{2k} \right) = \frac{8}{k}$$

$$V_2 \left(\frac{3}{k} \right) - V_3 \left(\frac{1}{k} \right) = -18/k$$

$$-V_2 \left(\frac{1}{k} \right) + V_3 \left(\frac{1}{k} \right) = \frac{8}{k}$$

$$\begin{bmatrix} 3 & -1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -18 \\ 8 \end{bmatrix}$$

$$\Delta = 3 - 1 = 2$$

$$\begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix} \begin{bmatrix} -18 \\ 8 \end{bmatrix} = \frac{1}{2} \begin{bmatrix} -10 \\ 6 \end{bmatrix} = \begin{bmatrix} -5 \\ 3 \end{bmatrix}$$

$$I_0 = \frac{V_2 - V_3}{2k} = \frac{-5 - 3}{2k} = \frac{-8}{2k} = -4mA$$

3.20 For the circuit in Fig. P3.20, find the node voltages using nodal analysis.


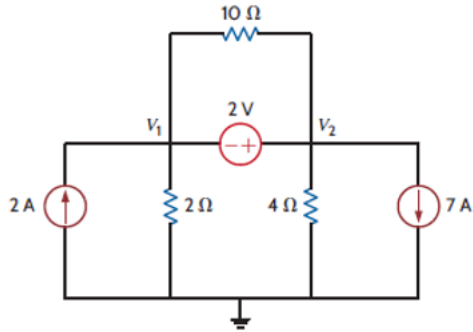


Figure P3.20

SOLUTION:

The supernode contains the 2-V source, nodes 1 and 2, and the 10-Ω resistor. Applying KCL to the supernode as shown in the figure below gives,

$$2 = i_1 + i_2 + 7$$

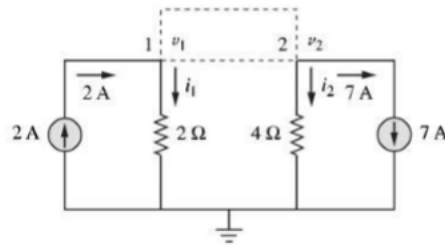

Expressing i_1 and i_2 in terms of the node voltages, we get,


$$2 = \frac{v_1 - 0}{2} + \frac{v_2 - 0}{4} + 7 \quad \Rightarrow \quad 8 = 2v_1 + v_2 + 28$$

Or, $v_2 = -20 - 2v_1$ (i)

To get the relationship between v_1 and v_2 , we apply KVL to the circuit shown in figure below.

Going around the loop, we obtain,
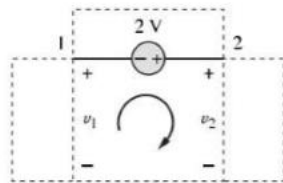
$$-v_1 - 2 + v_2 = 0 \quad \Rightarrow \quad v_2 = v_1 + 2 \quad \text{(ii)}$$



From (i) and (ii), we get,

$$v_1 = -7.333 \text{ V} \quad \text{And} \quad v_2 = -5.333 \text{ V}.$$

3.34 Find V_o in the circuit in Fig. P3.34 using nodal analysis.

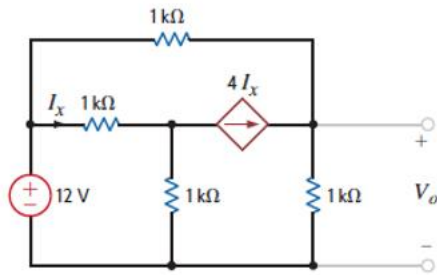


Figure P3.34

SOLUTION:

$$\frac{V_1 - 12}{k} + \frac{V_1}{k} + 4I_X = 0$$

$$\frac{V_o - 12}{k} + \frac{V_o}{k} = 4I_X \quad I_X = \frac{12 - V_1}{k}$$

$$V_1 - 12 + V_1 + 48 - 4V_1 = 0$$

$$V_o - 12 + V_o = 48 - 4V_1$$

$$-2V_1 + 36 = 0$$

$$2V_o + 4V_1 = 60$$

$$V_1 = 18V$$

$$2V_o = 60 - 72 = -12$$

$$V_o = -6V$$

3.62 Find V_o in the network in Fig. P3.62 using loop analysis.


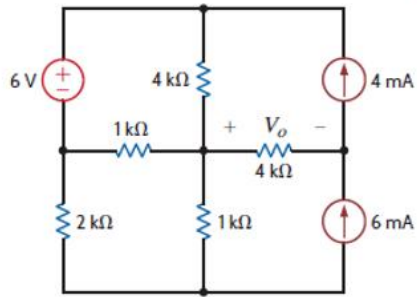


Figure P3.62

SOLUTION:

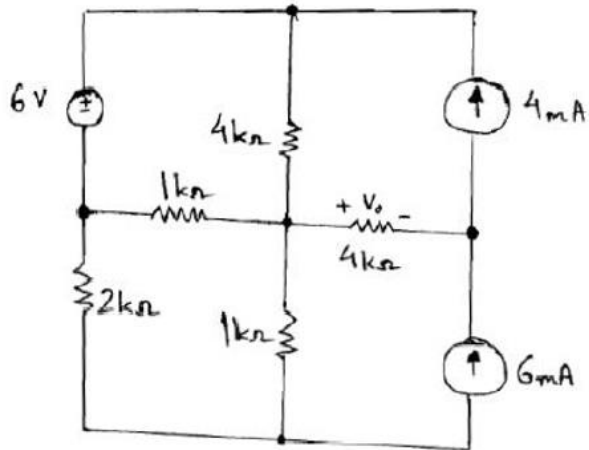

$$V_o = -(4k) \left(\frac{2}{2k} \right) = -4V$$

3.66 Find V_o in the network in Fig. P3.66 using loop analysis.


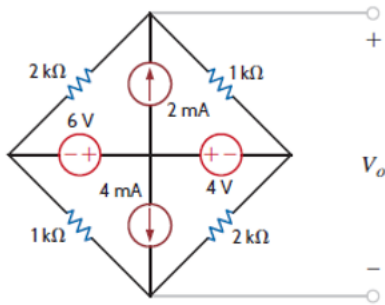


Figure P3.66

SOLUTION:

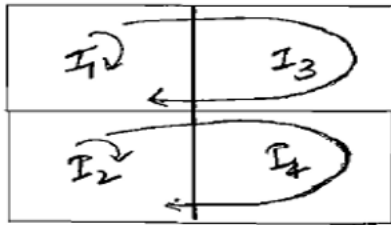

$$I_1 = -2/k$$

$$I_2 = 4/k$$

$$2k(I_1 + I_3) + 1kI_3 + 2 = 0$$

$$2k(I_4) + 1k(I_2 + I_4) - 2 = 0$$

$$2kI_1 + 3kI_3 = -2$$

$$3kI_4 + 1kI_2 = 2$$

$$3kI_3 = 2$$

$$I_3 = 2/3k$$

$$3kI_4 = -2$$

$$I_4 = -2/3k$$

$$V_o = 1kI_3 + 2kI_4 = \frac{2}{3} - \frac{4}{3} = -2/3V$$

3.83 Find the currents in the three meshes in Fig. P3.83.


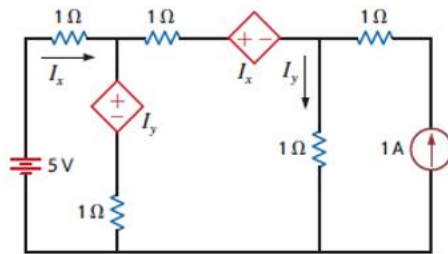


Figure P3.83

SOLUTION:

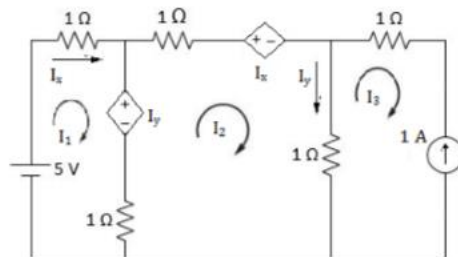Assigning clockwise currents in three meshes, we get,



From the figure,

$$I_x = I_1 \quad I_y = I_2 - I_3$$

But $I_3 = -1 \text{ A}$, so

$$I_y = I_2 + 1$$

Applying KVL to Mesh 1,

$$5 - I_1 - I_y - (I_1 - I_2) = 0 \quad \Rightarrow \quad -I_1 - I_2 - I_1 + I_2 = -5 + 1$$

$$\Rightarrow \quad I_1 = 2 \text{ A}$$

Applying KVL to Mesh 2,

$$-(I_2 - I_1) + I_y - I_2 - I_x - (I_2 - I_3) = 0$$

$$\Rightarrow \quad -I_2 + I_1 + (I_2 + 1) - I_2 - I_1 - I_2 + I_3 = 0$$

$$\Rightarrow \quad -2I_2 + 1 - 1 = 0 \quad \Rightarrow \quad I_2 = 0$$

3.89. Use both nodal analysis and mesh analysis to find V_o in the circuit in Fig. P3.89.


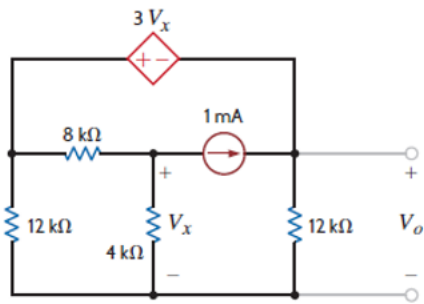


Figure P3.89

SOLUTION:

a)

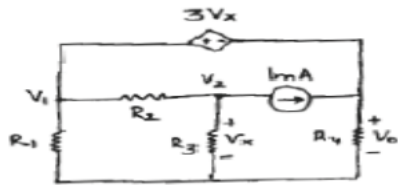

$$R_1 = R_4 = 12 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, V_x = V_2$$

$$V_1 - V_0 = 3V_x$$

$$\Rightarrow V_1 - V_0 = 3V_2 \quad \text{---} \quad \textcircled{1}$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + 1 \times 10^{-3} = 0$$

$$3V_2 - V_1 = -8$$


$$V_2 = \frac{-8 + V_1}{3} \quad \text{---} \quad \textcircled{2}$$

Substituting equation ② in ①, we get

$$V_1 - V_0 = \frac{3(V_1 - 8)}{3}$$

$$\boxed{V_0 = 8.00 \text{ V}}$$

b)

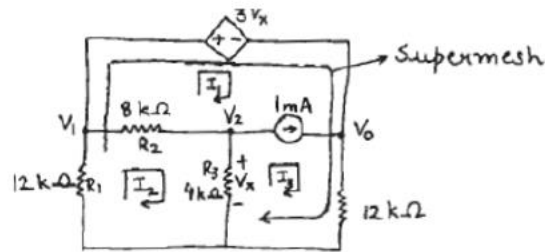

$$R_1 = R_4 = 12 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega$$

$$I_3 - I_1 = 10^{-3} \text{ A} \quad \text{---} \quad (1)$$

$$V_x = (I_2 - I_3) R_3$$

$$V_0 = I_3 R_4$$

$$\text{KVL @ Supermesh: } 3V_x + I_3 R_4 + I_2 R_1 = 0$$

$$3 I_2 R_3 - 3 I_3 R_3 + I_3 R_4 + I_2 R_1 = 0$$

$$I_2 = 0 \text{ A} \quad \text{---} \quad (2)$$

$$\text{KVL @ } I_2 : I_2 R_1 + (I_2 - I_1) R_2 + (I_2 - I_3) R_3 = 0$$

$$2 I_1 + I_3 = 0$$

$$I_1 = -\frac{I_3}{2} \quad \text{---} \quad (3)$$

Substituting equation (3) in (2), we get

$$I_3 = \frac{2}{3} \times 10^{-3} \text{ A}$$

$$V_0 = I_3 R_4$$

$$\boxed{V_0 = 8.00 \text{ V}}$$

3.90 Using mesh analysis, find V_o in the circuit in Fig. P3.90.


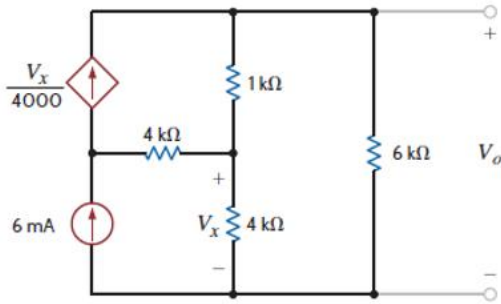


Figure P3.90

SOLUTION:

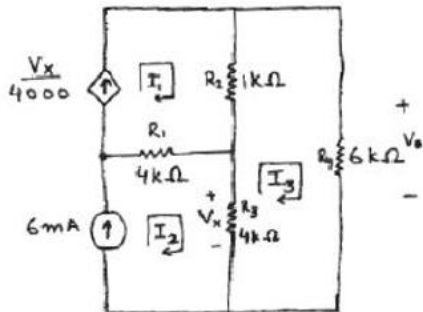

$$R_1 = R_3 = 4\text{ k}\Omega, R_2 = 1\text{ k}\Omega, R_4 = 6\text{ k}\Omega$$

$$I_2 = 6 \times 10^{-3} \text{ A} \quad \text{---} \quad \textcircled{1}$$

$$V_x = (I_2 - I_3) R_3 \quad \text{---} \quad \textcircled{2}$$

$$I_1 = \frac{V_x}{4000} \quad \text{---} \quad \textcircled{3}$$

$$V_o = I_3 R_4$$

$$\text{KVL @ } I_3: (I_3 - I_1) R_2 + I_3 R_4 + (I_3 - I_2) R_3 = 0$$

$$11 I_3 - I_1 = 24 \times 10^{-3} \quad \text{---} \quad \textcircled{4}$$

Substituting equations ① and ② in ③, we get

$$I_1 = 6 \times 10^{-3} - I_3 \quad \text{---} \quad \textcircled{5}$$

Substituting equation ⑤ in ④, we get

$$I_3 - \frac{30}{12} \times 10^{-3} \text{ A}$$

$$V_o = I_3 R_4$$

$$= \frac{30}{12} \times 10^{-3} \times 6 \times 10^3$$

$$\boxed{V_o = 150\text{ V}}$$

3.91 Find V_o in the network in Fig. P3.91.


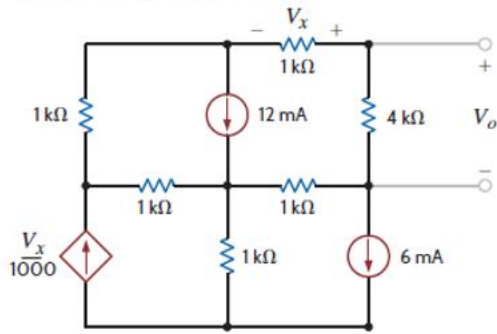


Figure P3.91

SOLUTION:

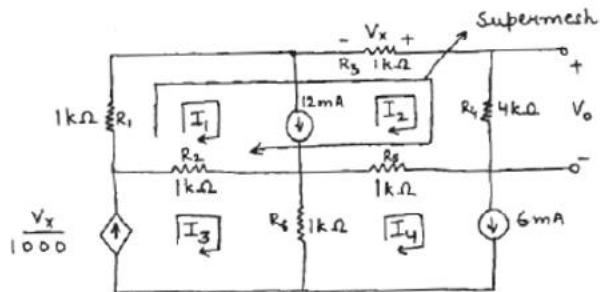

$$R_1 = R_2 = R_3 = R_5 = R_6 = 1 \text{ k}\Omega, R_4 = 4 \text{ k}\Omega$$

$$I_1 - I_2 = 12 \text{ mA} \quad \text{---} \quad \textcircled{1}$$

$$I_4 = 6 \text{ mA}$$

$$V_x = -I_2 R_3$$

$$I_3 = \frac{V_x}{1000}$$

$$V_o = I_2 R_4$$

$$\text{KVL @ Supermesh: } I_1 R_1 + I_2 R_3 + I_2 R_4 + (I_2 - I_4) R_5 + (I_1 - I_3) R_2 = 0$$

$$I_1 (R_1 + R_2) + I_2 (R_3 + R_4 + R_5) - I_3 R_2 - I_4 R_5 = 0$$

$$2 \times 10^3 I_1 + 6 \times 10^3 I_2 - 10^3 I_3 - 10^3 I_4 = 0$$

$$2 I_1 + 6 I_2 - I_3 - I_4 = 0$$

Substituting $I_3 = \frac{V_x}{1000}$ and $V_x = -I_2 R_3$

$$2 I_1 + 7 I_2 = 6 \times 10^{-3} \quad \text{---} \quad (2)$$

From equations (1) and (2), we get

$$I_2 = -2 \text{ mA}$$

$$V_0 = I_2 R_4$$

$$V_0 = -2 \times 10^{-3} \times 4 \times 10^3$$

$$\boxed{V_0 = -8.00 \text{ V}}$$