

PHYSICS 211
Final
TIME: 120 minutes
January 14, 2013

DO NOT OPEN THIS EXAM BEFORE YOU ARE TOLD TO BEGIN

NAME _____

ID Number _____

Grading

1	
2	
3	
4	
TOTAL	

1. (30) We consider an infinitely long wire with a diameter d and length l .
- a. (8) By applying Gauss's law, determine the electric field at a distance $r > d$ from the wire when the wire is charged with Q .

- b. (4) Determine the capacitance of the wire at r (in this case, C will depend on $r > d$)

c. (8) By Applying Ampere's law, determine the magnetic field at the same distance $r > d$ from the wire when there is a current flowing in the $+z$ -direction.


d. (6) At the position $r > d$, a proton moves in the $+z$ -direction parallel to the wire, determine its velocity assuming it is constant in the case where both $Q (> 0)$ and I are present.

e. (4) Any modifications if the proton is replaced by an electron? Justify briefly.

2. (12) A solenoid, with length l and area A is connected to an electromotive force \mathcal{E} .
- a. (6) If the magnetic field inside the solenoid has the expression $B = \mu_0 n I$, where n is the number of turns per unit length, find the expression of its inductance.

- b. (6) When the switch closes, hence the current is rising, show that the inductance of the solenoid can be written as $L = -\mathcal{E} / (di/dt)$ where i is the instantaneous current.

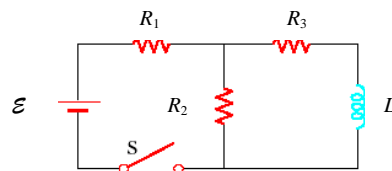3. (27) Consider the circuit below with the three resistors, R_1 , R_2 and R_3 and an electromotive force \mathcal{E} and an inductor L . (Hint: the solution of the differential equation $dx/dt + \alpha x = \beta$ is $x = \beta/\alpha(1 - e^{-\alpha t})$).



- a. (14) As a function of time, just after closing the switch, determine the expression of the current I_3 in R_3 and I_1 in R_1 .

b. (6) As time t tends to infinity, find the expression of the currents in the three resistors.

c. (7) Compare the power generated to the power dissipated as t tends to infinity. Take $\mathcal{E}=10\text{ V}$, $L=1\text{ H}$, $R_1=4\ \Omega$, $R_2=4\ \Omega$ and $R_3=8\ \Omega$.

Check if solution is continued on the back.

- d. (4) Determine the energy generated by the battery at an arbitrary time t_0 . And comment on the different contributions.

4. (27) We wish to study a circuit composed of an AC power source, supplying a current $I = I_m \sin(\omega t)$, a resistor R and an inductor L .


(a) (4) First, consider that the **resistance alone** is connected to the power supply, determine the expression of the potential difference across it.

(b) (4) Consider that the **inductor alone** is connected to the power supply, determine the expression of the potential difference across it.


(c)(6) When both R and L are put in the series, determine the impedance (denoted be Z or X) of the circuit.

(d)(3) Determine the expression of the circuit phase.

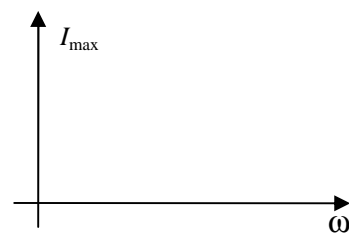(e)(4) Discuss the behavior of this circuit of low frequencies ($\omega \rightarrow 0$) and for ($\omega \rightarrow \infty$) and plot the current I_{\max} vs. ω



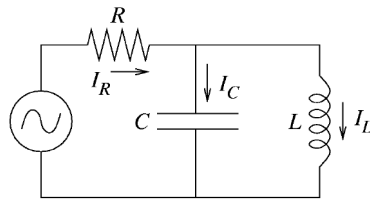We insert a capacitor in parallel to the inductor as shown in the figure below and the AC power source produces now a potential difference $\mathcal{E} = \mathcal{E}_0 \cos(\omega t)$.



(f)(3) What are the maximum values of I_L , I_C and I_R in the case where $\omega \rightarrow 0$

(g)(3) What are the maximum values of I_L , I_C and I_R in the case where $\omega \rightarrow \infty$

SCRATCH PAPER

Nothing on this page will be graded

Check if solution is continued on the back.