

**Physics 211 Final Exam**

*January 31, 2005*

Your name:

ID number:

Time given: 120 minutes

Please provide your reasoning for each step of your solution (providing an answer without a solution is not enough)

**Problem 1**

A conducting sphere of radius  $R$  carries total positive electric charge  $Q$  and is concentric with insulating uniformly charged shell with the internal and external radii equal to  $2R$  and  $3R$ , as shown on the Figure 1. The total electric charge carried by the shell is equal to  $2Q$ . 1) Find the electric field as a function of the distance from the origin  $O$  in the regions 1,2,3 and 4 (see the Figure 1).

2) Find the electric potential at the point  $P$ , located on the inner surface of the shell.

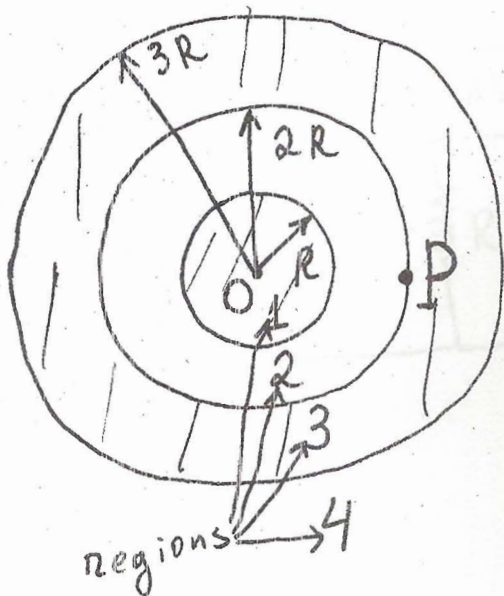


Figure 1

### Problem 2

An electric circuit consists of the 3 batteries with the voltages  $\Delta V_1 = 2V$ ,  $\Delta V_2 = 6V$  and  $\Delta V_3 = 8V$  and 3 resistors  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$  and  $R_3 = 8\Omega$ , as shown on the Figure 2. Find the electric currents in each of the resistors.

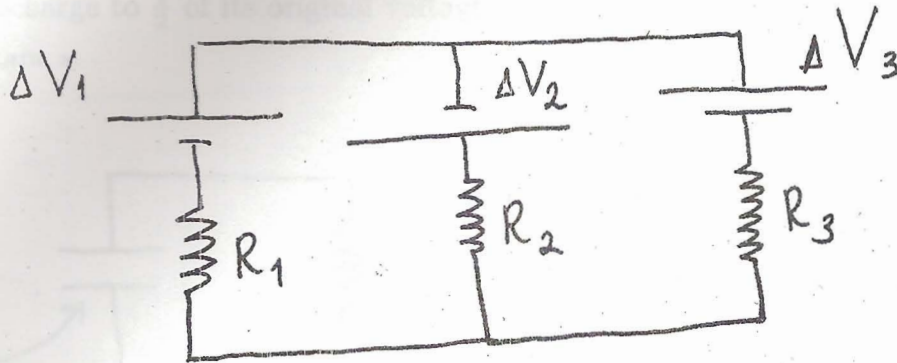



Figure 2

## Problem 3

The  $RC$ -circuit consists of the parallel plate capacitor  $C$  and the resistor  $R$ . (originally, the space between the plates is empty). Initially the capacitor has the voltage  $\Delta V$ . Once the switch is on, it takes the time  $T$  for the capacitor to discharge to  $\frac{1}{10}$  of its original voltage. The space between the plates of the capacitor is then fully filled with a dielectric with unknown constant  $\kappa$  and the capacitor is charged again to the same initial voltage  $\Delta V$ . With the dielectric is introduced, it then takes the same time  $T$  for the capacitor to discharge to  $\frac{1}{2}$  of its original voltage after the switch is turned on. Find the dielectric constant  $\kappa$ .



$$V_{\text{initial}} = \Delta V$$

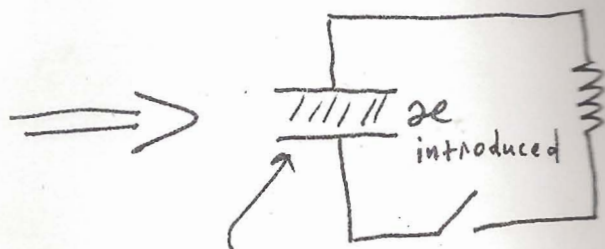

$$V_{\text{initial}} = \Delta V$$

Figure 3

### Problem 4

A part of an infinite straight conductor carrying the current  $I$  is deformed into a circular loop of the radius  $R$ , as shown on the Figure 4. Find the magnitude and the direction of the magnetic field at the center of the loop.

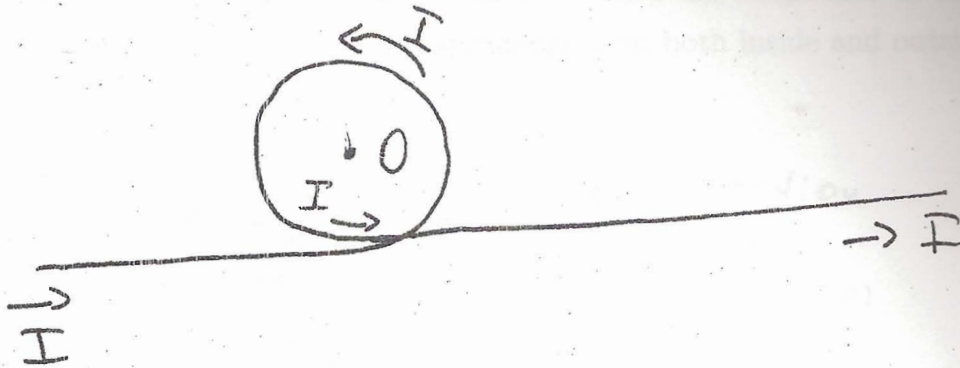


Figure 4

### Problem 5

An infinite cylindrical conductor with the radius  $R$  carries a non-uniform, but cylindrically symmetric current density given by  $j(r) = \alpha r^2$  where  $\alpha$  is some given constant and  $r$  is the distance to the symmetry axis of the conductor (note:  $j$  depends only on  $r$  but not on any angles) Find the direction and the magnitude of the magnetic field as a function of the distance to the symmetry axis, both inside and outside the conductor.

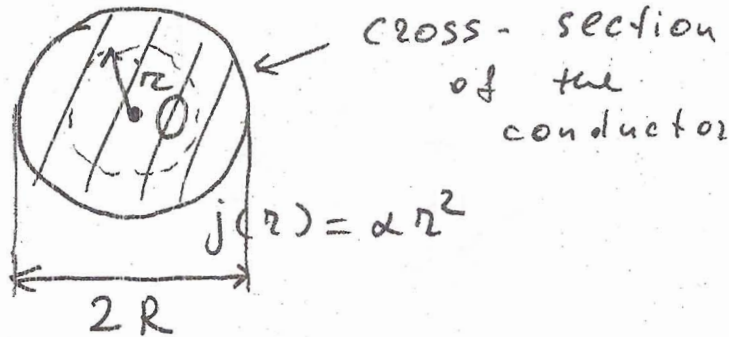


Figure 5

### Problem 6

A rectangular frame of the with the sides  $a$  and  $b$  is moving with constant velocity  $v$  away from the infinite straight conductor with the current  $I$ , as shown on the Figure 6. The sides  $AB$  and  $CD$  are always parallel to the conductor. The total resistance of the frame is equal to  $R$ . Find the magnitude and direction of the induced current in the frame as the function of the distance  $r$  between the conductor and the side  $AB$  of the frame.


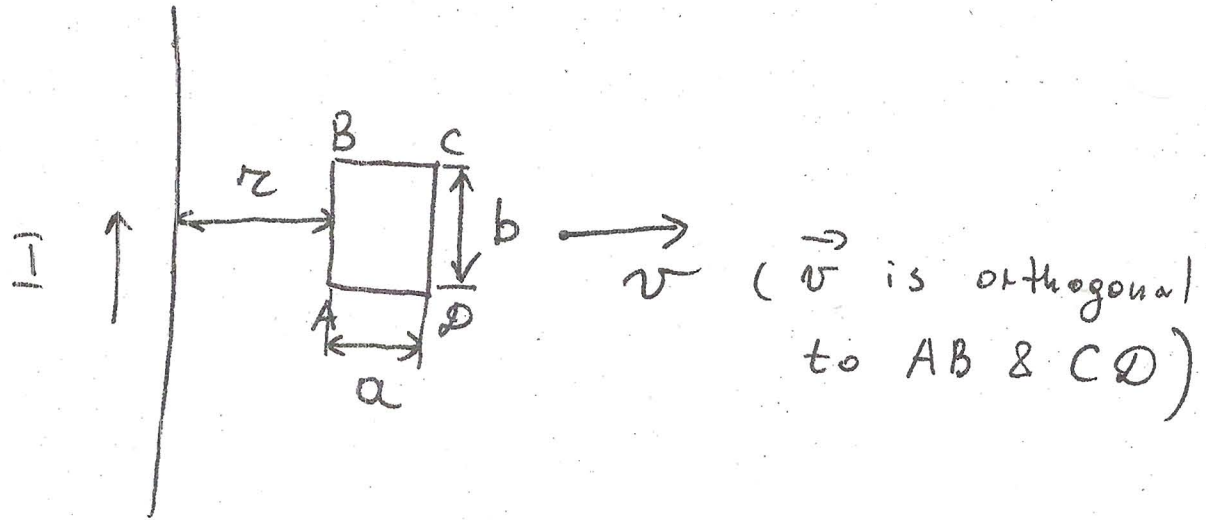


Figure 6

### Problem 7

An inductor  $L$  and a capacitor  $C$  are connected through the switch  $S$  to the battery with the constant voltage  $\Delta V$ , as shown on the Figure 7. switch is turned on at the moment  $t = 0$  and is then turned off at the moment of time  $t = t_0$  ( $t_0$  is given). 1) Find the current in the inductor and the charge on the plates of the capacitor at  $t = t_0$ . 2) After the switch is disconnected ( $t > t_0$ ) find the period of oscillations in the resulting LC-contour, the maximum value of the current in the coil and the maximum charge on the plates of the capacitor.

Figure 7

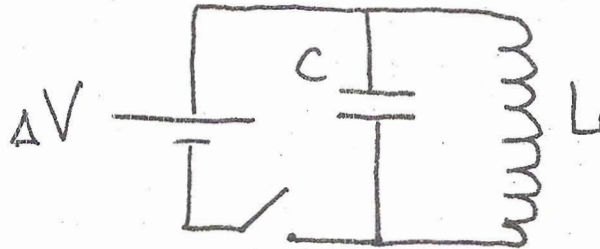



### Problem 8

[www.amal-aub.org](http://www.amal-aub.org) The alternating current source is connected in series to the resistor  $R$ , the inductor  $L$  and the capacitor  $C$ . The current leads the voltage by 60 degrees, the maximum value of the voltage is  $10V$  and the power delivered to the circuit is equal to  $50W$ . Find the values of the resistor  $R$  and of the difference  $X_L - X_C$ .

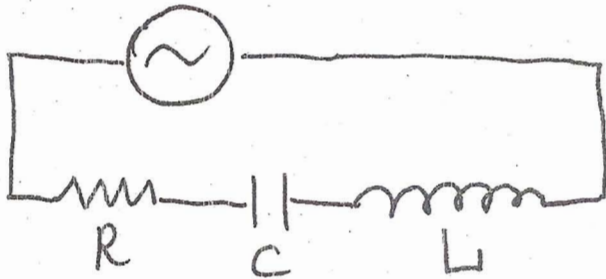


Figure 8