


Solution

American University of Beirut
Department of Electrical and Computer Engineering

EECE 320 – Digital Systems Design
 Test 3

14-11-2011

 A Half adder (HA) is a combinational circuit that adds two bits and generates a Sum bit and a Carry out bit.



1. Draw the truth table of this circuit, and derive minimal algebraic expressions for S and Cout.

X	Y	Cout	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C_{out} = XY$$

$$S = XY' + X'Y$$

2. Write the VHDL code to define the entity HA.

entity HA is
 port (X, Y: in std_logic;
 S, Cout: out std_logic);

3. Write the **Dataflow** architectural description for this entity.

architecture dataflow of HA is
 begin

Cout <= X and Y;

S <= (X and (Not Y)) OR ((Not X) AND Y);

end dataflow;