

Homework 7 - Solution

Problem 1

- Need state/output table and state diagrams

1) For JK flip-flops $Q^* = JQ' + K'Q$

A, B and C are the states of the circuit


$$\begin{aligned} J_A &= B+C \\ K_A &= 1 \end{aligned} \left\{ \begin{aligned} A^* &= JA' + K'A \\ \boxed{A^* &= (B+C)A'} \end{aligned} \right.$$

$$\begin{aligned} J_B &= C \\ K_B &= AC' \end{aligned} \left\{ \begin{aligned} B^* &= JB' + K'B \\ &= CB' + (A'+C)B \\ \boxed{B^* &= C + A'B} \end{aligned} \right.$$

$$\begin{aligned} J_C &= B' \\ K_C &= A \end{aligned} \left\{ \begin{aligned} C^* &= JC' + K'C \\ &= B'C' + A'C \end{aligned} \right.$$

Current State = ABC	$A^*B^*C^*$ = Next state
0 0 0 = L	0 0 1 = M
0 0 1 = M	1 1 1 = S
0 1 0 = N	1 1 0 = R
0 1 1 = O	1 1 1 = S
1 0 0 = P	0 0 1 = M
1 0 1 = Q	0 1 0 = N
1 1 0 = R	0 0 0 = L
1 1 1 = S	0 1 0 = N

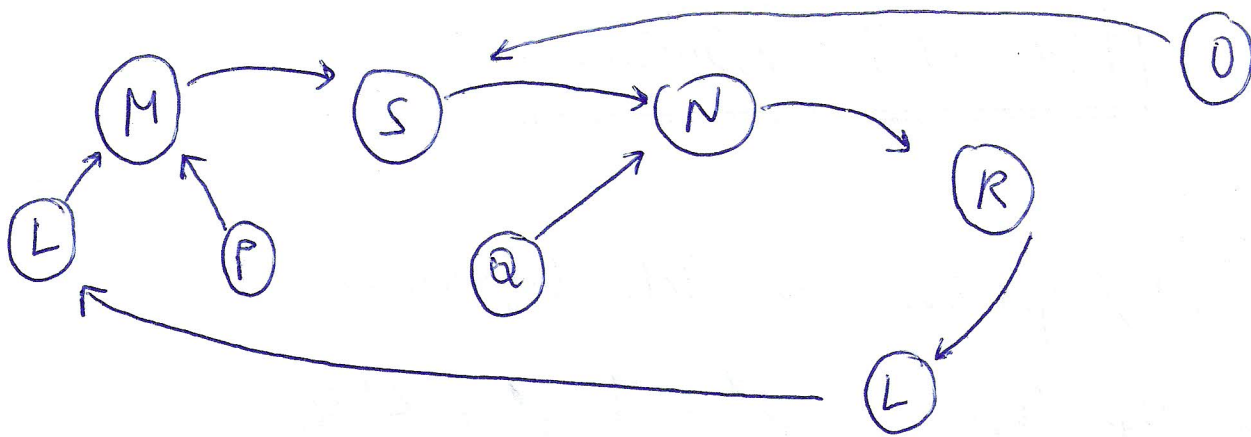← based on the equations that we just derived



2/ for D-flip flops $Q^* = D$.

$$D_A = 1 \cdot A' + 0 \cdot A = A' = D_A$$

$$\boxed{A^* = A'}$$

$$D_B = (U'A' + UA) \oplus B$$

$$= (U'A' + UA) \oplus B$$

$$\rightarrow \boxed{B^* = D_B}$$

$$D_C = (U'A'B' + UAB) \oplus C \rightarrow \boxed{C^* = D_C}$$

	A	B	C	U					
				0			1		
S ₀	0	0	0	1	1	1	1	0	0
S ₁	0	0	1	1	1	0	1	0	1
S ₂	0	1	0	1	0	0	1	1	0
S ₃	0	1	1	1	0	1	1	1	1
S ₄	1	0	0	0	0	0	0	1	0
S ₅	1	0	1	0	0	1	0	1	1
S ₆	1	1	0	0	1	0	0	0	1
S ₇	1	1	1	0	1	1	0	0	0

$$A^* B^* C^*$$

State/output table			U	
state	0	1		
S ₀	S ₇	S ₄		
S ₁	S ₆	S ₅		
S ₂	S ₄	S ₆		
S ₃	S ₅	S ₇		
S ₄	S ₀	S ₂		
S ₅	S ₁	S ₃		
S ₆	S ₂	S ₁		
S ₇	S ₃	S ₀		

$$state^*$$

do the circuit diagram (---)

Problem 2

input = X
output = Y

$Y=1$ if 1011

+ moore design

- D ffs.

state	0	1	Y
initial	initial	Get 1	0
Get 1	Get 10	Get 1	0
Get 10	initial	Get 101	0
Get 101	Get 10	Get 1011	0
Get 1011	Get 10	Get 10111	0
Get 10111	Get 10	Get 1	1

Next state

ABC	0	1	Y
000	000	001	0
001	010	001	0
010	000	011	0
011	010	100	0
100	010	101	0
101	010	001	1

Note:
used minimum
cost
design

$A^* B^* C^*$

A^*	B^*	C^*	
00	01	11	10
01		d	
01		d	
11	1	d	1
10		d	

$$A^* = AC'X + BCX$$

$$Y = AC'X + BCX + AC'$$

$$Y = AC'X + BCX$$

~~Handwritten text~~

B^* :

AB \ CX	00	01	11	10
00			1	1
01		1	1	
11			1	
10	1	1	1	1

$$B^* = CX' + AX' + BCX$$



C^*

AB \ CX	00	01	11	10
00			1	
01	1	1	1	1
11	1		1	1
10			1	


$$C^* = C'X + B'X$$

Since $Q^* = D$

$$Y = AB'C$$

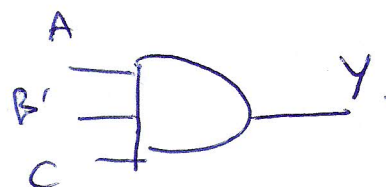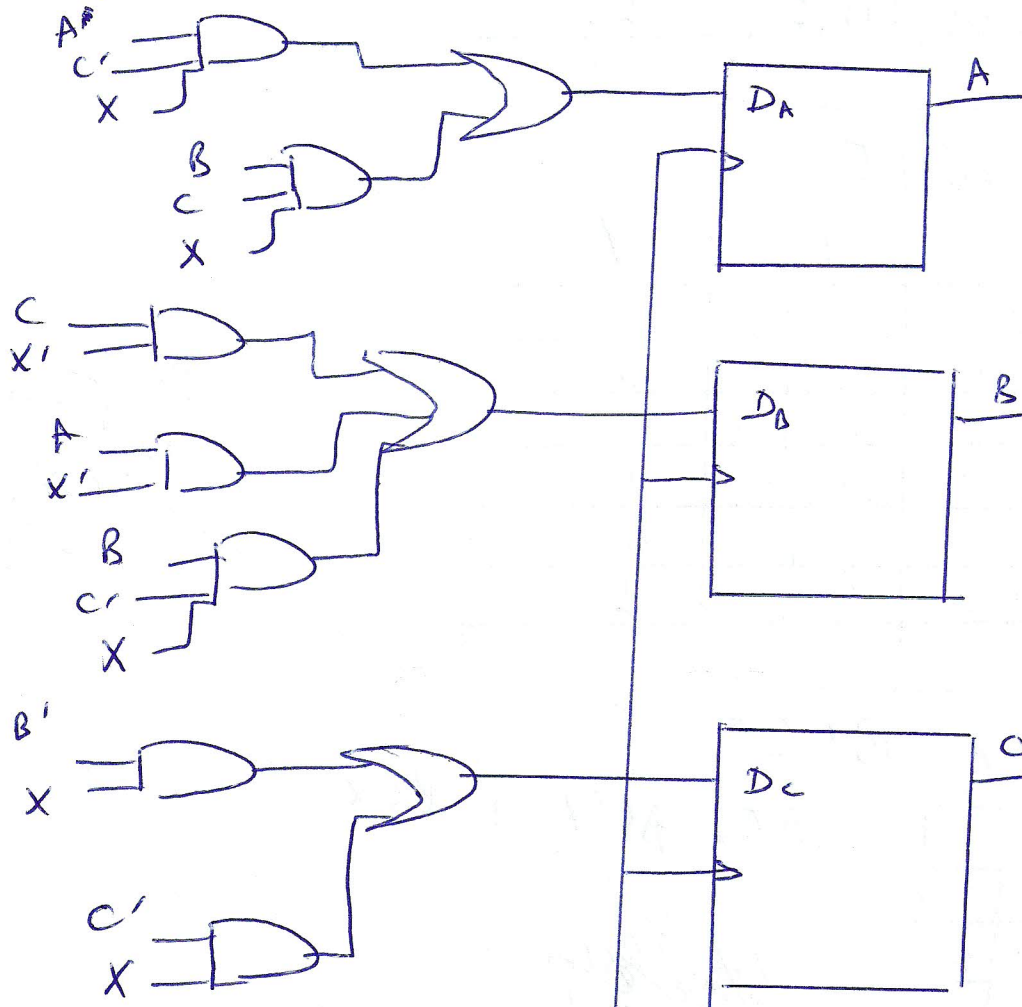

Problem 3

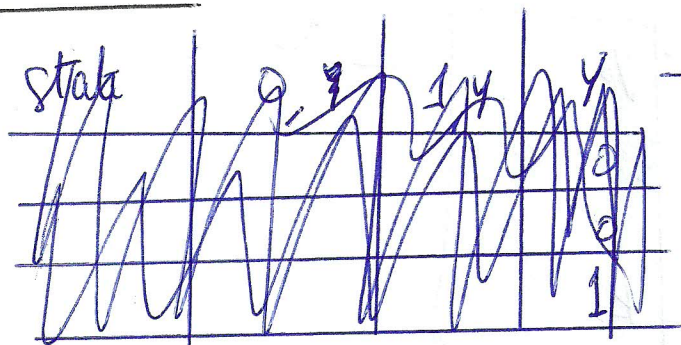

state/output table

state	0	1
S_0	$S_0, 0$	$S_1, 0$
S_1	$S_2, 0$	$S_0, 0$
S_2	$S_1, 1$	$S_0, 1$

state*, Y

transition/output table

Q_1, Q_0	0	1
0 0	00, 0	01, 0
0 1	10, 0	00, 0
1 0	01, 1	00, 1

Q, Q^*	J, K
0 0	0 d
0 1	1 d
1 0	d 1
1 1	d 0

excite table Q_1^*, Q_0^*, Y

Q_1, Q_0	0	1
0 0	0d, 0d, 0	0d, 1d, 0
0 1	1d, d1, 0	0d, d1, 0
1 0	d1, 1d, 1	d1, 0d, 1

$J_1^*, K_1^*, J_0^*, K_0^*, Y$

Need to find the expressions for $J_1^*, K_1^*, J_0^*, K_0^*$ and Y.

$$K_1^* = K_0^* = 1$$

using K-map \rightarrow

$$J_1 = Q_0 x'$$

$$J_0 = x \oplus Q_1$$

$$Y = Q_1$$

