

Midterm Solution**Problem 1: [20 points]**

1. very high speed integrated circuit hardware description language
2. true
3. true
4. $XY + XZ' = XY + X'Z + YZ$
5. 1101001 (maintain same number of bits)
6. 3122.22
7. false
8. $2^p X + 2^p - 1$
9. false
10. true
11. false
12. 2^{15}
13. entity decoder is

```
port ( a: in std_logic_vector(1 downto 0);
      b: out std_logic_vector (3 downto 0)
    );
end decoder;
```
14. architecture prime4_arch of prime is

```
begin
with N select Y <=
'1' when "0001" | "0010" | "0011" | "0101" | "0111" | "1011" | "1101",
'0' when others;
end prime4_arch;
```
15. architecture V2to4dec_b of V2to4dec is

```
signal Y_s: in std_logic_vector (0 to 3);
begin
process (IN, EN)
begin
case IN is
when "00" => Y_s <= "1000";
when "01" => Y_s <= "0100";
when "10" => Y_s <= "0010";
when "11" => Y_s <= "0001";
when others => Y_s <= "0000";
end case;

if EN = '1' then Y <= Y_s;
else Y <= "000";
```

```

        end if;
    end process;
end V2to4dec_b;

```

16. $F^D = (X' + Y' + Z)(X' + Y + Z)(X + Y' + Z)(X + Y + Z)$
 $= \prod(0,2,4,6) = F$

(it turns out that F is self dual)

17. possibility of a circuit producing a 0 glitch when the output is expected to remain at 1

18. 1

19. minimal sum is a sum of prime implicants

20. adjacent number differ by exactly one bit

Problem 2: [8 points]

$$F = \sum_{A,B,C,D}(1,3,4,5,10,11,12,13,14,15)$$

K-map:

	AB	00	01	11	10
CD					
00			1	1	
01		1	1	1	
11		1		1	1
10				1	1

a) prime implicants: BC' , AC , $B'CD$, $A'C'D$, $A'B'D$, AB

b) essential prime implicants: BC' , AC


c) minimum SOP expression: $BC' + AC + A'B'D$

d) minimum POS expression: $(A + B' + C')(A' + B + C)(A + B + D)$

Problem 3: [6 points]

$$F = (X_1 + X_2')(X_2 + X_3)$$


Gate implementation:

 


- a) static-0 Hazard
- b) $000 \rightarrow 010$
- c) Add an extra OR gate with inputs X_1 and X_3

Problem 4: [10 points]

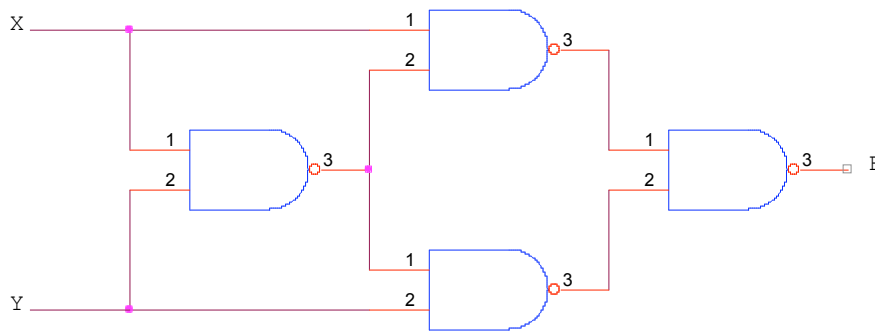- a) We want to implement $F = A \text{ XOR } B$ using minimum NAND gates:



- b) Recall that for a 1-bit adder:
 $S = A \text{ XOR } B \text{ XOR } C_{in}$
 $C_{out} = AC_{in} + BC_{in} + AB$

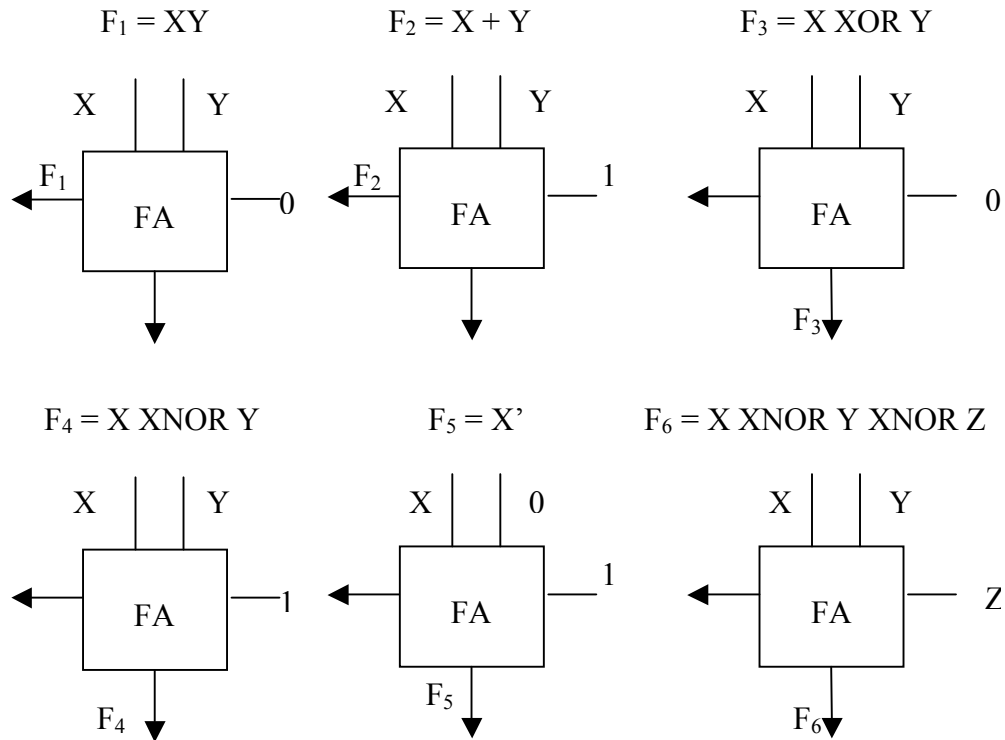

Problem 5: [10 points]

$$F(a,b,c,d,e,f,g,h) = a'b'c'd + ag'h + ag + a'b'ce + a'bf'$$

So $F = aF(a = 1) + a'F(a = 0)$ by Shannon's theorem

$$F(a = 1) = g'h + g = G$$


$$F(a = 0) = b'c'd + b'ce + bf' = H$$

$G = g(1) + g'h$: implemented using a mux having inputs 1 and h and select signal g

$H(b,c,d,e,f) = bH(b = 1) + b'H(b = 0)$: mux with inputs $H(b = 1)$ and $H(b = 0)$ and select signal b

$H(b = 1) = f' = f(0) + f'(1)$: mux with inputs 0 and 1 and select signal f

$H(b = 0) = c'd + ce$: mux with inputs d and e and select signal c

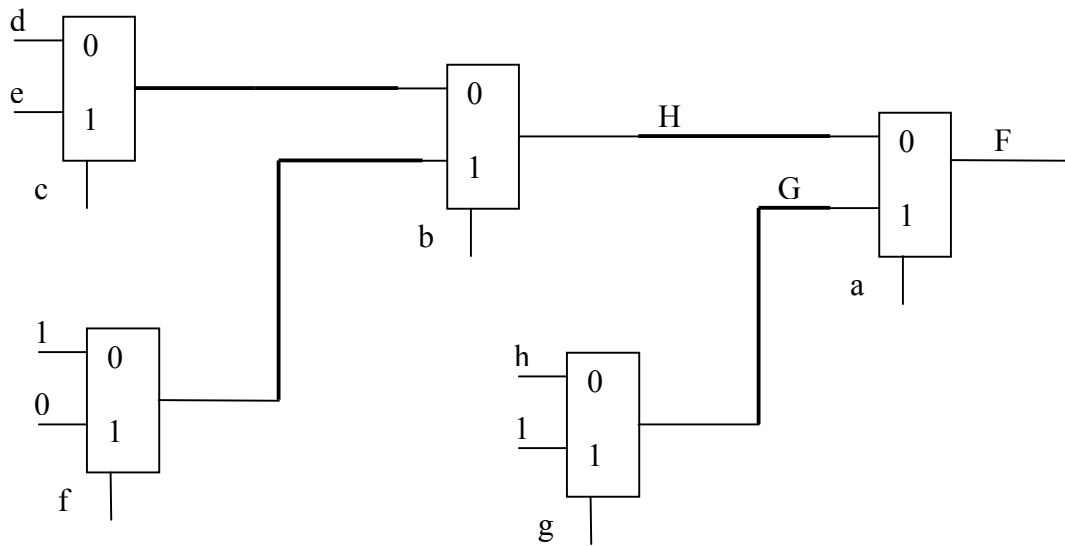

Problem 6: [10 points]

Let $D = D_3D_2D_1D_0$


We get the following truth table for the 4-bit majority function F:

D_2	D_1	D_0	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	D_3
1	0	0	0
1	0	1	D_3
1	1	0	D_3
1	1	1	1

This table can be further developed as follows:


D_2	D_1	F
0	0	0
0	1	D_2D_3
1	0	D_2D_3
1	1	$D_2 + D_3$

We obtain the following logic circuit:

 


Problem 7: [8 points]

a)

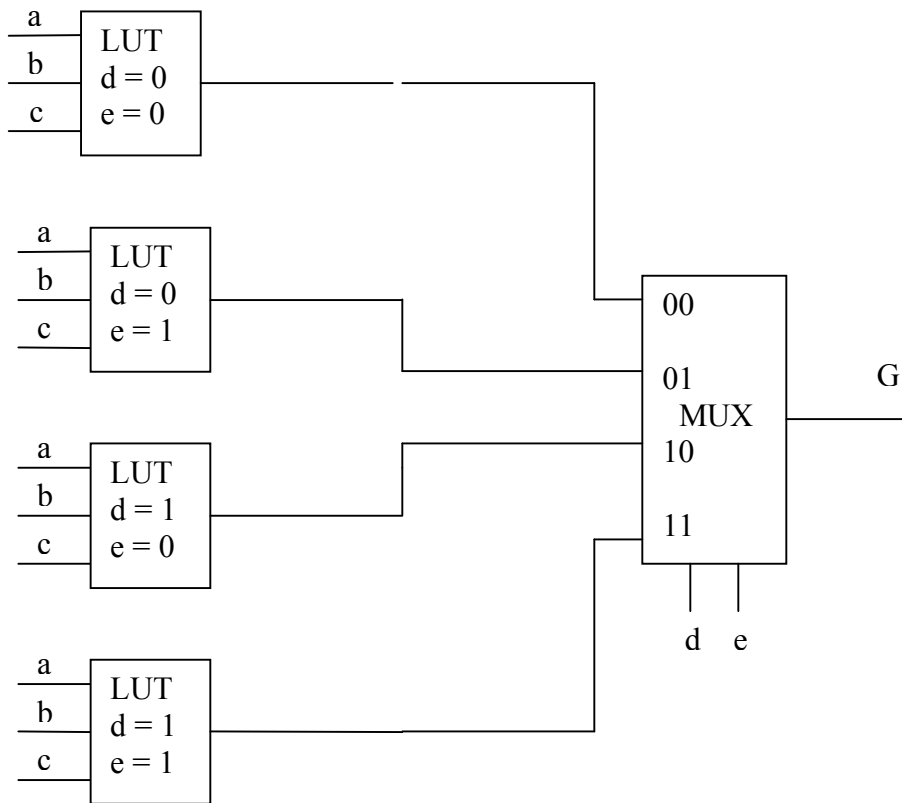


b)

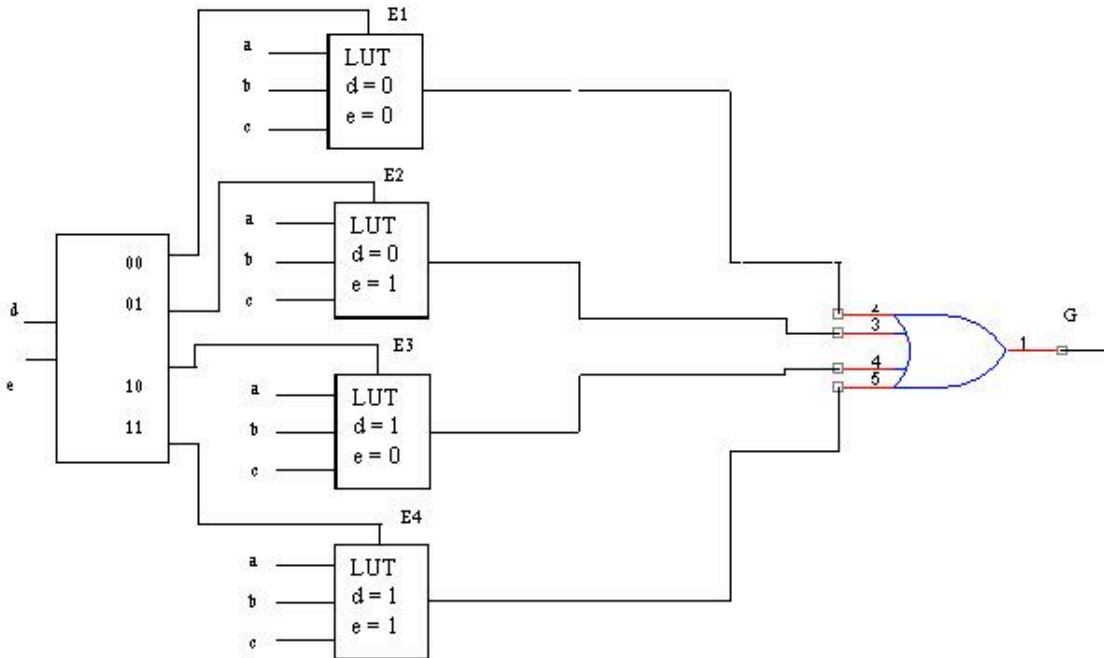

Problem 8: [10 points]

The ABS block is designed as follows:

 

Alternatively, the mux can be placed outside the block.
Set the carry input of the rightmost block to 0.

Problem 9: [8 points]

$$\text{Let } L(W,X,Y,Z) = WY + W'YZ' + WXZ + W'XY'$$

$$R(W,X,Y,Z) = WY + W'XZ' + X'YZ' + XY'Z$$

$$L(W = 0) = YZ' + XY'$$

$$L(W = 1) = Y + XZ$$

$$R(W = 0) = XZ' + X'YZ' + XY'Z$$

$$= (X + X'Y)Z' + XY'Z = XZ' + YZ' + XY'Z$$

$$= X(Z' + Y'Z) + YZ' = XZ' + XY' + YZ' = XY' + YZ' \text{ (By consensus)}$$

$$= L(W = 0)$$


$$R(W = 1) = Y + X'YZ' + XY'Z = Y + XY'Z = Y + XZ = L(W = 1)$$

Therefore $L = R$


Problem 10: [16 points]

We first build the 8-to-3 encoder from 4-to-2 encoders, and 3-to-8 decoders from 2-to-4 decoders.

8-3 encoder:

 

3-8 decoder:

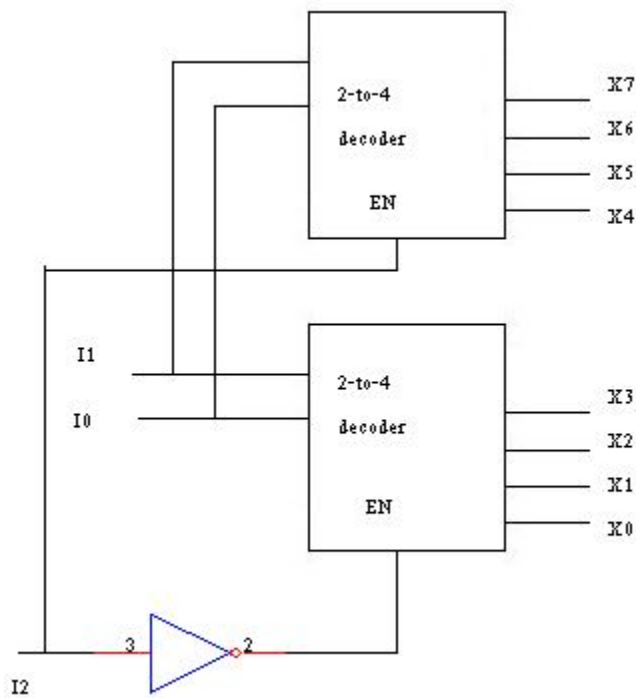

To put it all together: the input $A_7A_6\dots A_0$ is connected to a first 8-to-3 encoder. The output signals of this encoder, $B_2B_1B_0$ identifies the inputs with highest priority respectively. E_0B is asserted if a highest priority input is detected. We connect $B_2B_1B_0$ to the input of a 3-to-8 decoder. The output signals of this decoder are active-low and each one is ANDed with the respective bit from the original input A. The result of the AND gates is inputted into a second 8-to-3 priority encoder with output signals $C_2C_1C_0$, which identifies the inputs with second highest priority respectively, and EOC which is asserted if a second highest priority input is detected.

The encoders and the decoder share the same enable signal EN.

Problem 11: [16 points]

```

Entity comp1 is
port (      A, B: in std_logic;
          EQi: in std_logic;
          EQo : out std_logic);
End comp1;

```

```

Architecture comp1 of comp1 is
Signal X, XN: std_logic;
Begin
    X<= A XOR B;
    XN <= NOT X;
    EQo <= EQi AND XN;
End comp1;

```

```

Entity comp8 is
Port (      A,B: in std_logic_vector(7 downto 0);
          EQi: in std_logic;
          EQo: out std_logic);
End comp8;

```

```

Architecture comp8 of comp8 is
Signal EQ: std_logic_vector(8 downto 0);
Component comp1
port (      A, B: in std_logic;
          EQi: in std_logic;
          EQo : out std_logic);
End component;

```

```

Begin
    For i in 0 to 7 generate
        U1: comp port map (A(i), B(i), EQ(i), EQ(i + 1));
    End generate;
EQ(0) <= EQi;
EQo <= EQ(8);
End comp8;

```

Testbench:

Plug in the following values:

```

A<=0x"23"; B<=0x"32"; wait for 10 ns;
A<=0x"34"; B<=0x"34"; wait for 10 ns;
A<=0x"FF"; B<=0x"00"; wait for 10 ns;

```