

Homework 2

P10.2.4 In the circuit of Figure P10.2.4, the magnitude of the transfer function is unity at 1 Mrad/s and zero at 0.5 Mrad/s. Determine L_1 and L_2 .

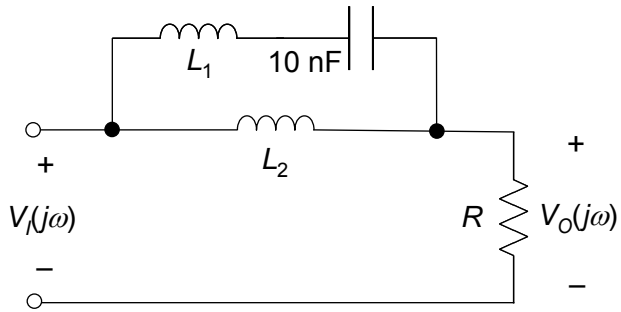


Figure P10.2.4

Solution P10.2.4 At 1 Mrad/s, L_1 is in

series resonance with the 10 nF capacitor; hence $L_1 = \frac{1}{10^{-8} \times 10^{12}} = 10^{-4}$ H, so $L_1 =$

0.1 mH. At 0.5 Mrad/s, the reactance of L_1 and C is capacitive and is in parallel resonance with L_2 . The reactance of L_1 and C at 0.5 Mrad/s is $0.5 \times 10^6 \times 10^{-4} -$

$\frac{1}{0.5 \times 10^6 \times 10^{-8}} = 50 - 200 = -150$; hence, $0.5 \times 10^6 \times L_2 = 150$, or $L_2 = \frac{150}{0.5 \times 10^6} =$

$300 \times 10^{-6} = 0.3$ mH.

P10.2.7 Determine: (a) the transfer function of the circuit of Figure P6.10.2.7; (b) the resonant frequency; (c) the Q; and (d) the bandwidth.

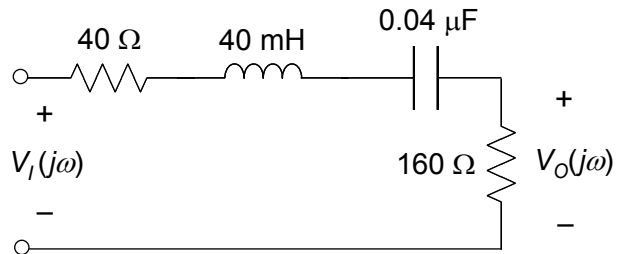


Figure P10.2.7

Solution P10.2.7 (a) $H(s) = \frac{160}{0.04s + 200 + \frac{1}{s \times 0.04 \times 10^{-6}}} = \frac{4000s}{s^2 + 5000s + 625 \times 10^6} =$

$$\frac{4s}{s^2 + 5s + 625}, \text{ where } s \text{ is in krad/s.}$$

(b) $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{40 \times 10^{-3} \times 4 \times 10^{-8}}} = 25$ krad/s.

(c) $Q = \frac{\omega_0 L}{R} = \frac{25 \times 10^3 \times 0.04}{200} = 5$; (d) $BW = \frac{\omega_0}{Q} = \frac{25}{5} = 5$ krad/s.

P10.2.9 Given the circuit of Figure P10.2.9, where k is a positive constant. Determine Q when: (a) $k = 1$; (b) k is very large. What is the interpretation of the value of Q when k is large?


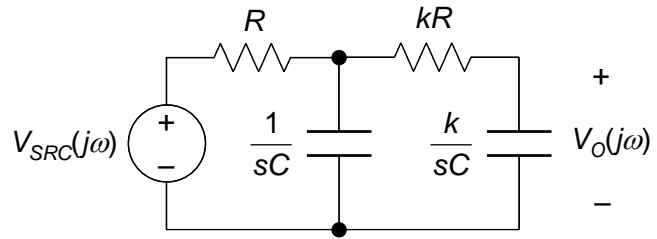


Figure P10.2.9

Solution P10.2.9 Q can be determined from the denominator in standard form of the transfer function $V_O(j\omega)/V_{SRC}(j\omega)$. The transfer function can be determined from node-voltage analysis, mesh-current analysis, or voltage division.

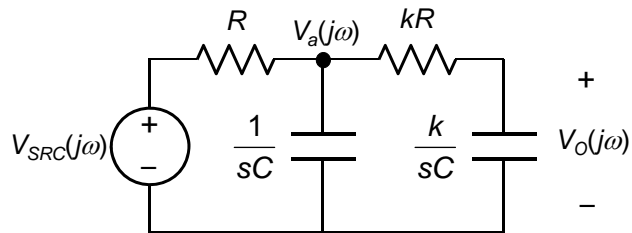To apply voltage division, the parallel impedance of the three branches between V_a and ground is:



$$\frac{1/sC(kR + k/sC)}{kR + (k+1)/sC} =$$

$$\frac{1}{sC} \frac{(1+sCR)}{(1+1/k)+sCR}. \text{ It follows that: } \frac{V_a(j\omega)}{V_{SRC}(j\omega)} = \frac{\frac{1}{sC} \frac{(1+sCR)}{(1+1/k)+sCR}}{R + \frac{1}{sC} \frac{(1+sCR)}{(1+1/k)+sCR}} =$$

$$\frac{(1+sCR)}{1+(2+1/k)sCR+s^2C^2R^2}; \frac{V_O(j\omega)}{V_a(j\omega)} = \frac{k/sC}{kR+k/sC} = \frac{1}{1+sCR}. \text{ Hence,}$$

$$\frac{V_O(j\omega)}{V_{SRC}(j\omega)} = \frac{1}{s^2C^2R^2 + (2+1/k)sCR + 1} = \frac{1/C^2R^2}{s^2 + (2+1/k)s/CR + 1/C^2R^2}. \text{ This is of the}$$

standard form for a second-order low-pass filter $\frac{\omega_n^2}{s^2 + (\omega_n/Q)s + \omega_n^2}$, where $\omega_n = 1/CR$

and $Q = 1/(2+1/k)$.

(a) If $k = 1$, $Q = 1/3$.

(b) if k is very large, $Q = 1/2$. The interpretation is that when k is large, the circuit composed of kR and C/k has a negligible loading effect on the first circuit. The two circuits, of identical time constant RC , are cascaded but effectively isolated. The overall transfer function becomes:

$$\frac{V_O(j\omega)}{V_{SRC}(j\omega)} = \frac{1}{(1+sCR)^2} = \frac{1}{1+2sCR+s^2C^2R^2} = \frac{1/C^2R^2}{s^2 + 2s/CR + 1/C^2R^2}, \quad Q = 1/2.$$

P10.2.10 In Figure P10.2.10, the response $I_C(j\omega)/I_{SRC}(j\omega)$ is to remain at -3dB at the same frequency, whether the switch is opened or closed. (a)

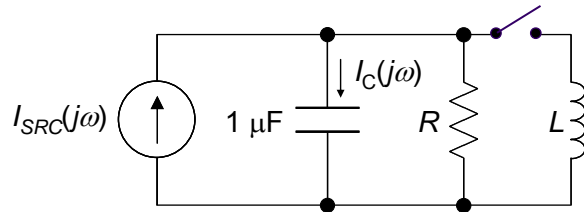


Figure P10.2.10

Determine R and the corner

frequency, assuming $L = 20$ mH. (b)

Calculate the response in dB at one-tenth the corner frequency for the two cases when the switch is open or closed.

Solution P10.2.10 (a) When the switch is open, $\frac{I_C(s)}{I_{SRC}(s)} = \frac{sCR}{1 + sCR} = \frac{1}{1 + 1/sCR}$, and $\omega_{ch} =$

$$\frac{1}{CR} = \frac{10^6}{R}. \text{ When the}$$

switch is closed,

$$\frac{I_C(s)}{I_{SRC}(s)} = \frac{sC}{sC + \frac{1}{R} + \frac{1}{sL}} =$$

$$\frac{s^2}{s^2 + \frac{s}{CR} + \frac{1}{LC}}; H(j\omega) = \frac{\omega^2}{\sqrt{\left(\omega^2 - \frac{1}{LC}\right)^2 + \left(\frac{\omega}{CR}\right)^2}}. \text{ At } \omega = \omega_{ch}, |H(j\omega)| = \frac{1}{\sqrt{2}} \text{ or}$$

$$2\omega_{ch}^4 = \omega_{ch}^4 - \frac{2\omega_{ch}^2}{LC} + \frac{1}{L^2C^2} + \frac{\omega_{ch}^2}{C^2R^2}. \text{ Substituting } \omega_{ch}^2 = \frac{1}{C^2R^2} \text{ gives: } \omega_{ch}^2 = \frac{1}{2LC}.$$

$$\text{With } C = 10^{-6} \text{ F and } L = 2 \times 10^{-2} \text{ H, } \omega_{ch} = 5 \text{ krad/s and } R = \frac{10^6}{\omega_{ch}} = \frac{10^6}{5 \times 10^3} = 200 \Omega.$$

(b) At $\omega_{ch}/10$, the response when the switch is open is $20 \log_{10} \frac{1}{\sqrt{1 + (\omega_{ch}/\omega)^2}} =$

$$20 \log_{10} \frac{1}{\sqrt{101}} = -20.04 \text{ dB. When the switch is closed, } \frac{1}{LC} = 2\omega_{ch}^2 \text{ and } \frac{1}{CR} = \omega_{ch}.$$

$$\text{This gives: } |H(j0.1\omega_{ch})| = \frac{1}{\sqrt{\left(1 - \frac{1}{\omega^2 LC}\right)^2 + \left(\frac{1}{\omega CR}\right)^2}} =$$

$$\frac{1}{\sqrt{\left(1 - \frac{2\omega_{ch}^2}{(0.1\omega_{ch})^2}\right)^2 + \left(\frac{\omega_{ch}}{0.1\omega_{ch}}\right)^2}} = \frac{1}{199.25}, \text{ and } 20 \log_{10} \frac{1}{199.25} = -46 \text{ dB.}$$

P10.3.3 Derive the transfer function of the circuit shown in Figure P10.3.3, and determine L and C so as to have a second-order, lowpass, normalized, Butterworth response. Scale the parameters so as to have $R_L = 10 \text{ k}\Omega$ and the 3-dB frequency $f_0 = 10 \text{ kHz}$.

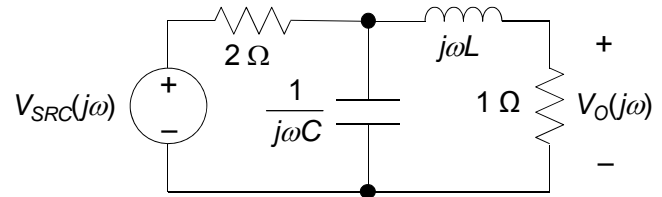


Figure P10.3.3

Solution P10.3.3 The impedance of C in parallel with L and R_2 is: $Z_p = \frac{(sL + R_2) / sC}{sL + R_2 + 1 / sC} =$

$$\frac{sL + R_2}{s^2LC + sCR_2 + 1}. \text{ It follows that: } \frac{V_O}{V_{SRC}} = \frac{Z_p}{R_1 + Z_p} \frac{R_2}{sL + R_2} =$$

$$\frac{R_2}{LCR_1} \frac{1}{s^2 + s\left(\frac{1}{CR_1} + \frac{R_2}{L}\right) + \frac{1}{LC} \frac{R_1 + R_2}{R_1}} \text{ Substituting } R_1 = 2 \Omega \text{ and } R_2 = 1 \Omega, \text{ the}$$

denominator becomes: $s^2 + s\left(\frac{1}{2C} + \frac{1}{L}\right) + \frac{3}{2LC}$. For a Butterworth response, $LC = \frac{3}{2}$

and $\frac{1}{2C} + \frac{1}{L} = \sqrt{2}$. Substituting $\frac{1}{2C} = \frac{L}{3}$, gives $\frac{L}{3} + \frac{1}{L} = \sqrt{2}$, or $L^2 - 3\sqrt{2}L + 3 = 0$.

Hence, $L = \frac{\sqrt{6}}{2}(\sqrt{3} \pm 1)$ H and $C = \frac{\sqrt{6}}{4}(\sqrt{3} \mp 1)$ F.

To scale, $R_L = R_2$ to $10 \text{ k}\Omega$, $k_m = 10^4$. For a normalized butterworth response, the 3-dB cut-off frequency is 1 rad/s. To scale $f_n = 10 \text{ kHz}$, $k_f = 2\pi \times 10^4$; hence,

$$L' = \frac{k_m}{k_f} L \equiv \frac{\sqrt{6}}{4\pi}(\sqrt{3} \pm 1) \text{ H and } C' = \frac{1}{k_m k_f} C \equiv \frac{5\sqrt{6}}{4\pi}(\sqrt{3} \mp 1) \text{ nF.}$$

Note that for a Butterworth filter, the corner frequency is the same as the -3dB cutoff frequency, the latter being always the same as the half-power frequency.

P10.4.4 Given the straight-line, Bode plot approximation of Figure P10.4.4. Determine: (a) the X dB level; (b) the transfer function approximated by this Bode plot.

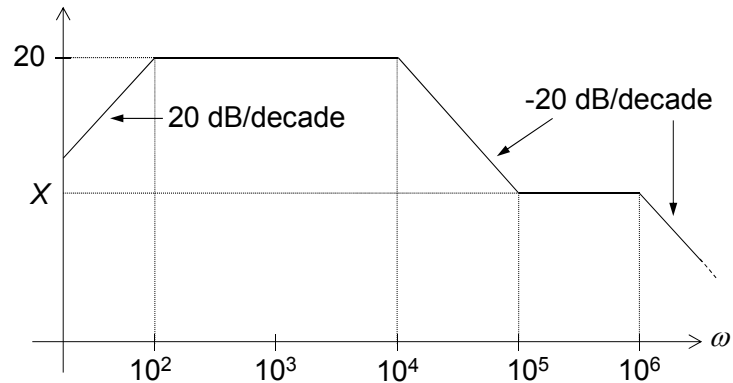


Figure P10.4.4

Solution P10.4.4 (a) Since the plot drops 20 dB in a decade from the 20 dB level, X must be at 0 dB.

(b) The response from very low frequencies up to $\omega = 10^4$ rad/s is a first-order high-pass response having $\omega_{ch} = 10^2$ rad/s. The transfer function up to $\omega = 10^4$ rad/s is

of the form $K \frac{j\omega}{j\omega + \omega_{ch}} = K \frac{s}{s + 10^2}$. At $\omega = 10^4$ rad/s there is a response of the

form $\frac{1}{j\omega + 10^4} = \frac{1}{s + 10^4}$ so that a corner frequency is obtained at $\omega = 10^4$ rad/s,

the response is 0 dB for $\omega < 10^4$ rad/s and the response decreases at a rate of -20 dB/decade for $\omega > 10^4$ rad/s. At $\omega = 10^5$ rad/s there is a response of the form $j\omega + 10^5 = s + 10^5$, so that a corner frequency is obtained at $\omega = 10^5$ rad/s, the response is 0 dB for $\omega < 10^5$ rad/s and the response increases at a rate of +20 dB/decade for $\omega > 10^5$ rad/s so as to give a horizontal asymptote $\omega > 10^5$ rad/s.

At $\omega = 10^6$ rad/s there is a response of the form $\frac{1}{j\omega + 10^6} = \frac{1}{s + 10^6}$ so that a corner frequency is obtained at $\omega = 10^6$ rad/s, the response is 0 dB for $\omega < 10^6$ rad/s and the response decreases at a rate of -20 dB/decade for $\omega > 10^6$ rad/s.

The transfer function is of the form: $H(s) = \frac{Ks(s + 10^5)}{(s + 100)(s + 10^4)(s + 10^6)}$. To

determine K, we note that at very low frequencies, $H(s) \approx \frac{Ks \times 10^5}{10^2 \times 10^4 \times 10^6}$. The

line passes through the point (100 rad/s, 20 dB) so that $|H(s)| = 10$ at $\omega = 100$

rad/s. This gives $K = \frac{10 \times 10^{12}}{10^2 \times 10^5} = \frac{10^{13}}{10^7} = 10^6$.