

## EECE 290 Analog Signal Processing – Quiz 2

April 9, 2011

1. The initial values at  $t = 0$  of  $i_L$  and  $i_R$  are:  $i_L = 0$  and

$i_R = K$  A. Determine  $\frac{di_L}{dt}$  at  $t = 0$ .

**Solution:**  $v = L \frac{di_L}{dt}$ , where  $v = -10K$ . Substituting,

$$\frac{di_L}{dt} = \frac{v}{L} = -\frac{10K}{4} = -2.5K \text{ A/s.}$$



**Version 1:**  $K = 1$ ,  $\frac{di_L}{dt} = -2.5K = -2.5 \text{ A/s}$

**Version 2:**  $K = 2$ ,  $\frac{di_L}{dt} = -2.5K = -5 \text{ A/s}$

**Version 3:**  $K = 3$ ,  $\frac{di_L}{dt} = -2.5K = -7.5 \text{ A/s}$

**Version 4:**  $K = 4$ ,  $\frac{di_L}{dt} = -2.5K = -10 \text{ A/s}$

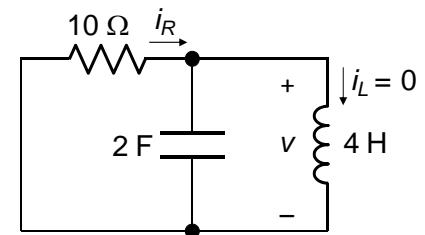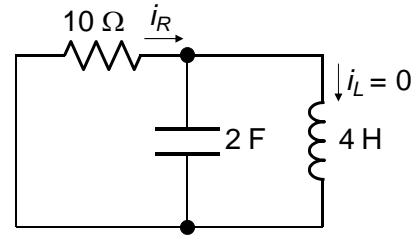**Version 5:**  $K = 5$ ,  $\frac{di_L}{dt} = -2.5K = -12.5 \text{ A/s}$



2. Determine  $\frac{di_R}{dt}$  at  $t = 0$  in Problem 1.

**Solution:**  $v = -10i_R$ ,  $\frac{di_R}{dt} = -\frac{1}{10} \frac{dv}{dt}$ ;  $\frac{dv}{dt} = \frac{i_C}{C} = \frac{i_R}{C} = \frac{K}{2}$ .

Substituting,  $\frac{di_R}{dt} = -\frac{K}{20} \text{ A/s} = -50K \text{ mA/s}$ .


**Version 1:**  $K = 1$ ,  $\frac{di_R}{dt} = -50K = -50 \text{ mA/s}$

**Version 2:**  $K = 2$ ,  $\frac{di_R}{dt} = -50K = -100 \text{ mA/s}$

**Version 3:**  $K = 3$ ,  $\frac{di_R}{dt} = -50K = -150 \text{ mA/s}$

**Version 4:**  $K = 4$ ,  $\frac{di_R}{dt} = -50K = -200 \text{ mA/s}$

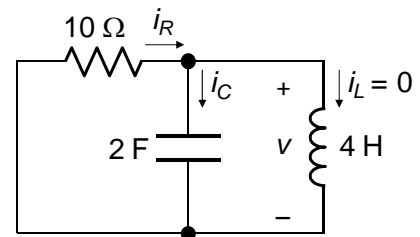**Version 5:**  $K = 5$ ,  $\frac{di_R}{dt} = -50K = -250 \text{ mA/s}$



3. Which of the following statements is true of the voltage  $v_C$  across  $C$  for large values of  $t$  in Problem 1?

**Version 1:**  $v_C$  approaches zero as an underdamped response

**Version 2:**  $v_C$  approaches a finite value as an underdamped response

**Version 3:**  $v_C$  approaches zero as an overdamped response

**Version 4:**  $v_C$  approaches a finite value as an overdamped response

**Version 5:**  $v_C$  approaches zero as a critically damped response


**Solution:** The circuit is a parallel circuit;  $\alpha_p = \frac{1}{2C_p R_p} = \frac{1}{2 \times 2 \times 10} = 0.025$ ;

$\omega_0 = \frac{1}{\sqrt{L_p C_p}} = \frac{1}{\sqrt{8}} = 0.354$ . Since  $\alpha_p$  is less than  $\omega_0$ , the response is oscillatory. Because of

the dissipating element, all responses in the circuit will eventually become zero. Hence,  $v_C$  approaches zero as an underdamped response.

4. A pulse of amplitude  $A$  units and 1 s duration, starting at the origin, is convolved with itself. Determine the value of the convolution integral at  $t = 1.8$  s.

**Solution:** Let the amplitude of the pulse be  $A$ . When one pulse is folded about the vertical axis and shifted by  $t = 1.8$  s, the graphical construction becomes as shown. The integration area is  $y(t) = A \times A \times 0.2 = 0.2A^2$ .

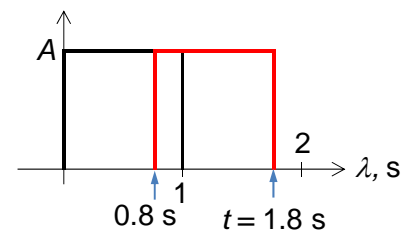

**Version 1:**  $A = 1$ ,  $y(t) = 0.2A^2 = 0.2 \times 1 = 0.2$

**Version 2:**  $A = 1.5$ ,  $y(t) = 0.2A^2 = 0.2 \times 2.25 = 0.45$


**Version 3:**  $A = 2$ ,  $y(t) = 0.2A^2 = 0.2 \times 4 = 0.8$

**Version 4:**  $A = 2.5$ ,  $y(t) = 0.2A^2 = 0.2 \times 6.25 = 1.25$

**Version 5:**  $A = 3$ ,  $y(t) = 0.2A^2 = 0.2 \times 9 = 1.8$

5. The delayed triangular pulse of unit height is convolved with the step function  $Au(t - 2)$ . Determine which of the following choices is a valid convolution integral for  $t \geq 5$  s.

**Solution:** Let the amplitude of the step be  $A$ . When the step is folded about the vertical axis and shifted by  $t = 5$  s, the graphical construction becomes as shown for  $A = 1$ . The integration area is  $A$  times the area of the triangle, which is 1. Thus,  $y(t) = Au(t - 5)$ , since this value is valid for  $t \geq 5$ .

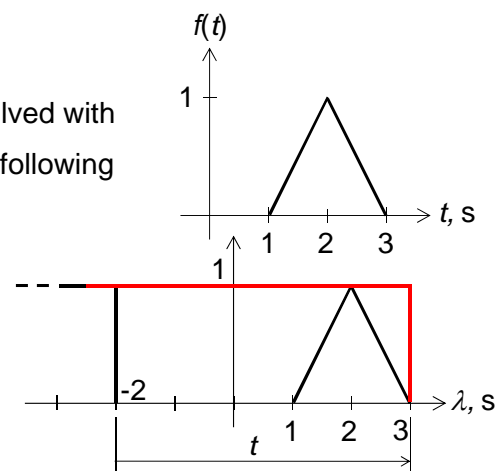

**Version 1:**  $A = 1$ ,  $y(t) = Au(t - 5) = u(t - 5)$

**Version 2:**  $A = 2, y(t) = Au(t - 5) = 2u(t - 5)$

**Version 3:**  $A = 3, y(t) = Au(t - 5) = 3u(t - 5)$


**Version 4:**  $A = 4, y(t) = Au(t - 5) = 4u(t - 5)$

**Version 5:**  $A = 5, y(t) = Au(t - 5) = 5u(t - 5)$

4%

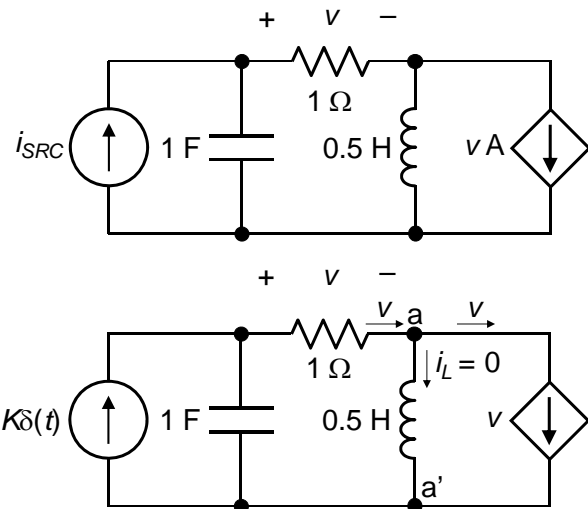**6.** Given that  $i_{SRC} = K\delta(t)$  As. Determine  $v$  as a function of  $t$  for  $t \geq 0^+$ .

**Solution:** The current through  $R$  is numerically equal to  $v$ , the same as the current of the dependent source. This makes  $i_L = 0$  and node  $a$  at the same voltage as  $a'$ . A current impulse  $K\delta(t)$  is thus applied to  $1 \Omega$  in parallel with  $1 F$ . At  $t = 0^+$ , the impulse deposits a charge  $K$  coulombs, which gives an initial voltage



$v(0) = K/1$  V across the capacitor. It follows that for  $t \geq 0^+$ ,  $v(t) = Ke^{-t}$  V.

**Version 1:**  $K = 0.5, v(t) = Ke^{-t} = 0.5e^{-t}$  V

**Version 2:**  $K = 1, v(t) = Ke^{-t} = e^{-t}$  V

**Version 3:**  $K = 1.5, v(t) = Ke^{-t} = 1.5e^{-t}$  V

**Version 4:**  $K = 2, v(t) = Ke^{-t} = 2e^{-t}$  V

**Version 5:**  $K = 2.5, v(t) = Ke^{-t} = 2.5e^{-t}$  V

**7.** Determine the quantity of charge that flows through the  $1 \text{ k}\Omega$  resistor, and its direction of flow, from when the switch is closed at  $t = 0$ , to  $t \rightarrow \infty$ , assuming  $v = 1$  V.

**Solution:**  $C_{eqs} = 1 \mu\text{F}$ ; the charge that flows through the  $1 \text{ k}\Omega$  resistor is the charge on this capacitor, which is  $q =$


$1 \times 3v \mu\text{C}$ . As a check, the initial charges on  $C_1$  and  $C_2$  are, respectively,  $2 \times v$  and  $2 \times 2v \mu\text{C}$ .

The final charges are  $2v - 3v = -v \mu\text{C}$  and  $4v - 3v = v \mu\text{C}$ , so the voltages are equal and opposite at  $-v/2$  and  $+v/2$ .

**Version 1:**  $v = 1, q = 3v = 3 \mu\text{C}$

**Version 2:**  $v = 2, q = 3v = 6 \mu\text{C}$

**Version 3:**  $v = 3, q = 3v = 9 \mu\text{C}$

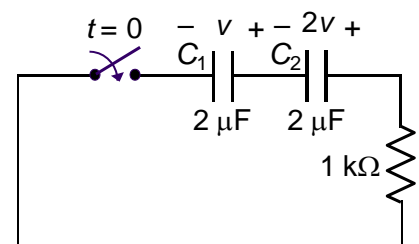

**Version 4:**  $v = 4$ ,  $q = 3v = 12 \mu\text{C}$

**Version 5:**  $v = 5$ ,  $q = 3v = 15 \mu\text{C}$

8. Determine the energy dissipated in the resistor from  $t = 0$  to  $t \rightarrow \infty$  in Problem 7.

**Solution: Method 1:** The power dissipated is that stored in  $C_{eqs}$ , where  $C_{eqs} = 1 \mu\text{F}$ , the initial voltage is  $3v$  and the charge on this capacitor is  $3v \mu\text{C}$ . The stored energy is  $w = qv/2 = 4.5v^2 \mu\text{J}$ .

**Method 2:** The initial current through the resistor is  $3v/1 = 3v \text{ mA}$ . As a function of time, the current is  $3ve^{-t/\tau} \text{ mA}$ , where  $\tau = (1 \mu\text{F}) \times (1 \text{ k}\Omega) = 1 \text{ ms}$ , so that  $t$  is in ms. The energy

dissipated is  $\int_0^\infty 9v^2 \times 1 \times e^{-2t/\tau} dt$ . The dimensions of the integrand are  $(\text{mA})^2 \times \text{k}\Omega \times \text{ms}$ , which

is  $\mu\text{J}$ . The value is  $\left[ -4.5v^2 e^{-2t/\tau} \right]_0^\infty = 4.5v^2 \mu\text{J}$ .

**Version 1:**  $v = 1$ ,  $w = 4.5v^2 = 4.5 \mu\text{J}$

**Version 2:**  $v = 2$ ,  $w = 4.5v^2 = 18 \mu\text{J}$

**Version 3:**  $v = 3$ ,  $w = 4.5v^2 = 40.5 \mu\text{J}$

**Version 4:**  $v = 4$ ,  $w = 4.5v^2 = 72 \mu\text{J}$

**Version 5:**  $v = 5$ ,  $w = 4.5v^2 = 112.5 \mu\text{J}$

9. The response of a circuit to a unit step is  $kte^{-t/10}$ , where  $t$  is in s. Determine the response at  $t = 10$  s to an impulse applied at  $t = 5$  s.

**Solution:** The response to an impulse at  $t = 0$  is the time derivative of the response to a unit impulse and is:  $ke^{-t/10} - (k/10)te^{-t/10}$ . The response to an impulse at  $t = 5$  s is

$ke^{-(t-5)/10} [1 - (t-5)/10]$ . The response at  $t = 10$  s is  $ke^{-(10-5)/10} [1 - (10-5)/10] = 0.5ke^{-0.5}$ .

**Version 1:**  $k = 1$ ,  $0.5ke^{-0.5} = 0.303$


**Version 2:**  $k = 2$ ,  $0.5ke^{-0.5} = 0.607$

**Version 3:**  $k = 3$ ,  $0.5ke^{-0.5} = 0.910$

**Version 4:**  $k = 4$ ,  $0.5ke^{-0.5} = 1.21$

**Version 5:**  $k = 5$ ,  $0.5ke^{-0.5} = 1.52$

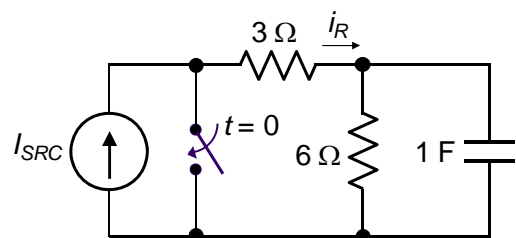10. The switch is closed at  $t = 0$  after being open for a long time. Determine  $i_R$  as a function of time, assuming  $I_{SRC} = 1 \text{ A}$ .



**Solution:** After the switch has been open for a long time,  $V_C = 6I_{SRC}$ . After the switch is closed, the initial value of  $i_R$  is  $-2I_{SRC}$ . The final value of  $i_R$  is zero. The time constant, with the switch closed, is  $(3||6) \times 1 = 2$  s. Hence,  $i_R =$

$$-2I_{SRC}e^{-t/2}$$


**Version 1:**  $I_{SRC} = 1$  A,  $i_R = -2I_{SRC}e^{-t/2} = -2e^{-t/2}$  A

**Version 2:**  $I_{SRC} = 2$  A,  $i_R = -2I_{SRC}e^{-t/2} = -4e^{-t/2}$  A

**Version 3:**  $I_{SRC} = 3$  A,  $i_R = -2I_{SRC}e^{-t/2} = -6e^{-t/2}$  A

**Version 4:**  $I_{SRC} = 4$  A,  $i_R = -2I_{SRC}e^{-t/2} = -8e^{-t/2}$  A

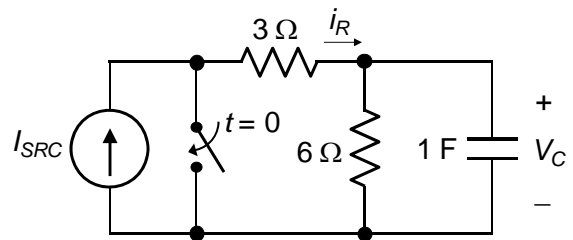**Version 5:**  $I_{SRC} = 5$  A,  $i_R = -2I_{SRC}e^{-t/2} = -10e^{-t/2}$  A




11. A current impulse of  $K$  mAs is applied at  $t = 0$ , with zero initial conditions.

6% (a) Determine the values of  $v_C$  and  $i_L$  at  $t = 0^+$ .

7% (b) Derive the form of the expression for  $i_L$  as a function of time for  $t > 0^+$  in terms of the two arbitrary constants of the differential equation. Assume that these arbitrary constants are unknown but specify the values of all other quantities in the expression for  $i_L$ .

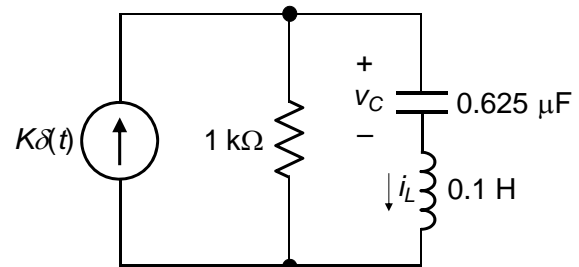7% (c) Determine the values of the arbitrary constants assuming,  $v_C = 200$  V and  $i_L = 1$  A at  $t = 0^+$ .



**Solution:** (a) The current source impulse in parallel with  $R \Omega$  can be transformed to a voltage source impulse of  $(KR)\delta(t)$  Vs in series with  $R$ . As argued in the book for a series  $RLC$  circuit, the voltage impulse appears across  $L$  and produces a jump in  $i_L$  equal to  $KR/L = K \times 10^{-3} \times 10^3 / (0.1) = 10K$  A. The finite jump in  $i_L$  does not change  $v_C$ , which remains at zero. Alternatively, it can be argued that the current impulse will flow through  $R$  and not through  $L$  and  $C$ . If the current impulse flows through  $L$  and  $C$ ,  $v_C$  will jump in value by a finite amount, and the voltage across  $L$  will change proportionately to  $\delta^{(1)}(t)$ . The voltage across  $L$  and  $C$  will be inconsistent with the voltage across  $R$ , which can be only be proportional to either  $\delta(t)$  or to a finite quantity.

The current impulse through  $R$  will cause a voltage impulse  $KR\delta(t)$  across  $R$ . This impulse will appear across  $L$  and cause a jump in current of  $KR/L$ .

(b) For  $t > 0^+$ , the source is zero, and the circuit reduces to a series  $RLC$  circuit.

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \times 0.625 \times 10^{-6}}} = 4 \text{ krad/s}; \alpha = \frac{R}{2L} = \frac{1000}{2 \times 0.1} = 5 \text{ krad/s. Since } \alpha > \omega_0, \text{ the}$$

response is overdamped,  $s_1 = -5 + \sqrt{5^2 - 4^2} = -2 \text{ krad/s}$  and  $s_2 = -5 - \sqrt{5^2 - 4^2} = -8 \text{ krad/s}$ . It follows that  $i_L = Ae^{-2t} + Be^{-8t} \text{ A}$ , where  $t$  is in ms.

(c) At  $t = 0^+$ ,  $A + B = 1$ ;  $q = -\frac{A}{2000} e^{-2000t} - \frac{B}{8000} e^{-8000t} \text{ C}$ , where the constant of integration

is zero since  $q \rightarrow 0$  as  $t \rightarrow \infty$ ; at  $t = 0^+$ ,  $v_C = \frac{q}{C} = \frac{A \times 10^3}{1.25} - \frac{B \times 10^3}{5}$  or

$$200 = -\frac{A \times 10^3}{1.25} - \frac{B \times 10^3}{5}, \text{ or } 4A + B = -1. \text{ This gives } A = -2/3 \text{ A and } B = 5/3 \text{ A.}$$

Alternatively,  $v_L = L \frac{di_L}{dt} = 0.1(-2Ae^{-2t} - 8Be^{-8t}) \text{ H} \times \text{A/ms}$ , or  $v_L = 100(-2Ae^{-2t} - 8Be^{-8t}) \text{ V}$ ,

or  $-v_L/100 = 2A + 8B$  at  $t = 0^+$ . But  $v_L + v_C + v_R = 0$ , or  $-v_L = v_C + v_R$ . This gives,  $2A + 8B = (200 + 1000)/100$ . Hence,  $A + 4B = 6$ , which gives the same values for  $A$  and  $B$ .

**Version 1:** (a)  $K = 0.1$ ;  $i_L(0^+) = 10K = 1 \text{ A}$ ,  $v_C(0^+) = 0$

**Version 2:** (a)  $K = 0.2$ ;  $i_L(0^+) = 10K = 2 \text{ A}$ ,  $v_C(0^+) = 0$

**Version 3:** (a)  $K = 0.3$ ;  $i_L(0^+) = 10K = 3 \text{ A}$ ,  $v_C(0^+) = 0$



**Version 4:** (a)  $K = 0.4$ ;  $i_L(0^+) = 10K = 4 \text{ A}$ ,  $v_C(0^+) = 0$

**Version 5:** (a)  $K = 0.5$ ;  $i_L(0^+) = 10K = 5 \text{ A}$ ,  $v_C(0^+) = 0$

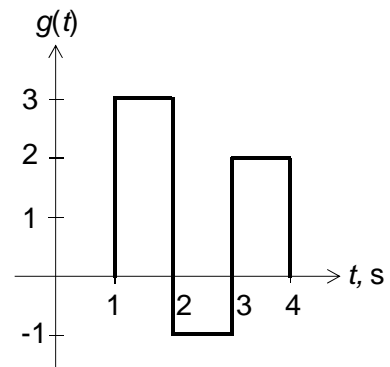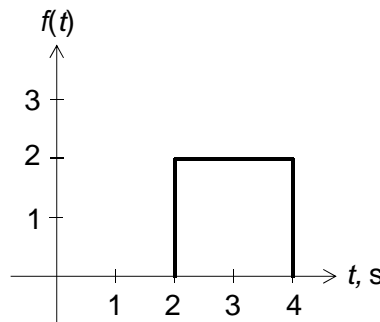
**12.** Given the two functions  $f(t)$  and  $g(t)$  shown.

15% (a) Sketch  $y(t) = f(t) * g(t)$  as function of  $t$ .


5% (b) Verify  $y(t)$  from the product of two polynomials.



**Solution:** (a) When  $f(t)$  is folded, it becomes as shown. The convolution integral is zero until  $t = 3$ , when side  $aa'$  coincides with  $g(1)$ . At  $t = 4$ ,  $aa'$  coincides with  $g(2)$ , and the area under the product of the two functions is  $3 \times 2 = 6$ . At  $t = 5$ ,  $aa'$  coincides with  $g(3)$ , and the area under the product of the two functions is  $3 \times 2 - 1 \times 2 = 4$ . At  $t = 6$ ,  $aa'$  coincides with  $g(4)$ , and the area

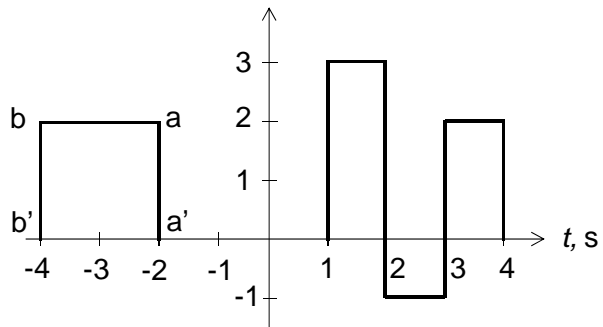


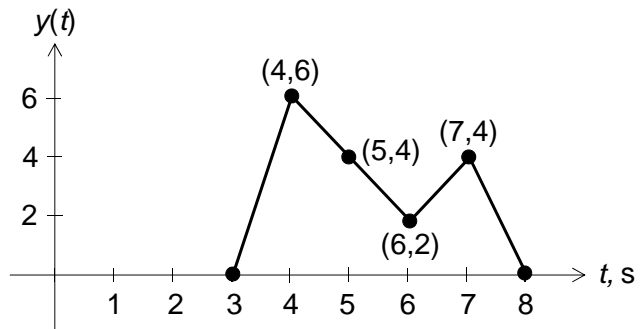under the product of the two functions is  $1 \times 2 + 2 \times 2 = 2$ . At  $t = 7$ ,  $bb'$  coincides with  $g(3)$ , and the area under the product of the two functions is  $2 \times 2 = 4$ . At  $t = 8$ ,  $bb'$  coincides with  $g(4)$ , and the area under the product of the two functions is back to zero. The convolution function  $y(t)$  is as shown.



(b) To derive  $y(t)$  in terms of a polynomial,  $f(t)$  and  $g(t)$  are assumed to both start at  $t = 0$ .  $f(t)$  is divided into two successive 1 s intervals, each of amplitude 2 units. Thus, as polynomials in  $x$ ,  $f(x) = 2x + 2$ , and  $g(x) = 3x^2 - x + 2$ . The product  $f(x)g(x) = 6x^3 + 4x^2 + 2x + 4$ . The non-zero breakpoints are thus at (1,6), (2,4), (3,2), and (4,4). For the given functions, the total shift in time from the origin is 3 s. Because the system is linear and time-invariant, as assumed in the derivation of the convolution integral, the 3 s is added to the time coordinates of the breakpoints from the product of polynomials to give the non-zero breakpoints of  $y(t)$  in the figure.

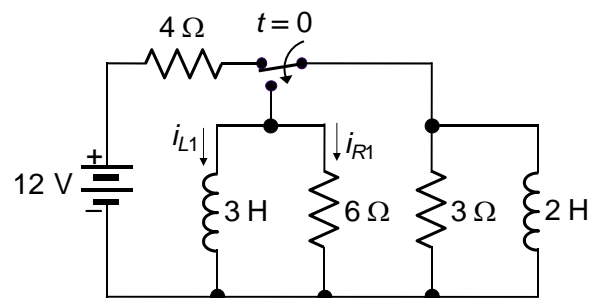13. The switch is moved at  $t = 0$  after having been in the first position for a long time, with  $i_{L1}$  initially zero. Determine, as a function of  $t$ , for  $t \geq 0^+$ :




10% (a)  $i_{R1}$

10% (b)  $i_{L1}$

**Solution:** After switching, the circuit becomes as shown, where at  $t = 0^+$ :  $i_{L2} = 12/4 = 3$  A,  $i_{L1} = 0$ ,  $i_R = 3$  A,  $v = 3 \times 2 = 6$  V. As  $t \rightarrow \infty$ ,  $v = 0$ . The time constant is  $(2||3)/2 = 1.2/2 = 0.6$  s. Hence  $v = 6e^{-t/0.6}$  V.

(a) It follows that  $i_{R1} = -\frac{v}{6} = -e^{-t/0.6}$  A

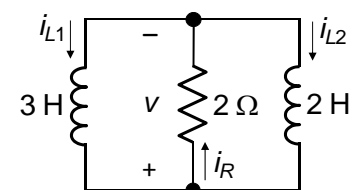(b)  $i_{L1}$  can be determined from conservation of flux linkage in the loop formed by the two inductors. At  $t = 0^+$ , going clockwise around the loop, the total flux linkage is  $3 \times 2 + 0 = 6$  Wb-T. As  $t \rightarrow \infty$ , the currents in the two inductors are equal in magnitude. Going clockwise around the loop,  $i_{L2} \times 5 = 6$  Wb-T, so that  $i_{L1} = -i_{L2} = -1.2$  A. It follows that  $i_{L1} = -1.2 + (0 + 1.2)e^{-t/0.6} = -1.2(1 - e^{-t/0.6})$  A.



Alternatively,  $i_{L1} = -\frac{1}{L} \int_0^t v dt + i_{L1}(0) = -\frac{1}{3} \int_0^t 6e^{-t/0.6} dt = -2[-e^{-t/0.6}]_0^t = -1.2(1 - e^{-t/0.6})$  A.