

Homework 1

P10.1.5 Determine the response $V_O(j\omega)/V_{SRC}(j\omega)$, both in magnitude and phase, the passband gain, and the corner frequency in Figure P10.1.5.

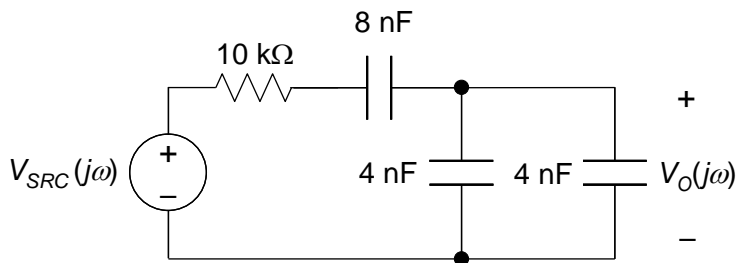


Figure P10.1.5

Solution P10.1.5 The impedance of

the 8 nF capacitor is $\frac{0.125}{j\omega}$

k Ω , where ω is in Mrad/s.

Hence,

$$H(j\omega) = \frac{V_O(j\omega)}{V_{SRC}(j\omega)} = \frac{0.125/j\omega}{10 + 0.25/j\omega}$$

$$= \frac{0.5}{1 + j40\omega}. \text{ It follows that } |H(j\omega)| = \frac{0.5}{\sqrt{1 + (40\omega)^2}}, \angle H(j\omega) = -\tan^{-1}(40\omega). \text{ The}$$

response is lowpass; the passband gain, when $\omega \rightarrow 0$ is 0.5; the corner frequency is when $40\omega_{cl} = 1$, or $\omega_{cl} = 25$ krad/s.

P10.1.7 Determine the response $V_O(j\omega)/I_{SRC}(j\omega)$, both in magnitude and phase, the passband gain, and the corner frequency in Figure P10.1.7.

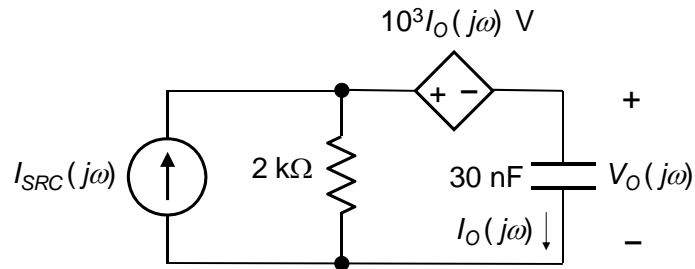


Figure P10.1.7

Solution P10.1.7 The impedance of the capacitor is $\frac{100}{j3\omega}$ k Ω , where ω is in krad/s. The

dependent source of voltage $10^3 I_O(j\omega)$, where $I_O(j\omega)$, is the current through

the source, is equivalent to a resistance of $\frac{10^3 I_O(j\omega)}{I_O(j\omega)} \equiv 1$ k Ω . Hence,

$$H(j\omega) = \frac{V_O(j\omega)}{I_{SRC}(j\omega)} = \frac{100 \times 10^3}{j3\omega} \times \frac{2}{3 + 100/j3\omega} = \frac{2 \times 10^3}{1 + j0.09\omega} \text{ V/A. It follows that}$$

$$|H(j\omega)| = \frac{2 \times 10^3}{\sqrt{1 + (0.09\omega)^2}} \text{ V/A, } \angle H(j\omega) = -\tan^{-1}(0.09\omega). \text{ The response is}$$

lowpass; the passband gain, when $\omega \rightarrow 0$ is 2×10^3 ; the corner frequency is when $0.09\omega_{cl} = 1$, or $\omega_{cl} = 100/9$ krad/s.

P10.1.10 Determine the response $V_O(j\omega)/V_{SRC}(j\omega)$, both in magnitude and phase, the passband gain, and the corner frequency in Figure P10.1.10.

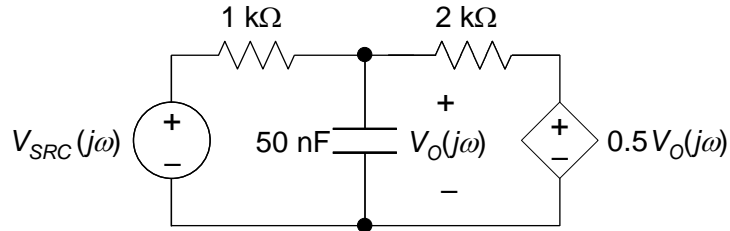


Figure P10.1.10

Solution P10.1.10 Let the current in the capacitor be $I_O(j\omega)$. Then $V_O(j\omega) = I_O(j\omega)/j\omega C$.

The current in the $2\text{ k}\Omega$ resistor is $\frac{0.5V_O(j\omega)}{2000}$, and the total current is $I_O(j\omega) +$

$$\frac{0.5V_O(j\omega)}{2000} = V_O(j\omega)[j\omega C + 1/4000].$$

It is seen that a $4\text{ k}\Omega$ resistor appears in parallel with the capacitor. TEC as seen by the capacitor will have

$$V_{Th}(j\omega) = \frac{4}{5}V_{SRC}(j\omega) = 0.8V_{SRC}(j\omega); R_{Th} = \frac{4}{5} = 0.8\text{ k}\Omega.$$

TEC could have been derived directly. Thus, on open circuit, the current is

$$\frac{V_O(j\omega) - 0.5V_O(j\omega)}{2} \text{ mA, so that } V_{SRC}(j\omega) = V_O(j\omega) + \frac{V_O(j\omega)}{4}, \text{ so that}$$

$$V_{Th}(j\omega) = \frac{4}{5}V_{SRC}(j\omega) = 0.8V_{SRC}(j\omega). \text{ On short circuit, } I_{sc}(j\omega) = \frac{V_{SRC}(j\omega)}{1} \text{ mA.}$$

$$\text{Hence, } R_{Th} = \frac{V_{Th}(j\omega)}{I_{sc}} = 0.8\text{ k}\Omega.$$

The impedance of the capacitor is $\frac{20}{j\omega}\text{ k}\Omega$, where ω is in krad/s . Hence,

$$\frac{V_O(j\omega)}{0.8V_{SRC}(j\omega)} = \frac{20/j\omega}{0.8 + 20/j\omega}, \text{ or } H(j\omega) = \frac{V_O(j\omega)}{V_{SRC}(j\omega)} = \frac{0.8}{1 + 0.04j\omega}. \text{ It follows that}$$

$$|H(j\omega)| = \frac{0.8}{\sqrt{1 + (0.04\omega)^2}}. \angle H(j\omega) = -\tan^{-1}(0.04\omega). \text{ The response is lowpass;}$$

the passband gain, when $\omega \rightarrow 0$ is 0.8. The corner frequency is when $0.04\omega_{cl} = 1$, or $\omega_{cl} = 25\text{ krad/s}$.

P10.1.12 Determine the response $V_O(j\omega)/V_{SRC}(j\omega)$, both in magnitude and phase, the passband gain, and the corner frequency in Figure P10.1.12.

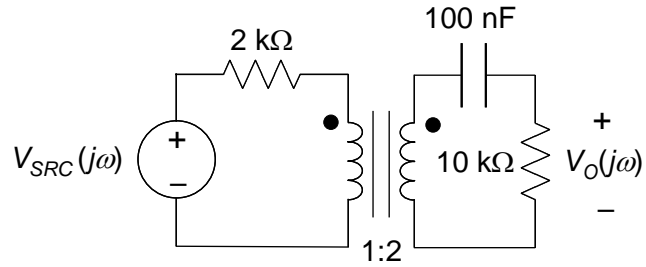


Figure P10.1.12

Solution P10.1.12 The impedance of the capacitor is

$$\frac{1}{j\omega 100 \times 10^{-9}} \equiv \frac{10}{j\omega} \text{ k}\Omega,$$

where ω is in krad/s.

When the source and 2

k Ω resistor are reflected to the secondary side, they become a source of


$2V_{SRC}(j\omega)$ in series with 8 k Ω . Hence, $\frac{V_O(j\omega)}{2V_{SRC}(j\omega)} = \frac{10}{18 + 10/j\omega}$, or

$$H(j\omega) = \frac{V_O(j\omega)}{V_{SRC}(j\omega)} = \frac{20}{18 + 10/j\omega} = \frac{2j\omega}{1 + j1.8\omega}. \text{ It follows that}$$

$$|H(j\omega)| = \frac{2\omega}{\sqrt{1 + (1.8\omega)^2}}, \quad \angle H(j\omega) = 90^\circ - \tan^{-1}(1.8\omega). \text{ The response is}$$

highpass; the passband gain, when $\omega \rightarrow \infty$ is $10/9 \equiv 0.915$ dB; the corner

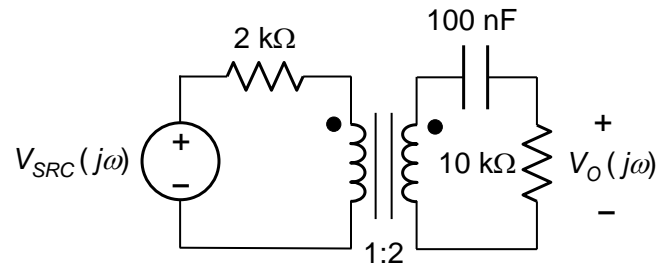frequency is $\omega_{cl} = \frac{5}{9}$ krad/s $\equiv 88.4$ Hz



P10.2.2 Determine R , L , and C in Figure P10.2.2 such that:

- (a) the maximum response of $V_O(s)$ is 1 V; (b) the bandwidth is 4 krad/s; and (c) the center frequency is 100 krad/s.

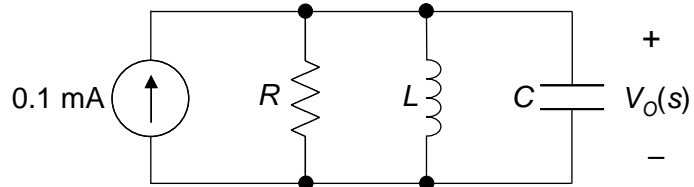


Figure P10.2.2

Solution P10.2.2 Maximum response, which occurs at ω_0 , is R/I ; hence $R = 10 \text{ k}\Omega$. $Q =$

$$\omega_0/BW = 100/4 = 25; \text{ it follows that } C = \frac{Q}{\omega_0 R} = \frac{25}{10^5 \times 10^4} \cong 25 \text{ nF, and } L =$$

$$\frac{R}{\omega_0 Q} = \frac{10^4}{25 \times 10^5} \cong 4 \text{ mH.}$$

P10.2.3 Given the transfer function $H(s) = \frac{4s^2 + 1000s + 100}{5s^2 + 500s + 125}$. Determine the maximum response in dB.

Solution P10.2.3. $H(s) = \frac{4}{5} \left[\frac{s^2 + 250s + 25}{s^2 + 100s + 25} \right] = 0.8 \left[\frac{s^2 + 25}{s^2 + 100s + 25} + \frac{250s}{s^2 + 100s + 25} \right]$.

The first term is a bandstop response of magnitude 0.8 at low and high frequencies and zero at $\omega = 5 \text{ rad/s}$. The second term is a bandpass response of zero at low and high frequencies and magnitude of 2 at $\omega = 5 \text{ rad/s}$. The sum will have a maximum magnitude of 2, or $20 \log_{10} 2 = 6 \text{ dB}$, at $\omega = 5 \text{ rad/s}$.