

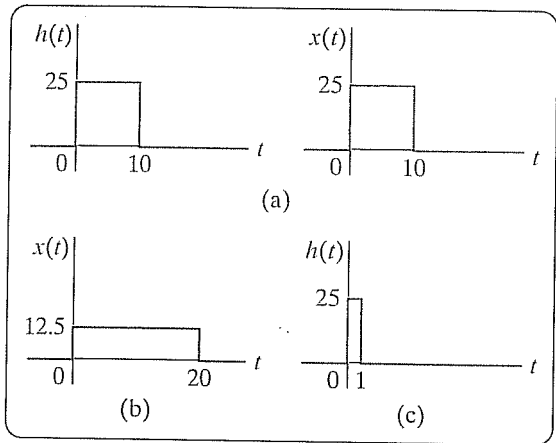


- a) Find $h(t) * x(t)$ when $h(t)$ and $x(t)$ are the rectangular pulses shown in Fig. P13.59(a).
- b) Repeat (a) when $x(t)$ changes to the rectangular pulse shown in Fig. P13.59(b).
- c) Repeat (a) when $h(t)$ changes to the rectangular pulse shown in Fig. P13.59(c).

Figure P13.59

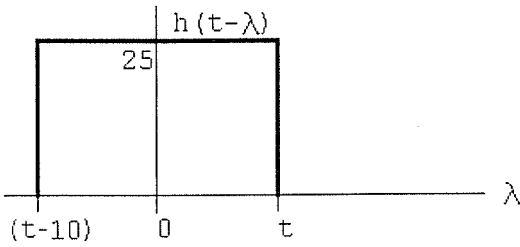

P 13.59 [a]

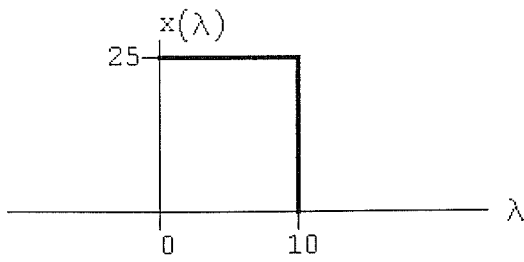


$$t < 0: \quad y(t) = 0$$



$$0 \leq t \leq 10: \quad y(t) = \int_0^t 625 \, d\lambda = 625t$$

$$10 \leq t \leq 20: \quad y(t) = \int_{t-10}^{10} 625 \, d\lambda = 625(10 - t + 10) = 625(20 - t)$$

$$20 \leq t < \infty: \quad y(t) = 0$$

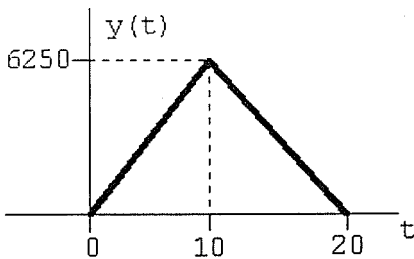

[b]

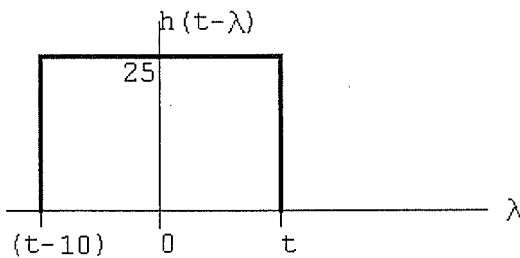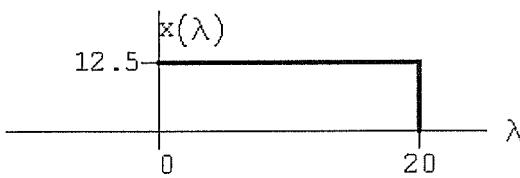


$$t < 0: \quad y(t) = 0$$

$$0 \leq t \leq 10: \quad y(t) = \int_0^t 312.5 \, d\lambda = 312.5t$$


$$10 \leq t \leq 20: \quad y(t) = \int_{t-10}^t 312.5 \, d\lambda = 3125$$

$$20 \leq t \leq 30: \quad y(t) = \int_{t-10}^{20} 312.5 \, d\lambda = 312.5(30 - t)$$

$$30 \leq t < \infty: \quad y(t) = 0$$

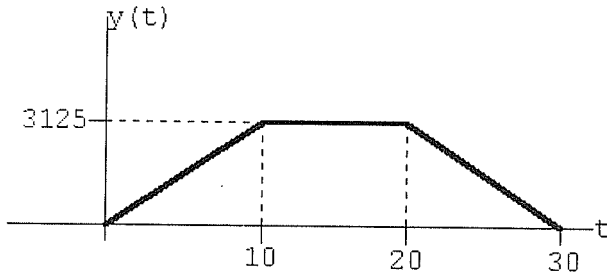

[c]

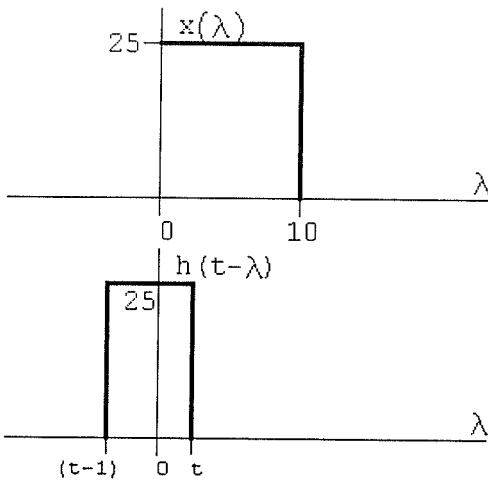


$$t < 0: \quad y(t) = 0$$

$$0 \leq t \leq 1: \quad y(t) = \int_0^t 625 \, d\lambda = 625t$$

$$1 \leq t \leq 10: \quad y(t) = \int_{t-1}^t 625 \, d\lambda = 625$$

$$10 \leq t \leq 11: \quad y(t) = \int_{t-1}^{10} 625 \, d\lambda = 625(11 - t)$$

$$11 \leq t < \infty: \quad y(t) = 0$$

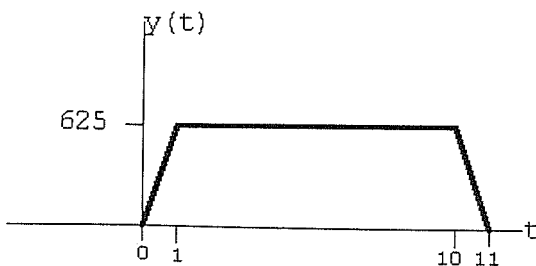


13.61

The voltage impulse response of a circuit is shown in Fig. P13.61(a). The input signal to the circuit is the rectangular voltage pulse shown in Fig. P13.61(b).

- Derive the equations for the output voltage. Note the range of time for which each equation is applicable.
- Sketch v_o for $-1 \leq t \leq 34$ s.

Figure P13.61

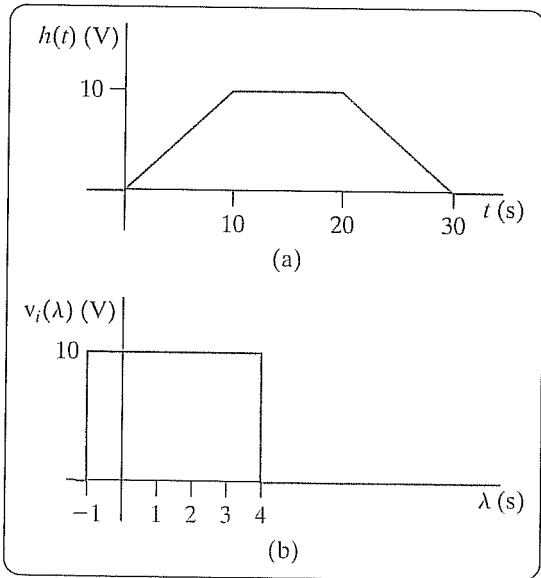

P 13.61 [a] $-1 \leq t \leq 4$:

$$v_o = \int_0^{t+1} 10\lambda d\lambda = 5\lambda^2 \Big|_0^{t+1} = 5t^2 + 10t + 5 \text{ V}$$

$4 \leq t \leq 9$:

$$v_o = \int_{t-4}^{t+1} 10\lambda d\lambda = 5\lambda^2 \Big|_{t-4}^{t+1} = 50t - 75 \text{ V}$$

$9 \leq t \leq 14$:

$$\begin{aligned} v_o &= 10 \int_{t-4}^{10} \lambda d\lambda + 10 \int_{10}^{t+1} 10 d\lambda \\ &= 5\lambda^2 \Big|_{t-4}^{10} + 100\lambda \Big|_{10}^{t+1} = -5t^2 + 140t - 480 \text{ V} \end{aligned}$$

$14 \leq t \leq 19$:

$$v_o = 100 \int_{t-4}^{t+1} d\lambda = 500 \text{ V}$$

$19 \leq t \leq 24$:

$$\begin{aligned} v_o &= \int_{t-4}^{20} 100 d\lambda + \int_{20}^{t+1} 10(30 - \lambda) d\lambda \\ &= 100\lambda \Big|_{t-4}^{20} + 300\lambda \Big|_{20}^{t+1} - 5\lambda^2 \Big|_{20}^{t+1} \\ &= -5t^2 + 190t - 1305 \text{ V} \end{aligned}$$

$24 \leq t \leq 29$:

$$\begin{aligned} v_o &= 10 \int_{t-4}^{t+1} (30 - \lambda) d\lambda = 300\lambda \Big|_{t-4}^{t+1} - 5\lambda^2 \Big|_{t-4}^{t+1} \\ &= 1575 - 50t \text{ V} \end{aligned}$$

$29 \leq t \leq 34$:

$$\begin{aligned} v_o &= 10 \int_{t-4}^{30} (30 - \lambda) d\lambda = 300\lambda \Big|_{t-4}^{30} - 5\lambda^2 \Big|_{t-4}^{30} \\ &= 5t^2 - 340t + 5780 \text{ V} \end{aligned}$$

Summary:

$$v_o = 0 \quad -\infty \leq t \leq -1$$

$$v_o = 5t^2 + 10t + 5 \text{ V} \quad -1 \leq t \leq 4$$

$$v_o = 50t - 75 \text{ V} \quad 4 \leq t \leq 9$$

$$v_o = -5t^2 + 140t - 480 \text{ V} \quad 9 \leq t \leq 14$$

$$v_o = 500 \text{ V} \quad 14 \leq t \leq 19$$


$$v_o = -5t^2 + 190t - 1305 \text{ V} \quad 19 \leq t \leq 24$$

$$v_o = 1575 - 50t \text{ V} \quad 24 \leq t \leq 29$$

$$v_o = 5t^2 - 340t + 5780 \text{ V} \quad 29 \leq t \leq 34$$

$$v_o = 0 \text{ V} \quad 34 \leq t \leq \infty$$


[b]

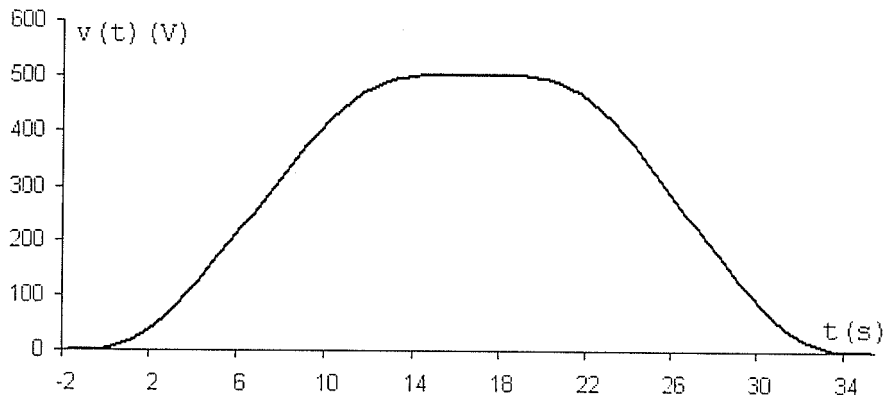

3.62 Assume the voltage impulse response of a circuit can be modeled by the triangular waveform shown in Fig. P13.62. The voltage input signal to this circuit is the step function $10u(t)$ V.



- Use the convolution integral to derive the expressions for the output voltage.
- Sketch the output voltage over the interval 0 to 15 s.
- Repeat parts (a) and (b) if the area under the voltage impulse response stays the same but the width of the impulse response narrows to 4 s.
- Which output waveform is closer to replicating the input waveform: (b) or (c)? Explain.

Figure P13.62

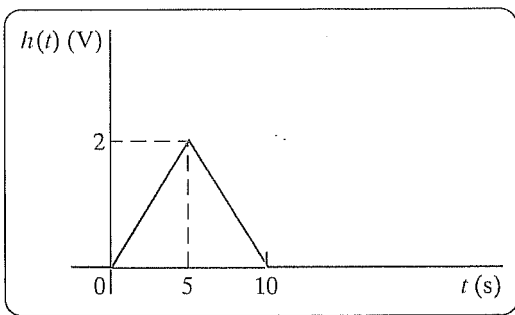

P 13.62 [a] $h(\lambda) = \frac{2}{5}\lambda \quad 0 \leq \lambda \leq 5$
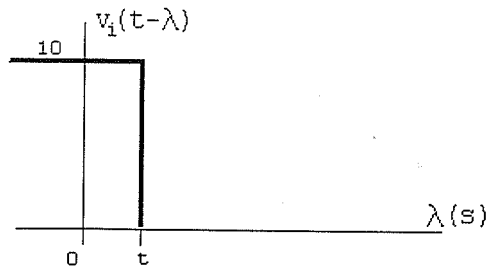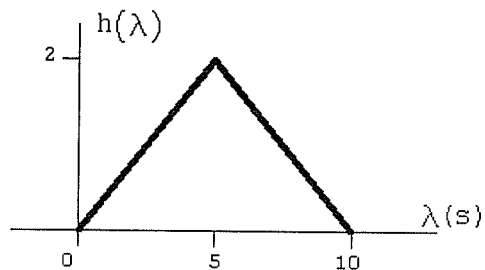
$$h(\lambda) = \left(4 - \frac{2}{5}\lambda\right) \quad 5 \leq \lambda \leq 10$$



$$0 \leq t \leq 5:$$

$$v_o = 10 \int_0^t \frac{2}{5}\lambda d\lambda = 2t^2$$

$$5 \leq t \leq 10:$$

$$\begin{aligned} v_o &= 10 \int_0^5 \frac{2}{5} \lambda d\lambda + 10 \int_5^t \left(4 - \frac{2}{5} \lambda\right) d\lambda \\ &= \frac{4\lambda^2}{2} \Big|_0^5 + 40\lambda \Big|_5^t - \frac{4\lambda^2}{2} \Big|_5^t \\ &= -100 + 40t - 2t^2 \end{aligned}$$

$$10 \leq t \leq \infty:$$

$$\begin{aligned} v_o &= 10 \int_0^5 \frac{2}{5} \lambda d\lambda + 10 \int_5^{10} \left(4 - \frac{2}{5} \lambda\right) d\lambda \\ &= \frac{4\lambda^2}{2} \Big|_0^5 + 40\lambda \Big|_5^{10} - \frac{4\lambda^2}{2} \Big|_5^{10} \\ &= 50 + 200 - 150 = 100 \end{aligned}$$


Summary:

$$v_o = 2t^2 \text{ V} \quad 0 \leq t \leq 5$$

$$v_o = 40t - 100 - 2t^2 \text{ V} \quad 5 \leq t \leq 10$$

$$v_o = 100 \text{ V} \quad 10 \leq t \leq \infty$$



[b]

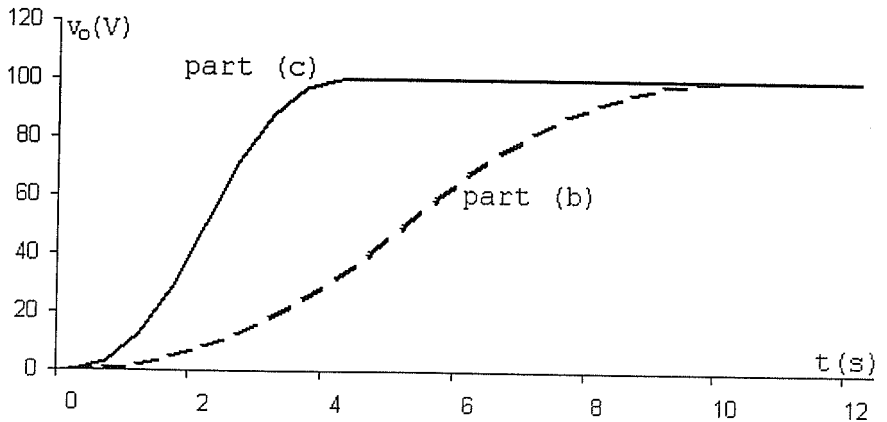

$$[c] \text{ Area} = \frac{1}{2}(10)(2) = 10 \quad \therefore \quad \frac{1}{2}(4)h = 10 \quad \text{so} \quad h = 5$$

$$h(\lambda) = \frac{5}{2} \lambda \quad 0 \leq \lambda \leq 2$$
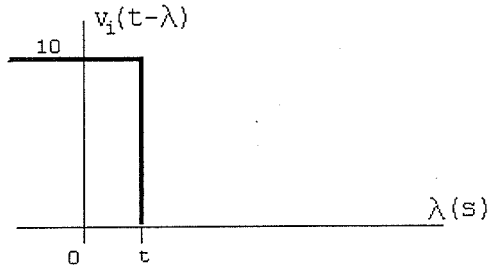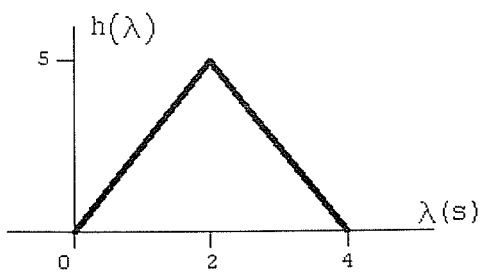
$$h(\lambda) = \left(10 - \frac{5}{2} \lambda\right) \quad 2 \leq \lambda \leq 4$$



$$0 \leq t \leq 2:$$

$$v_o = 10 \int_0^t \frac{5}{2} \lambda d\lambda = 12.5t^2$$

$$2 \leq t \leq 4:$$

$$\begin{aligned} v_o &= 10 \int_0^2 \frac{5}{2} \lambda d\lambda + 10 \int_2^t \left(10 - \frac{5}{2} \lambda\right) d\lambda \\ &= \frac{25\lambda^2}{2} \Big|_0^2 + 100\lambda \Big|_2^t - \frac{25\lambda^2}{2} \Big|_2^t \\ &= -100 + 100t - 12.5t^2 \end{aligned}$$

$$4 \leq t \leq \infty:$$

$$\begin{aligned} v_o &= 10 \int_0^2 \frac{5}{2} \lambda d\lambda + 10 \int_2^4 \left(10 - \frac{5}{2} \lambda\right) d\lambda \\ &= \frac{25\lambda^2}{2} \Big|_0^2 + 100\lambda \Big|_2^4 - \frac{25\lambda^2}{2} \Big|_2^4 \\ &= 50 + 200 - 150 = 100 \end{aligned}$$

$$v_o = 12.5t^2 \text{ V} \quad 0 \leq t \leq 2$$

$$v_o = 100t - 100 - 12.5t^2 \text{ V} \quad 2 \leq t \leq 4$$


$$v_o = 100 \text{ V} \quad 4 \leq t \leq \infty$$

[d] The waveform in part (c) is closer to replicating the input waveform because in part (c) $h(\lambda)$ is closer to being an ideal impulse response. That is, the area is preserved as the base was shortened.

13.66

- a) Use the convolution integral to find v_o in the circuit in Fig. P13.66(a) if i_g is the pulse shown in Fig. P13.66(b).
- b) Use the convolution integral to find i_o .
- c) Show that your solutions for v_o and i_o are consistent by calculating i_o at 100^- ms, 100^+ ms, 200^- ms, and 200^+ ms.



Figure P13.66

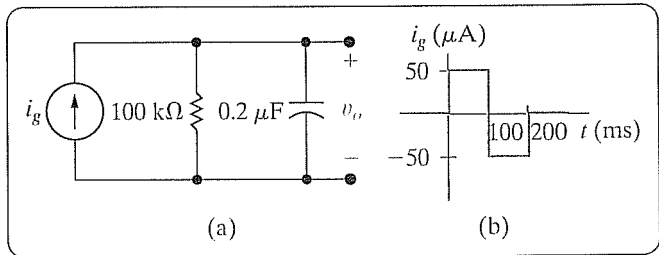

$$P\ 13.66\ [a]\ I_g = \frac{V_o}{10^5} + \frac{V_o s}{5 \times 10^6} = \frac{V_o(s + 50)}{5 \times 10^6}$$

$$\frac{V_o}{I_g} = H(s) = \frac{5 \times 10^6}{s + 50}$$
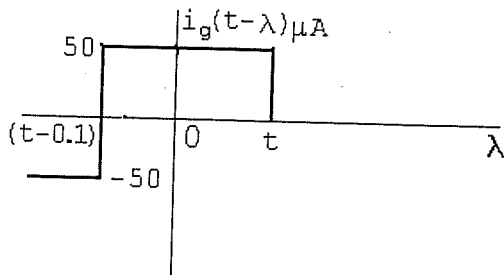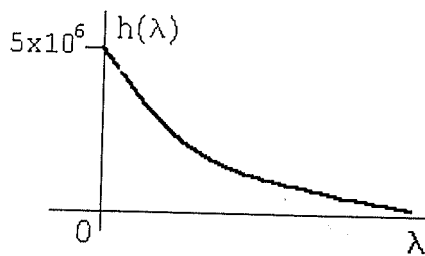
$$h(\lambda) = 5 \times 10^6 e^{-50\lambda} u(\lambda)$$




$$0 \leq t \leq 0.1 \text{ s:}$$

$$v_o = \int_0^t (50 \times 10^{-6})(5 \times 10^6) e^{-50\lambda} d\lambda = 250 \frac{e^{-50\lambda}}{-50} \Big|_0^t$$

$$= 5(1 - e^{-50t}) \text{ V}$$
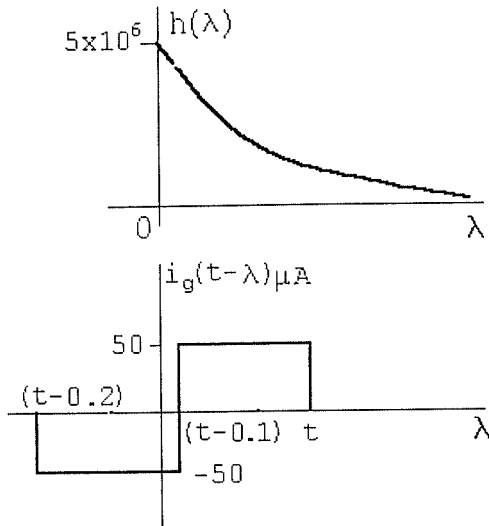
$$0.1 \text{ s} \leq t \leq 0.2 \text{ s:}$$



$$v_o = \int_0^{t-0.1} (-50 \times 10^{-6})(5 \times 10^6 e^{-50\lambda} d\lambda)$$


$$+ \int_{t-0.1}^t (50 \times 10^{-6})(5 \times 10^6 e^{-50\lambda} d\lambda)$$

$$= -250 \frac{e^{-50\lambda}}{-50} \Big|_0^{t-0.1} + 250 \frac{e^{-50\lambda}}{-50} \Big|_{t-0.1}^t$$

$$= 5 [e^{-50(t-0.1)} - 1] - 5 [e^{-50t} - e^{-50(t-0.1)}]$$

$$v_o = [10e^{-50(t-0.1)} - 5e^{-50t} - 5] \text{ V}$$

$$0.2 \text{ s} \leq t \leq \infty:$$

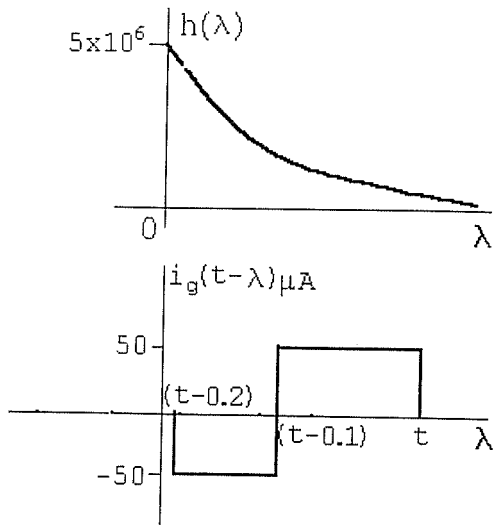

$$\begin{aligned} v_o &= \int_{t-0.2}^{t-0.1} -250e^{-50\lambda} d\lambda + \int_{t-0.1}^t 250e^{-50\lambda} d\lambda \\ &= 5e^{-50\lambda} \Big|_{t-0.2}^{t-0.1} - 5e^{-50\lambda} \Big|_{t-0.1}^t \\ v_o &= [10e^{-50(t-0.1)} - 5e^{-50(t-0.2)} - 5e^{-50t}] \text{ V} \end{aligned}$$

Summary:

$$v_o = 5(1 - e^{-50t}) \text{ V} \quad 0 \leq t \leq 0.1 \text{ s}$$

$$v_o = [10e^{-50(t-0.1)} - 5e^{-50t} - 5] \text{ V} \quad 0.1 \text{ s} \leq t \leq 0.2 \text{ s}$$

$$v_o = [10e^{-50(t-0.1)} - 5e^{-50(t-0.2)} - 5e^{-50t}] \text{ V} \quad 0.2 \text{ s} \leq t \leq \infty$$

$$[\text{b}] I_o = \frac{V_o s}{5 \times 10^6} = \frac{s}{5 \times 10^6} \cdot \frac{5 \times 10^6 I_g}{s + 50}$$

$$\frac{I_o}{I_g} = H(s) = \frac{s}{s + 50} = 1 - \frac{50}{s + 50}$$

$$h(\lambda) = \delta(\lambda) - 50e^{-50\lambda}$$


$$0 < t < 0.1 \text{ s:}$$

$$i_o = \int_0^t (50 \times 10^{-6}) [\delta(\lambda) - 50e^{-50\lambda}] d\lambda$$

$$= 50 \times 10^{-6} - \left[50 \times 50 \times 10^{-6} \frac{e^{-50\lambda}}{-50} \right] \Big|_0^t$$

$$= 50 \times 10^{-6} + 50 \times 10^{-6} [e^{-50t} - 1] = 50e^{-50t} \mu\text{A}$$

$0.1 \text{ s} < t < 0.2 \text{ s}$:

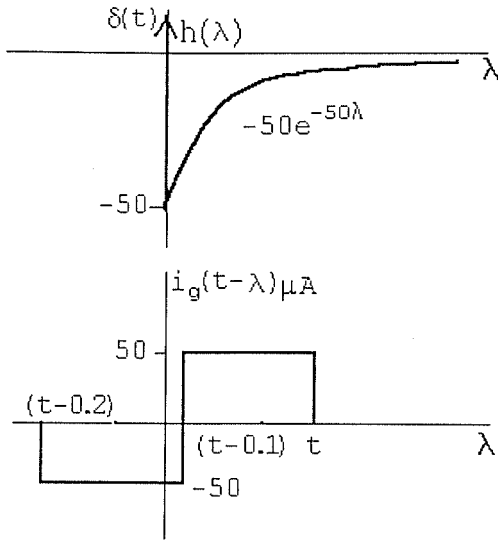

$$i_o = \int_0^{t-0.1} (-50 \times 10^{-6}) [\delta(\lambda) - 50e^{-50\lambda}] d\lambda$$


$$+ \int_{t-0.1}^t (50 \times 10^{-6}) (-50e^{-50\lambda}) d\lambda$$

$$= -50 \times 10^{-6} + 2500 \times 10^{-6} \frac{e^{-50\lambda}}{-50} \Big|_0^{t-0.1} - 2500 \times 10^{-6} \frac{e^{-50\lambda}}{-50} \Big|_{t-0.1}^t$$

$$= -50 \times 10^{-6} - 50 \times 10^{-6} [e^{-50(t-0.1)} - 1] + 50 \times 10^{-6} [e^{-50t} - e^{-50(t-0.1)}]$$

$$= 50e^{-50t} - 100e^{-50(t-0.1)} \mu\text{A}$$

$$0.2 \text{ s} < t < \infty:$$

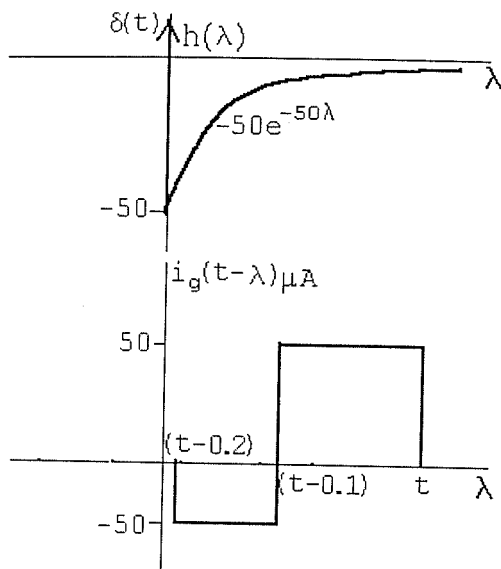

$$\begin{aligned} i_o &= \int_{t-0.2}^{t-0.1} (-50 \times 10^{-6})(-50e^{-50\lambda}) d\lambda \\ &\quad + \int_{t-0.1}^t (50 \times 10^{-6})(-50e^{-50\lambda}) d\lambda \\ &= 50e^{-50t} - 100e^{-50(t-0.1)} + 50e^{-50(t-0.2)} \mu\text{A} \end{aligned}$$

Summary:

$$i_o = 50e^{-50t} \mu\text{A} \quad 0 \leq t \leq 0.1 \text{ s}$$

$$i_o = 50e^{-50t} - 100e^{-50(t-0.1)} \mu\text{A} \quad 0.1 \text{ s} \leq t \leq 0.2 \text{ s}$$

$$i_o = 50e^{-50t} - 100e^{-50(t-0.1)} + 50e^{-50(t-0.2)} \mu\text{A} \quad 0.2 \text{ s} \leq t \leq \infty$$

[c] At $t = 0.1^-$:

$$v_o = 5(1 - e^{-5}) = 4.97 \text{ V}; \quad i_{100\text{k}\Omega} = \frac{4.97}{0.1} = 49.66 \mu\text{A}; \quad i_g = 50 \mu\text{A}$$

$$\therefore i_o = 50 - 49.66 = 0.34 \mu\text{A}$$

From the solution for i_o we have $i_o(0.1^-) = 50e^{-5} = 0.34 \mu\text{A}$ (Checks)

At $t = 0.1^+$:

$$v_o(0.1^+) = v_o(0.1^-) = 4.97 \mu\text{V}; \quad i_{100\text{k}\Omega} = 49.66 \mu\text{A}; \quad i_g = -50 \mu\text{A}$$

$$\therefore i_o(0.1^+) = -(50 + 49.66) = -99.66 \mu\text{A}$$

From the solution for i_o we have

$$i_o(0.1^+) = 50e^{-5} - 100 = -99.66 \mu\text{A} \quad (\text{Checks})$$

At $t = 0.2^-$:

$$v_o = 10e^{-5} - 5e^{-10} - 5 = -4.93 \mu\text{V}$$

$$i_{100\text{k}\Omega} = -49.33 \mu\text{A} \quad i_g = -50 \mu\text{A}$$

$$i_o = i_g - i_{100\text{k}\Omega} = -50 + 49.33 = -0.67 \mu\text{A}$$

From the solution for i_o , $i_o(0.2^-) = 50e^{-10} - 100e^{-5} = -0.67 \mu\text{A}$ (Checks)

At $t = 0.2^+$:

$$v_o(0.2^+) = i_o(0.2^-) = -4.93 \text{ V}; \quad i_{100\text{k}\Omega} = -49.33 \mu\text{A}; \quad i_g = 0$$

$$i_o = i_g - i_{100\text{k}\Omega} = 49.33 \mu\text{A}$$


From the solution for i_o ,


$$i_o(0.2^+) = 50e^{-10} - 100e^{-5} + 50 = 49.33 \mu\text{A}(\text{Checks})$$

13.70

The current source in the circuit shown in Fig. P13.70(a) is generating the waveform shown in Fig. P13.70(b). Use the convolution integral to find v_o at $t = 5$ ms.

Figure P13.70

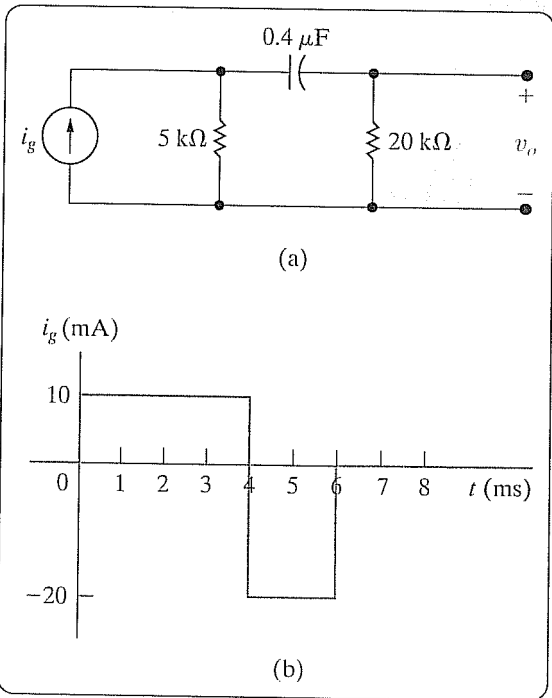

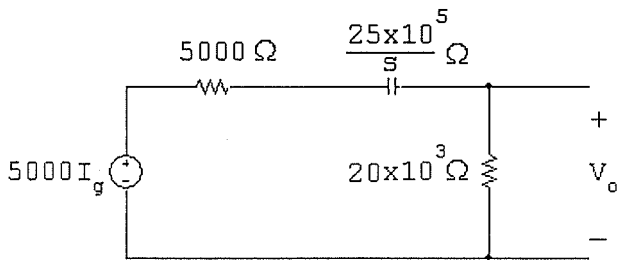

$$V_o = \frac{20 \times 10^3}{5000 + 25 \times 10^5/s + 20 \times 10^3} (5000 I_g)$$

$$\frac{V_o}{I_g} = H(s) = \frac{4000s}{s + 100}$$

$$H(s) = 4000 \left[1 - \frac{100}{s + 100} \right] = 4000 - \frac{4 \times 10^5}{s + 100}$$

$$h(\lambda) = 4000\delta(\lambda) - 400,000e^{-100\lambda}u(\lambda)$$

$$\begin{aligned}
v_o &= \int_0^{10^{-3}} (-20 \times 10^{-3}) [40000\delta(\lambda) - 400,000e^{-100\lambda}] d\lambda \\
&\quad + \int_{10^{-3}}^{5 \times 10^{-3}} (10 \times 10^{-3}) [-400,000e^{-100\lambda}] d\lambda \\
&= -80 + 8000 \int_0^{10^{-3}} e^{-100\lambda} d\lambda - \int_{10^{-3}}^{5 \times 10^{-3}} 4000e^{-100\lambda} d\lambda \\
&= -80 - 80(e^{-0.1} - 1) + 40(e^{-0.5} - e^{-0.1})
\end{aligned}$$

$$v_o(5 \times 10^{-3}) = 40e^{-0.5} - 120e^{-0.1} = 24.26 - 108.58 = -84.32 \text{ V}$$