
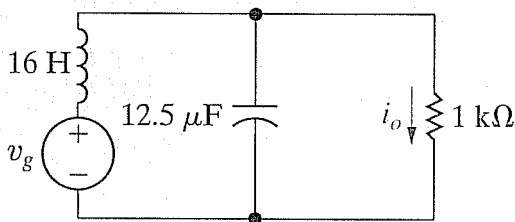


16.26 The full-wave rectified sine-wave voltage shown in Fig. P16.26(a) is applied to the circuit shown in Fig. P16.26(b).

Figure P16.26

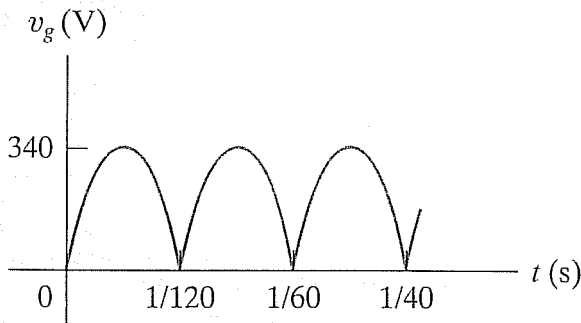

- Find the first four nonzero terms in the Fourier series representation of v_o .
- Does your solution for v_o make sense? Explain.

P 16.26 [a] Note – find $i_o(t)$

$$\frac{V_0 - V_g}{16s} + V_0(12.5 \times 10^{-6}s) + \frac{V_0}{1000} = 0$$

$$V_0 \left[\frac{1}{16s} + 12.5 \times 10^{-6}s + \frac{1}{1000} \right] = \frac{V_g}{16s}$$

$$V_0(1000 + 0.2s^2 + 16s) = 1000V_g$$

$$V_0 = \frac{5000V_g}{s^2 + 80s + 5000}$$

$$I_0 = \frac{V_0}{1000} = \frac{5V_g}{s^2 + 80s + 5000}$$

$$H(s) = \frac{I_0}{V_g} = \frac{5}{s^2 + 80s + 5000}$$

$$H(nj\omega_0) = \frac{5}{(5000 - n^2\omega_0^2) + j80n\omega_0}$$

$$\omega_0 = \frac{2\pi}{T} = 240\pi; \quad \omega_0^2 = 57.600\pi^2; \quad 80\omega_0 = 19.200\pi$$

$$H(jn\omega_0) = \frac{5}{(5000 - 57.600\pi^2 n^2) + j19.200\pi n}$$

$$H(0) = 10^{-3}$$

$$H(j\omega_0) = 8.82 \times 10^{-6} / \underline{-173.89^\circ}$$

$$H(j2\omega_0) = 2.20 \times 10^{-6} / \underline{-176.96^\circ}$$

$$H(j3\omega_0) = 9.78 \times 10^{-7} / \underline{-177.97^\circ}$$

$$H(j4\omega_0) = 5.5 \times 10^{-7} / \underline{-178.48^\circ}$$

$$v_g = \frac{680}{\pi} - \frac{1360}{\pi} \left[\frac{1}{3} \cos \omega_0 t + \frac{1}{15} \cos 2\omega_0 t + \frac{1}{35} \cos 3\omega_0 t + \frac{1}{63} \cos 4\omega_0 t + \dots \right]$$

$$i_0 = \frac{680}{\pi} \times 10^{-3} - \frac{1360}{3\pi} (8.82 \times 10^{-6}) \cos(\omega_0 t - 173.89^\circ)$$

$$- \frac{1360}{15\pi} (2.20 \times 10^{-6}) \cos(2\omega_0 t - 176.96^\circ)$$

$$- \frac{1360}{35\pi} (9.78 \times 10^{-7}) \cos(3\omega_0 t - 177.97^\circ)$$

$$- \frac{1360}{63\pi} (5.5 \times 10^{-7}) \cos(4\omega_0 t - 178.48^\circ) - \dots$$

$$= 216.45 \times 10^{-3} - 1.27 \times 10^{-3} \cos(\omega_0 t - 173.89^\circ)$$

$$- 6.35 \times 10^{-5} \cos(2\omega_0 t - 176.96^\circ)$$

$$- 1.21 \times 10^{-5} \cos(3\omega_0 t - 177.97^\circ)$$

$$- 3.8 \times 10^{-6} \cos(4\omega_0 t - 178.48^\circ) - \dots$$

$$i_0 \cong 216.45 - 1.27 \cos(\omega_0 t - 173.89^\circ) \text{ mA}$$

Note that the sinusoidal component is very small compared to the dc component, so

$$i_0 \cong 216.45 \text{ mA} \quad (\text{a dc current})$$

- [b]** Yes, the solution makes sense. The circuit is a low-pass filter which nearly eliminates all but the dc component.


16.37

- a) Use the first four nonzero terms in the Fourier series approximation of the periodic voltage shown in Fig. P16.37 to estimate its rms value.

- b) Calculate the true rms value of the voltage.

- c) Calculate the percentage of error in the estimated value.

Figure P16.37

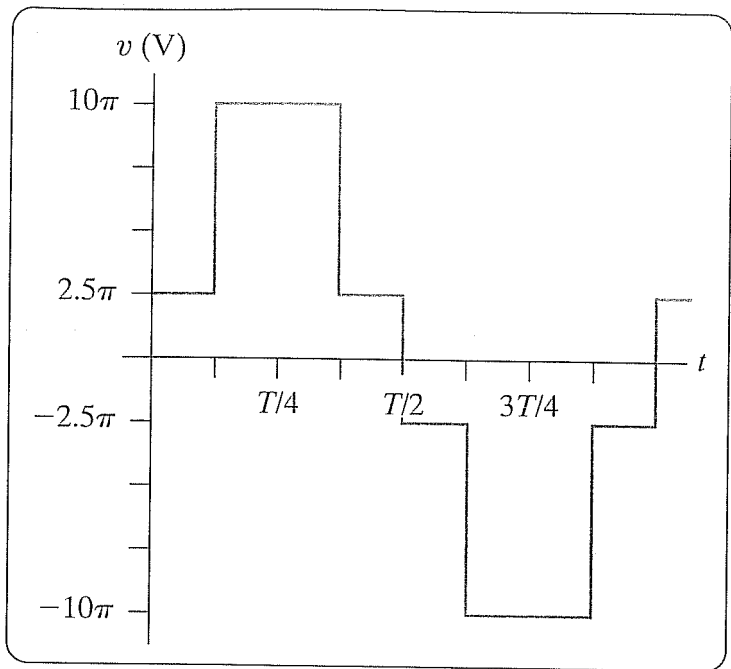

P 16.37 [a] v has half-wave symmetry, quarter-wave symmetry, and is odd

$$\therefore a_v = 0, a_k = 0 \text{ all } k. b_k = 0 \text{ } k\text{-even}$$

$$\begin{aligned} b_k &= \frac{8}{T} \int_0^{T/4} f(t) \sin k\omega_o t \, dt, \quad k\text{-odd} \\ &= \frac{8}{T} \left\{ \int_0^{T/8} \frac{V_m}{4} \sin k\omega_o t \, dt + \int_{T/8}^{T/4} V_m \sin k\omega_o t \, dt \right\} \\ &= \frac{8V_m}{4T} \left[-\frac{\cos k\omega_o t}{k\omega_o} \Big|_0^{T/8} \right] + \frac{8V_m}{T} \left[-\frac{\cos k\omega_o t}{k\omega_o} \Big|_{T/8}^{T/4} \right] \\ &= \frac{8V_m}{4k\omega_o T} \left[1 - \cos \frac{k\pi}{4} \right] + \frac{8V_m}{Tk\omega_o} \left[\cos \frac{k\pi}{4} - 0 \right] \end{aligned}$$

$$\begin{aligned}
&= \frac{8V_m}{k\omega_o T} \left\{ \frac{1}{4} - \frac{1}{4} \cos \frac{k\pi}{4} + \cos \frac{k\pi}{4} \right\} \\
&= \frac{4V_m}{\pi k} \left\{ \frac{1}{4} + 0.75 \cos \frac{k\pi}{4} \right\} = \frac{1}{k} [10 + 30 \cos(k\pi/4)]
\end{aligned}$$

$$b_1 = 10 + 30 \cos(\pi/4) = 31.21$$

$$b_3 = \frac{1}{3} [10 + 30 \cos(3\pi/4)] = -3.74$$

$$b_5 = \frac{1}{5} [10 + 30 \cos(5\pi/4)] = -2.24$$

$$b_7 = \frac{1}{7} [10 + 30 \cos(7\pi/4)] = 4.46$$

$$V(\text{rms}) \approx V_m \sqrt{\frac{31.21^2 + 3.74^2 + 2.24^2 + 4.46^2}{2}} = 22.51$$

$$[\mathbf{b}] \text{ Area under } v^2 = 2 \left[2(2.5\pi)^2 \left(\frac{T}{8}\right) + 100\pi^2 \left(\frac{T}{4}\right) \right] = 53.125\pi^2 T$$


$$V(\text{rms}) = \sqrt{\frac{1}{T} (53.125\pi^2) T} = \sqrt{53.125\pi} = 22.90$$

$$[\mathbf{c}] \text{ \% Error} = \left(\frac{22.51}{22.90} - 1 \right) (100) = -1.7\%$$


16.43 The periodic voltage source in the circuit shown in Fig. P16.43(a) has the waveform shown in Fig. P16.43(b).

- Derive the expression for C_n .
- Find the values of the complex coefficients $C_0, C_{-1}, C_1, C_{-2}, C_2, C_{-3}, C_3, C_{-4}$, and C_4 for the input voltage v_g if $V_m = 54$ V and $T = 10\pi \mu\text{s}$.

Figure P16.43

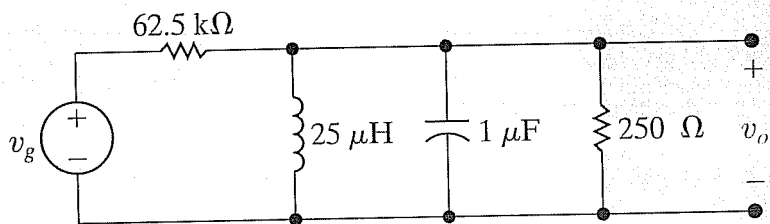

(a)

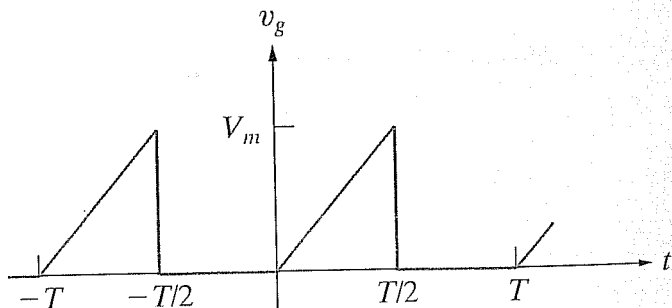

(b)

- c) Repeat (b) for v_o .
- d) Use the complex coefficients found in (c) to estimate the average power delivered to the $250\ \Omega$ resistor.

$$\text{P 16.43 [a]} \quad C_o = a_v = \frac{(1/2)(T/2)V_m}{T} = \frac{V_m}{4}$$

$$\begin{aligned} C_n &= \frac{1}{T} \int_0^{T/2} \frac{2V_m}{T} t e^{-jn\omega_o t} dt \\ &= \frac{2V_m}{T^2} \left[\frac{e^{-jn\omega_o t}}{-n^2\omega_o^2} (-jn\omega_o t - 1) \right]_0^{T/2} \\ &= \frac{V_m}{2n^2\pi^2} [e^{-jn\pi} (jn\pi + 1) - 1] \end{aligned}$$

Since $e^{-jn\pi} = \cos n\pi$ we can write

$$C_n = \frac{V_m}{2\pi^2 n^2} (\cos n\pi - 1) + j \frac{V_m}{2n\pi} \cos n\pi$$

$$\text{[b]} \quad C_o = \frac{54}{4} = 13.5 \text{ V}$$

$$C_{-1} = \frac{-54}{\pi^2} + j \frac{27}{\pi} = 10.19 / \underline{122.48^\circ} \text{ V}$$

$$C_1 = 10.19 / \underline{-122.48^\circ} \text{ V}$$

$$C_{-2} = -j \frac{13.5}{\pi} = 4.30 / \underline{-90^\circ} \text{ V}$$

$$C_2 = 4.30 / \underline{90^\circ} \text{ V}$$


$$C_{-3} = \frac{-6}{\pi^2} + j \frac{9}{\pi} = 2.93 / \underline{101.98^\circ} \text{ V}$$

$$C_3 = 2.93 / \underline{-101.98^\circ} \text{ V}$$

$$C_{-4} = -j \frac{6.75}{\pi} = 2.15 / -90^\circ \text{ V}$$

$$C_4 = 2.15 / 90^\circ \text{ V}$$

[c]

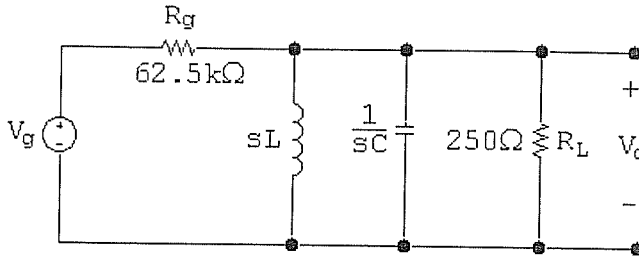

$$\frac{V_o}{250} + \frac{V_o}{sL} + V_o sC + \frac{V_o - V_g}{62.5 \times 10^3} = 0$$

$$\therefore (250LCs^2 + 1.004sL + 250)V_o = 0.004sLV_g$$

$$\frac{V_o}{V_g} = H(s) = \frac{(1/62,500C)s}{s^2 + 1/249C + 1/LC}$$

$$H(s) = \frac{16s}{s^2 + 1/249Cs + 4 \times 10^{10}}$$

$$\omega_o = \frac{2\pi}{T} = \frac{2\pi}{10\pi} \times 10^6 = 2 \times 10^5 \text{ rad/s}$$

$$H(j0) = 0$$

$$H(j2 \times 10^5 k) = \frac{jk}{12,500(1 - k^2) + j251k}$$

Therefore,

$$H_{-1} = 0.0398 / 0^\circ; \quad H_1 = 0.0398 / 0^\circ$$

$$H_{-2} = \frac{-j2}{-37,500 - j20} = 5.33 \times 10^{-5} / 86.23^\circ; \quad H_2 = 5.33 \times 10^{-5} / -89.2^\circ$$

$$H_{-3} = \frac{-3j}{-10^{-5} - j753} = 3.00 \times 10^{-5} / 89.57^\circ; \quad H_2 = 3.00 \times 10^{-5} / -89.57^\circ$$

$$H_{-4} = \frac{-4j}{-187,500 - j1004} = 2.13 \times 10^{-5} / 89.69^\circ; \quad H_2 = 2.13 \times 10^{-5} / -89.69^\circ$$

The output voltage coefficients:

$$C_0 = 0$$

$$C_{-1} = (10.19 / 122.48^\circ)(0.00398 / 0^\circ) = 0.0406 / 122.48^\circ \text{ V}$$

$$C_1 = 0.0406 / \underline{-122.48^\circ} \text{ V}$$

$$C_{-2} = (4.30 / \underline{-90^\circ})(5.33 \times 10^{-5} / \underline{86.23^\circ}) = 2.29 \times 10^{-4} / \underline{-3.77^\circ} \text{ V}$$

$$C_2 = 2.29 \times 10^{-4} / \underline{3.77^\circ} \text{ V}$$

$$C_{-3} = (2.93 / \underline{101.98^\circ})(3.00 \times 10^{-5} / \underline{89.57^\circ}) = 8.79 \times 10^{-5} / \underline{191.55^\circ} \text{ V}$$

$$C_3 = 8.79 \times 10^{-5} / \underline{-191.55^\circ} \text{ V}$$

$$C_{-4} = (2.15 / \underline{-90^\circ})(2.13 \times 10^{-5} / \underline{89.69^\circ}) = 4.58 \times 10^{-5} / \underline{-0.31^\circ} \text{ V}$$

$$C_4 = 4.58 \times 10^{-5} / \underline{0.31^\circ} \text{ V}$$


$$\begin{aligned} \text{[d]} \quad V_{\text{rms}} &\cong \sqrt{C_o^2 + 2 \sum_{n=1}^4 |C_n|^2} \cong \sqrt{2 \sum_{n=1}^4 |C_n|^2} \\ &\cong \sqrt{2(0.0406^2 + (2.29 \times 10^{-4})^2 + (8.79 \times 10^{-5})^2 + (4.58 \times 10^{-5})^2)} \cong \end{aligned}$$

$$P = \frac{(0.0574)^2}{250} = 13.2 \mu\text{W}$$


16.47 A periodic voltage is represented by a truncated Fourier series. The amplitude and phase spectra are shown in Fig. P16.47(a) and (b), respectively. (See page 802.)

- a) Write an expression for the periodic voltage using the form given by Eq. 16.38.
- b) Is the voltage an even or odd function of t ?
- c) Does the voltage have half-wave symmetry?
- d) Does the voltage have quarter-wave symmetry?

Figure P16.47

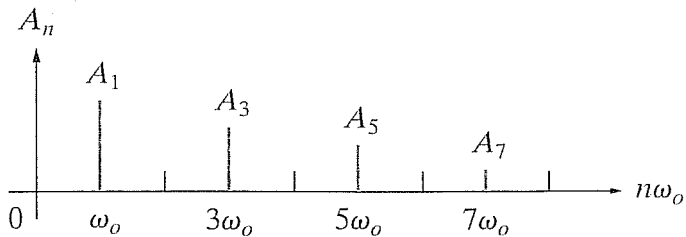

(a)

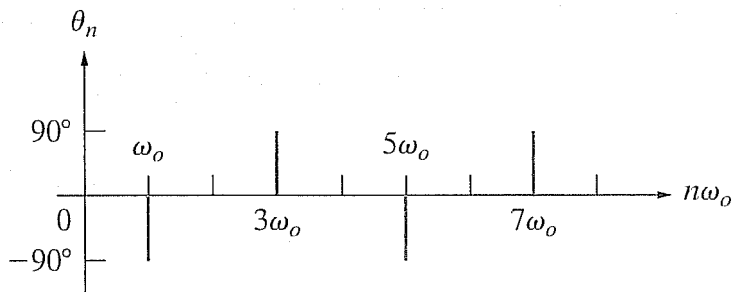

(b)

P 16.47 [a] $v = A_1 \cos(\omega_o t + 90^\circ) + A_3 \cos(3\omega_o t - 90^\circ)$

$$+ A_5 \cos(5\omega_o t + 90^\circ) + A_7 \cos(7\omega_o t - 90^\circ)$$

$$v = -A_1 \sin \omega_o t + A_3 \sin 3\omega_o t - A_5 \sin 5\omega_o t + A_7 \sin 7\omega_o t$$

[b] $v(-t) = A_1 \sin \omega_o t - A_3 \sin 3\omega_o t + A_5 \sin 5\omega_o t - A_7 \sin 7\omega_o t$

$$\therefore v(-t) = -v(t); \quad \text{odd function}$$

[c] $v(t - T/2) = -A_1 \sin(\omega_o t - \pi) + A_3 \sin(3\omega_o t - 3\pi)$

$$- A_5 \sin(5\omega_o t - 5\pi) + A_7 \sin(7\omega_o t - 7\pi)$$

$$= A_1 \sin \omega_o t - A_3 \sin 3\omega_o t + A_5 \sin 5\omega_o t - A_7 \sin 7\omega_o t$$

$$\therefore v(t - T/2) = -v(t), \text{ yes, the function has half-wave symmetry}$$

[d] Since the function is odd, with hws, we test to see if

$$f(T/2 - t) = f(t)$$

$$f(T/2 - t) = -A_1 \sin(\pi - \omega_0 t) + A_3 \sin(3\pi - 3\omega_0 t)$$

$$A_5 \sin(5\pi - 5\omega_0 t) + A_7 \sin(7\pi - 7\omega_0 t)$$

$$= -A_1 \sin \omega_0 t + A_3 \sin 3\omega_0 t - A_5 \sin 5\omega_0 t + A_7 \sin 7\omega_0 t$$

$\therefore f(T/2 - t) = f(t)$ and the voltage has quarter-wave symmetry

16.49

The input signal to a third-order low-pass Butterworth filter is a half-wave rectified sinusoidal voltage. The corner frequency of the filter is 100 rad/s . The amplitude of the sinusoidal voltage is $54\pi \text{ V}$ and its period is $5\pi \text{ ms}$. Write the first three terms of the Fourier series that represents the steady-state output voltage of the filter.

P 16.49 From Table 15.1 we have

$$H(s) = \frac{1}{(s+1)(s^2+s+1)}$$

After scaling we get

$$H'(s) = \frac{10^6}{(s+100)(s^2+100s+10^4)}$$

$$\omega_o = \frac{2\pi}{T} = \frac{2\pi}{5\pi} \times 10^3 = 400 \text{ rad/s}$$

$$\therefore H'(jn\omega_o) = \frac{1}{(1+j4n)[(1-16n^2)+j4n]}$$

It follows that

$$H(j0) = 1/\underline{0^\circ}$$

$$H(j\omega_o) = \frac{1}{(1 + j4)(-15 + j4)} = 0.0156 \underline{-241.03^\circ}$$

$$H(j2\omega_o) = \frac{1}{(1 + j8)(-63 + j8)} = 0.00195 \underline{-255.64^\circ}$$

$$\begin{aligned} v_g(t) &= \frac{A}{\pi} + \frac{A}{2} \sin \omega_o t - \frac{2A}{\pi} \sum_{n=2,4,6,\dots}^{\infty} \frac{\cos n\omega_o t}{n^2 - 1} \\ &= 54 + 27\pi \sin \omega_o t - 36 \cos 2\omega_o t - \dots \text{ V} \end{aligned}$$

$$\therefore v_o = 54 + 1.33 \sin(400t - 241.03^\circ) - 0.07 \cos(800t - 255.64^\circ) - \dots \text{ V}$$