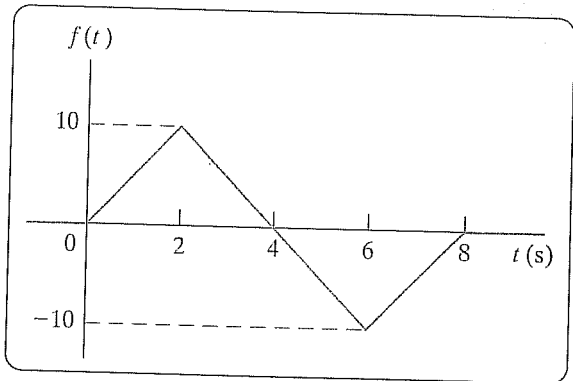


× 12.19

- Find the Laplace transform of the function illustrated in Fig. P12.19.
- Find the Laplace transform of the first derivative of the function illustrated in Fig. P12.19.
- Find the Laplace transform of the second derivative of the function illustrated in Fig. P12.19.

Figure P12.19



P 12.19 [a]  $f(t) = 5t[u(t) - u(t - 2)]$

$$+(20 - 5t)[u(t - 2) - u(t - 6)]$$


$$+(5t - 40)[u(t - 6) - u(t - 8)]$$

$$= 5tu(t) - 10(t - 2)u(t - 2)$$

$$+10(t - 6)u(t - 6) - 5(t - 8)u(t - 8)$$

$$\therefore F(s) = \frac{5[1 - 2e^{-2s} + 2e^{-6s} - e^{-8s}]}{s^2}$$

[b]

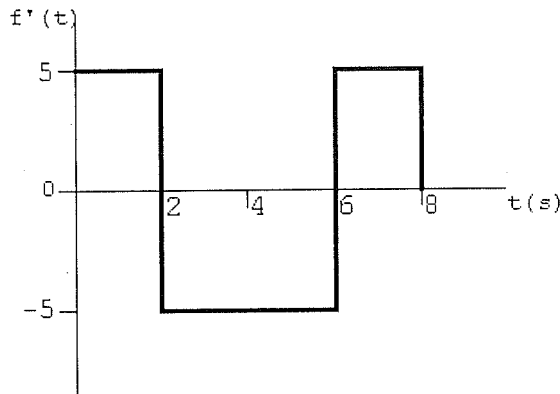


$$f'(t) = 5[u(t) - u(t - 2)] - 5[u(t - 2) - u(t - 6)]$$

$$+5[u(t - 6) - u(t - 8)]$$

$$= 5u(t) - 10u(t - 2) + 10u(t - 6) - 5u(t - 8)$$

$$\mathcal{L}\{f'(t)\} = \frac{5[1 - 2e^{-2s} + 2e^{-6s} - e^{-8s}]}{s}$$

[c]

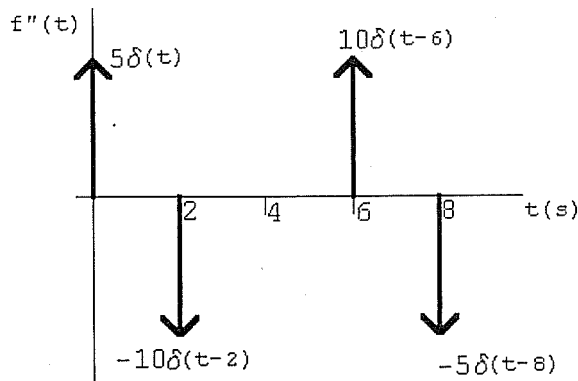

$$f''(t) = 5\delta(t) - 10\delta(t - 2) + 10\delta(t - 6) - 5\delta(t - 8)$$

$$\mathcal{L}\{f''(t)\} = 5[1 - 2e^{-2s} + 2e^{-6s} - e^{-8s}]$$

12.21

Find the Laplace transform of each of the following functions:

a)  $f(t) = 40e^{-8(t-3)}u(t-3).$

b)  $f(t) = (5t - 10)[u(t - 2) - u(t - 4)] + (30 - 5t)[u(t - 4) - u(t - 8)] + (5t - 50)[u(t - 8) - u(t - 10)].$

P 12.21 [a]  $\mathcal{L}\{40e^{-8(t-3)}u(t-3)\} = \frac{40e^{-3s}}{(s+8)}$

[b] First rewrite  $f(t)$  as

$$\begin{aligned}f(t) &= (5t - 10)u(t - 2) + (40 - 10t)u(t - 4) \\ &\quad + (10t - 80)u(t - 8) + (50 - 5t)u(t - 10) \\ &= 5(t - 2)u(t - 2) - 10(t - 4)u(t - 4) \\ &\quad + 10(t - 8)u(t - 8) - 5(t - 10)u(t - 10)\end{aligned}$$

$$\therefore F(s) = \frac{5[e^{-2s} - 2e^{-4s} + 2e^{-8s} - e^{-10s}]}{s^2}$$

In the circuit shown in Fig. 12.16, the dc current source is replaced with a sinusoidal source that delivers a current of  $1.2 \cos t$  A. The circuit components are  $R = 1 \Omega$ ,  $C = 625$  mF, and  $L = 1.6$  H. Find the numerical expression for  $V(s)$ .

$$\text{P 12.26 } I_g(s) = \frac{1.2s}{s^2 + 1}; \quad \frac{1}{RC} = 1.6; \quad \frac{1}{LC} = 1; \quad \frac{1}{C} = 1.6$$

$$\frac{V(s)}{R} + \frac{1}{L} \frac{V(s)}{s} + C[sV(s) - v(0^-)] = I_g(s)$$

$$V(s) \left[ \frac{1}{R} + \frac{1}{Ls} + sC \right] = I_g(s)$$

$$V(s) = \frac{I_g(s)}{\frac{1}{R} + \frac{1}{Ls} + sC} = \frac{LsI_g(s)}{\frac{L}{R}s + 1 + s^2LC} = \frac{\frac{1}{C}sI_g(s)}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$$= \frac{(1.6)(1.2)s^2}{(s^2 + 1.6s + 1)(s^2 + 1)} = \frac{1.92s^2}{(s^2 + 1.6s + 1)(s^2 + 1)}$$

**X 12.31**


There is no energy stored in the circuit shown in Fig. P12.31 at the time the switch is opened.

- a) Derive the integrodifferential equations that govern the behavior of the node voltages  $v_1$  and  $v_2$ .

b) Show that

$$V_2(s) = \frac{sI_g(s)}{C[s^2 + (R/L)s + (1/LC)]}$$

Figure P12.31

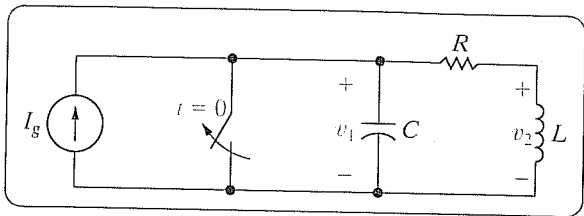



P 12.31 [a]  $C \frac{dv_1}{dt} + \frac{v_1 - v_2}{R} = i_g$

$$\frac{1}{L} \int_0^t v_2 d\tau + \frac{v_2 - v_1}{R} = 0$$

or

$$C \frac{dv_1}{dt} + \frac{v_1}{R} - \frac{v_2}{R} = i_g$$

$$-\frac{v_1}{R} + \frac{v_2}{R} + \frac{1}{L} \int_0^t v_2 d\tau = 0$$

[b]  $CsV_1(s) + \frac{V_1(s)}{R} - \frac{V_2(s)}{R} = I_g(s)$

$$-\frac{V_1(s)}{R} + \frac{V_2(s)}{R} + \frac{V_2(s)}{sL} = 0$$

or

$$(RCs + 1)V_1(s) - V_2(s) = RI_g(s)$$

$$-sLV_1(s) + (R + sL)V_2(s) = 0$$

Solving,

$$V_2(s) = \frac{sI_g(s)}{C[s^2 + (R/L)s + (1/LC)]}$$

\* 12.32

**P**

The circuit parameters in the circuit in Fig. P12.31 are  $R = 1600 \Omega$ ;  $L = 200 \text{ mH}$ ; and  $C = 0.2 \mu\text{F}$ . If  $i_g(t) = 6 \text{ mA}$ , find  $v_2(t)$ .

$$\text{P 12.32} \quad \frac{1}{C} = 5 \times 10^6; \quad \frac{1}{LC} = 25 \times 10^6; \quad \frac{R}{L} = 8000$$

$$V_2(s) = \frac{(6 \times 10^{-3})(5 \times 10^6)}{s^2 + 8000s + 25 \times 10^6}$$

$$s_{1,2} = -4000 \pm j3000$$

$$V_2(s) = \frac{30,000}{(s + 4000 - j3000)(s + 4000 + j3000)}$$

$$= \frac{K_1}{s + 4000 - j3000} + \frac{K_1^*}{s + 4000 + j3000}$$

$$K_1 = \frac{30.000}{j6000} = -j5 = 5 \underline{\angle -90^\circ}$$

$$\begin{aligned} v_2(t) &= 10e^{-4000t} \cos(3000t - 90^\circ) \\ &= [10e^{-4000t} \sin 3000t]u(t) \text{ V} \end{aligned}$$