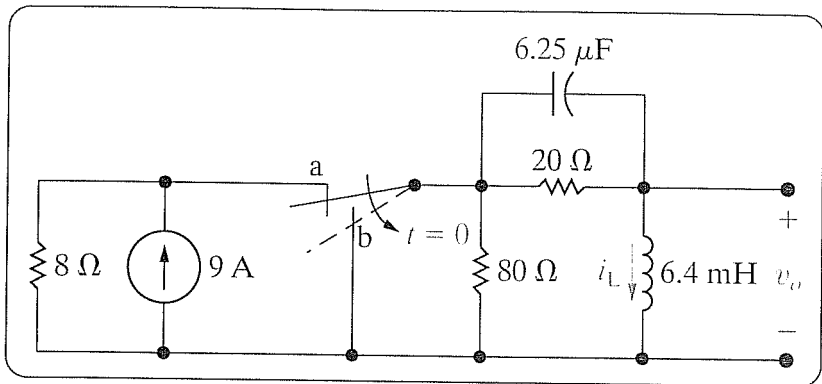


13.10




The switch in the circuit in Fig. P13.10 has been in position a for a long time. At $t = 0$, the switch moves instantaneously to position b.

Figure P13.10



- Construct the s -domain circuit for $t > 0$.
- Find V_o .
- Find I_L .
- Find v_o for $t > 0$.
- Find i_L for $t > 0$.

P 13.10 [a] For $t < 0$:

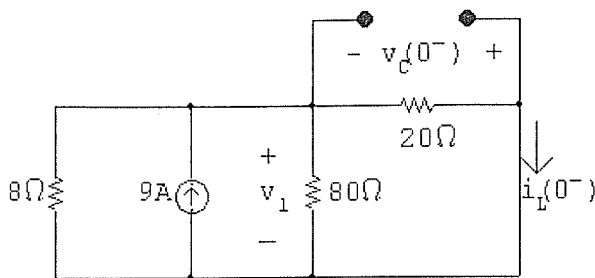


$$\frac{1}{R_e} = \frac{1}{8} + \frac{1}{80} + \frac{1}{20} = 0.1875; \quad R_e = 5.33 \Omega$$

$$v_1 = (9)(5.33) = 48 \text{ V}$$


$$i_L(0^-) = \frac{48}{20} = 2.4 \text{ A}$$

$$v_C(0^-) = -v_1 = -48 \text{ V}$$

For $t = 0^+$:

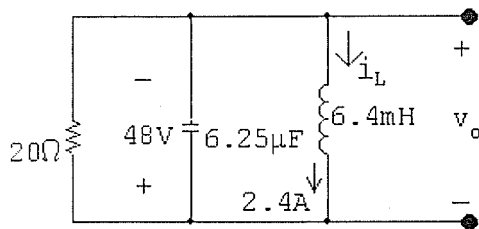

s -domain circuit:

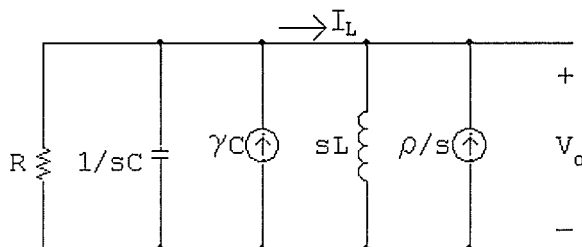

where

$$R = 20 \Omega; \quad C = 6.25 \mu\text{F}; \quad \gamma = -48 \text{ V};$$

$$L = 6.4 \text{ mH}; \quad \text{and} \quad \rho = -2.4 \text{ A}$$

$$[b] \quad \frac{V_o}{R} + V_o s C - \gamma C + \frac{V_o}{s L} - \frac{\rho}{s} = 0$$

$$\therefore V_o = \frac{\gamma[s + (\rho/\gamma C)]}{s^2 + (1/RC)s + (1/LC)}$$

$$\frac{\rho}{\gamma C} = \frac{-2.4}{(-48)(6.25 \times 10^{-6})} = 8000$$

$$\frac{1}{RC} = \frac{1}{(20)(6.25 \times 10^{-6})} = 8000$$

$$\frac{1}{LC} = \frac{1}{(6.4 \times 10^{-3})(6.25 \times 10^{-6})} = 25 \times 10^6$$

$$V_o = \frac{-48(s + 8000)}{s^2 + 8000s + 25 \times 10^6}$$

$$\begin{aligned} \text{[c]} \quad I_L &= \frac{V_o}{sL} - \frac{\rho}{s} = \frac{V_o}{0.0064s} + \frac{2.4}{s} \\ &= \frac{-7500(s + 8000)}{s(s^2 + 8000s + 25 \times 10^6)} + \frac{2.4}{s} = \frac{2.4(s + 4875)}{(s^2 + 8000s + 25 \times 10^6)} \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad V_o &= \frac{-48(s + 8000)}{s^2 + 8000s + 25 \times 10^6} \\ &= \frac{K_1}{s + 4000 - j3000} + \frac{K_1^*}{s + 4000 + j3000} \end{aligned}$$

$$K_1 = \frac{-48(s + 8000)}{s + 4000 + j3000} \Big|_{s=-4000+j3000} = 40/\underline{126.87^\circ}$$

$$v_o(t) = [80e^{-4000t} \cos(3000t + 126.87^\circ)]u(t) \text{ V}$$

$$\begin{aligned} \text{[e]} \quad I_L &= \frac{2.4(s + 4875)}{s^2 + 8000s + 25 \times 10^6} \\ &= \frac{K_1}{s + 4000 - j3000} + \frac{K_1^*}{s + 4000 + j3000} \end{aligned}$$

$$K_1 = \frac{2.4(s + 4875)}{s + 4000 + j3000} \Big|_{s=-4000+j3000} = 1.25/\underline{-16.26^\circ}$$

$$i_L(t) = [2.5e^{-4000t} \cos(3000t - 16.26^\circ)]u(t) \text{ A}$$


13.15


There is no energy stored in the circuit in Fig. P13.15 at the time the switch is closed.

P

- Find v_o for $t \geq 0$.
- Does your solution make sense in terms of known circuit behavior? Explain.

Figure P13.15

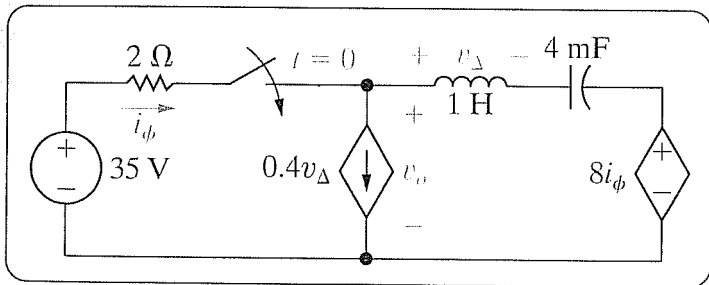

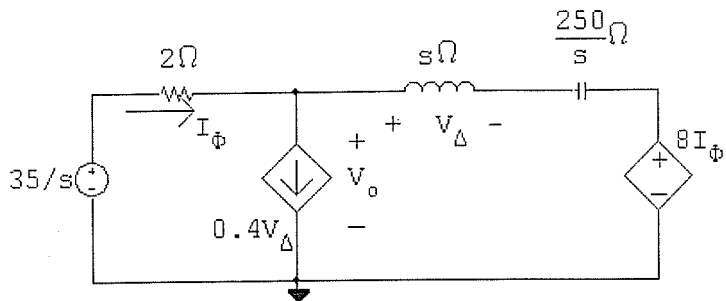

$$\frac{V_o - 35/s}{2} + 0.4V_\Delta + \frac{V_o - 8I_\phi}{s + (250/s)} = 0$$

$$V_\Delta = \left[\frac{V_o - 8I_\phi}{s + (250/s)} \right] s; \quad I_\phi = \frac{(35/s) - V_o}{2}$$

Solving for V_o yields:

$$V_o = \frac{29.4s^2 + 56s + 1750}{s(s^2 + 2s + 50)} = \frac{29.4s^2 + 56s + 1750}{s(s + 1 - j7)(s + 1 + j7)}$$

$$V_o = \frac{K_1}{s} + \frac{K_2}{s + 1 - j7} + \frac{K_2^*}{s + 1 + j7}$$


$$K_1 = \left. \frac{29.4s^2 + 56s + 1750}{s^2 + 2s + 50} \right|_{s=0} = 35$$

$$K_2 = \left. \frac{29.4s^2 + 56s + 1750}{s(s + 1 + j7)} \right|_{s=-1+j7}$$

$$= -2.8 + j0.6 = 2.86/167.91^\circ$$

$$\therefore v_o(t) = [35 + 5.73e^{-t} \cos(7t + 167.91^\circ)]u(t) \text{ V}$$

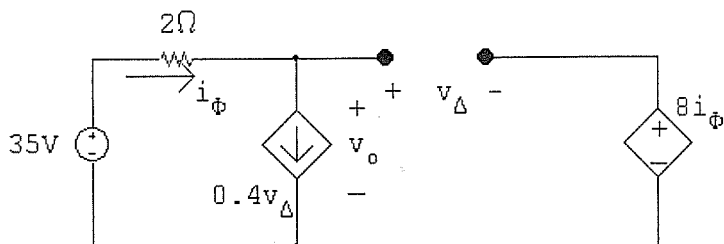[b] At $t = 0^+$ $v_o = 35 + 5.73 \cos(167.91^\circ) = 29.4 \text{ V}$




$$\frac{v_o - 35}{2} + 0.4v_\Delta = 0; \quad v_o - 35 + 0.8v_\Delta = 0$$

$$v_o = v_\Delta + 8i_\phi = v_\Delta + 8(0.4v_\Delta) = 4.2v_\Delta$$

$$v_o + (0.8) \frac{v_o}{4.2} = 35; \quad \therefore v_o(0^+) = 29.4 \text{ V (Checks)}$$

At $t = \infty$, the circuit is

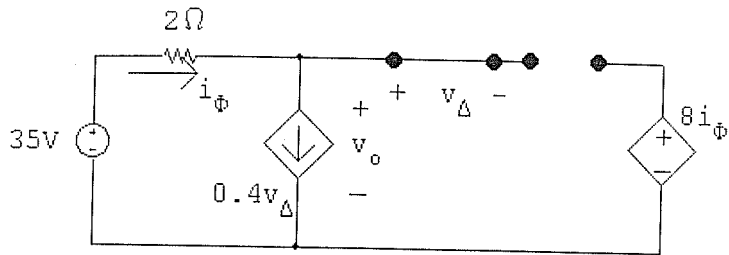


$$v_\Delta = 0. \quad i_\phi = 0 \quad \therefore v_o = 35 \text{ V (Checks)}$$


- 13.17 Find v_o in the circuit shown in Fig. P13.17 if $i_g = 5u(t)$ mA. There is no energy stored in the circuit at $t = 0$.



Figure P13.17

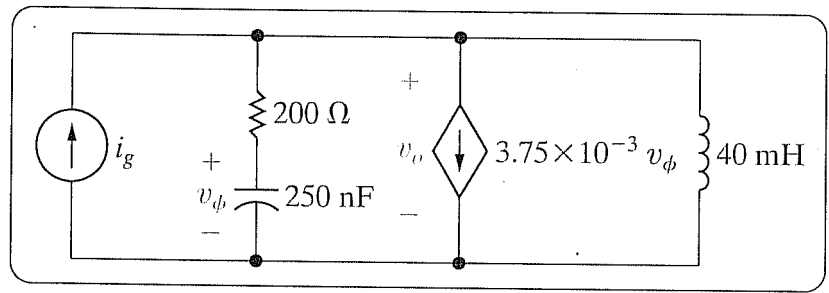

P 13.17

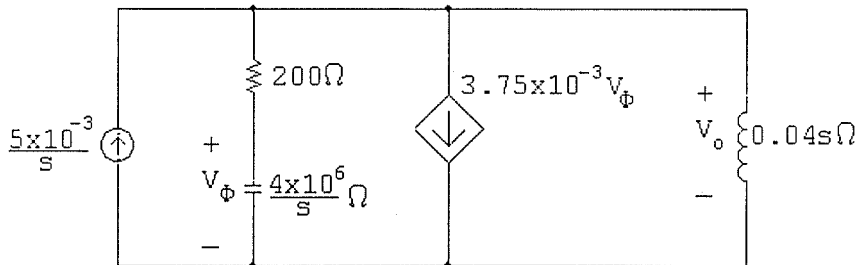

$$\frac{5 \times 10^{-3}}{s} = \frac{V_o}{200 + 4 \times 10^6/s} + 3.75 \times 10^{-3} V_\phi + \frac{V_o}{0.04s}$$

$$V_\phi = \frac{4 \times 10^6/s}{200 + 4 \times 10^6/s} V_o = \frac{4 \times 10^6 V_o}{200s + 4 \times 10^6}$$

$$\therefore \frac{5 \times 10^{-3}}{s} = \frac{V_o s}{200s + 4 \times 10^6} + \frac{15,000 V_o}{200s + 4 \times 10^6} + \frac{25 V_o}{s}$$

$$\therefore V_o = \frac{s + 20,000}{s^2 + 20,000s + 10^8} = \frac{K_1}{(s + 10,000)^2} + \frac{K_2}{s + 10,000}$$

$$K_1 = 10,000; \quad K_2 = 1$$

$$V_o = \frac{10,000}{(s + 10,000)^2} + \frac{1}{s + 10,000}$$


$$v_o(t) = [10,000te^{-10,000t} + e^{-10,000t}]u(t) \text{ V}$$



The magnetically coupled coils in the circuit seen in Fig. P13.38 carry initial currents of 15 and 10 A, as shown.

- Find the initial energy stored in the circuit.
- Find I_1 and I_2 .
- Find i_1 and i_2 .
- Find the total energy dissipated in the 120 Ω and 270 Ω resistors.
- Repeat (a)–(d), with the dot on the 18 H inductor at the lower terminal.

Figure P13.38

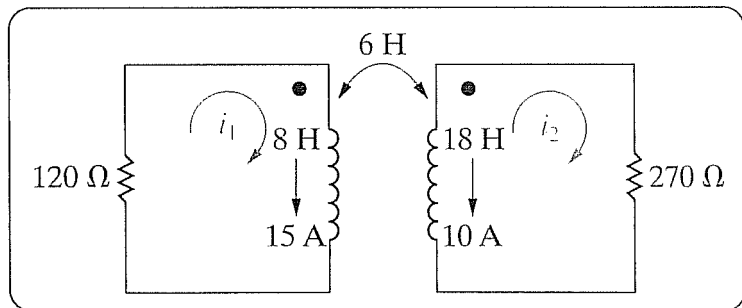

P 13.38 [a] $W = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + Mi_1i_2$

$$W = 4(15)^2 + 9(100) + 150(6) = 2700 \text{ J}$$

[b] $120i_1 + 8\frac{di_1}{dt} - 6\frac{di_2}{dt} = 0$

$$270i_2 + 18\frac{di_2}{dt} - 6\frac{di_1}{dt} = 0$$

Laplace transform the equations to get

$$120I_1 + 8(sI_1 - 15) - 6(sI_2 + 10) = 0$$

$$270I_2 + 18(sI_2 + 10) - 6(sI_1 - 15) = 0$$

In standard form,

$$(8s + 120)I_1 - 6sI_2 = 180$$

$$-6sI_1 + (18s + 270)I_2 = -270$$

$$\Delta = \begin{vmatrix} 8s + 120 & -6s \\ -6s & 18s + 270 \end{vmatrix} = 108(s + 10)(s + 30)$$

$$N_1 = \begin{vmatrix} 180 & -6s \\ -270 & 18s + 270 \end{vmatrix} = 1620(s + 30)$$

$$N_2 = \begin{vmatrix} 8s + 120 & 180 \\ -6s & -270 \end{vmatrix} = -1080(s + 30)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{1620(s+30)}{108(s+10)(s+30)} = \frac{15}{s+10}$$

$$I_2 = \frac{N_2}{\Delta} = \frac{-1080(s+30)}{108(s+10)(s+30)} = \frac{-10}{s+10}$$

[c] $i_1(t) = 15e^{-10t}u(t)$ A; $i_2(t) = -10e^{-10t}u(t)$ A

[d] $W_{120\Omega} = \int_0^{\infty} (225e^{-20t})(120) dt = 27,000 \frac{e^{-20t}}{-20} \Big|_0^{\infty} = 1350$ J

$$W_{270\Omega} = \int_0^{\infty} (100e^{-20t})(270) dt = 27,000 \frac{e^{-20t}}{-20} \Big|_0^{\infty} = 1350$$
 J

$$W_{120\Omega} + W_{270\Omega} = 2700$$
 J (Checks)

[e] $W = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + Mi_1i_2 = 900 + 900 - 900 = 900$ J

With the dot reversed the s -domain equations are

$$(8s + 120)I_1 + 6sI_2 = 60$$

$$6sI_1 + (18s + 270)I_2 = -90$$

As before, $\Delta = 108(s+10)(s+30)$. Now,

$$N_1 = \begin{vmatrix} 60 & 6s \\ -90 & 18s + 270 \end{vmatrix} = 1620(s+10)$$

$$N_2 = \begin{vmatrix} 8s + 120 & 60 \\ 6s & -90 \end{vmatrix} = -1080(s+10)$$

$$I_1 = \frac{N_1}{\Delta} = \frac{15}{s+30}; \quad I_2 = \frac{N_2}{\Delta} = \frac{-10}{s+30}$$

$$i_1(t) = 15e^{-30t}u(t)$$
 A; $i_2(t) = -10e^{-30t}u(t)$ A


$$W_{270\Omega} = \int_0^{\infty} (100e^{-60t})(270) dt = 450$$
 J

$$W_{120\Omega} = \int_0^{\infty} (225e^{-60t})(120) dt = 450$$
 J

$$W_{120\Omega} + W_{270\Omega} = 900$$
 J (Checks)

13.67 The sinusoidal voltage pulse shown in Fig. P13.67(a) is applied to the circuit shown in Fig. P13.67(b). Use the convolution integral to find the value of v_o at $t = 2.2$ s.

Figure P13.67

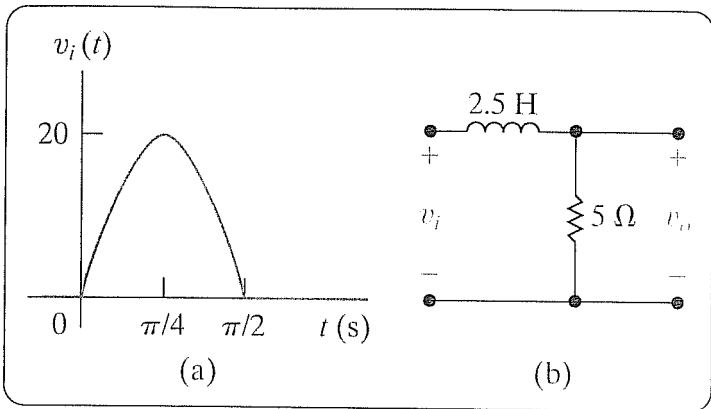

$$\text{P 13.67 } H(s) = \frac{V_o}{V_i} = \frac{5}{5 + 2.5s} = \frac{2}{s + 2}$$

$$h(\lambda) = 2e^{-2\lambda}; \quad h(t - \lambda) = 2e^{-2(t-\lambda)} = 2e^{-2t}e^{2\lambda}$$

$$\frac{T}{2} = \frac{\pi}{2}; \quad T = \pi \text{ s}; \quad f = \frac{1}{\pi} \text{ Hz}$$

$$v_i(\lambda) = (20 \sin 2\lambda)[u(\lambda) - u(\lambda - \pi/2)]$$

$$(\pi/2) \text{ s} \leq t \leq \infty:$$

$$\begin{aligned} v_o &= \int_0^{\pi/2} (2e^{-2t}e^{2\lambda})(20 \sin 2\lambda) d\lambda = 40e^{-2t} \int_0^{\pi/2} e^{2\lambda} \sin 2\lambda d\lambda \\ &= 40e^{-2t} \left[\frac{e^{2\lambda}}{8} (2 \sin 2\lambda - 2 \cos 2\lambda) \right]_0^{\pi/2} = 10e^{-2t} [e^\pi (\sin \pi - \cos \pi) - 1(0 - 1)] \\ &= 10e^{-2t} (e^\pi + 1) = 10(e^\pi + 1)e^{-2t} \text{ V} \end{aligned}$$

$$v_o(2.2) = 241.41e^{-4.4} = 2.96 \text{ V}$$

