


## 13.39

In the circuit in Fig. P13.39, switch 1 closes at  $t = 0$ , and the make-before-break switch moves instantaneously from position a to position b.




- Construct the  $s$ -domain equivalent circuit for  $t > 0$ .
- Find  $I_1$ .
- Use the initial- and final-value theorems to check the initial and final values of  $i_1$ .
- Find  $i_1$  for  $t \geq 0^+$ .

Figure P13.39

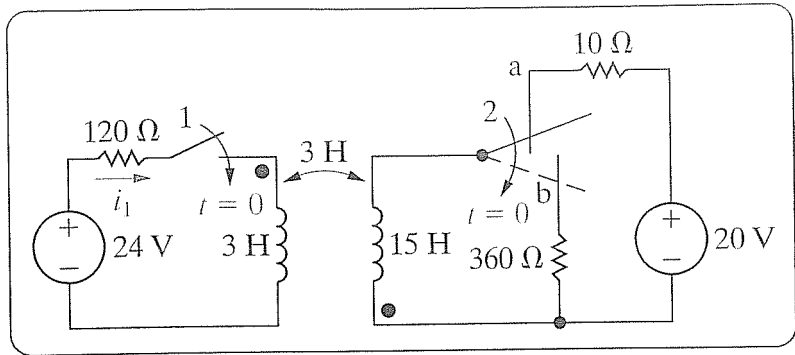

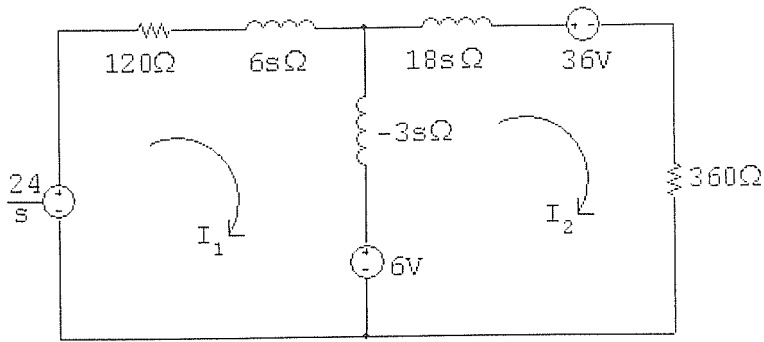P 13.39 [a]  $s$ -domain equivalent circuit is



Note:  $i_2(0^+) = -\frac{20}{10} = -2 \text{ A}$

[b]  $\frac{24}{s} = (120 + 3s)I_1 + 3sI_2 + 6$

$0 = -6 + 3sI_1 + (360 + 15s)I_2 + 36$

In standard form,

$(s + 40)I_1 + sI_2 = (8/s) - 2$

$sI_1 + (5s + 120)I_2 = -10$

$\Delta = \begin{vmatrix} s + 40 & s \\ s & 5s + 120 \end{vmatrix} = 4(s + 20)(s + 60)$

$N_1 = \begin{vmatrix} (8/s) - 2 & s \\ -10 & 5s + 120 \end{vmatrix} = \frac{-200(s - 4.8)}{s}$

$I_1 = \frac{N_1}{\Delta} = \frac{-50(s - 4.8)}{s(s + 20)(s + 60)}$

[c]  $sI_1 = \frac{-50(s - 4.8)}{(s + 20)(s + 60)}$

$\lim_{s \rightarrow \infty} sI_1 = i_1(0^+) = 0 \text{ A}$

$\lim_{s \rightarrow 0} sI_1 = i_1(\infty) = \frac{(-50)(-4.8)}{(20)(60)} = 0.2 \text{ A}$

[d]  $I_1 = \frac{K_1}{s} + \frac{K_2}{s + 20} + \frac{K_3}{s + 60}$

$K_1 = \frac{240}{1200} = 0.2; \quad K_2 = \frac{-50(-20) + 240}{(-20)(40)} = -1.55$

$$K_3 = \frac{-50(-60) + 240}{(-60)(-40)} = 1.35$$


$$i_1(t) = [0.2 - 1.55e^{-20t} + 1.35e^{-60t}]u(t) \text{ A}$$


13.44



Find  $v_o(t)$  in the circuit shown in Fig. P13.44 if the ideal op amp operates within its linear range and  $v_g = 4.8u(t)$  V.

Figure P13.44

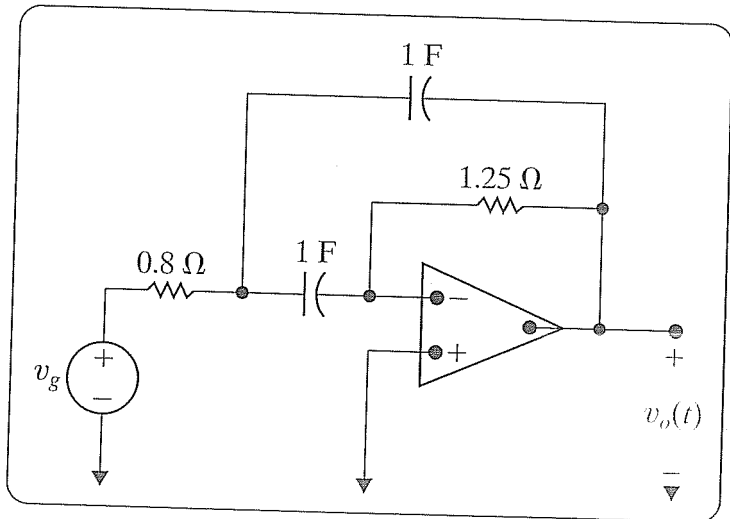

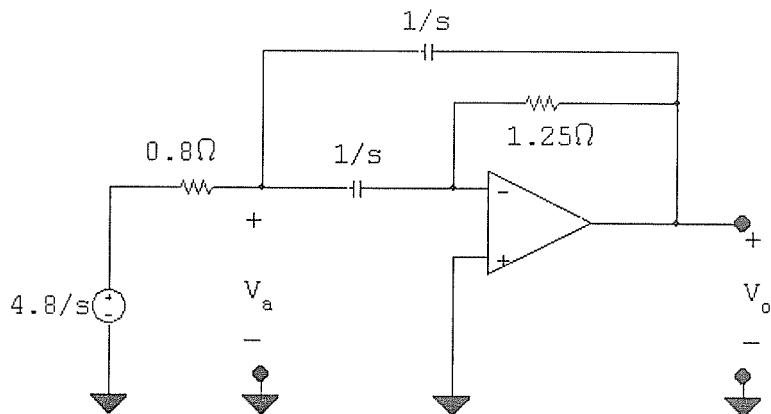

$$\frac{V_a - 4.8/s}{0.8} + \frac{V_a}{1/s} + \frac{V_a - V_o}{1/s} = 0$$

$$\frac{0 - V_a}{1/s} + \frac{0 - V_o}{1.25} = 0$$

$$V_a = \frac{-V_o}{1.25s}$$

$$V_a(2s + 1.25) - sV_o = 6/s$$

$$-V_o \left[ \frac{(2s + 1.25)}{1.25s} + s \right] = 6/s$$

$$-V_o \left[ \frac{125s^2 + 2s + 1.25}{1.25s} \right] = 6/s$$

$$V_o = \frac{-7.5}{1.25s^2 + 2s + 1.25} = \frac{-6}{s^2 + 1.6s + 1}$$

$$= \frac{K_1}{s + 0.8 - j0.6} + \frac{K_1^*}{s + 0.8 + j0.6}$$


$$K_1 = \frac{-6}{s + 0.8 + j0.6} \Big|_{s=-0.8+j0.6} = 5 \angle 90^\circ$$

$$v_o(t) = 10e^{-0.8t} \cos(0.6t + 90^\circ)u(t) \text{ V} = -10e^{-0.8t} \sin(0.6t)u(t) \text{ V}$$

**13.52** The operational amplifier in the circuit in Fig. P13.52 is ideal.

- Find the numerical expression for the transfer function  $H(s) = V_o/V_g$ .
- Give the numerical value of each zero and pole of  $H(s)$ .

**Figure P13.52**

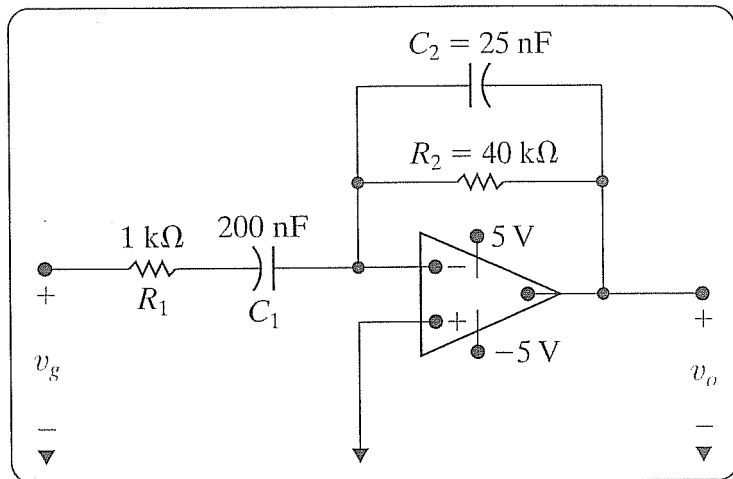



$$\text{P 13.52 [a]} \quad Z_i = 1000 + \frac{5 \times 10^6}{s} = \frac{1000(s + 5000)}{s}$$

$$Z_f = \frac{40 \times 10^6}{s} \parallel 40,000 = \frac{40 \times 10^6}{s + 1000}$$


$$H(s) = -\frac{Z_f}{Z_i} = \frac{-40 \times 10^6 / (s + 1000)}{1000(s + 5000) / s} = \frac{-40,000s}{(s + 1000)(s + 5000)}$$


**[b]** Zero at  $s = 0$ ;      Poles at  $-p_1 = -1000$  rad/s and  $-p_2 = -5000$  rad/s

13.54

In the circuit of Fig. P13.54  $v_o$  is the output signal and  $v_g$  is the input signal. Find the poles and zeros of the transfer function.

Figure P13.54

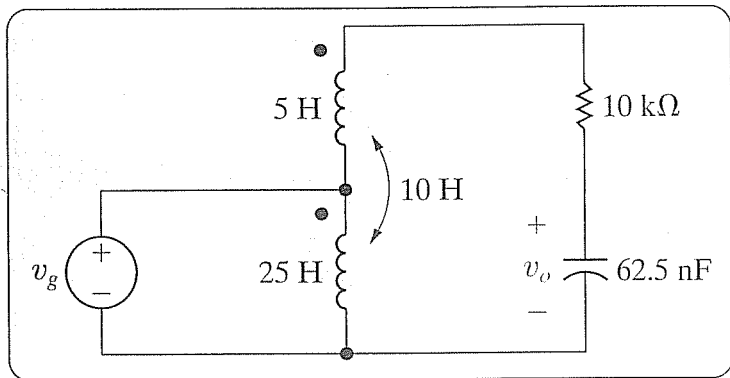

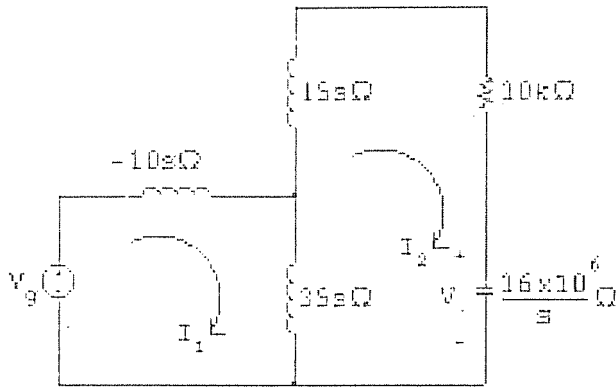

$$V_g = 25sI_1 - 35sI_2$$

$$0 = -35sI_1 + \left( 50s + 10,000 + \frac{16 \times 10^6}{s} \right) I_2$$

$$\Delta = \begin{vmatrix} 25s & -35s \\ -35s & 50s + 10,000 + 16 \times 10^6/s \end{vmatrix} = 25(s + 2000)(s + 8000)$$

$$N_2 = \begin{vmatrix} 25s & V_g \\ -35s & 0 \end{vmatrix} = 35sV_g$$

$$I_2 = \frac{N_2}{\Delta} = \frac{35sV_g}{25(s + 2000)(s + 8000)}$$

$$V_o = \frac{16 \times 10^6}{s} I_2 = \frac{22.4 \times 10^6 V_g}{(s + 2000)(s + 8000)}$$

$$H(s) = \frac{V_o}{V_g} = \frac{22.4 \times 10^6}{(s + 2000)(s + 8000)}$$


$$\therefore -p_1 = -2000 \text{ rad/s}; \quad -p_2 = -8000 \text{ rad/s}$$

13.56



- a) Find the transfer function  $I_o/I_g$  as a function of  $\mu$  for the circuit seen in Fig. P13.56.
- b) Find the largest value of  $\mu$  that will produce a bounded output signal for a bounded input signal.
- c) Find  $i_o$  for  $\mu = -3, 0, 4, 5,$  and  $6$  if  $i_g = 5u(t)$  A.

P 13.56 [a]

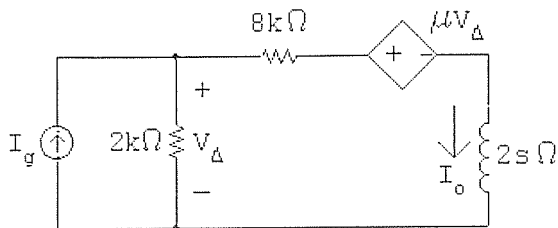

$$2000(I_o - I_g) + 8000I_o + \mu(I_g - I_o)(2000) + 2sI_o = 0$$

$$\therefore I_o = \frac{1000(1 - \mu)}{s + 1000(5 - \mu)} I_g$$

$$\therefore H(s) = \frac{1000(1 - \mu)}{s + 1000(5 - \mu)}$$

[b]  $\mu < 5$

[c]

$\mu$	$H(s)$	$I_o$
-3	$4000/(s + 8000)$	$20,000/s(s + 8000)$
0	$1000/(s + 5000)$	$5000/s(s + 5000)$
4	$-3000/(s + 1000)$	$-15,000/s(s + 1000)$
5	$-4000/s$	$-20,000/s^2$
6	$-5000/(s - 1000)$	$-25,000/s(s - 1000)$

$\mu = -3$ :

$$I_o = \frac{2.5}{s} - \frac{2.5}{(s + 8000)}; \quad i_o = [2.5 - 2.5e^{-8000t}]u(t) \text{ A}$$

$\mu = 0$ :

$$I_o = \frac{1}{s} - \frac{1}{s + 5000}; \quad i_o = [1 - e^{-5000t}]u(t) \text{ A}$$

$\mu = 4$ :

$$I_o = \frac{-15}{s} + \frac{15}{s + 1000}; \quad i_o = [-15 + 15e^{-1000t}]u(t) \text{ A}$$

$\mu = 5$ :

$$I_o = \frac{-20,000}{s^2}; \quad i_o = -20,000t u(t) \text{ A}$$

$$\mu = 6:$$

$$I_o = \frac{25}{s} - \frac{25}{s - 1000};$$

$$i_o = 25[1 - e^{1000t}]u(t) \text{ A}$$