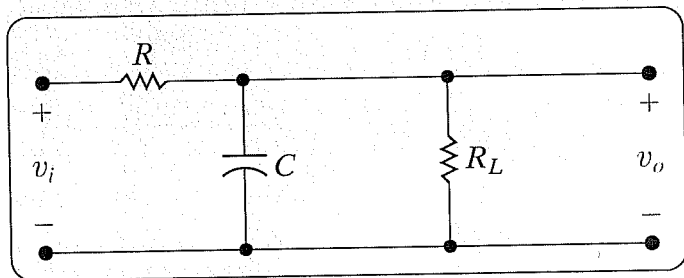


**14.5** A resistor denoted as  $R_L$  is connected in parallel with the capacitor in the circuit in Fig. 14.7. The loaded low-pass filter circuit is shown in Fig. P14.5.

- Derive the expression for the voltage transfer function  $V_o/V_i$ .
- At what frequency will the magnitude of  $H(j\omega)$  be maximum?
- What is the maximum value of the magnitude of  $H(j\omega)$ ?
- At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by  $\sqrt{2}$ ?
- Assume a resistance of  $10\text{ k}\Omega$  is added in parallel with the  $100\text{ nF}$  capacitor in the circuit in Fig. P14.4. Find  $\omega_c$ ,  $H(j0)$ ,  $H(j\omega_c)$ ,  $H(j0.1\omega_c)$ , and  $H(j10\omega_c)$ .

**Figure P14.5**



P 14.5 [a] Let  $Z = \frac{R_L(1/sC)}{R_L + 1/sC} = \frac{R_L}{R_LCs + 1}$

$$\begin{aligned} \text{Then } H(s) &= \frac{Z}{Z + R} \\ &= \frac{R_L}{RR_LCs + R + R_L} \\ &= \frac{(1/RC)}{s + \left(\frac{R + R_L}{RR_LC}\right)} \end{aligned}$$

[b]  $|H(j\omega)| = \frac{(1/RC)}{\sqrt{\omega^2 + [(R + R_L)/RR_LC]^2}}$

$|H(j\omega)|$  is maximum at  $\omega = 0$

[c]  $|H(j\omega)|_{\max} = \frac{R_L}{R + R_L}$

[d]  $|H(j\omega_c)| = \frac{R_L}{\sqrt{2}(R + R_L)} = \frac{(1/RC)}{\sqrt{\omega_c^2 + [(R + R_L)/RR_LC]^2}}$

$$\therefore \omega_c = \frac{R + R_L}{RR_LC} = \frac{1}{RC} (1 + (R/R_L))$$

[e]  $\omega_c = \frac{1}{(10^3)(10^{-7})} [1 + (10^3/10^4)] = 10,000(1 + 0.1) = 11,000 \text{ rad/s}$

$$H(j0) = \frac{10,000}{11,000} = 0.9091 \underline{0^\circ}$$

$$H(j\omega_c) = \frac{10,000}{11,000 + j11,000} = 0.6428 \underline{\underline{-45^\circ}}$$

$$H(j0.1\omega_c) = \frac{10,000}{11,000 + j1100} = 0.9046 \underline{\underline{-5.71^\circ}}$$

$$H(j10\omega_c) = \frac{10,000}{11,000 + j110,000} = 0.0905 \underline{\underline{-84.29^\circ}}$$

**14.6** Use a  $0.5 \mu\text{F}$  capacitor to design a low-pass passive filter with a cutoff frequency of  $50 \text{ krad/s}$ .



- a) Specify the cutoff frequency in hertz.
- b) Specify the value of the filter resistor.
- c) Assume the cutoff frequency cannot increase by more than 5%. What is the smallest value of load resistance that can be connected across the output terminals of the filter?
- d) If the resistor found in (c) is connected across the output terminals, what is the magnitude of  $H(j\omega)$  when  $\omega = 0$ ?

P 14.6 [a]  $f_c = \frac{\omega_c}{2\pi} = \frac{50,000}{2\pi} = \frac{50}{2\pi} \times 10^3 = 7957.75 \text{ Hz}$

[b]  $\frac{1}{RC} = 50 \times 10^3$

$$R = \frac{1}{(50 \times 10^3)(0.5 \times 10^{-6})} = 40 \Omega$$

[c]  $\omega_c = \frac{1}{RC} \left(1 + \frac{R}{R_L}\right)$

$$\therefore \frac{R}{R_L} = 0.05 \quad \therefore R_L = 20R = 800 \Omega$$

[d]  $H(j0) = \frac{R_L}{R + R_L} = \frac{800}{840} = 0.9524$

14.9



Using a  $100 \text{ nF}$  capacitor, design a high-pass passive filter with a cutoff frequency of  $300 \text{ Hz}$ .

- a) Specify the value of  $R$  in kilohms.
  
- b) A  $47 \text{ k}\Omega$  resistor is connected across the output terminals of the filter. What is the cutoff frequency, in hertz, of the loaded filter?

P 14.9 [a]  $\omega_c = \frac{1}{RC} = 2\pi(300) = 600\pi \text{ rad/s}$

$$\therefore R = \frac{1}{\omega_c C} = \frac{1}{(600\pi)(100 \times 10^{-9})} = 5305.16 \Omega$$

$$[\mathbf{b}] \quad R_e = 5305.16 \parallel 47,000 = 4767.08 \, \Omega$$

$$\omega_c = \frac{1}{R_e C} = \frac{1}{(4767.08)(100 \times 10^{-9})} = 2097.7 \text{ rad/s}$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{2097.7}{2\pi} = 333.86 \text{ Hz}$$



14.14



Use a 5 nF capacitor to design a series  $RLC$  band-pass filter, as shown at the top of Fig. 14.27. The center frequency of the filter is 8 kHz, and the quality factor is 2.

- a) Specify the values of  $R$  and  $L$ .
- b) What is the lower cutoff frequency in kilohertz?

- c) What is the upper cutoff frequency in kilohertz?
- d) What is the bandwidth of the filter in kilohertz?

P 14.14 [a]  $\omega_o^2 = \frac{1}{LC}$  so  $L = \frac{1}{[8000(2\pi)]^2(5 \times 10^{-9})} = 79.16 \text{ mH}$

$$R = \frac{\omega_o L}{Q} = \frac{8000(2\pi)(79.16 \times 10^{-3})}{2} = 1.99 \text{ k}\Omega$$

$$[\text{b}] f_{c1} = 8000 \left[ -\frac{1}{4} + \sqrt{1 + \frac{1}{16}} \right] = 6.25 \text{ kHz}$$

$$[\text{c}] f_{c2} = 8000 \left[ \frac{1}{4} + \sqrt{1 + \frac{1}{16}} \right] = 10.25 \text{ kHz}$$


$$[\text{d}] \beta = f_{c2} - f_{c1} = 4 \text{ kHz}$$

or

$$\beta = \frac{f_o}{Q} = \frac{8000}{2} = 4 \text{ kHz}$$

**14.15**

For the bandpass filter shown in Fig. P14.15, find (a)  $\omega_o$ , (b)  $f_o$ , (c)  $Q$ , (d)  $\omega_{c1}$ , (e)  $f_{c1}$ , (f)  $\omega_{c2}$ , (g)  $f_{c2}$ , and (h)  $\beta$ .

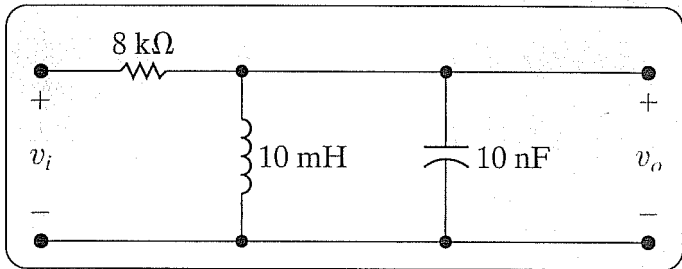**Figure P14.15**

$$\text{P 14.15 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(10 \times 10^{-3})(10 \times 10^{-9})} = 10^{10}$$

$$\omega_o = 10^5 \text{ rad/s} = 100 \text{ krad/s}$$

$$\text{[b]} \quad f_o = \frac{\omega_o}{2\pi} = \frac{10^5}{2\pi} = 15.92 \text{ kHz}$$

$$\text{[c]} \quad Q = \omega_o RC = (100 \times 10^3)(8000)(10 \times 10^{-9}) = 8$$

$$\text{[d]} \quad \omega_{c1} = \omega_o \left[ -\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] = 10^5 \left[ -\frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 93.95 \text{ krad/s}$$

$$\text{[e]} \quad \therefore f_{c1} = \frac{\omega_{c1}}{2\pi} = 14.96 \text{ kHz}$$

$$\text{[f]} \quad \omega_{c2} = \omega_o \left[ \frac{1}{2Q} + \sqrt{1 + \left( \frac{1}{2Q} \right)^2} \right] = 10^5 \left[ \frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 106.45 \text{ krad/s}$$

$$\text{[g]} \quad \therefore f_{c2} = \frac{\omega_{c2}}{2\pi} = 16.94 \text{ kHz}$$

$$\text{[h]} \quad \beta = \frac{\omega_o}{Q} = \frac{10^5}{8} = 12.5 \text{ krad/s or } 1.99 \text{ kHz}$$