

\angle -9- Find : $\mathcal{L}^{-1}\{(s-1)^{-3} + (s^2+2s-8)^{-1}\}$ p(13)

a. $0.5e^t t^2 + (2/3)e^t \cdot \text{Cosh}(3t)$

c. $0.5e^t t^2 + (1/3)e^t \cdot \text{Cosh}(3t)$

e. None of the above

b. $0.5e^t t^2 + (1/3)e^{-t} \cdot \text{Sinh}(3t)$

d. $0.5e^t t^2 + (2/3)e^{-t} \cdot \text{Cosh}(3t)$

L ✓ -1- The Laplace transform of $f(t) = \frac{\sin 5t}{t}$ is (p12)

- a. $(\pi/2) - \tan^{-1}(s/2)$ b. $(\pi/2) - \tan^{-1}(s)$ c. $(\pi/5) - \tan^{-1}(s/5)$
d. $(\pi/2) - \tan^{-1}(s/5)$ e. None of the above

L -2- The inverse Laplace transform of $F(s) = \frac{s+3}{s^2-s-2}$, is (p12)

- a. $(2/3)e^{2t} + (5/3)e^{-t}$ b. $(2/3)e^{2t} - (2/3)e^{-t}$
c. $(5/3)e^{2t} + (2/3)e^{-t}$ d. $(2/3)e^{2t} - (5/3)e^{-t}$ e. None of the above

L X

-5-

Find the Laplace transform of $f(t) = \begin{cases} t, & 0 \leq t \leq 2 \\ 2, & t > 2 \end{cases}$

(p 12)

a. $(1 - e^{-2s})/s^2$

b. $(1 - s - e^{-2s})/s^2$

c. $(1 - 2s - e^{-2s})/s^2$


d. $(1 - se^{-2s})/s^2$

e. None of the above


L

21. Find $I(t)$ for $t > 0$. (p34)

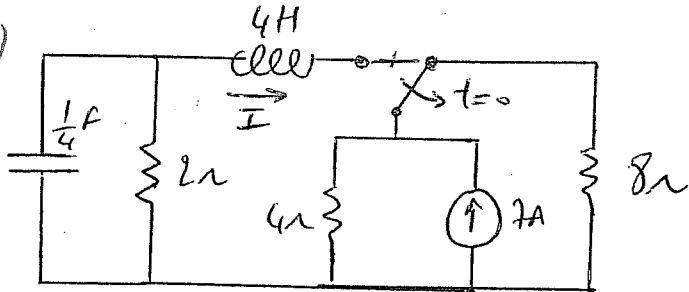- a) $e^{-2t}(4\cos t + 2\sin t)$
- b) $e^{-2t}(-4\cos t + 2\sin t)$
- c) $e^{-2t}(4\cos t - 2\sin t)$
- d) $-e^{-2t}(4\cos t + 2\sin t)$
- e) None of the above



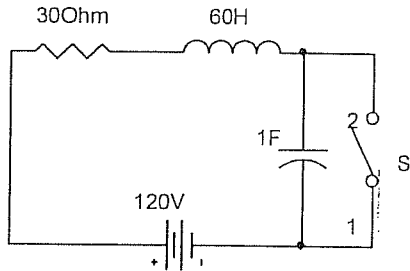-2- In the following circuit, the switch is opened at $t=0$. Find $I(s)$. (p14)



a. $\frac{240s+120}{60s^2+30s+1}$


b. $\frac{120}{s+0.46}$

c. $\frac{40s+2}{(s+46)(s+0.36)}$

d. $\frac{4s}{(s+0.46)(s+0.0036)}$

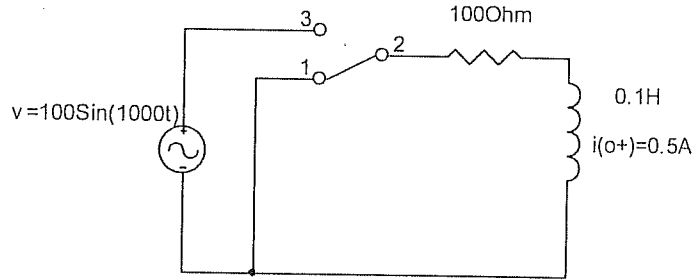e. None of the above

↳ -3- In the circuit shown, the switch has been for a long time at position 1. At $t=0$, it is moved to position 3. Find $I(s)$. (p15)




- a. $(0.5s^2 + 1.5 \times 10^6) / (s^2 + 10^6)(s + 1000)$
- b. $(10^6 s^2) / (s + 10^6)(s - 1000)$
- c. $(s^2 + 1.5 \times 10^6) / (s + 10^6)(s + 1000)$
- d. $(1.5 \times 10^6) / (s^2 + 10^6)(s + 1000)$
- e. None of the above

↳ -4- Calculate $I(t)$ for problem 3, for $t > 0$. (p15)

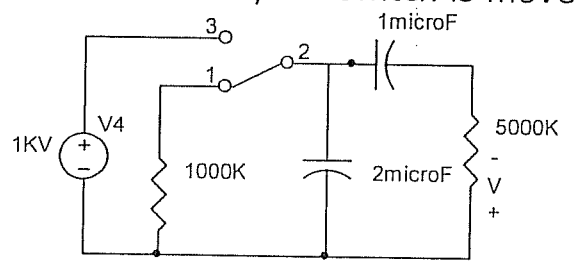- a. $[\sin(1000t + 45^\circ) + e^{-1000t}] \cdot u(t)$
- b. $[(1/\sqrt{2})\sin(1000t + 45^\circ) + e^{-1000t}] \cdot u(t)$
- c. $[(1/\sqrt{2})\sin(1000t - 45^\circ) + e^{-1000t}] \cdot u(t)$
- d. $[\sqrt{2} \cdot \sin(1000t - 45^\circ) - e^{-1000t}] \cdot u(t)$
- e. None of the above

Eng & Arch. Library

↳ -5- In the circuit shown, the switch has been for a long time at position 3. At $t=0$, the switch is moved to position 1. Find $V(s)$ p(15)




- a. $500 / (s + 0.1)$
- b. $1020 / (s^2 + 0.8s + 0.1)$
- c. $-1020 / (s + 0.155)$
- d. $500 / (s^2 + 0.8s + 0.1)$
- e. None of the above

↳ -6- Find $v(t)$ for $t > 0$ for problem 5. (p15)

- a. $500(e^{-0.1t}) \cdot U(t)$
- b. $1020(e^{-0.645t} - e^{-0.155t}) \cdot U(t)$
- c. $-1020(e^{-0.155t}) \cdot U(t)$
- d. $500(e^{-0.645t} - e^{-0.155t}) \cdot U(t)$
- e. None of the above

✓ -10- Consider the cascaded connection of 2-RC low-pass filters and determine the impulse response at the output. Let $RC=1$. (p16)

- a. $t \cdot e^{-2t} U(t)$
- b. $e^{-t} U(t)$
- c. $t^2 \cdot e^{-2t} U(t)$
- ✓ d. $t \cdot e^{-t} U(t)$
- e. None of the above

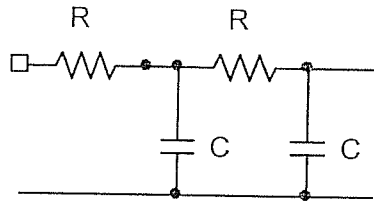

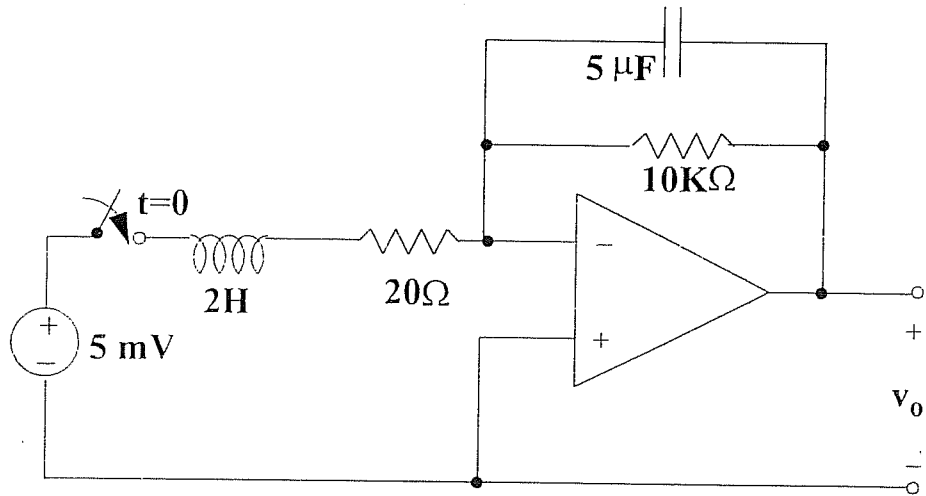


Figure 22

↳ 23. The inductor and capacitor in figure 22 have no initial stored energy and the op amp is ideal. The switch is closed at $t = 0$. Determine v_o for $t > 0$. (p57)

- a) $5e^{-10t} - 2.5e^{-20t} - 2.5 \text{ V}$
 b) $10e^{-10t} - 5e^{-20t} - 5 \text{ V}$
 c) $8e^{-10t} - 4e^{-20t} - 4 \text{ V}$
 d) $6e^{-10t} - 3e^{-20t} - 3 \text{ V}$
 e) None of the above

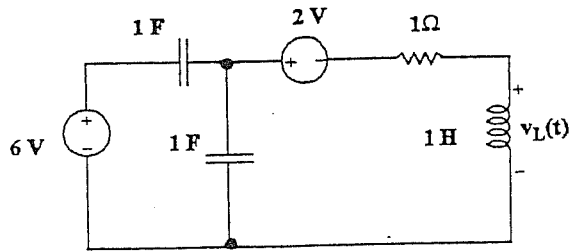


Figure 1.

L 1. Derive $V_L(s)$ in Fig. 1, assuming zero initial conditions. (p65)

- A. $(s + 2) / (s^2 + s + 1)$
- B. $2s^2 / (s^2 + 3s + 1)$
- C. $(s + 1) / (3s^2 + 2s + 1)$
- D. $2s / (2s^2 + 2s + 1)$
- E. None of the above

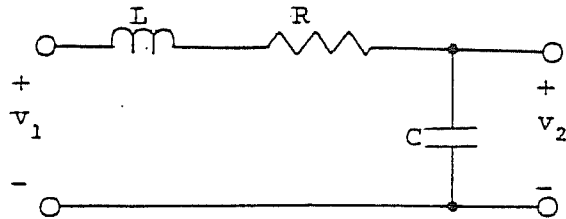


Figure 3.

4. The voltage ratio $V_2(s) / V_1(s)$ in Fig. 3 has a pole at $-100 + j700$ rad/s. If $R = 500$ ohms, find L and C . *(p66)*

- A. $L = 1.5$ H, $C = 1.388$ μ F
- B. $L = 1.0$ H, $C = 2.083$ μ F
- C. $L = 2.5$ H, $C = 0.800$ μ F
- D. $L = 2.0$ H, $C = 1.040$ μ F
- E. None of the above

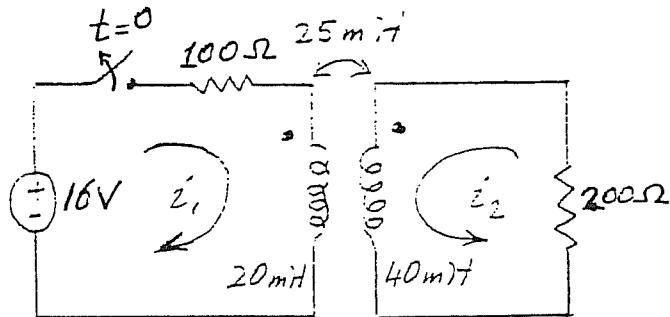


Figure 9.

11. In the circuit of Fig. 9. steady current i_1 is flowing, with $i_2 = 0$, for $t < 0$. At $t = 0$, the switch is opened. Determine i_2 as a function of time in ms. (p69)

- A. $0.15e^{-4t} \text{ A}$
- B. $0.1e^{-5t} \text{ A}$
- C. $0.2e^{-2t} \text{ A}$
- D. $0.4e^{-3t} \text{ A}$
- E. None of the above

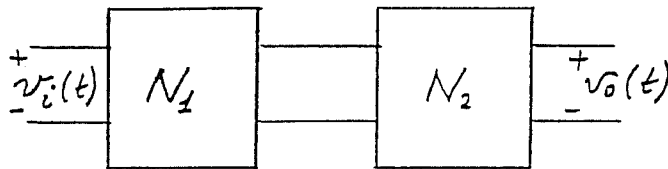


Figure 6.

7.

Two networks N_1 and N_2 are cascaded as shown in Fig. 6. The impulse response of N_1 is $2\delta'(t)$, where $\delta'(t)$ is the first time derivative of the unit impulse. The impulse response of N_2 is $e^{-t}\sin 2t$. Determine the impulse response of N_1 cascaded with N_2 . (p67)

- A. $2e^{-2t}(\cos t - 2\sin t)$
- B. $2e^{-t}(2\cos 2t - \sin 2t)$
- C. $\delta(t) - e^{-t}\cos 2t - 2e^{-t}\sin 2t$
- D. $\delta(t) - 2e^{-2t}\cos t - 2e^{-2t}\sin t$
- E. None of the above

8.

A function $x(t)$ when convolved with the function $(1 - e^{-2t})$ gives the function $1 - e^{-2t} - 2te^{-t}$, $t \geq 0$. Determine $x(t)$. (p67)

- A. te^{-t}
- B. te^{-2t}
- C. $te^{-t}\sin t$
- D. $te^{-2t}\cos t$
- E. None of the above

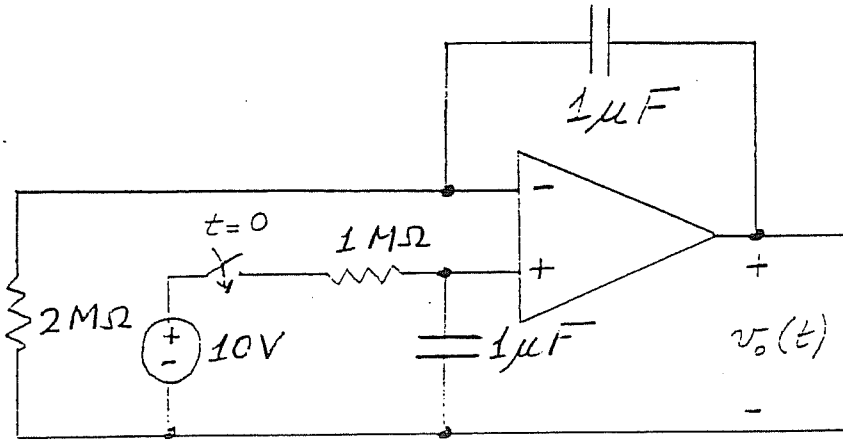


Figure 7.

9. In the circuit of Fig. 7, the capacitors have zero initial energy storage. The switch is closed at $t = 0$. Determine $v_o(t)$ (p68)

- A. $6(t - 1 + e^{-2t})$ V
- B. $6(t + 1 - e^{-t})$ V
- C. $5(t + 1 - e^{-t})$ V
- D. $5(t - 1 + e^{-t})$ V
- E. None of the above

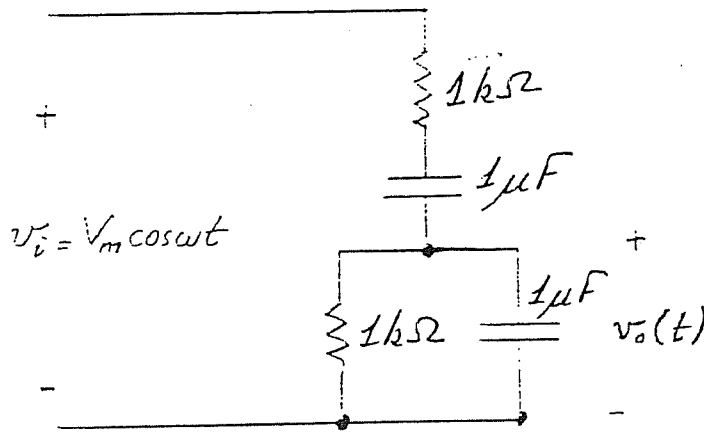


Figure 8.

10. Given the circuit of Fig. 8. Determine: (a) whether the response is bandpass or bandstop, (b) the frequency of maximum, or minimum, response, and (c) the half-power bandwidth.

- A. Bandstop; 3000 rad/s; 1000 rad/s
- B. Bandpass; 3000 rad/s; 1000 rad/s
- C. Bandstop; 1000 rad/s; 3000 rad/s
- D. Bandpass; 1000 rad/s; 3000 rad/s
- E. None of the above

5. Find the Laplace transform of the non-periodic staircase function shown in Fig. 4.

- A. $V(s) = 15(e^{-2s} + e^{-4s} + e^{-6s} + 3e^{-8s}) / s$
B. $V(s) = 5(e^{-2s} + e^{-4s} + e^{-6s} - 3e^{-8s}) / s$
C. $V(s) = 10(e^{-2s} + e^{-4s} + e^{-6s} - 3e^{-8s}) / s$
D. $V(s) = 5(e^{-2s} - e^{-4s} - e^{-6s} + 3e^{-8s}) / s$
E. None of the above

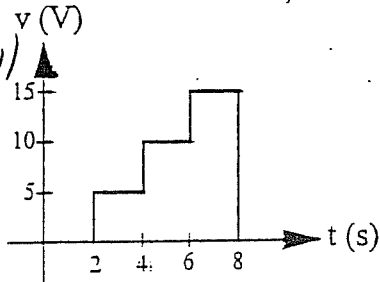


Figure 4.

L 24. Determine the zeros and poles of the transfer (p 76)

function $\frac{V_o}{V_i}(s)$ in the circuit of Fig. 21

assuming $R = 1 \Omega$, $L = 1 H$, and $C = 1 F$.

- A. zeros: $s = 0, -2$; poles: $-0.5 \pm 0.5j, \infty$
- B. zeros: $s = 0, -1$; poles: $-0.5 \pm 0.5j, \infty$
- C. zeros: $s = 0, -1$; poles: $-0.5 \pm 0.5j$
- D. zeros: $s = 0, -2$; poles: $-1 \pm j$
- E. None of the above

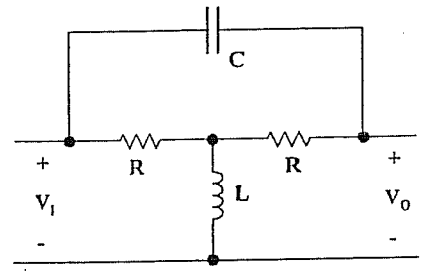


Figure 21

L 5. The current through a 0.1 H inductor is given by (p100)


$$I_L(s) = \left(\frac{-s + 100}{s(s + 100)} \right)$$

If $I_L(0^+) = -1\text{A}$, find $v_L(t)$.


- a) $20e^{-100t}$, V
- b) $-0.2e^{-100t}$, V
- c) $-20e^{-100t}$, V
- d) $0.2e^{-100t}$, V
- e) None of the above

8. An unknown voltage $v(t)$ is applied to the circuit shown. If $v_1(t) = e^{-t}$, determine $v_2(t)$, given that $R = 1 \Omega$ and $C = 1 \text{ F}$. (p101)

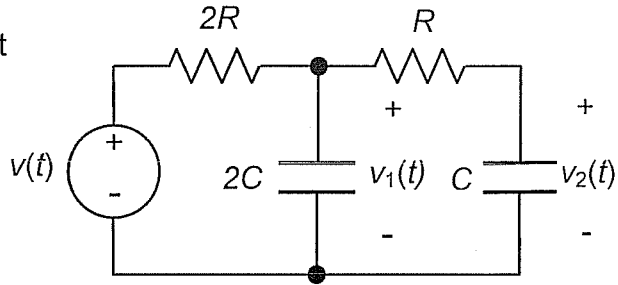- A. $2te^{-t} \text{ V}$
- B. $te^{-t} \text{ V}$
- C. $2(e^{-t} - e^{-2t}) \text{ V}$
- D. $1.5(e^{-t} - e^{-3t}) \text{ V}$
- E. None of the above



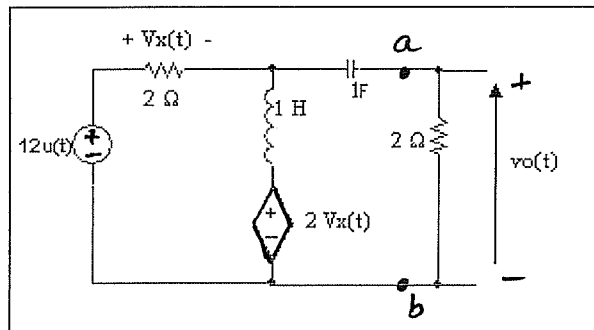- L 11. Determine the Thevenin equivalent voltage seen from terminals ab in the circuit shown below. (p102)



- a) $V_{th} = \frac{12}{s(s+6)}$
- b) $V_{th} = \frac{(s+4)}{s(s+6)}$
- ~~c) $V_{th} = \frac{12(s+4)}{s(s+6)}$~~
- d) $V_{th} = \frac{12(s+4)}{(s+6)}$
- e) None of the above

12. The transfer function is given as: $H(s) = V_o/V_i = (10/s)/(4 + 0.4s + (10/s))$ and the input voltage is given as $v_i = 10 [u(t) - u(t-0.1)]$ V. Use the convolution integral to find v_o for $t \geq 0.1$. (p103)

a) $10 - 10e^{-5t}(5t + 1)$

b) $10e^{-5t}(5t + 1)$

c) $10e^{-5(t-0.1)}(5t + 0.5) - 10e^{-5t}(5t + 1)$

d) $10e^{-5(t-0.1)}(5t + 0.5)$

e) None of the above

✓ 6. Solve for $i(t)$ in the circuit shown. (p10s)


a. $I(s) = \frac{10}{4s+1}$

b. $I(s) = \frac{40}{4s+1}$

✓ c. $I(s) = \frac{20}{4s+1}$

d. $I(s) = \frac{60}{4s+1}$

e. None of the above

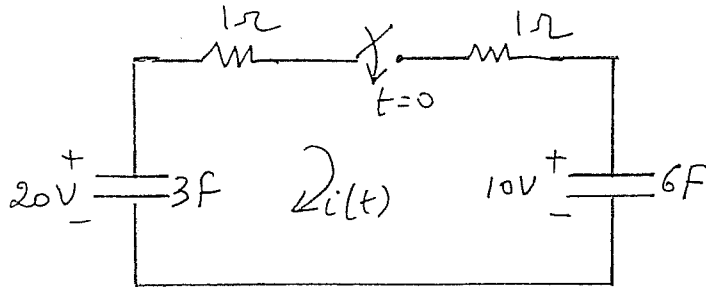

✓ 7. In problem 6, determine the voltage on the 3F capacitor.. (p10s)

a. $V(s) = \frac{24s+40}{3(4s+1)}$


b. $V(s) = \frac{240s+40}{4s(s+1/3)}$

✓ c. $V(s) = \frac{240s+40}{3s(4s+1)}$

d. $V(s) = \frac{240s+40}{12s^2+1}$

e. None of the above

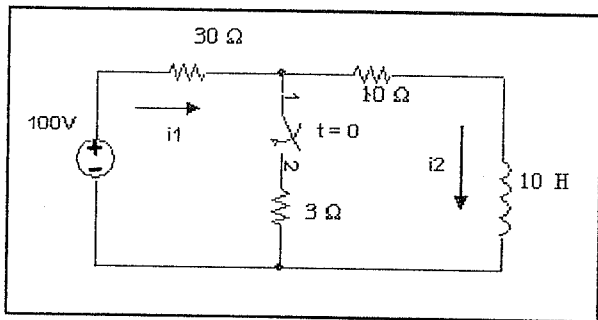7. Determine the current $I_1(s)$ for the circuit shown below. (p123)



- a) $\frac{20 + 55s}{s(28 + 22s)}$
- b) $\frac{2860}{s(28 + 22s)}$
- c) $\frac{86.67 + 71.67s}{s(28 + 22s)}$
- d) $\frac{2860 + 2365s}{s(28 + 22s)}$
- e) None of the above

L 6. Given $F(s) = \frac{1 + e^{-s}}{(s + 1)^2}$. Determine $f(t)$ at $t = 2$ s. (p132)

A. -0.64

B. 0.64

C. 1.28

D. -1.28

E. None of the above

7. The current in a circuit is given by (p140)

$$\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + i = 0$$

If the initial conditions are $i(0^+) = 1$ and $(di/dt) = 0$ at $(t=0^+)$. Find $i(t)$

- A. $e^{-t} (1 + 2t)$, A
- B. $e^{-2t} (1 + t)$, A
- C. $e^{-t} (1 + t^2)$, A
- D. $e^{-t} (1 + t)$, A
- E. None of the above

12. Find $f(t)$ if $F(s) = [40 + 2(s^2 + 4s + 5)^2] / (s^2 + 4s + 5)^2$. (p 141)

a. $f(t) = 2 t \delta(t) + 20 e^{-2t} \sin t u(t) - 20 e^{-2t} \cos t u(t)$

b. $f(t) = 2 d(\delta(t))/dt + 20 t e^{-2t} \sin t u(t) - 20 e^{-2t} \cos t u(t)$

c. $f(t) = -10 t e^{-2t} \cos t u(t) + \delta(t) + 20 e^{-2t} \sin t u(t)$

d. $f(t) = -20 t e^{-2t} \cos t u(t) + 2\delta(t) + 20 e^{-2t} \sin t u(t)$

e. None of the above

17. source of unknown voltage is applied to the circuit shown. Given that $i_C(t) = (1 + t)u(t)$ A, determine $i(t)$. (p143)


A. $(e^{-t} + t + t^2/2)u(t)$ A

B. $(e^{-t} + t - t^2/2)u(t)$

C. $(1 + t + t^2/2)u(t)$ A

D. $(1 - t + t^2/2)u(t)$ A

E. None of the above

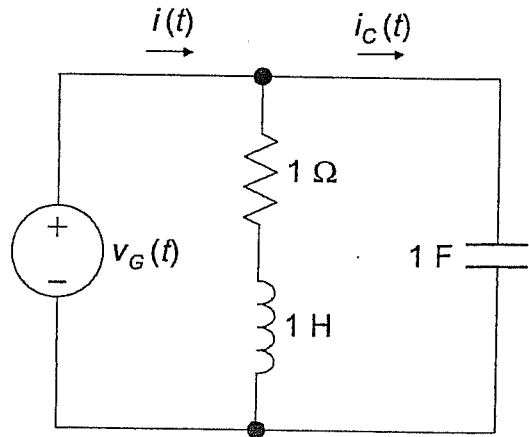


19. The response of a given circuit to a unit voltage impulse is $(e^t - e^{-t})$ Vs, with no initial energy stored in the circuit. Determine the response to a sawtooth waveform defined by $f(t) = t$ V for $0 \leq t < 1$ s, and $f(t) = 0$ for $t < 0$ and $t > 1$ s. (p.144)

- A. $[e^t + e^{-t} - 2t]u(t) + [e^t + e^{-t} - 2t]u(t - 1)$ V
- B. $[e^t + e^{-t} - 2t]u(t) + [e^{t-1} + e^{-t+1} - 2t + 2]u(t)$ V
- C. $[e^t - e^{-t} - 2t]u(t) - [e^{t-1} - e^{-t+1} - 2t + 2]u(t - 1)$ V
- D. $[e^t + e^{-t} - 2t]u(t) + [e^{t-1} + e^{-t+1} - 2t + 2]u(t - 1)$ V
- E. None of the above

8. Determine $v_C(t)$ given zero initial conditions and $v_{SRC}(t) = \delta^{(1)}(t)$, the derivative of the unit impulse at the origin. (p.158)

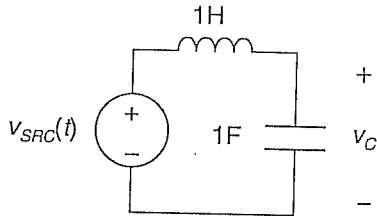- A. $\sin t$ ✓
B. $\cos t$ ✓
C. $\sin 2t$ ✓
D. $2\cos 2t$ ✓
E. None of the above



16. What is the transfer function $H(s)$ that relates V_o and V_i as $H(s)=V_i/V_o$ (p. 161)


a. $\frac{(500 \times 10^{-3})(10^{12} - s^2)}{s^2 + 200 \times 10^3 x s + 10^{12}}$

b. $\frac{2x(10^{12} - s^2)}{s^2 + 200 \times 10^3 x s + 10^{12}}$

c. $\frac{10^{12} - s^2}{s^2 + 200 \times 10^3 x s + 10^{12}}$

d. $\frac{10^{12} + s^2}{s^2 + 200 \times 10^3 x s + 10^{12}}$

e. None of the above

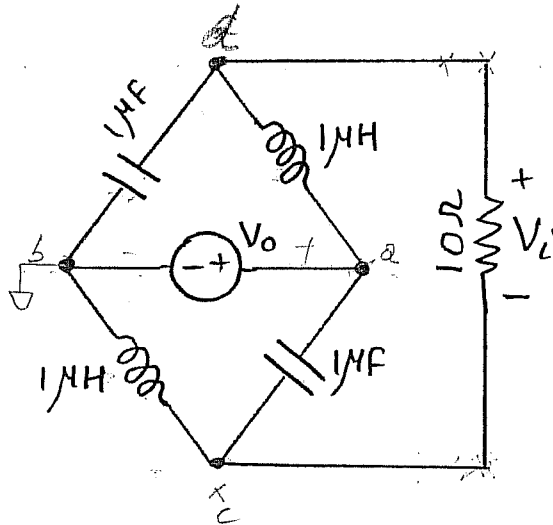

17. The time domain representation of a certain periodic signal is:

$$f(t) = 2\delta(t+3T/8) - 2\delta(t+T/8) + 2\delta(t-T/8) - 2\delta(t-3T/8)$$

The correct truncated Fourier series for $T=1$ is

a. $8\sqrt{2} \cos(2\pi t) - 8\sqrt{2} \cos(6\pi t) - 8\sqrt{2} \cos(10\pi t) + 8\sqrt{2} \cos(14\pi t)$

b. $-8\sqrt{2} \sin(2\pi t) - 8\sqrt{2} \sin(6\pi t) + 8\sqrt{2} \sin(10\pi t) + 8\sqrt{2} \sin(14\pi t)$

c. $16 \sin(4\pi t) - 16 \sin(12\pi t)$

d. $-16 \cos(8\pi t) + 16 \cos(16\pi t) + 8$

e. None of the above

5. In the circuit shown $V_s = 12V$, find the expression of the current $i(t)$ for $t > 0$ flowing through the source when the switch opens at $t=0$ after being closed for a long time. (p.175)

Remarks: $u(t)$ is the unit step function, its Laplace transform is $1/s$; $\delta(t)$ is the impulse function, its Laplace transform is 1.

- A. $i(t) = u(t)$ A
- B. $i(t) = 2u(t)$ A
- C. $i(t) = \delta(t)$ A
- D. $i(t) = 2\delta(t)$ A
- E. None of the above

