

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics
Midterm – October 30, 2014
Closed Book – No Programmable Calculators
90 minutes

There are 21 problems and 7 pages. All problems are equally graded.

Penalty is 5 to 1

(1 to 4 wrong answers do not result in a penalty; 5 to 9 wrong answers cancel one correct answer; 10 to 14 wrong answers cancel two correct answers; and so on)

Name: _____ ID number: _____

Unless otherwise specified, assume that:

$$V_T = 25 \text{ mV}$$

$$n = 1$$

$$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$J_p = -qD_p \frac{dp}{dx} \quad J_n = qD_n \frac{dn}{dx}$$

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$$

$$J_d = (qp\mu_p + qn\mu_n)E$$

$$I = J \times A$$


1. The current gain of an amplifier is 20 dB. Its power gain is 40 dB. What is its voltage gain (in dB)?

- a) 60 b) 50 c) 70 d) 65 e) 55

2. At the output of an amplifier, a resistive load $R_L = 3 \text{ k}\Omega$ is connected to Ground. The current gain of the amplifier is 50 A/A. The input signal current is $i_i = 0.1 \sin(\omega t) \text{ mA}$. A 9 V battery feeds the amplifier with a DC current of 10 mA. What is the efficiency of the amplifier?

- a) 69.4% b) 41.7% c) 55.6% d) 27.8% e) 13.9%

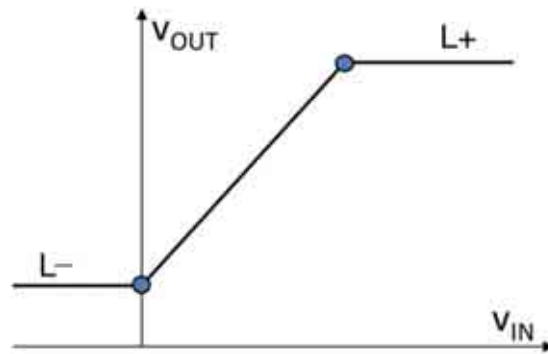3. The voltage transfer characteristics for an amplifier are shown below. The output voltage saturation levels are $L_- = 1 \text{ V}$ and $L_+ = 10 \text{ V}$. What is the gain of the amplifier (in the non-zero gain region), if the largest sinusoidal input voltage that can be applied without causing distortion is 160 mV peak-to-peak? This sinusoidal input is applied with a proper bias value.




- a) 90.0 b) 75.0 c) 64.3 d) 56.3 e) 50.0

4. Assume in the previous question that the amplifier has the same output voltage saturation levels, $L_- = 1 \text{ V}$ and $L_+ = 10 \text{ V}$, but that the gain in the non-zero gain region is 160 V/V. Find the DC bias value at the input V_{IQ} (in mV) needed to obtain the largest undistorted sinusoidal output voltage.

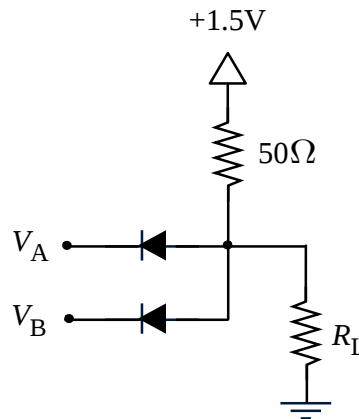- a) 40.9 b) 37.5 c) 32.1 d) 28.1 e) 45.0

For the next two questions, refer to the circuit shown below.



Assume that R_L is 1 k Ω and that the diodes drop 0.7 V when conducting, and that they are open-circuits when OFF.

5. The combination of inputs (V_A , V_B) that leads to both diodes being OFF is:

- a) (0V, 0V) b) (0V, 1V) **c) (1.5V, 1.5V)** d) (0V, 1.5V) e) (1.5V, 0V)


6. Assume that $V_A = 1.5$ V and $V_B = 0$ V. Find the power dissipated in the resistor R_L (in mW).

- a) 0.56 b) 0.64 c) 0.36 d) 0.42 e) **0.49**

7. Two diodes D_1 and D_2 are connected in series and carry the same forward current. Diode D_1 has $n_1 = 1$ and $I_{s1} = 10^{-12}$ A, and diode D_2 has $n_2 = 1.3$ and $I_{s2} = I_{s1} = 10^{-12}$ A. The total forward voltage drop across both diodes is 1.3 V. Find the forward voltage drop across diode D_1 (v_{D1} in mV).

- a) 541.7 b) 590.9 c) 577.8 d) **565.2** e) 553.2

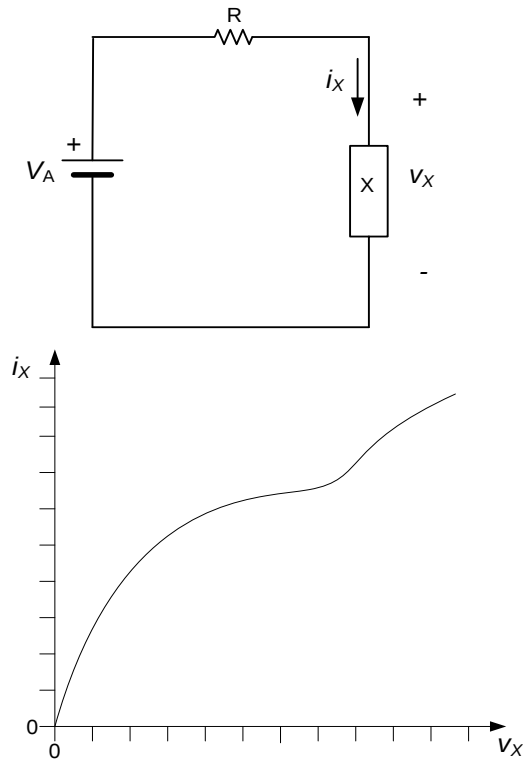
8. The current-voltage characteristics of device X are shown on the $i_X - v_X$ plot in the figure below. The x-axis division is 0.6 V, and the y-axis division is 50 μ A. When device X is replaced with an open circuit, the voltage v_X is 6 V. When device X is replaced with a short circuit, the current i_X is 0.35 mA. Find the value of v_X (in V) when the actual device X is connected in the circuit.



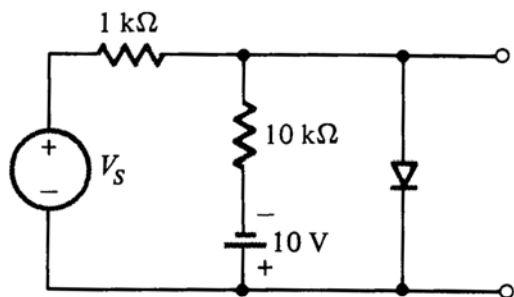- a) 1.96 b) 1.40 c) 1.12 d) 0.84 e) 1.68

=====

The diode in the circuit shown below is ideal, and $V_S = V_p \sin(\omega t)$. Refer to this circuit for the next two questions.




9. Find the value of V_p (in V) if the diode PIV is 15 V.

- a) 16.6 b) 12.2 c) 13.3 d) 14.4 e) 15.5

10. Find the value of V_p (in V) if the maximum forward diode current is 5 mA.

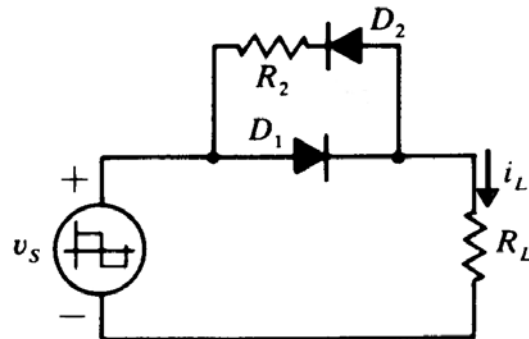- a) 8 b) 9 c) 5 d) 6 e) 7
- =====

Each of the two diodes in the circuit shown below is modeled by a fixed 0.8 V drop when conducting, and by an open circuit when OFF. Assume $R_2 = R_L = 1 \text{ k}\Omega$. The square-wave input voltage v_s is -12 V for 50% of the time, and $+12 \text{ V}$ for 50% of the time.



11. Find the power dissipated in R_L (in mW) when v_s is positive.


- a) 174.2 b) 27.0 c) 51.8 d) 84.6 e) 125.4

12. Find the average (DC) value of the load current i_L (in mA).

- a) 2.8 b) 2.3 c) 1.3 d) 1.8 e) 3.3

13. The rectifier circuit shown below uses a center-tapped transformer with turns-ratio a , i.e. $v_2 = v_s / a$. The voltage source v_s is sinusoidal with zero average and an RMS value of 48 V. The average (DC) value of the load voltage v_L is 21.61 V. Assuming that the diodes are ideal, find the maximum value of load current (in mA) flowing in R_L when $R_L = 1 \text{ k}\Omega$.

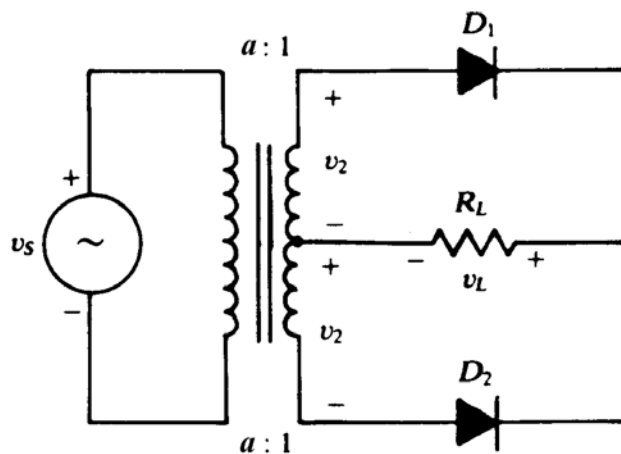
- a) 19.4 b) 33.9 c) 27.2 d) 22.6 e) 45.2



14. In the previous problem, find the value of a .

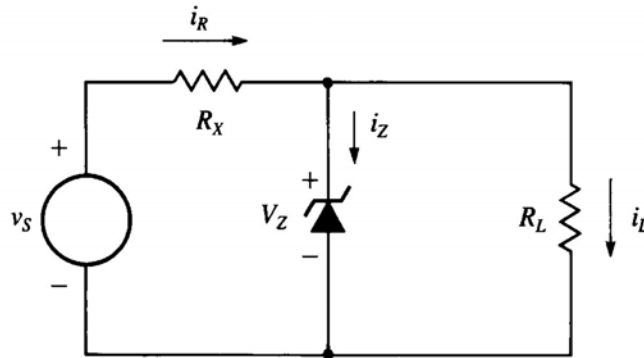- a) 3.5 b) 3 c) 2.5 d) 1.5 e) 2

The Zener diode in the circuit shown below has $V_{Z0} = 20\text{ V}$, $r_Z = 0\ \Omega$, and $I_{ZK} = 0.3\text{ mA}$. Refer to this circuit for the following two questions.



15. The source voltage is $v_S = 25\text{ V}$ and $R_X = 50\ \Omega$. What value of R_L (in Ω) makes the Zener diode dissipate 1.2 W ?

- a) 666.7 b) 285.7 c) 333.3 d) 400.0 e) 500.0

16. The source voltage is $v_S = 25 + 2 \sin(\omega t)\text{ V}$ and $R_L = 5\text{ k}\Omega$. What is the maximum value of R_X (in Ω) for which the Zener diode remains in the breakdown region?

- a) 666.7 b) 638.3 c) 612.2 d) 588.2 e) 697.7

17. A circuit consists of a 4 V DC source, a $2\text{ k}\Omega$ resistor, and a forward-biased diode. The diode has $n = 1$. Starting with an initial guess for the diode current of 2 mA , the value of the diode current after completing one iteration is found to be 1.7784 mA . If $I_S = K \times 10^{-11}\text{ A}$, find the value of the constant K . Hint: Use high precision in your calculations.

- a) 2 b) 3 c) 4 d) 5 e) 6

18. Small-signal sinusoidal variations in a diode voltage are measured to be $v_d = 3.6 \sin(\omega t)\text{ mV}$. The total diode current is measured to be $i_D = I_D + 0.1 \times I_D \sin(\omega t)$. Find the value of n for this diode.

- a) 1.92 b) 1.12 c) 1.28 d) 1.44 e) 1.68

The doping concentration (density) profile of donor atoms in a piece of semiconductor material of length L is given by $N_D(x) = N_0 + N_1(x/L)^3$ for $0 \leq x \leq L$ with $N_0 = 10^{16} \text{ cm}^{-3}$, $N_1 = 3 \times 10^{16} \text{ cm}^{-3}$, and $L = 0.1 \text{ cm}$. The mobility of free electrons is $1000 \text{ cm}^2/\text{V.s}$, and the mobility of holes is $500 \text{ cm}^2/\text{V.s}$.

19. The free electron concentration (density) is largest at $x = x_1$, and the hole concentration (density) is largest at $x = x_2$. Find x_1 and x_2 .

a) $x_1 = L, x_2 = 0$

b) $x_1 = L/2, x_2 = L/2$

c) $x_1 = 0, x_2 = 0$

d) $x_1 = 0, x_2 = L$

e) $x_1 = L, x_2 = L$

20. What is free electron diffusion current density (in A/cm^2) at $x = L/2$?

a) 0.6

b) 0.9

c) 1.2

d) 1.5

e) 1.8

21. Assume in this question that the total diffusion current density at $x = L$ is 8 A/cm^2 . Under equilibrium conditions, the *total current* density should be zero. Find the magnitude of the electric field E (in V/cm) at $x = L$ that must exist to maintain the equilibrium.

a) 1.00

b) 0.83

c) 1.25

d) 1.67

e) 0.71

=====