

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics
Midterm – November 16, 2012
Closed Book – No Programmable Calculators

120 minutes

There are 24 problems and 7 pages. All problems are equally graded.

Penalty is 5 to 1

(1 to 4 wrong answers do not result in a penalty; 5 to 9 wrong answers cancel one correct answer; 10 to 14 wrong answers cancel two correct answers; and so on)

Name: _____ ID number: _____

Unless otherwise specified, assume that:

$$V_T = 25 \text{ mV}$$

$$n = 1$$

$$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$J_p = -qD_p \frac{dp}{dx}$$

$$J_n = qD_n \frac{dn}{dx}$$

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$$

$$V_O = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$$J_d = (qp\mu_p + qn\mu_n)E$$


$$I = J \times A$$

1. A diode has a reverse saturation current $I_s = 10^{-12}$ A and $n = 1.2$. What is the diode forward voltage drop (in mV) at a current of 4 mA?


- a) 717.0 b) 704.9 c) **663.3** d) 684.1 e) 696.2

2. The diode in the circuit shown below is ideal. Find the forward current in the diode (in mA) if $V_x = 5.5$ V.

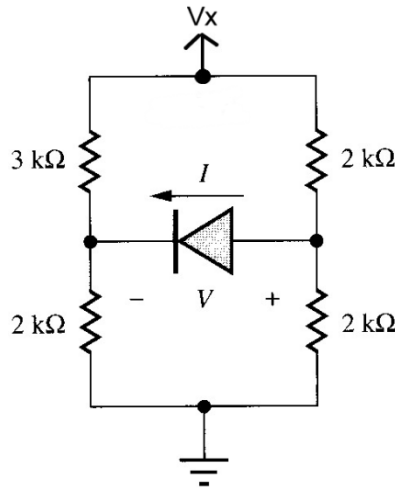- a) 0.3 b) 0.35 c) 0.2 d) **0.25** e) 0.15



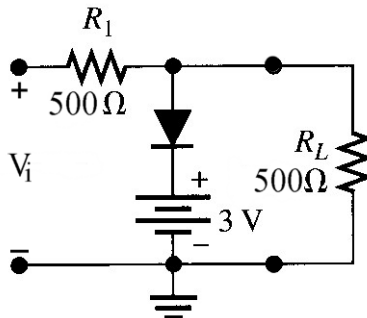In the circuit shown below, the pure sine-wave input V_i has a peak value of 14 V. The diode is modeled by a fixed 0.8 V drop when conducting, and by an open circuit when OFF. Refer to this circuit for questions 3 and 4.



3. Find the peak inverse voltage (PIV) of the diode (in V).

- a) 12 b) 8 c) 9 d) **10** e) 11

4. Find the peak value of the diode current (in mA).

- a) 4.8 b) 8.8 c) **12.8** d) 16.8 e) 20.8

5. The average (DC) value of the output voltage of a *half-wave* rectifier is 6 V. If the diode is ideal and the load is purely resistive, find the RMS value of the sinusoidal AC supply voltage (in V rms) at the transformer secondary.


- a) 31.1 b) **13.3** c) 17.8 d) 26.6 e) 22.2

6. A *full-wave* bridge rectifier with a filter capacitor is fed with a sinusoidal voltage source $v_1 = V_p \times \sin(2\pi ft)$ V. The diode is ideal, the frequency $f = 50$ Hz, the capacitance $C = 100 \mu\text{F}$, and the load resistance $R = 50 \text{ k}\Omega$. Find $(V_r/V_p) \times 100$, where V_r is the output ripple voltage.

- a) 0.4 b) 0.5 c) 1 d) **0.2** e) 0.25

7. The Zener diode shown below has $V_Z = 15.1 \text{ V}$ at $I_Z = 5 \text{ mA}$, with $r_Z = 20 \Omega$ and $I_{ZK} = 0.5 \text{ mA}$. Assume that $R_X = 980 \Omega$ and the supply voltage $v_S = 20 \text{ V}$. What is the power dissipation in the Zener diode (in mW)?

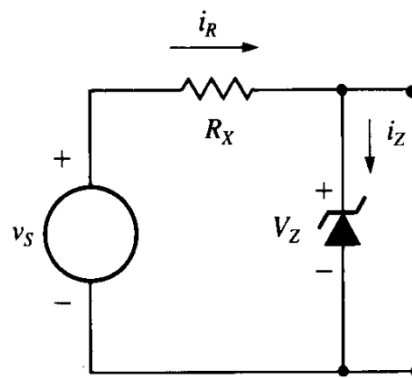- a) 83.9 b) 94.5 c) 108.2 d) **75.5** e) 126.4



8. The total voltage across a diode is $v_D = 800 + 4 \times \sin(\omega t)$ mV when the total current is $i_D = I_D + i_{dm} \times \sin(\omega t)$ mA. The diode has $n = 1.4$ and negligible reverse saturation current. If the diode incremental small-signal resistance $r_d = 50 \Omega$, find maximum value of the total current i_D (in mA).

- a) 1.08 b) 0.88 c) 0.98 d) 0.68 e) **0.78**

The drain current of an enhancement N-channel MOSFET is measured at several values of V_{GS} and V_{DS} , as shown in the table below. Refer to this table to answer questions 9 to 12.

V_{GS} (V)	V_{DS} (V)	I_D (mA)
2	3	0.393
2	5	0.454
3	3	1.433
3	0.1	I_X

9. Find the Early Voltage $V_A = 1/\lambda$ (in V).

- a) 8 b) **10** c) 12 d) 14 e) 16

10. Find the value of V_t (in V).

- a) 0.6 b) 0.7 c) 1.0 d) **0.9** e) 0.8

11. Find the value of $k' \left(\frac{W}{L}\right)$ (in mA/V²).

- a) 0.4 b) **0.5** c) 0.6 d) 0.8 e) 0.9

12. Find the value of I_X (in mA), assuming in this question that $V_t = 0.75$ V, $k' \left(\frac{W}{L}\right) = 0.65$ mA/V², and $\lambda = 0$.


- a) 0.187 b) 0.165 c) 0.099 d) 0.121 e) **0.143**

13. An enhancement N-channel MOSFET is operated at a value of $v_{GS} = V_{GS1} > V_t$, and has the $i_D - v_{DS}$ characteristics illustrated below. At point B (which is the edge between triode and saturation), $v_{DS,B} = 5$ V and $i_{D,B} = 9$ mA. Find the value of $k' \left(\frac{W}{L}\right)$ (in mA/V²) for this MOSFET.

- a) 0.48 b) 0.56 c) 0.72 d) 0.64 e) 0.80


14. In the previous problem, find the slope of the $i_D - v_{DS}$ curve (in mA/V) near $v_{DS} = 0$.

- a) 3.2 b) 2.8 c) 2.4 d) 4.0 e) 3.6

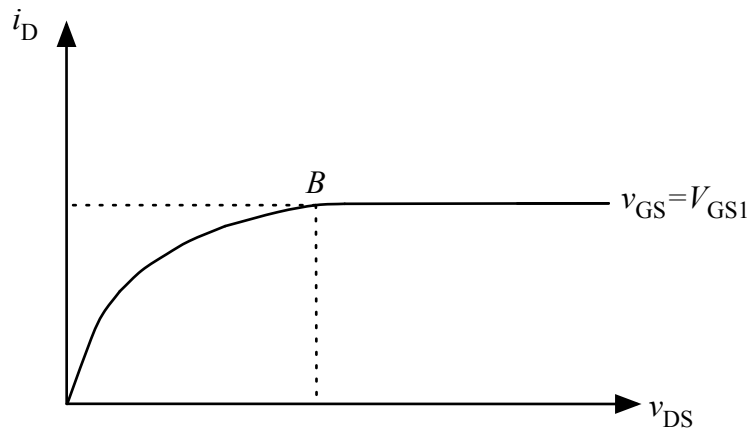


15. In the circuit shown below, the MOSFETs are designed such that $k'_n \left(\frac{W}{L}\right)_n = k'_p \left(\frac{W}{L}\right)_p$ and $V_{tn} = |V_{tp}| = 1$ V, and have negligible λ . The P-channel MOSFET should operate in SATURATION. Find the value of V_{GG} (in V) that results in the condition $V_{IN} = V_{DD}/2 \Rightarrow V_{OUT} = V_{DD}/2$. Assume $V_{DD} = 10$ V.

- a) 6.0 b) 4.0 c) 4.5 d) 5.0 e) 5.5

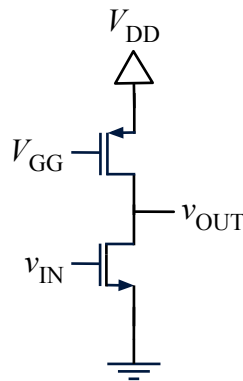

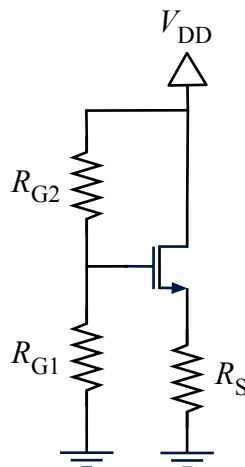16. In the circuit shown below $R_{G1} = 2R_{G2}$, and the N-channel enhancement MOSFET has negligible λ , $k'_n \left(\frac{W}{L}\right) = 0.8 \text{ mA/V}^2$, and $V_{tn} = 1 \text{ V}$. The supply voltage is $V_{DD} = 7.0 \text{ V}$. The voltage at the source terminal of the MOSFET is 3 V. Find R_S (in $\text{k}\Omega$).



- a) 4.22 b) 5.51 c) 7.50 d) 10.8 e) **16.9**

17. The transfer characteristics of a voltage amplifier are described by the equation: $v_O = 15 - 15(v_I - 2)^4$, where v_O and v_I are in V, and v_I is limited to the range between 2 and 3 V. Find the value of the DC input voltage at the bias point (V_{IQ} in V) in order to obtain a voltage gain of 33 dB.

- a) 2.67 b) 2.81 c) **2.91** d) 2.42 e) 2.55

18. The efficiency of an amplifier powered from a single 9 V DC supply is 12% when the RMS voltage across a 100Ω resistive load, connected from the amplifier output to ground, is 3 V. Find the DC current drawn from the supply (in mA).

- a) **83.3** b) 66.7 c) 22.2 d) 28.6 e) 40.0

19. In the previous problem, find the power lost in the amplifier (in mW).

- a) 510 b) **660** c) 167 d) 270 e) 110

20. The transfer characteristics of a voltage amplifier are described by the following equation:
 $v_O = 3 + 12v_I$ with saturation levels at $v_O = -3$ V and at $v_O = +4.2$ V.
The input voltage $v_I = A + B \sin(t)$ produces the largest undistorted output (i.e. largest D in $v_O = C + D \sin(t)$). Find this maximum value of D (in V).

- a) 3.60 b) 3.45 c) 3.30 d) 3.90 e) 3.75

21. In the previous problem, find the value of A (in V).

- a) -0.175 b) -0.225 c) -0.213 d) -0.200 e) -0.188

22. A semiconductor volume with length $L = 1$ cm and cross-sectional area $A = 1$ cm² carries a current of 1 mA when a voltage $V = 6.1$ μ V is applied across its length. Find the doping density (in cm⁻³) in the semiconductor when the majority carriers are electrons with a mobility of 1330 cm²/V.s. Note that the electric field is $E = V/L$.

- a) 1.5×10^{18} b) 1.1×10^{18} c) 7.7×10^{17} d) 5.2×10^{17} e) 4.7×10^{18}

23. A doped semiconductor with a free electron density $n(x) = a_0 + a_1 x$, is also subjected to an electric field E with intensity $E(x) = 3V_T a_1 / (a_0 + a_1 x)$, where V_T is the thermal voltage. Find the ratio of electron drift current density to electron diffusion current density ($J_{\text{drift}} / J_{\text{diffusion}}$).

- a) 4 b) 5 c) 6 d) 2 e) 3

24. The potential barrier across a PN junction doped such that $N_A = 2A n_i$, and $N_D = 3A n_i$, is $20V_T$. Find the value of A .

- a) 14800 b) 24400 c) 40300 d) 66400 e) 9000