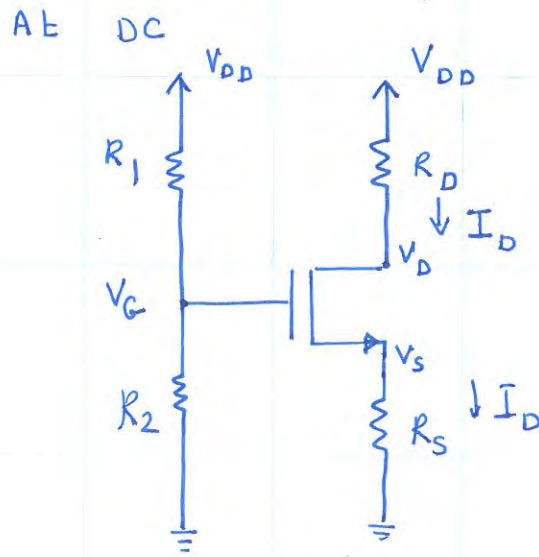


Homework 7 - solution

Problem 1

a) To design this amplifier, we must find R_D , R_S , R_1 , and R_2 .



We have $A_V = -10 \text{ V/V}$ and $A_V = -\frac{g_m I_D}{V_{OV}} (R_D \parallel R_L \parallel R_o)$

- Finding V_{OV} :

$$I_D = \frac{1}{2} K' \frac{W}{L} V_{OV}^2 (1 + \lambda V_{DS}) \quad (\text{saturation region})$$

$$V_{OV}^2 = \frac{I_D}{\frac{1}{2} K' \frac{W}{L} (1 + \lambda V_{DS})}$$

$$= \frac{0.2}{\frac{1}{2} \times 1.1 \times (1 + 3 \times 0.12)} \quad ; \text{ thus } V_{OV} = 0.517 \text{ V}$$

- finding r_o :

$$r_o = \frac{V_{DS} + V_A}{I_D} = \frac{3 + \frac{1}{0.12}}{0.2} = 56.67 \text{ k}\Omega$$

- Finding R_D

$$A_v = - \frac{2I_D}{V_{ov}} (R_D \parallel R_L \parallel r_o)$$

$$A_v = - \frac{2I_D}{V_{ov}} \left(\frac{1}{\frac{1}{R_D} + \frac{1}{R_L} + \frac{1}{r_o}} \right)$$

$$\frac{1}{R_D} = - \frac{2I_D}{V_{ov} \cdot A_v} = \frac{1}{R_L} + \frac{1}{r_o}$$

$$= - \frac{2 \times 0.2}{0.517 \times (-10)} = \frac{1}{39} + \frac{1}{56.67}$$

$$R_D = 29.34 \text{ k}\Omega$$

• Finding R_S

$$\begin{aligned} V_{DD} - V_D &= R_D I_D \quad \text{thus} \quad V_D = V_{DD} - R_D I_D \\ &= 9 - 29.34 \times 0.2 \\ &= 3.132 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{DS} &= V_D - V_S \quad \text{thus} \quad V_S = V_D - V_{DS} \\ &= 3.132 - 3 \\ &= 0.132 \text{ V} \end{aligned}$$

$$R_S = \frac{V_S}{I_D} = \frac{0.132}{0.2} = 0.66 \text{ V}$$

• Finding R_1 and R_2 .

$$\begin{aligned} V_{OV} &= V_{GS} - V_E = V_G - V_S - V_t \quad \text{thus} \quad V_G = V_{OV} + V_S + V_t \\ &= 0.517 + 0.132 + 0.8 \\ &= 1.449 \text{ V} \end{aligned}$$

We have $R_{in} = 3 \text{ M}\Omega$.

$$\text{and } R_{in} = \frac{R_1 R_2}{R_1 + R_2} \Leftrightarrow R_1 + R_2 = \frac{R_1 R_2}{R_{in}}$$

$$\text{We have } \frac{V_G}{V_{DD}} = \frac{R_2}{R_1 + R_2}$$

$$\frac{V_G}{V_{DD}} = \frac{R_2}{\frac{R_1 R_2}{R_{in}}} = \frac{R_{in}}{R_1}$$

$$\text{Thus } R_1 = \frac{R_{in}}{\frac{V_G}{V_{DD}}} = \frac{3 \text{ M}}{\frac{1.449}{9}} = 18.63 \text{ M}.$$

$$R_2 = \frac{V_G}{\frac{V_{DD} - V_G}{R_1}} = \frac{1.449}{\frac{9 - 1.449}{18.63}} = 3.575 \text{ M}.$$

b)

When we have an input signal $v_s = 0 \text{ V}$ and $v_i = v_{gs}$

1) $I_D = 0 \Leftrightarrow$ Mosfet in cutoff region.

To compute the largest input signal that results in $I_D = 0$, we have $v_{gs} = V_t$

$$v_{gs} = V_t$$

$$v_{gs} + V_{GS} = V_t$$

$$v_{gs} = 0.8 - (1.449 - 0.132)$$

$$= -0.517 \text{ V}$$

Thus $v_{i\max} = -0.517 \text{ V}$.

Therefore $v_{i\text{peak}} = 0.517 \text{ V}$

$$2) \quad v_{DS} = v_{OV}$$

$$V_{DS} + v_o = V_{OV} + v_i$$

$$-10 v_i - v_i = V_{OV} - V_{DS}$$

$$-11 v_i = 0.517 - 3$$

$$v_i = 0.226 \text{ V}$$

$$3) \quad v_{gs} = 0.1 \times V_{OV}$$

$$v_i = 0.1 \times 0.517$$

$$= 0.0517 \text{ V}$$

$$= 51.7 \text{ mV}$$


Thus

$$v_{i, \text{peak}} \ll 51.7 \text{ mV}$$

Problem 2

$V_E = 0.7V$; $K' \frac{W}{L} = 1.1 \text{ mA/V}^2$

$V_A = \frac{1}{\lambda} = 22V$

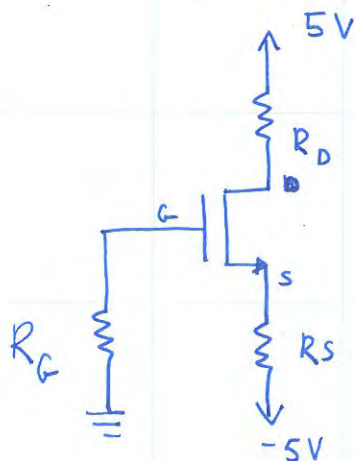


a) $R_G = 3 \text{ M}\Omega$.

$V_{DS} > V_{GS} - V_t$ ($V_G = 0$ at DC since $I_G = 0$, and $V_G = R_G I_G$)

$V_D > V_G - V_E = 0 - 0.7 = -0.7V$

$V_{Dmin} = -0.7V$

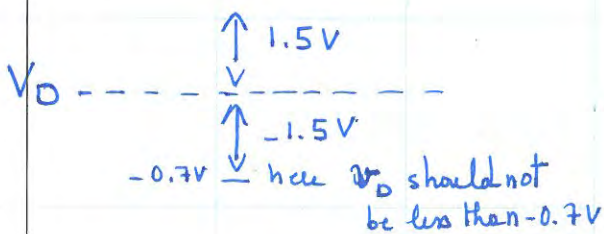

Thus $V_D - 1.5 = -0.7$

$V_D = -0.7 + 1.5 = 0.8V$

$R_D = \frac{5 - V_D}{I_D} = \frac{5 - 0.8}{0.4} = 10.5 \text{ k}\Omega$

$I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_E)^2 (1 + \frac{V_{DS}}{V_A})$

$I_D = \frac{1}{2} K' \frac{W}{L} (-V_S - V_E)^2 (1 + \frac{V_D - V_S}{V_A})$

F. E. PAPER

$$(V_S + V_T)^2 \left(1 + \frac{V_D - V_S}{V_A} \right) = \frac{2I_D}{K' \frac{W}{L}}$$

$$(V_S + 0.7)^2 \left(1 + \frac{0.8 - V_S}{22} \right) = \frac{2 \times 0.4}{1.1}$$

$$(V_S + 0.7)^2 (22 + 0.8 - V_S) = 16$$

$$(V_S^2 + 1.4V_S + 0.49)(22.8 - V_S) = 16$$

$$22.8V_S^2 - V_S^3 + 31.92V_S - 1.4V_S^2 + 11.172 - 0.49V_S = 16$$

$$-V_S^3 + 21.4V_S^2 + 31.43V_S - 4.828 = 0$$

$$V_S = 22.77 \text{ or } -1.511 \text{ or } 0.14$$

We need $V_{GS} > V_T \rightarrow -V_S > V_T \rightarrow V_S < -0.7$

$$\text{Thus } V_S = -1.511 \text{ V}$$

$$R_S = \frac{V_S + 5}{I_D} = \frac{-1.511 + 5}{0.4} = 8.7225 \text{ k}\Omega$$

$$\text{b) } V_{DS} = V_D - V_S = 0.8 + 1.511 = 2.311 \text{ V}$$

$$V_{GS} = -V_S = 1.511 \text{ V}$$


$$V_{OV} = V_{GS} - V_T = 1.511 - 0.7 = 0.811 \text{ V}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.4}{0.811} = 0.986 \text{ mA/V}$$

$$r_o = \frac{V_{DS} + V_A}{I_D} = \frac{2.311 + 22}{0.4} = 60.78 \text{ k}\Omega$$

c) ~~Small~~ Finding A_{vo}

Small signal model

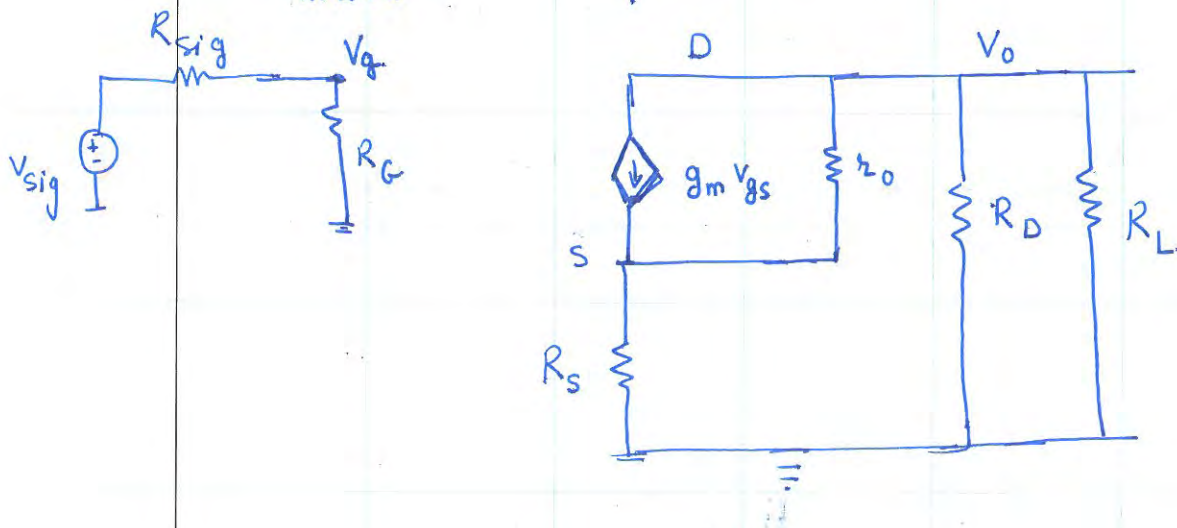

$$g_m V_{gs} + \frac{V_s - V_o}{r_o} = \frac{V_s}{R_s} \quad ; \quad \frac{V_s}{R_s} = - \frac{V_o}{(R_D \parallel R_L)}$$

$$g_m V_g - g_m V_s + \frac{1}{r_o} (V_o - V_s) = \frac{1}{R_s} V_s$$

$$g_m V_g = g_m V_s - \frac{1}{r_o} (V_o - V_s) + \frac{1}{R_s} V_s$$

$$= \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right) V_s = \frac{1}{r_o} V_o$$

$$g_m V_g = \left[\frac{R_s}{R_D \parallel R_L} \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right) - \frac{1}{r_o} \right] V_o$$

$$\frac{V_o}{V_g} = \frac{g_m}{\frac{R_s}{(R_D \parallel R_L)} \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right) - \frac{1}{r_o}} = \frac{g_m r_o (R_D \parallel R_L)}{r_o (R_s g_m + 1) + R_s + (R_D \parallel R_L)}$$

$$\frac{V_g}{V_{sig}} = \frac{R_G}{R_G + R_{sig}}$$

$$A_v = \frac{V_o}{V_{sig}} = \frac{R_G}{R_G + R_{sig}} \cdot \frac{g_m r_o (R_D \parallel R_L)}{r_o (1 + g_m R_S) + R_D \parallel R_L + R_S}$$

$$= \frac{3 \times 10^3}{3 \times 10^3 + 39} \cdot \frac{0.986 \times 60.78 (10.5 \parallel 120)}{60.78 (1 + 0.986 \times 8.7225) + (10.5 \parallel 120) + 8.7225}$$

$$= -0.949 \text{ V/V}$$

$$A_i = \frac{i_o}{i_i} = \frac{V_o / R_L}{\frac{V_{sig}}{R_{sig} + R_G}} = A_v \cdot \frac{R_{sig} + R_G}{R_L}$$

$$= -0.949 \cdot \frac{3 \times 10^3 + 39}{120}$$

$$= -24.03 \text{ A/A}$$

$$A_p = A_i A_v = 22.8 \text{ W/W}$$

d) If we try to $\downarrow R_S$, $A_v \uparrow$ (from the above equation).


Since we need the bias conditions to not be disrupted, a capacitor can be used to bypass part of the resistor R_S .

(The capacitor should be very large so that it has infinite impedance at DC).

HW 8

Nadim Hachem
201100705

Problem 1:

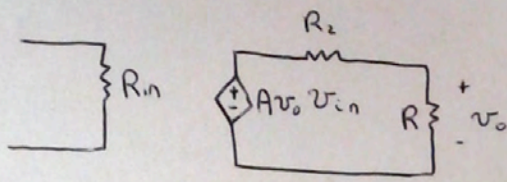

a) b)

* For $R = 33 \text{ k}\Omega$

$$v_o = \frac{33}{33 + R_2} A v_o v_{in}$$

$$\frac{v_o}{v_{in}} = \frac{33}{33 + R_2} A v_o = 99$$

* For $R = 39 \text{ k}\Omega$,

$$\frac{v_o}{v_{in}} = \frac{39}{39 + R_2} A v_o = 108$$

$$\begin{cases} 33 A v_o = 99 (33 + R_2) \\ 39 A v_o = 108 (39 + R_2) \end{cases}$$

Solving these 2 equations with 2 unknowns we get:

$$A v_o = 216 \text{ V/V}$$

$$R_2 = 39 \text{ k}\Omega$$

c) with $47 \text{ k}\Omega$ resistance,

$$v_{in} = \frac{R_{in}}{R_{in} + 47} v_{sig} = 0.76 v_{sig}$$


$$\Rightarrow R_{in} = 0.76 (R_{in} + 47)$$

$$R_{in} (1 - 0.76) = 47 \times 0.76$$

$$R_{in} = 148.83 \text{ k}\Omega$$

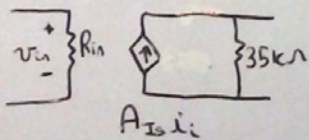
Problem 2:

$$R_{in} = 150 \text{ k}\Omega \quad A_{is} = 200 \text{ A/V}$$




$$A v_o = G_m R_{out} = \frac{A_{is}}{R_{in}} \times R_{out} = 46.67 \text{ V/V}$$

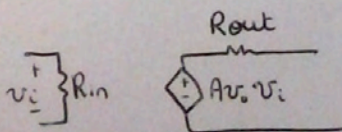
$$G_m = \frac{A v_o}{R_o} = \frac{46.67}{35} = 1.33 \text{ mA/V}$$



$$A v_o = 46.67 \text{ V/V}$$

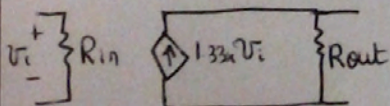

$$G_m = 1.33 \text{ mA/V}$$

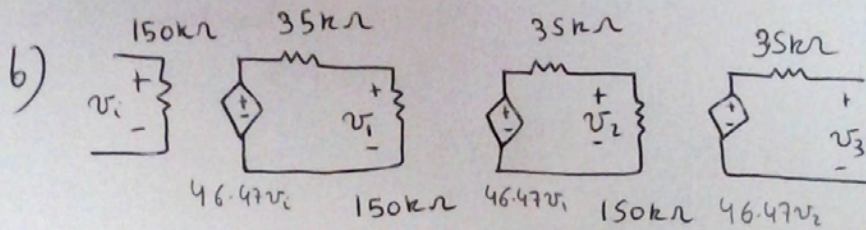

$$R_{in} = \frac{v_i}{i_i} = 150 \text{ k}\Omega$$

$$R_{out} = \frac{v_x}{i_x} \Big|_{v_{in}=0} = 35 \text{ k}\Omega \quad (v_x \text{ and } i_x \text{ are test voltage and current})$$

$$v_1 = \frac{150}{150+35} \times 46.47 v_i \Rightarrow A v_1 = \frac{v_1}{v_{in}} = 36.68 \text{ V/V}$$


$$v_2 = \frac{150}{150+35} \times 46.47 v_1 \Rightarrow A v_2 = 36.68 \text{ V/V}$$

$$v_3 = 46.47 v_2 \Rightarrow A v_3 = 46.47$$

$$A v_o = \frac{v_{out}}{v_{in}} = \frac{v_3}{v_i} = \frac{v_3}{v_2} \times \frac{v_2}{v_1} \times \frac{v_1}{v_i} = A v_3 \times A v_2 \times A v_1 = 65971 \text{ V/V}$$

$$A_{is} = \frac{R_{in}}{R_{out}} A v_o = 282732 \text{ A/A}$$
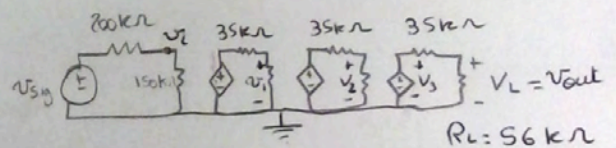
$$G_m = \frac{A v_o}{R_{out}} = 1.88 \text{ A/V}$$



$$c) v_o = v_L = \frac{56}{56+35} \times v_3 = 28.6 v_2$$

$$v_i = \frac{150}{150+200} v_{sig} = 0.428 v_{sig}$$

$$\frac{v_{out}}{v_i} = \frac{v_{out}}{v_3} \times \frac{v_3}{v_2} \times \frac{v_2}{v_1} \times \frac{v_1}{v_i} = 0.614 A v_o = 40597 \text{ V/V}$$


$$\frac{v_{out}}{v_{sig}} = \frac{v_{out}}{v_i} \times \frac{v_i}{v_{sig}} = 17399 \text{ V/V}$$

$$\text{in dB, } \frac{v_{out}}{v_{sig}} = 84.8 \text{ dB}$$

$$\frac{i_{out}}{i_{sig}} = \frac{v_{out} / R_L}{v_{sig} / (R_{in} + R_{sig})} = \frac{v_{out}}{v_{sig}} \times \frac{150 + 200}{56} = 108743 \text{ A/A}$$


$$\text{in dB, } A_i = 20 \log(A_{i(\text{norm})}) = 100 \text{ dB}$$

$$A_p = \frac{v_{out}}{v_{sig}} \times \frac{i_{out}}{i_{sig}} = 1.89 \times 10^9 \text{ W/W}$$

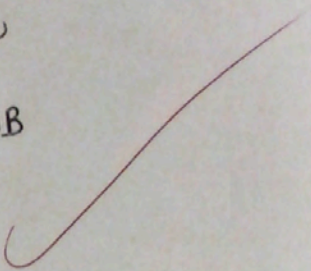
$$\text{in dB, } A_p = 20 \log A_{p(\text{W/W})} = 92.77 \text{ dB}$$


EECE 310 - Homework 9

Problem 1

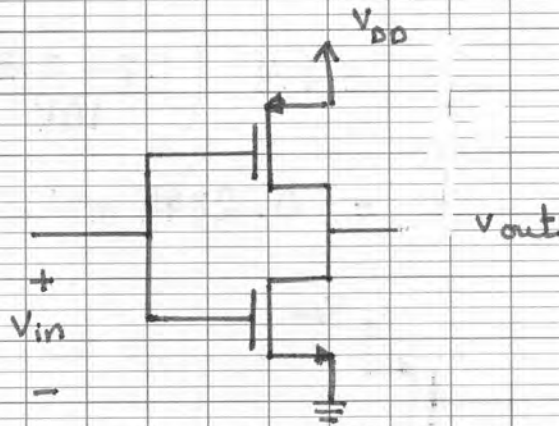

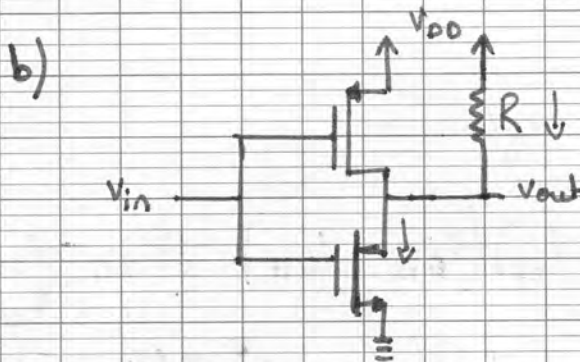a) $V_{OH} = V_{DD} = 1.8V$
 $V_{OL} = 0V.$



For Nmos: $\begin{cases} V_{GSN} = 1.8V \\ V_{OL} \text{ is small} \end{cases} \rightarrow \text{triode region.}$

For Pmos: $\begin{cases} V_{GSP} = V_{DD} - V_{DD} = 0V \\ \end{cases} \rightarrow \text{cutoff region}$

$$\frac{1}{2} K'_n \left(\frac{W}{L}\right)_n \left(2(V_{GSN} - V_{TN}) V_{OL} - V_{OL}^2 \right) = \frac{V_{DD} - V_{OL}}{R}$$


$$\frac{1}{2} \times 330 \times \frac{0.4 \times 10^{-3}}{0.18} \left(2(1.8 - 0.6) V_{OL} - V_{OL}^2 \right) = \frac{1.8 - V_{OL}}{10}$$

$$\frac{11}{3} \left(2.4 V_{OL} - V_{OL}^2 \right) = 1.8 - V_{OL}$$

$$-\frac{11}{3} V_{OL}^2 + 9.8 V_{OL} - 1.8 = 0 \rightarrow \boxed{V_{OL} = \frac{0.222V}{0.198V}}$$

$$\begin{aligned}
 \text{Power dissipated: } P &= V_{DD} I_D = V_{DD} \cdot \left(\frac{V_{DD} - V_{OL}}{R} \right) \\
 &= 1.8 \left(\frac{1.8 - 0.158}{10K} \right) \\
 &= 0.288 \text{ mW}
 \end{aligned}$$

c)

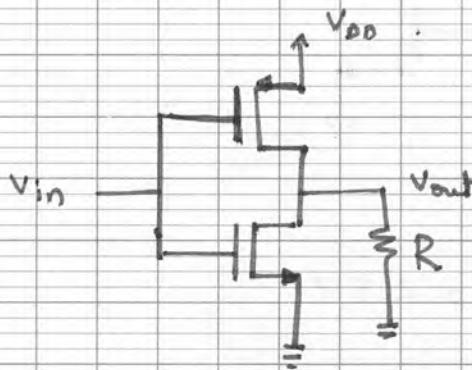

Nmos → cutoff
Pmos → triode region

$$\frac{1}{2} K'_P \left(\frac{W}{L} \right)_P \left[(V_{GSP} - V_{TP}) (V_{OH} - V_{DD}) - \frac{1}{2} (V_{OH} - V_{DD})^2 \right] = \frac{V_{OH}}{R}$$

$$\frac{1}{2} \times 170 \times 10^{-3} \times \frac{0.8}{0.18} \left[2 \times (-1.8 + 0.7) (V_{OH} - 1.8) - (V_{OH} - 1.8)^2 \right] = \frac{V_{OH}}{10}$$

$$\frac{34}{9} \left[-2.2 (V_{OH} - 1.8) - (V_{OH} - 1.8)^2 \right] = V_{OH}$$

$$\frac{34}{9} \left(-2.2 V_{OH} + 3.96 - V_{OH}^2 + 3.6 V_{OH} - 3.24 \right) = V_{OH}$$


$$-34 V_{OH}^2 + 38.6 V_{OH} + 24.48 = 0$$

$$\boxed{V_{OH} = 1.59 \text{ V}}$$

$$P = V_{DD} \cdot I_D = V_{DD} \cdot \frac{V_{OH}}{R} = 1.8 \times \frac{1.59}{10} = 0.2862 \text{ mW}$$

$$\begin{aligned}
 d) P_{\text{dyn}} &= C f \cdot V_{\text{DD}}^2 \\
 &= 50 \times 10^{-15} \times \frac{1}{2 \times 10^{-9}} \times (1.8)^2 \\
 &= 81 \mu\text{W}.
 \end{aligned}$$

Problem 2

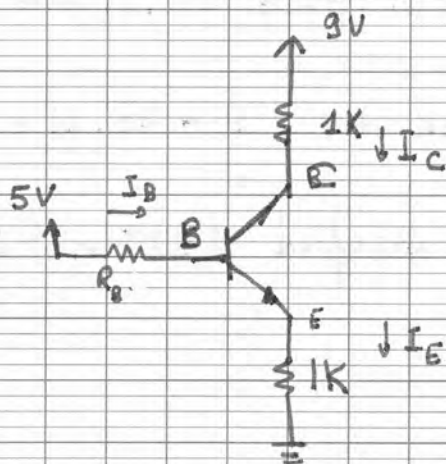

$$\begin{aligned}
 |V_{\text{BE}}| &= 0.7 \\
 I_B &= 30 \mu\text{A} \\
 \beta &= 120
 \end{aligned}$$

a) BJT active

$$I_E = (\beta + 1) I_B = 121 \times 30 = 3630 \mu\text{A} = 3.63 \text{ mA}$$

$$R_B = \frac{5 - V_B}{I_B} = \frac{5 - (V_{\text{BE}} + V_E)}{I_B} = \frac{5 - (V_{\text{BE}} + 1\text{k} \times I_E)}{I_B}$$

$$= \frac{5 - 0.7 - 3.63}{30 \times 10^{-3}} = 22.33 \text{ k}\Omega$$

b) $I_C = \beta I_B = 120 \times 30 = 3.6 \text{ mA}$

$$9 - V_C = 1\text{k} \times I_C = 3.6 \rightarrow V_C = 5.4 \text{ V}$$

$$V_{\text{CE}} = V_C - V_E = 5.4 - 3.63 = 1.77 \text{ V}$$

$$V_{\text{CE}} > 0.3 \text{ V} \rightarrow \text{BJT active region}$$

c) Assume BJT is still in active region.

$$V_{BE} = 0.7 \text{ V} \rightarrow V_B = 0.7 \text{ V}.$$


$$I_B = \frac{5 - 0.7}{22.33} = 0.192 \text{ mA}.$$

$$I_C = \beta I_B = 120 \times 0.192 = 23.11 \text{ mA}.$$

$$V_{CE} = V_C = -I_C \times 1\text{K} + 9 = 9 - 23.11 = -14.11 < 0.3 \text{ V}$$

→ Condition not satisfied (BJT not in active region).

Problem 3

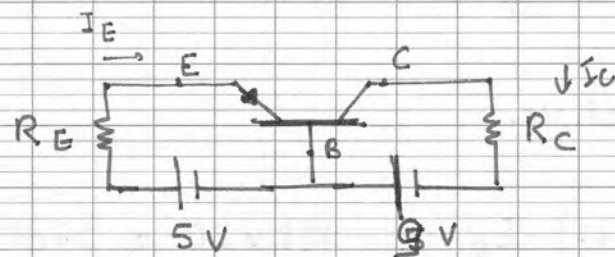

$$\alpha = 0.989$$

$$I_E = 0.15 \text{ mA}$$

$$V_{EC} = 3.3 \text{ V}$$

Assume BJT in active region.

$$V_{EB} = 0.7 \text{ V}$$

$$V_{EB} - 5 + R_E I_E = 0$$

$$0.7 - 5 + R_E \times 0.15 = 0$$

$$R_E = \frac{5 - 0.7}{0.15} = 28.67 \text{ K}\Omega$$

$$I_c = \alpha I_E = 0.989 \times 0.15 \\ = 0.1485 \text{ mA}$$

$$-9 - 5 + R_E I_E + V_{EC} + R_C I_C = 0$$


$$-14 + 4.3 + 3.3 + R_C \times 0.1485 = 0$$

$$\boxed{R_C = 43.10 \text{ K}\Omega}$$

EECE 310 - Homework 10

Problem 1

a)

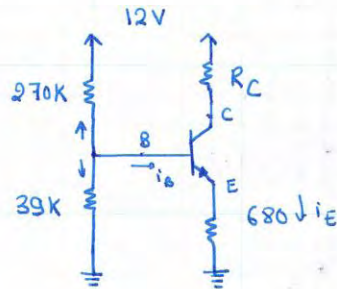

$$\beta = 150$$

(1) KCL at B: $\frac{V_B - 12}{270} + \frac{V_B}{39} + i_B = 0$ (i_B in mA)

(2) $V_B = V_{BE} + V_E = 0.7 + 680 \times 10^{-3} i_E$; $i_E = (\beta + 1) i_B$
 $= 0.7 + 680 \times 10^{-3} \times 151 i_B$

$$V_B = 0.7 + 103.38 i_B$$

From (1) $\frac{0.7 + 103.38 i_B - 12}{270} + \frac{0.7 + 103.38 i_B}{39} + i_B = 0$

$$i_B = 5.926 \times 10^{-3} \text{ mA}$$

$$V_E = 680 \times 10^{-3} \times 151 \times i_B = 0.608 \text{ V}$$

$$V_{CE} > 0.3 \text{ V (active region)}$$

$$V_C > V_E + 0.3 = 0.908 \text{ V}$$

b) $V_C = \frac{12 + 0.908}{2} = 6.454 \text{ V}$


$$R_C = \frac{12 - V_C}{\beta i_B} = \frac{12 - 6.454}{150 \times 5.926 \times 10^{-3}} = 6.24 \text{ K}\Omega$$

F. E. PAPER

Problem 2

$$\beta = 160, V_A = 80V, V_T = 26mV$$

a) DC

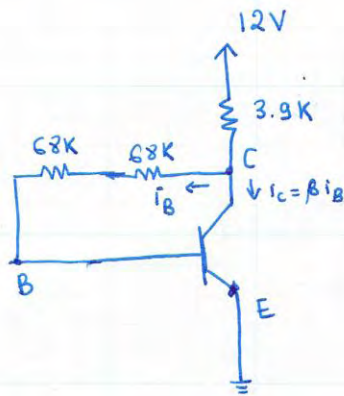

$$V_{BE} = 0.7V \rightarrow V_B = 0.7V$$

$$(1) \frac{12 - V_C}{3.9k} = (\beta + 1) I_B$$

$$(2) \frac{V_C - 0.7}{136k} = I_B$$

$$\frac{12 - V_C}{3.9} = \beta + 1 = 161$$

$$\frac{V_C - 0.7}{136}$$

$$\frac{12 - V_C}{3.9} = \frac{161}{136} (V_C - 0.7)$$

$$\left(\frac{161}{136} + \frac{1}{39}\right) V_C = \frac{12}{39} + 0.7 \cdot \frac{161}{136} \quad ; \quad V_C = 2.711V = V_{CE}$$

$$I_B = \frac{V_C - 0.7}{136k} = \frac{2.711 - 0.7}{136k} = 14.787 \times 10^{-3} \text{ mA}$$

$$I_C = \beta I_B = 160 \times 14.787 \times 10^{-3} = \frac{2.366}{2.366} \text{ mA}$$


$$b) \quad g_m = \frac{I_c}{V_T} = \frac{2.366}{26} = 0.091 \text{ A/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{160}{0.091} = 1.76 \text{ k}\Omega$$

$$r_e = \frac{\alpha}{g_m} = \frac{\beta}{(\beta+1)g_m} = \frac{160}{161 \times 0.091} = 10.92 \Omega$$


$$r_o = \frac{V_A + V_{CE}}{I_c} = \frac{80 + 2.711}{2.366} = 34.96 \text{ k}\Omega$$

c) Small signal analysis

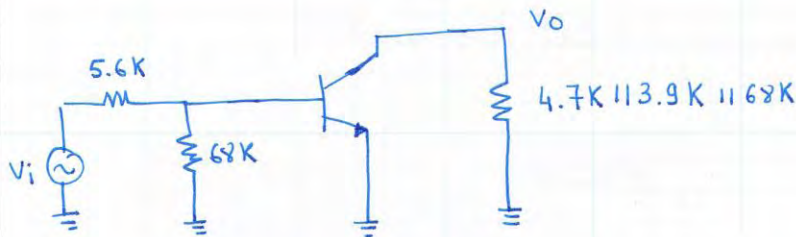

F. E. PAPER

Small signal model

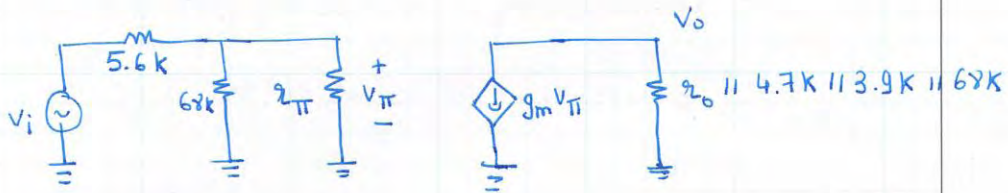

$$V_o = -g_m V_{\pi} (r_o \parallel 4.7 \text{ k}\Omega \parallel 3.9 \text{ k}\Omega \parallel 68 \text{ k}\Omega)$$

$$\frac{V_o}{V_{\pi}} = -0.091 \times (34.96 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega \parallel 3.9 \text{ k}\Omega \parallel 68 \text{ k}\Omega) = -177.56 \text{ V/V}$$

$$\frac{V_{\pi}}{V_i} = \frac{68 \text{ k}\Omega \parallel r_{\pi}}{5.6 \text{ k}\Omega + 68 \text{ k}\Omega \parallel r_{\pi}} = \frac{68 \text{ k}\Omega \parallel 1.76 \text{ k}\Omega}{5.6 \text{ k}\Omega + 68 \text{ k}\Omega \parallel 1.76 \text{ k}\Omega} = 0.234 \text{ V/V}$$

$$\frac{V_o}{V_i} = -177.56 \times 0.234 = -41.55 \text{ V/V}$$

d) In active region

$$v_{CE} > 0.3$$


$$V_{CE} + v_{ce} > 0.3$$

$$2.711 + v_{ce} > 0.3$$

$$2.711 - v_{peak2} > 0.3$$

$$v_{peak2} < 2.711 - 0.3 = 2.411 \text{ V}$$
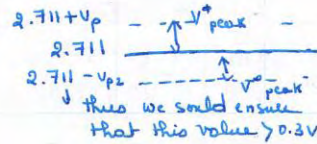
$$v_{\text{peak-to-peak max}} = 2 \times 2.411 = 4.822 \text{ V}$$



$$v_{bc} \leq 5 \text{ mV}$$

$$\text{We have } \frac{v_o}{v_i} = \frac{v_c}{v_b} = -117.56 \text{ V/V}$$

$$v_c = -117.56 v_b ; \text{ we have } v_b \leq 5 \times 10^{-3} \text{ V}$$

$$v_c \gg -117.56 \times 5 \times 10^{-3} = -0.8878 \text{ V}$$


$$v_c \approx -0.8878 \text{ V}$$

$$V_{p-p} = 2 \times 0.8878 = 1.7756 \text{ V}$$

Thus the maximum signal swing is 1.7756V.


$$v_o = -41.55 v_i$$
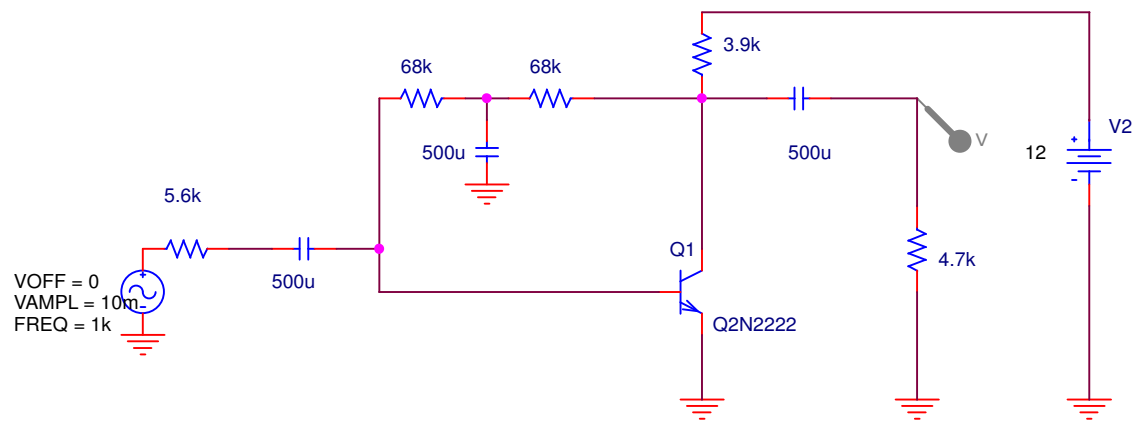
$$v_{i \text{ p-p}} = \frac{1.7756}{41.55} = 42.73 \text{ mV}$$




Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Monday, January 09, 2012	Sheet 1 of 1

(A) dasdf-SCHEMATIC1-zxx.dat (active)

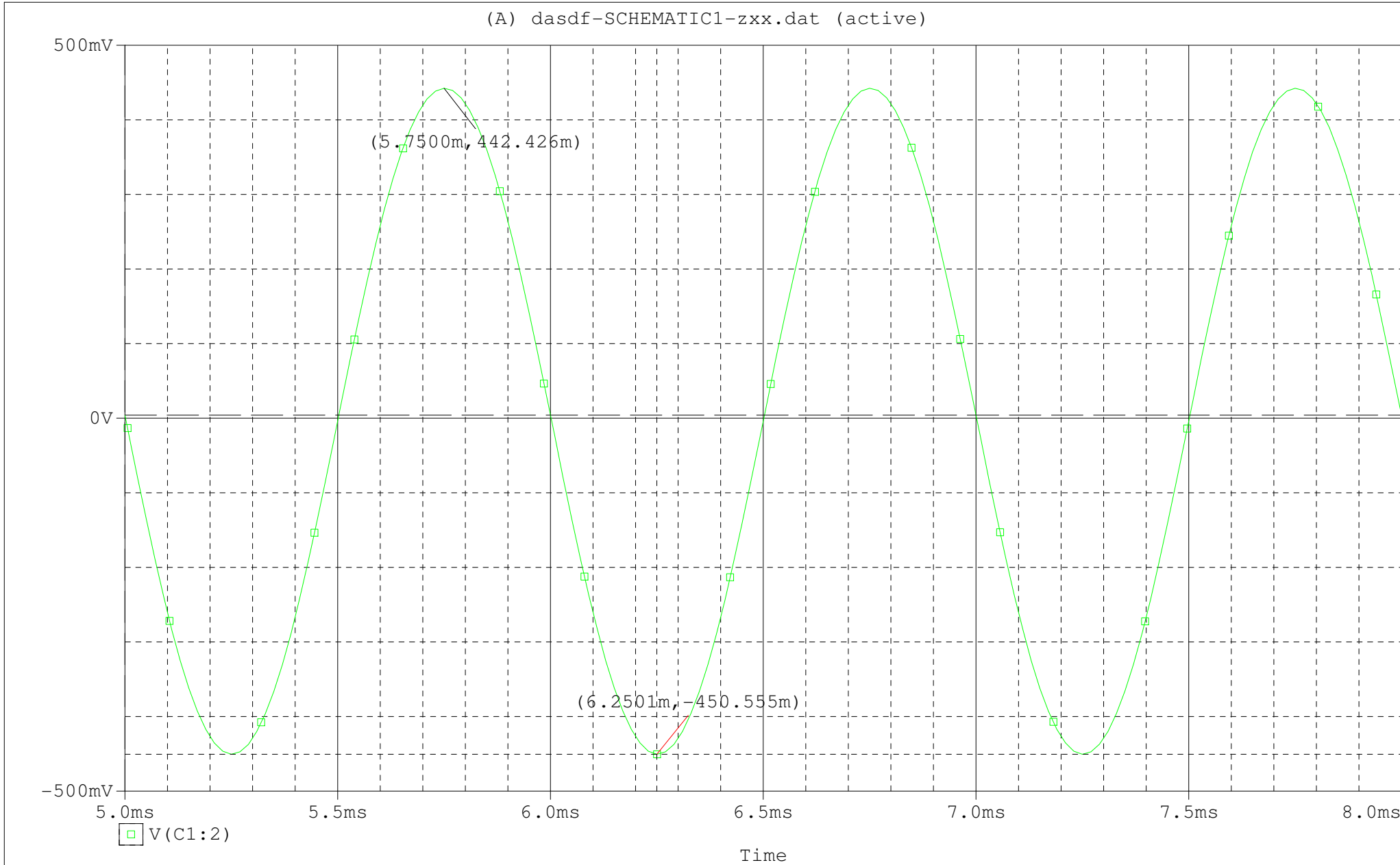


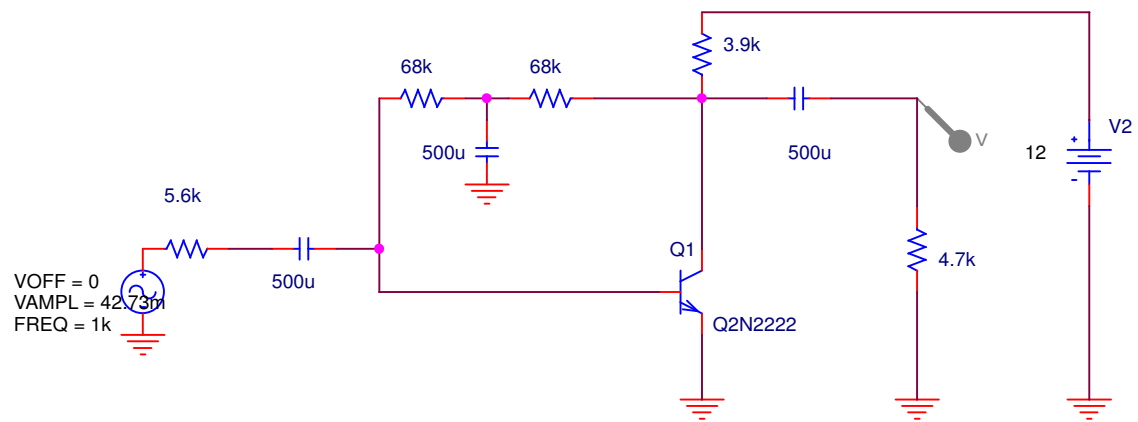A1: (6.2501m, -450.555m) A2: (5.0000m, 4.0598m) DIFF (A): (1.2501m, -454.615m)




Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Monday, January 09, 2012	Sheet 1 of 1

(A) dasdf-SCHEMATIC1-zxx.dat (active)

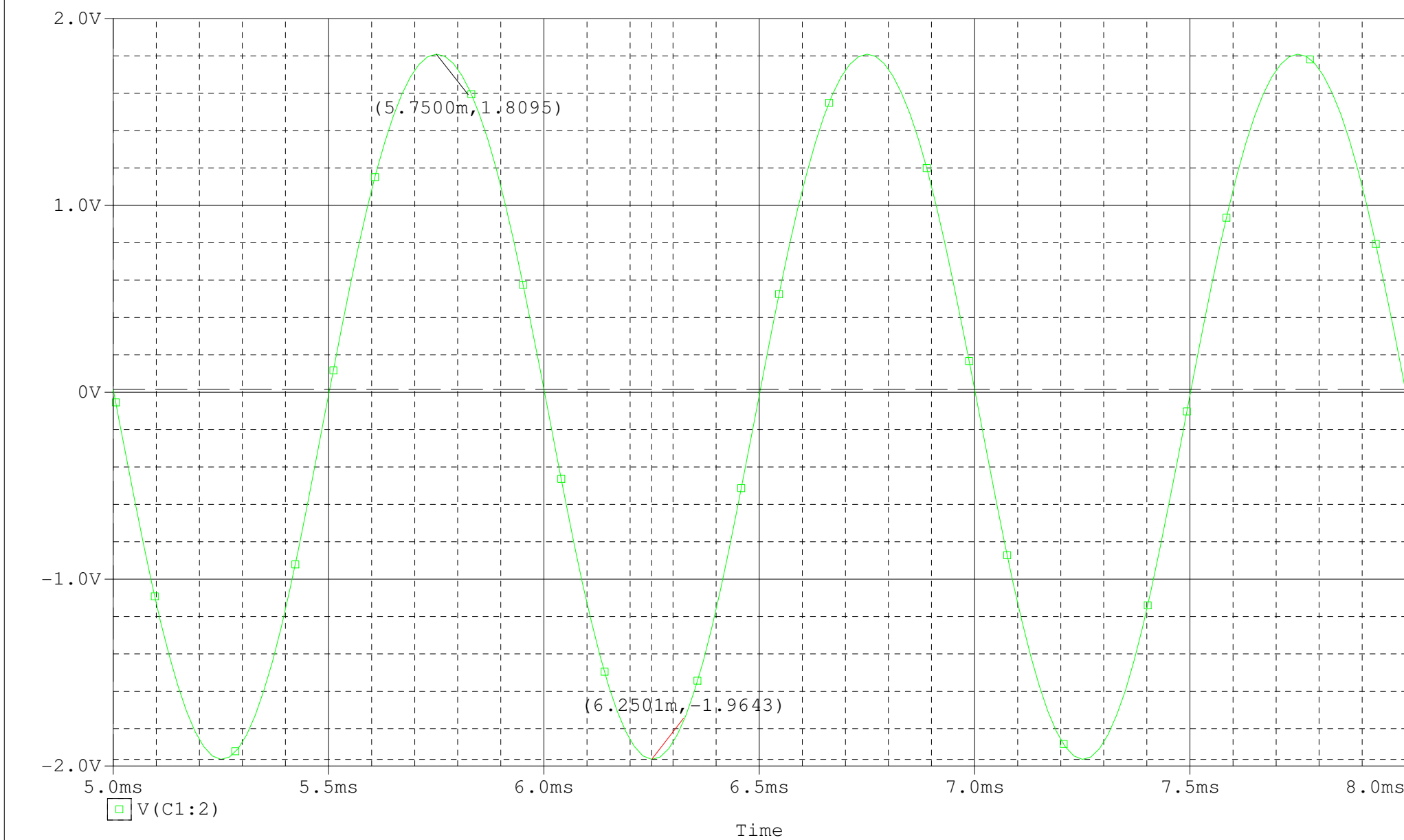


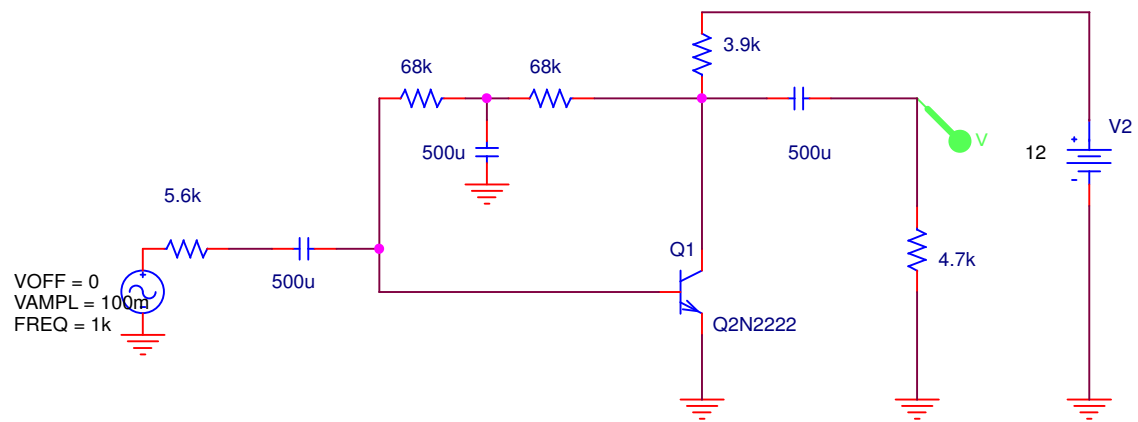A1: (6.2501m, -1.9643) A2: (5.0000m, 15.608m) DIFF (A): (1.2501m, -1.9799)



Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Monday, January 09, 2012	Sheet 1 of 1

(A) dasdf-SCHEMATIC1-zxx.dat (active)

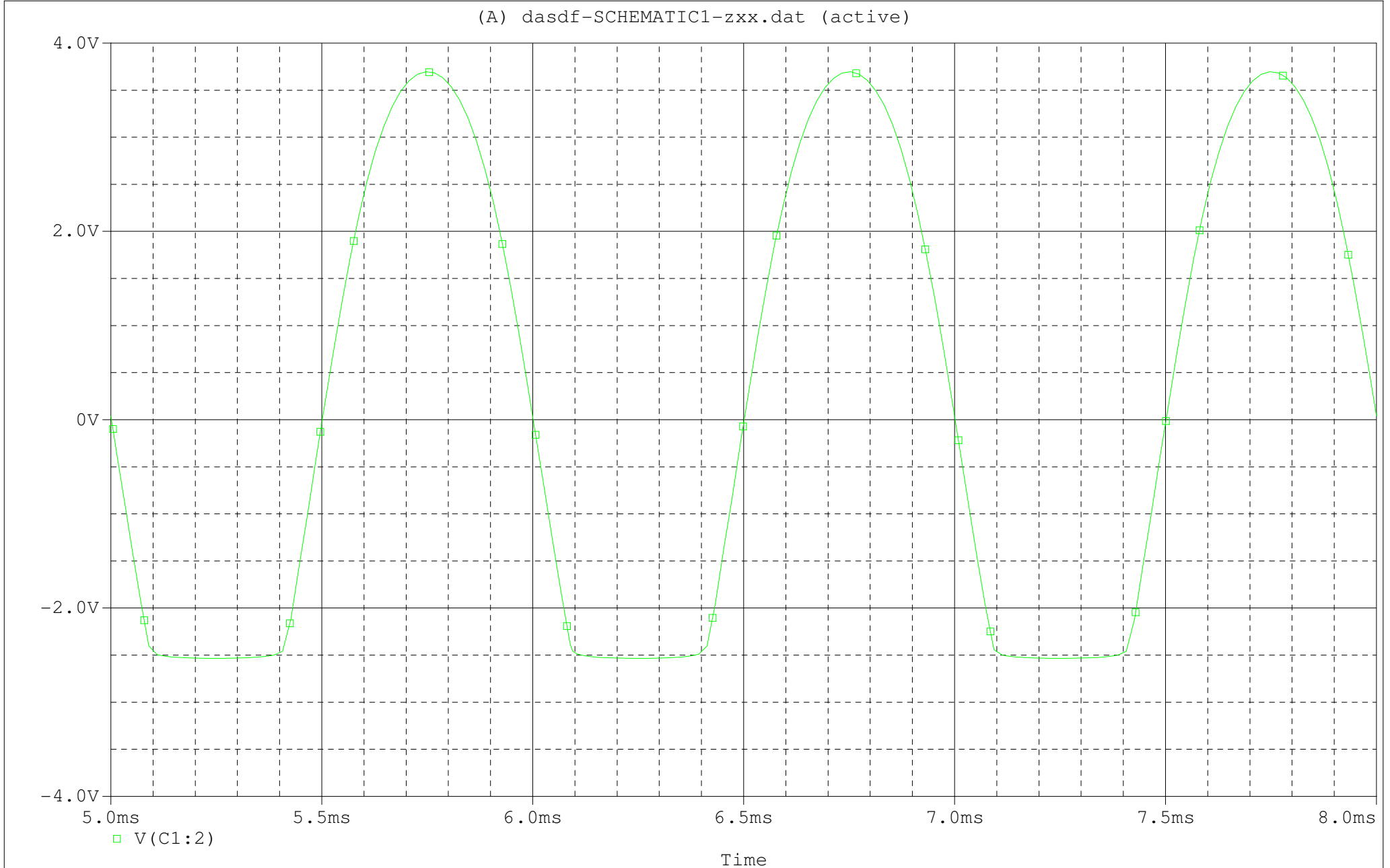

If we try to increase the input above 42.37 mV we can see how the output will be distorted.