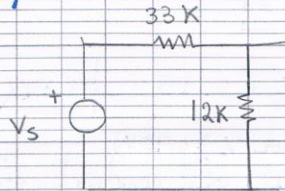


EECE 310. Homework 5

Problem 1


a)



let's find the thevenin equivalent of this circuit

$$V_{TH} = \frac{12K}{33K+12K} V_s = \frac{4}{15} V_s$$

$$R_{TH} = 33K \parallel 12K = 8.8K$$

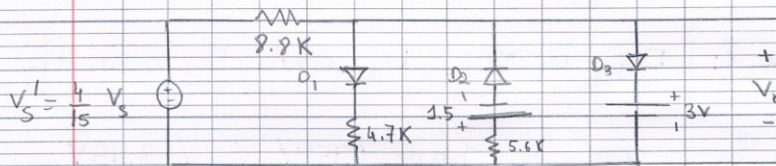

Case 1:  $D_1$ ,  $D_2$  and  $D_3$  are off

•  $D_1$  is off  $\rightarrow$   $\rightarrow V_{D1} < 0 \rightarrow V_o - 0.75 < 0$

$$V_o < 0.75V$$

•  $D_2$  is off  $\rightarrow$   $\rightarrow V_{D2} < 0 \rightarrow V_o - 2.25 < 0$

$$V_o > -2.25V$$

•  $D_3$  is off  $\rightarrow$   $\rightarrow V_{D3} < 0 \rightarrow V_o - 3.75 < 0$

$$V_o < 3.75V$$

Therefore

$$-2.25 < V_o < 0.75 \text{ V}$$


In this case  $V_o = \frac{4}{15} V_s$

$$-2.25 < \frac{4}{15} V_s < 0.75 \quad \rightarrow \quad \boxed{2.8125 < V_s < 2.8125}$$

Now if  $V_o > 0.75 \text{ V}$ ,  $D_1$  will conduct but  $D_2$  and  $D_3$  will remain off; this brings us to the second case.

Case 2:  $D_1$  is on,  $D_2$  and  $D_3$  are off.

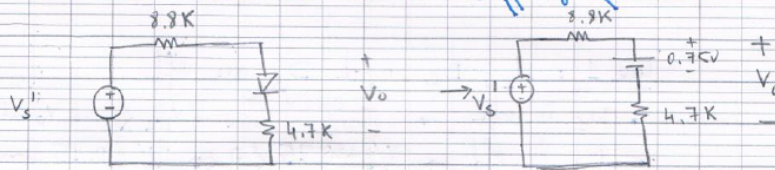In this case we have  $0.75 \text{ V} < V_o < 3.75 \text{ V}$



$$V_o = 0.75 + \frac{V_s' - 0.75}{8.9\text{K} + 4.7\text{K}} \times 4.7\text{K}$$

$$V_o = \frac{47}{135} V_s' + \frac{22}{45} ; \quad V_o = \frac{47}{135} \times \frac{4}{15} V_s + \frac{22}{45}$$

$$\boxed{V_o = \frac{188}{2025} V_s + \frac{22}{45}}$$

$$0.75 < V_o < 3.75 ; \quad \rightarrow \quad \boxed{2.8125 < V_s < 35.13 \text{ V}}$$



low, if  $V_o = 3.75V$   $D_1$  and  $D_3$  will conduct and  $D_2$  will remain off  $\rightarrow$  Case 3

Case 3:


$D_1$  and  $D_3$  : ON

$D_2$  : OFF

$$V_o = 3.75V$$

$$V_s \gg 35.13V$$

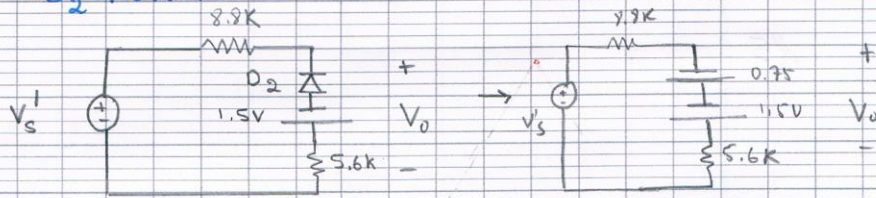Case 4:  $V_o \ll -2.25V$   
 $D_1$  and  $D_3$  : off.  
 $D_2$  : on





$$V_o = -2.25 + \frac{5.6}{7.8 + 5.6} (V_s' + 2.25)$$

$$V_o = \frac{7}{18} V_s' - 1.375 = \frac{7}{18} \times \frac{4}{15} V_s - 1.375$$

$$\boxed{V_o = \frac{14}{135} V_s - 1.375} \rightarrow \begin{cases} V_o \ll -2.25V \\ V_s \ll -8.4375V \end{cases}$$


Transfer characteristics

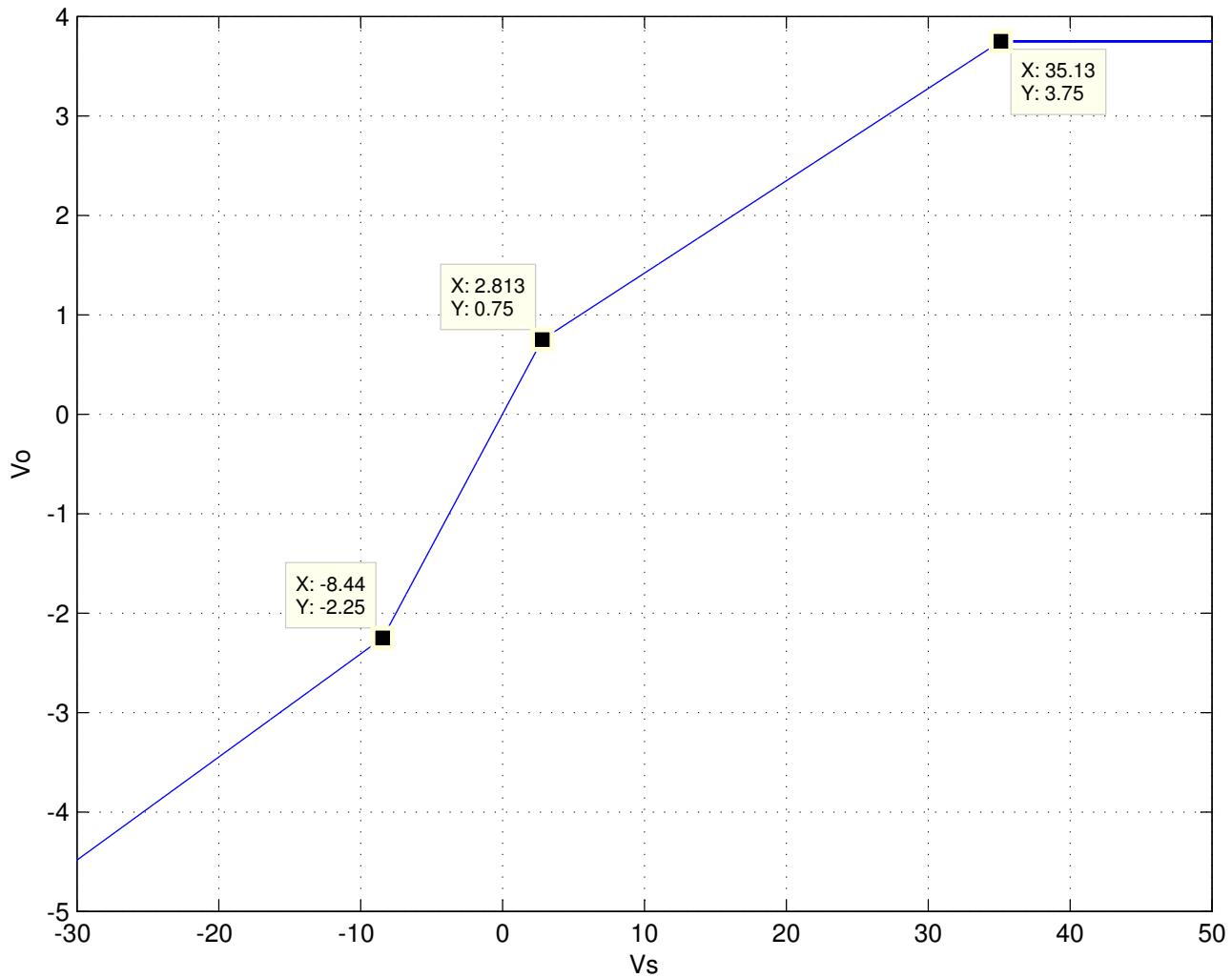

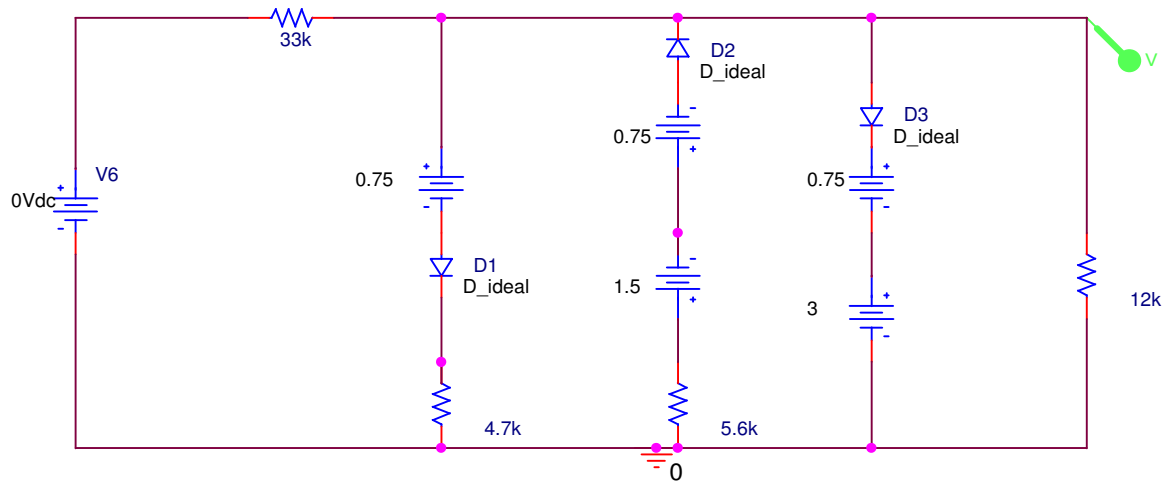

Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Sunday, October 30, 2011	Sheet 1 of 1

(A) tchar-SCHEMATIC1-vds.dat (active)

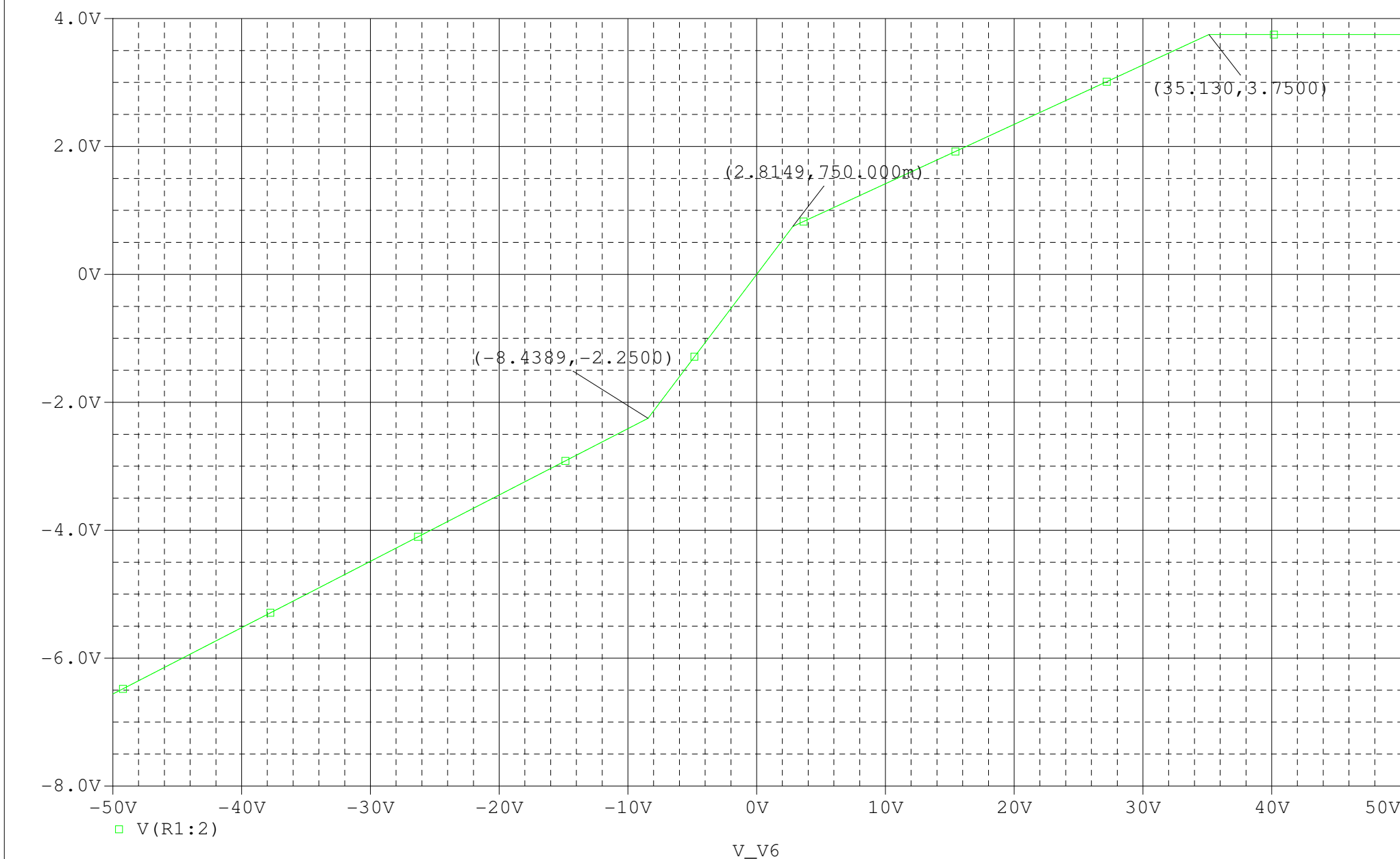




$$c) (1) -8.4375 < V_s < 2.8125 \rightarrow V_o = \frac{4}{15} V_s \quad \begin{cases} V_s = 0 \rightarrow V_o = 0V \\ V_s = 2.8125 \rightarrow V_o = 0.75V \\ V_s = -8.4375 \rightarrow V_o = -2.25V \end{cases}$$

$$(2) 2.8125 < V_s < 25 \rightarrow V_o = \frac{18}{2025} V_s + \frac{22}{45}$$

$$\begin{cases} V_s = 2.8125V \rightarrow V_o = 0.75V \\ V_s = 25V \rightarrow V_o = 2.81V \end{cases}$$

$$(3) -25 < V_s < -8.4375V \rightarrow V_o = \frac{14}{135} V_s - 1.375$$
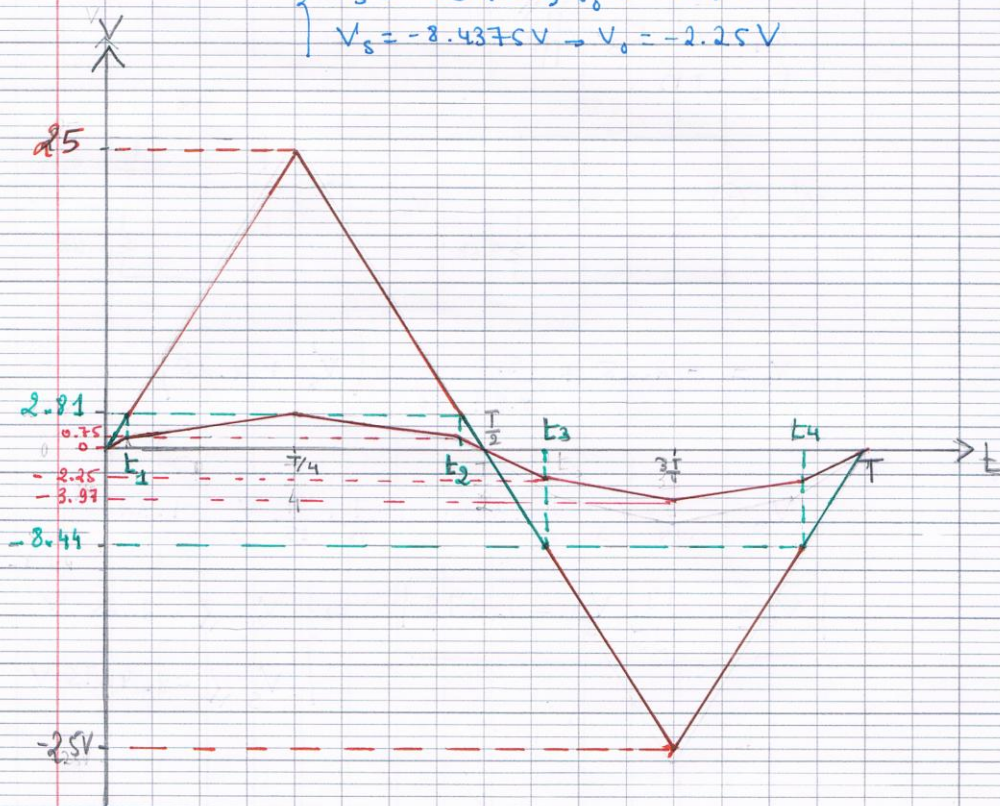
$$\begin{cases} V_s = -25V \rightarrow V_o = -3.97V \\ V_s = -8.4375V \rightarrow V_o = -2.25V \end{cases}$$



### Problem 2

a) n-type: electrons are majority carriers  
doping level:  $N_D = 3.5 \times 10^{17} \text{ cm}^{-3} = n$   
At 300 K,  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3} \Rightarrow p = \frac{n_i^2}{N_D} = 643 \ll n$   
hence we can neglect p to find  $N_D$   
 $J_n$

$$J_n = q \cdot n \cdot v_n = 1.6 \times 10^{-19} \times 3.5 \times 10^{17} \times 10^{10} \\ = 5.6 \times 10^5 \text{ A/cm}^2$$

$$\text{b) } \sigma = q(p\mu_p + n\mu_n) \approx qn\mu_n \\ = 1.6 \times 10^{-19} \times 3.5 \times 10^{17} \times 950 \\ = 53.2 \text{ } \Omega^{-1} \text{ cm}^{-1}$$

$$\rho = \frac{1}{\sigma} = 0.0188 \text{ } \Omega \cdot \text{cm}$$

$$\text{c) } V = RI = \frac{\rho L}{A} I = \rho L J = 0.0188 \times 5 \times 5.6 \times 10^5 \\ = 52640 \text{ V}$$

### Problem 3

$$n(x) = 10^5 + 10^{17} e^{-\frac{x}{L_n}} ; L_n = 2.5 \mu\text{m}$$

$$\text{a) } \bar{J}_n = q D_n \frac{dn}{dx}$$

$$\frac{dn}{dx} = -\frac{10^{17}}{L_n} e^{-\frac{x}{L_n}} = -\frac{10^{17}}{2.5 \times 10^{-4}} e^{-\frac{x}{L_n}} = -4 \times 10^{20} e^{-\frac{x}{L_n}}$$

$$\bar{J}_n = 1.6 \times 10^{-19} \times 13 \times (-4 \times 10^{20}) e^{-\frac{x}{L_n}} \\ = -832 e^{-\frac{x}{L_n}} \text{ A/cm}^2$$



$$b) \quad J_n = -832 e^{-0.75} = -393 \text{ A/cm}^2$$

$$I = J_n A = -393 \times 5000 \times 10^{-8}$$

$$= -0.01965 \text{ A}$$

$$= -19.65 \text{ mA}$$

#### Problem 4

$$N_A = 2 \times 10^{17} \text{ cm}^{-3} \quad \text{p-side}$$

$$N_D = 7 \times 10^{15} \text{ cm}^{-3} \quad \text{n-side}$$

$$a) \quad \begin{array}{l} \text{p-type: } P_p = N_A = 2 \times 10^{17} \text{ cm}^{-3} \\ \text{n-type: } P_n = \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{10})^2}{7 \times 10^{15}} = 32143 \text{ cm}^{-3} \end{array}$$

$$b) \quad \text{p-type: } n_p = \frac{n_i^2}{N_A} = 1125 \text{ cm}^{-3}$$

$$\text{n-type: } n_n = N_D = 7 \times 10^{15} \text{ cm}^{-3}$$

$$c) \quad V_0 = V_T \ln \frac{N_A N_D}{n_i^2}$$

$$= \frac{k \cdot T}{q} \ln \frac{N_A N_D}{n_i^2}$$

$$= \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} \times \ln \left( \frac{2 \times 10^{17} \times 7 \times 10^{15}}{(1.5 \times 10^{10})^2} \right) = 0.762 \text{ V}$$