
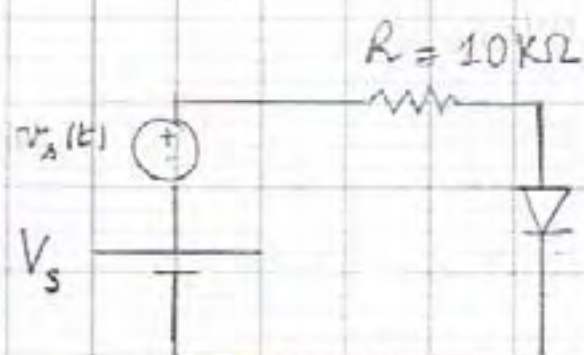


EECE 310 - Homework 3

Problem 1

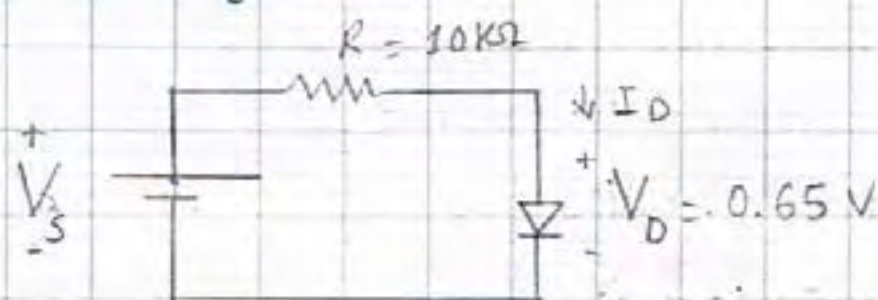

DC analysis




The diode is conducting:

$$V_D = 0.65\text{V}$$

$$I_D = \frac{V_s - V_D}{R} = \frac{9 - 0.65}{10\text{K}} = 0.835\text{mA}$$

Small signal analysis

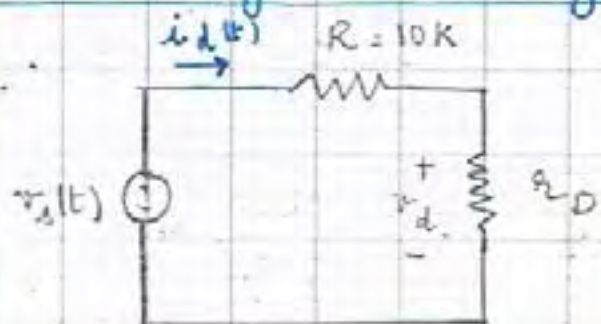

The diode can be replaced by a resistor $r_d = \frac{nV_T}{I_D}$

$$v_d = \frac{r_d}{r_d + R} v_s(t) \quad ; \quad r_d = \frac{nV_T}{I_D} = \frac{1.7 \times 25}{0.835} = 50.898\ \Omega$$

$$v_d = \frac{50.888}{50.888 + 10000} v_s(t) = 5.064 \times 10^{-3} v_s(t)$$

$v_s(t)$ varies between 1.5V and -1.5V.

$$v_{d(\max)} = 5.064 \times 10^{-3} \times 1.5 = 7.596 \text{ mV}$$

$$v_{d(\min)} = -7.596 \text{ mV}$$

$$\text{Thus } v_d = \pm 7.596 \text{ mV}, v_{d,p-p} = 7.596 \times 2 = 15.192 \text{ mV}$$

For $n=1.7$, we have $|v_d(t)|_{\max} = 7.596 \text{ mV}$; the small signal analysis is justified:

~~$$i_D = I_S e^{\frac{v_D}{nV_T}} = I_S e^{\frac{V_D + v_d}{nV_T}} = I_D e^{\frac{v_d}{nV_T}}$$~~

~~Taylor series:~~

~~$$i_D = I_D \left(1 + \frac{v_d}{nV_T} + \frac{1}{2} \left(\frac{v_d}{nV_T} \right)^2 + \dots \right)$$~~

~~$$\left(\frac{v_d}{nV_T} \right)_{\max} = \frac{7.596}{1.7 \times 25} = 0.178$$~~

< 0.2 (limit of small-signal analysis for diodes)

~~$$\frac{1}{2} \left(\frac{v_d}{nV_T} \right)_{\max}^2 = 0.0156 \quad \left(\begin{array}{l} \text{lower} \\ \text{10 times} \\ \text{than} \\ \text{the above term} \end{array} \right)$$~~

~~$$\text{Thus } i_D \approx I_D \left(1 + \frac{v_d}{nV_T} \right)$$~~

~~Thus the small signal analysis is justified. (The higher order non-linear terms are neglected because of their small values relative to the linear term).~~

Total diode current

$$i_D(t) = \underbrace{I_D}_{\text{DC component}} + i_d(t)$$

$$I_D = 0.835 \text{ mA}$$

$$i_d(t) = \frac{v_s(t)}{R + r_d} \quad (\text{referring to the figure of small signal analysis})$$


$$i_D(t) = 0.835 + \frac{1}{10 + 50.838 \times 10^{-3}} v_s(t) \quad \begin{matrix} \text{[in mA]} \\ \text{[in V]} \end{matrix}$$

$$\underbrace{i_D(t)}_{\text{triangular signal}} = 0.835 + 0.099 \underbrace{v_s(t)}_{\text{triangular signal}} \quad \text{[in mA]}$$

$$i_D(t)_{\text{max}} = 0.835 + 0.099 \times 1.5 = 0.984 \text{ mA}$$


$$i_D(t)_{\text{min}} = 0.835 - 0.099 \times 1.5 = 0.686 \text{ mA}$$

$i_D(t)$ has a triangular waveform that varies between 0.984 mA and 0.686 mA, crossing the line of 0.835 mA.

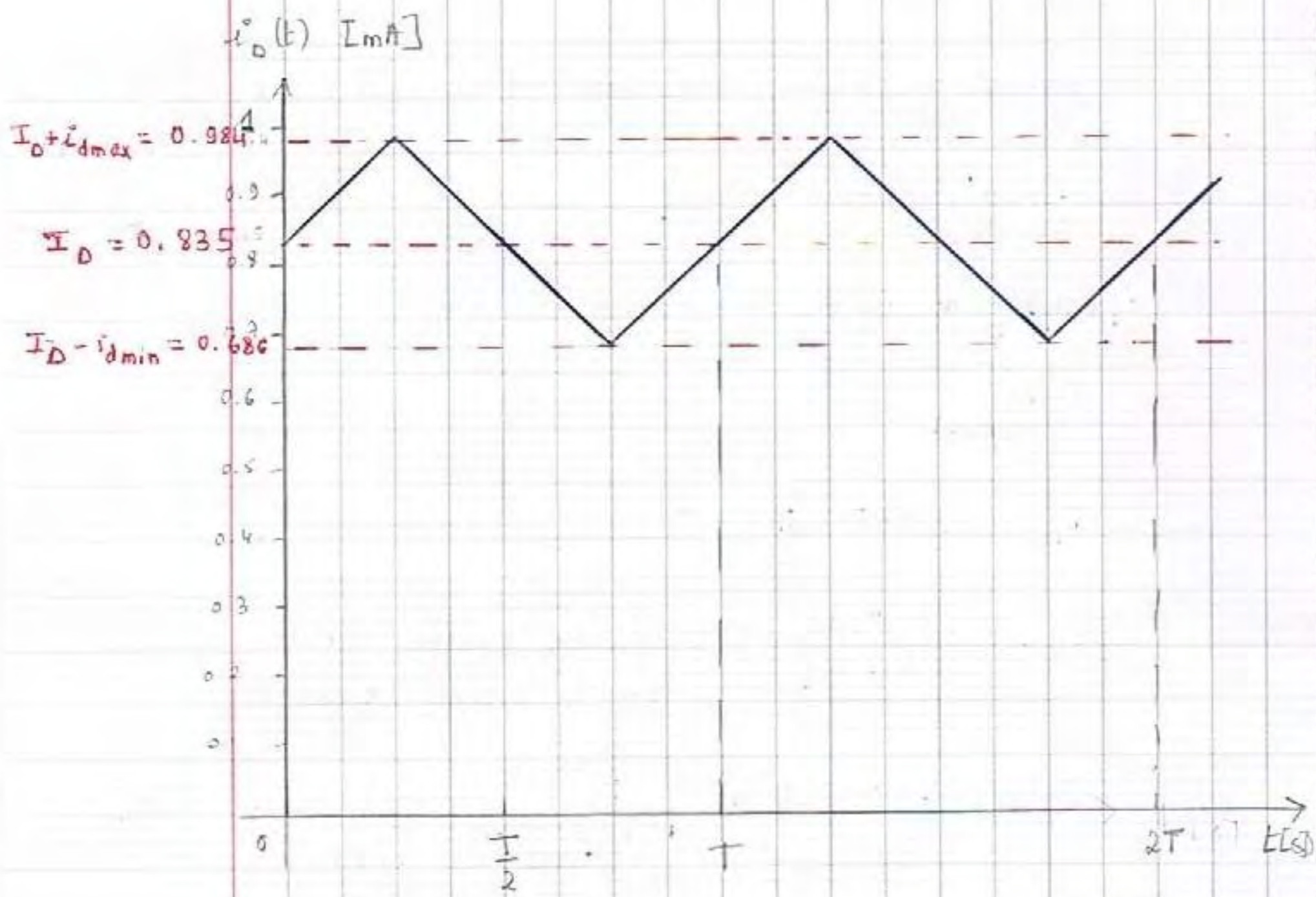

Problem 2

a)

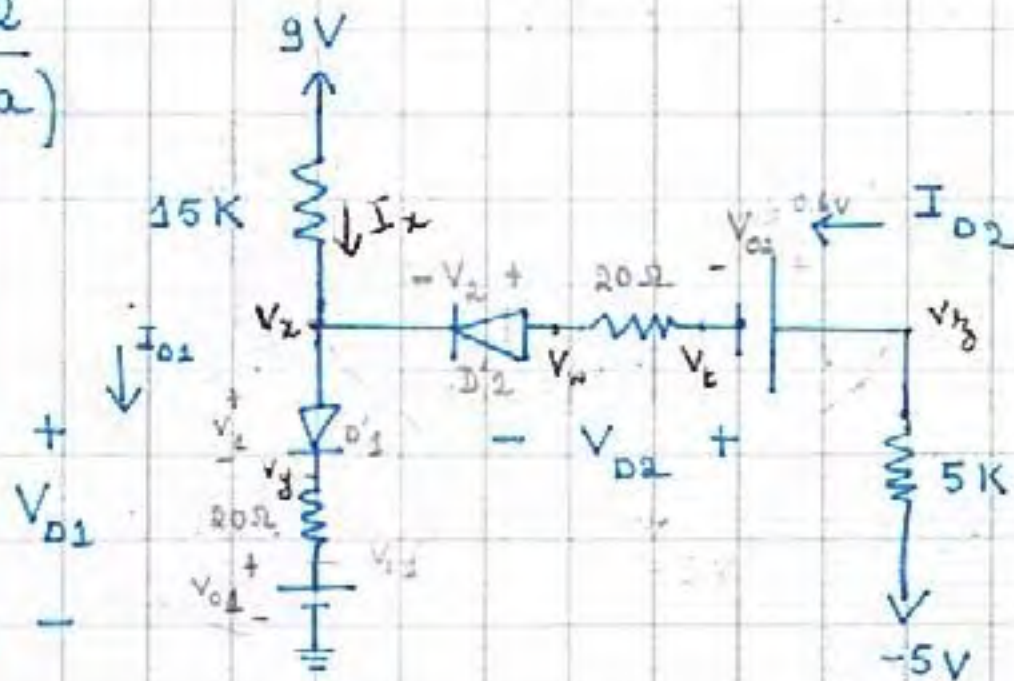

Assume D'_1 is ON and D'_2 is OFF

Thus $\begin{cases} V_1 = 0V \\ I_{02} = 0A \end{cases}$ and we have to get $\begin{cases} I_{01} > 0 \\ V_2 < 0 \end{cases}$

Since $V_1 = 0V$, $V_x = V_y$

Since $I_{02} = 0A$, $I_x = I_{01}$

$$I_x = \frac{9 - V_x}{15K} = \frac{V_y - 0.6}{20}$$

$$\frac{9 - V_x}{15000} = \frac{V_x - 0.6}{20}$$

$$180 - 20V_x = 15000V_x - 9000$$

$$V_x = \frac{9180}{15020} = 0.611V$$

$$I_{01} = \frac{V_x - 0.6}{20} = \frac{0.611 - 0.6}{20} = 0.55mA \quad (I_{01} > 0)$$

$$\text{Since } I_{D2} = 0A, V_g = -5V$$

$$V_{D2} = V_g - V_E; V_E = V_g - V_{D2} = -5 - 0.6 = -5.6V$$

$$V_E = V_W = -5.6V \quad (\text{since } I_{D2} = 0A)$$


$$V_2 = V_W - V_x = -5.6 - 0.611 = -6.211V \quad (V_2 < 0)$$

The assumptions are correct.

$$D_1: \quad I_{D1} = 0.55 \text{ mA} \quad \Rightarrow D_1: (0.55 \text{ mA}, 0.611V) \\ V_{D1} = V_x = 0.611V$$

$$D_2: \quad I_{D2} = 0 \text{ mA} \\ V_{D2} = V_{D2} + V_2 = 0.6 - 6.211 = -5.611V$$
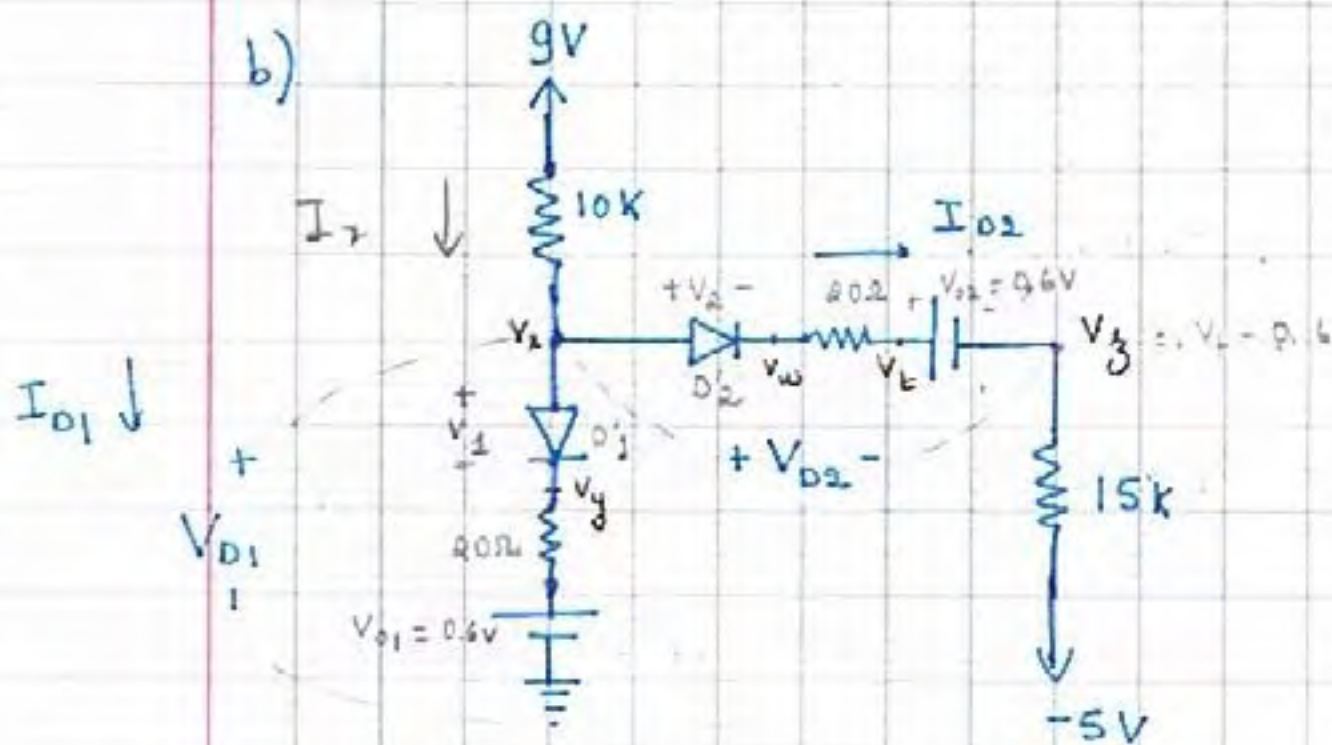
$$\Rightarrow D_2: (0 \text{ mA}, -5.611V)$$



Assume D_1 and D_2 are on.

We have $\begin{cases} V_1 = 0V \\ V_2 = 0V \end{cases}$ and we have $\begin{cases} I_1 > 0 \\ I_2 > 0 \end{cases}$ to get

Since $V_1 = 0$, $V_x = V_y$

Since $V_2 = 0$, $V_x = V_w$

KCL : $I_x = I_{D1} + I_{D2}$

$$\frac{9 - V_x}{10K} = \frac{V_x - 0.6}{20} + \frac{V_x - V_E}{20}$$

$$\left| \left(\frac{1}{20} + \frac{1}{20} + \frac{1}{10K} \right) V_x - \frac{1}{20} V_E = \frac{9}{10K} + \frac{0.6}{20} \right| \quad (1)$$

$$I_{D2} = \frac{V_x - V_E}{20} = \frac{V_z + 5}{15K}, \quad V_z = V_E - 0.6$$

$$\frac{V_x}{20} - \frac{V_E}{20} = \frac{V_E}{15K} + \frac{4.4}{15K}$$

$$\left| \frac{1}{20} V_x - \left(\frac{1}{15K} + \frac{1}{20} \right) V_E = \frac{4.4}{15K} \right| \quad (2)$$

Solving the 2 equations (1) & (2) gives:

$$V_x = 0.6101V$$

$$V_t = 0.6034V$$

$$I_{D1} = \frac{V_x - 0.6}{20} = \frac{0.6101 - 0.6}{20} = 0.505 \text{ mA } (> 0)$$

$$I_{D2} = \frac{V_x - V_t}{20} = \frac{0.6101 - 0.6034}{20} = 0.335 \text{ mA } (> 0)$$


The two assumptions are correct.

$$D_1: V_{D1} = V_x = 0.6101V$$

$$I_{D1} = 0.505 \text{ mA} \rightarrow D_1: (0.505 \text{ mA}, 0.6101V)$$

$$D_2: V_{D2} = V_x - V_t + 0.6 = 0.6071V$$
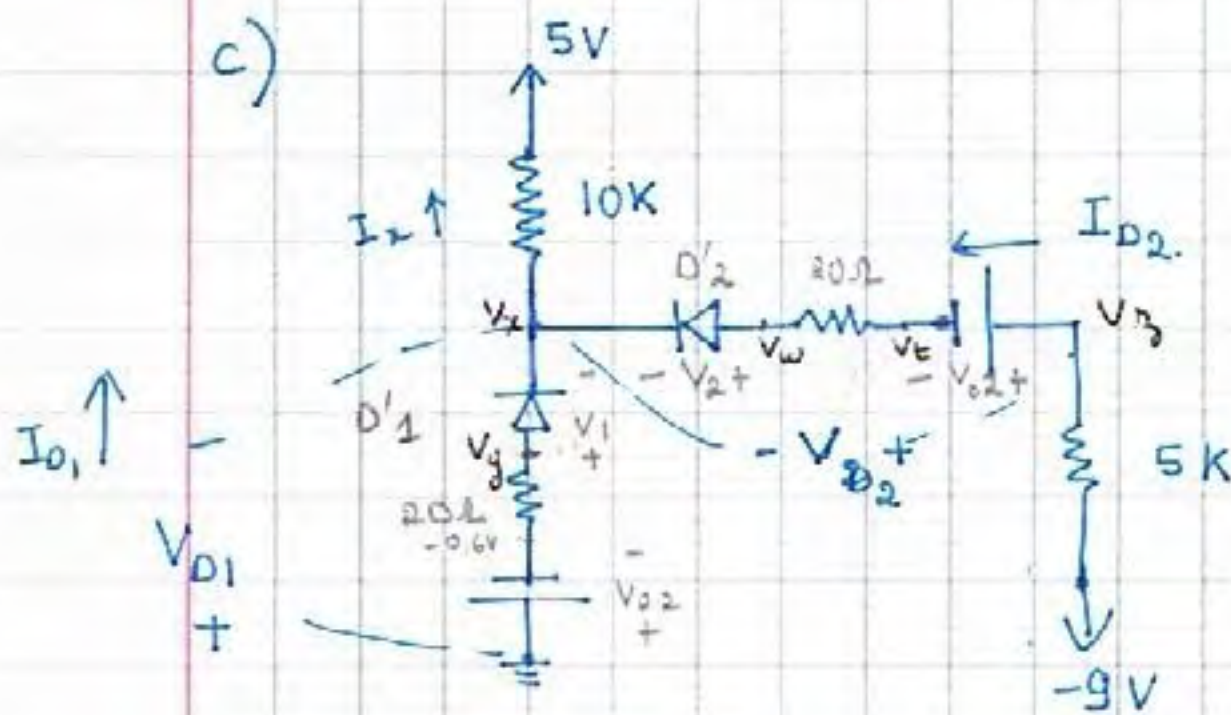
$$I_{D2} = 0.335 \text{ mA} \rightarrow D_2: (0.335 \text{ mA}, 0.6071V)$$



Assume D'_1 and D'_2 are OFF.

Thus we have $\begin{cases} V_1 = 0V \\ V_2 = 0V \end{cases}$ and we have $\begin{cases} I_{D1} > 0 \\ I_{D2} > 0 \end{cases}$ to get

Since $I_{D2} = 0A$, $V_3 = -9V \Rightarrow V_E = -9 - 0.6V = -9.6V$

$V_w = V_E = -9.6V$

Since $I_{D1} + I_{D2} = 0 + 0 = 0$, $I_x (= I_1 + I_2) = 0A$
 Thus $V_x = 5V$


$V_2 = V_w - V_x = -9.6 - 5 = -14.6V (< 0)$

$V_y = -0.6V$; $V_1 = V_y - V_x = -0.6 - 5 = -5.6V (< 0)$


The two assumptions are correct.

D_1 : $V_{D1} = -V_x = -5V$
 $I_{D1} = 0A \rightarrow D_1: (0; -5V)$

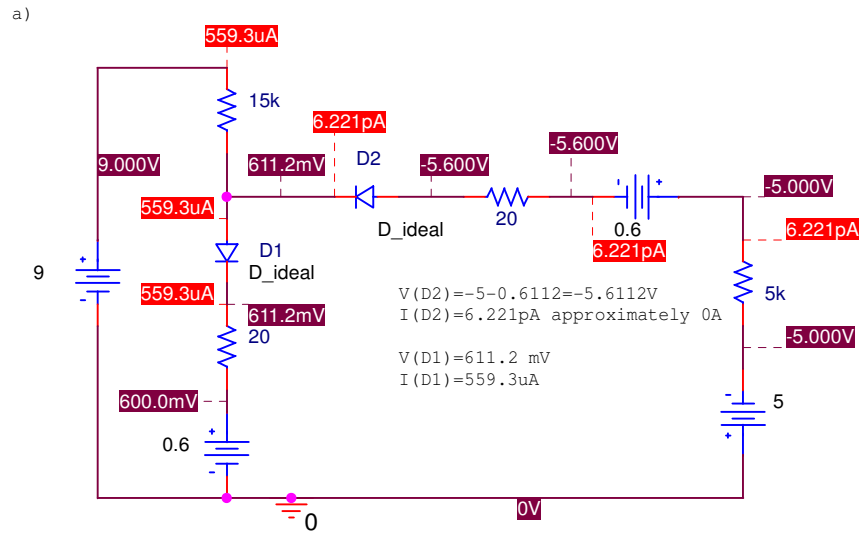
D_2 : $V_{D2} = 0.6 - 14.6 = -14V$
 $I_{D2} = 0A \rightarrow D_2: (0; -14V)$



Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Sunday, October 16, 2011	Sheet 1 of 1

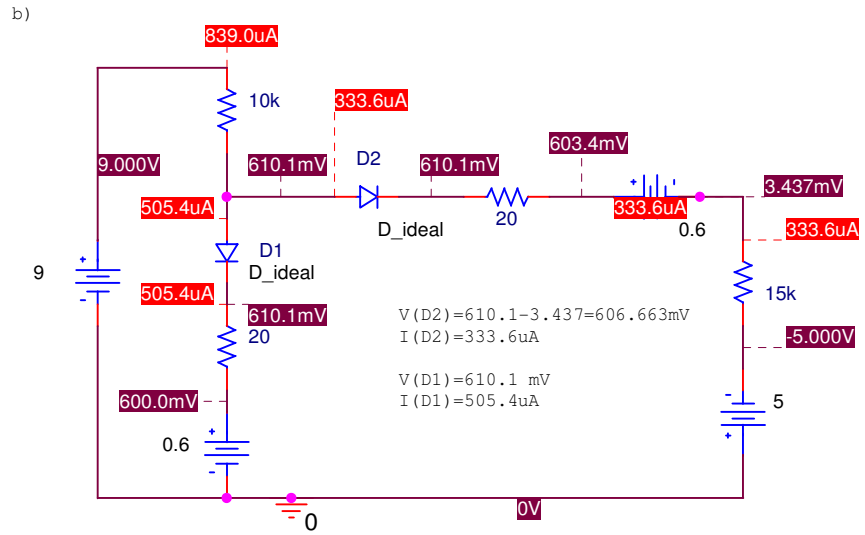

Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Sunday, October 16, 2011	Sheet 1 of 1

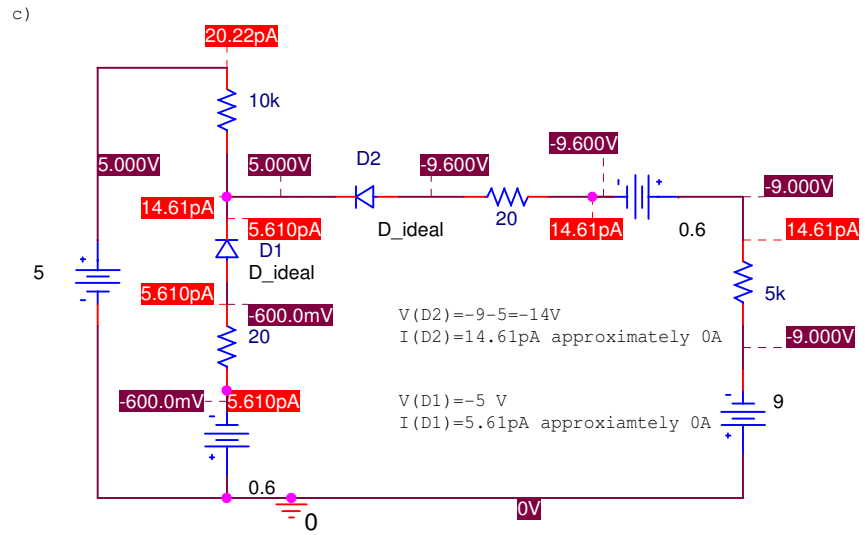

Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Sunday, October 16, 2011	Sheet 1 of 1