

**American University of Beirut**  
**Department of Electrical and Computer Engineering**

EECE 310 – Electronics

Quiz 2 – December 9, 2011

Closed Book – *No Programmable Calculators*

90 minutes

**Penalty is 5 to 1**

(1 to 4 wrong answers do not result in a penalty; 5 to 9 wrong answers cancel one correct answer; 10 to 14 wrong answers cancel two correct answers; and so on)

All questions are equally graded.

Name: \_\_\_\_\_ ID number: \_\_\_\_\_

1. An amplifier has an open-circuit voltage gain of 10 V/V, an input resistance of 12 k $\Omega$ , and an output resistance of 10 k $\Omega$ . Find the amplifier short-circuit transconductance  $G$  (in mA/V).

- a) 1.5      b) 2.0      c) 2.5      d) 0.5      e) **1.0**
- 

2. A transconductance amplifier has an input resistance of 9 k $\Omega$ , an output resistance of 1 k $\Omega$ , and a short-circuit transconductance of 50 mA/V. If two of these transconductance amplifiers are cascaded, find the voltage gain (in V/V), from input of first stage to load, when a 4 k $\Omega$  load is connected across the output terminals.

- a) **1800**      b) 1152      c) 72      d) 288      e) 648
- 

3. A particular MOSFET operating in the saturation region has an output resistance ( $r_o$ ) of 50 k $\Omega$  at  $I_D = 1$  mA and  $V_{DS} = 3$  V. Find the Early voltage  $V_A$  (in V) of this MOSFET.

- a) 57      b) 37      c) 42      d) **47**      e) 52
- 

The drain current of an enhancement N-channel MOSFET is measured at several values of  $V_{GS}$  and  $V_{DS}$ , as shown in the table below. For this MOSFET,  $V_t = 1$  V.

$V_{GS}$ (V)	$V_{DS}$ (V)	$I_D$ (mA)
3	3	0.8960
3	4	0.9280
$V_x$	0.2	0.2320

4. Find the value of  $\lambda$  (in  $V^{-1}$ ).

- a) 0.05      b) **0.04**      c) 0.03      d) 0.02      e) 0.01

5. Find the value of  $k'_n(W/L)$  in mA/V<sup>2</sup>.


- a) 0.56      b) 0.32      c) 0.64      d) **0.40**      e) 0.48

6. Find  $V_x$  (in V).

- a) 5.5      b) 4.5      c) 5.0      d) 3.5      e) **4.0**
-

7. For the PMOS transistor in the circuit shown in the figure below,  $k'_p = 80 \mu\text{A}/\text{V}^2$ ,  $W/L = 2.5$ ,  $\lambda = 0$ , and  $V_t = -1.4 \text{ V}$ . Find the voltage  $V_{GS}$  (in V) for  $I = 100 \mu\text{A}$  and  $R = 8 \text{ k}\Omega$ .

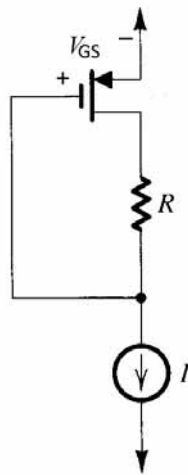- a) -2.8      b) **-2.4**      c) -2.0      d) -2.2      e) -2.6




8. The N-channel enhancement MOSFET has  $V_t = 1.1 \text{ V}$ ,  $\lambda = 0$ , and  $k'_n(W/L) = 1 \text{ mA}/\text{V}^2$ . If  $R_D = 1.5 \text{ k}\Omega$  and the MOSFET operates at the *boundary* between the triode and saturation regions, find  $V_D$  (in V).

- a) 3.6      b) 3.7      c) 3.8      d) **3.9**      e) 4.0

9. Find the value of  $R_S$  (in  $\text{k}\Omega$ ) in the previous problem.

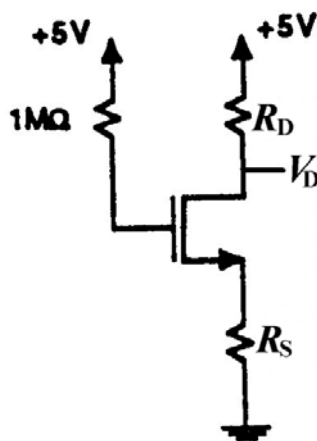
- a) 6.39      b) 8.35      c) 2.59      d) 5.88      e) **3.67**



10. An N-channel enhancement MOSFET having  $k'_n(W/L) = 1 \text{ mA}/\text{V}^2$  is used for small signals as a linear resistance between drain and source whose value is  $2 \text{ k}\Omega$  when  $V_{GS}$  is  $1 \text{ V}$ . If  $V_{GS}$  is increased to  $3.5 \text{ V}$ , what would the value of this resistance become (in  $\Omega$ )?

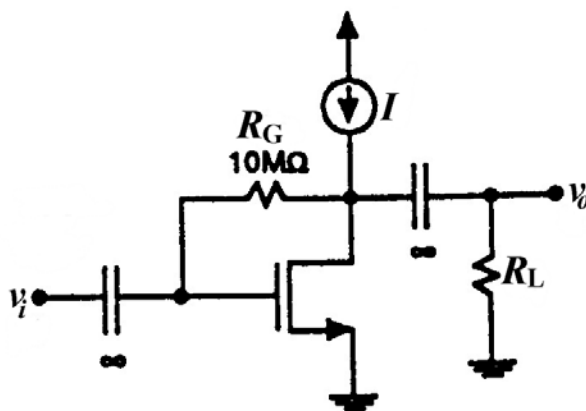- a) **333.3**      b) 1000      c) 666.7      d) 500      e) 400

In the circuit shown below,  $R_G = 10\text{ M}\Omega$ , the capacitors are very large, and  $\lambda = 0$ . The transistor is biased in the saturation region such that the gate to source overdrive voltage  $V_{OV}$  is 1.8 V.



11. Find the value of the MOSFET transconductance  $g_m$  (in mA/V) if the current source carries  $I = 1\text{ mA}$ .

- a) 0.91      b) 1.43      c) 1.25      d) 1.11      e) 1.67

12. If the MOSFET transconductance  $g_m = 1\text{ mA/V}$  and the input resistance of the amplifier  $v_i/i_i$  was measured to be  $1.0\text{ M}\Omega$ , find the value of the load resistance  $R_L$  (in  $\text{k}\Omega$ ).

- a) 8.1      b) 11.5      c) 10.1      d) 9.0      e) 7.3

13. Assume that the DC component of  $v_{GS}$  is  $V_{GS} = 2.8\text{ V}$  and that the small-signal voltage gain  $v_o/v_i$  of  $-8\text{ V/V}$ . Neglecting distortion, find the largest input signal amplitude  $v_{gs(\text{max})}$  (in mV) such that the MOSFET remains in saturation.


- a) 166.7      b) 142.8      c) 125.0      d) 111.1      e) 100.0

In the circuit shown below, the transistor is biased in the saturation region.

The capacitors are very large,  $\lambda = 0$ ,  $k'_n(W/L) = 0.5\text{ mA/V}^2$ ,

$R_A = R_B = 380\text{ k}\Omega$ ,  $R_{\text{sig}} = 10\text{ k}\Omega$ ,  $R_D = 8\text{ k}\Omega$ ,  $R_L = 12\text{ k}\Omega$ ,

and  $R_S = 1.4\text{ k}\Omega$ .

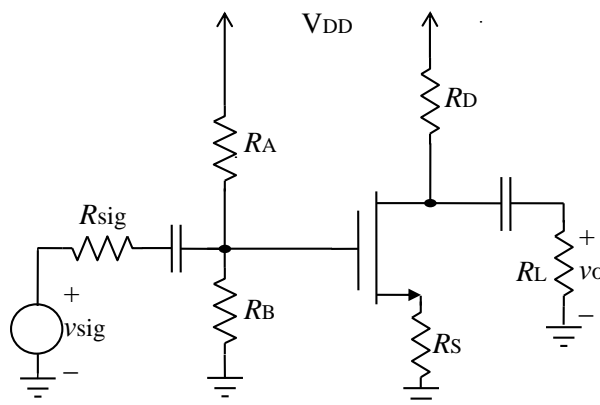

14. Find the value of the MOSFET transconductance  $g_m$  (in mA/V) if the transistor is biased such that  $I_D = 1.4$  mA.

- a) 1.304      b) **1.183**      c) 0.707      d) 0.894      e) 1.05

15. If the MOSFET transconductance  $g_m = 1$  mA/V and  $v_{sig}$  is a 0.2 V peak-to-peak sinusoid, find the peak-to-peak variation of  $v_{gs}$  (in mV).

- a) **79.2**      b) 73.08      c) 86.36      d) 118.75      e) 105.55


16. Assume now that a *large capacitor is connected in parallel with  $R_S$*  and that the MOSFET is biased such that  $g_m = 0.9$  mA/V and  $r_o = 25$  k $\Omega$ . Find the small-signal current gain  $i_o/i_i$  (in A/A). Note that  $i_o$  flows in  $R_L$ , and  $i_i$  flows in  $R_{sig}$ .

- a) -31.9      b) -38.3      c) -44.6      d) -51.0      e) **-57.4**

17. A MOSFET is biased at  $V_{OV} = 1$  V,  $V_{DS} = 5$  V, with  $I_D = 0.2$  mA. Find the resistance value (in k $\Omega$ ) that appears between gate and source in the small-signal **T-model**.

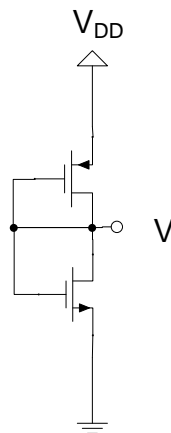- a) **2.5**      b) 2.0      c) 1.7      d) 5.0      e) 3.3

In the circuit shown below, the N-channel MOSFET is characterized by  $k'_n(W/L) = 4$  mA/V<sup>2</sup>,  $V_{tn} = 1$  V and  $\lambda = 0$ . The PMOS transistor is characterized by  $k'_p(W/L) = 2$  mA/V<sup>2</sup>,  $V_{tp} = -1$  V and  $\lambda = 0$ .



18. If  $V_{DD}$  is large enough for the MOSFETs to conduct, in what region would the MOSFETs be operating?

- a) N is TRIODE, P is TRIODE  
 b) N is SAT, P is TRIODE  
 c) **N is SAT, P is SAT**  
 d) N is TRIODE, P is SAT  
 e) N is OFF, P is OFF; the MOSFETs cannot conduct for any value of  $V_{DD}$ .

19. Given that the voltage  $V$  is 4 V, what is the value of  $I_D$  (in mA)?

- a) 2      b) **18**      c) 8      d) 50      e) 32

20. If  $V_{DD} = 6$  V, what is the voltage  $V$  (in V) at the connected gates?

- a) 3.49      b) 3.90      c) 4.31      d) 3.07      e) **2.66**