

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics
Quiz 1 – November 4, 2011
Closed Book – No Programmable Calculators

90 minutes

There are 20 problems. All problems are equally graded.

Penalty is 5 to 1

(1 to 4 wrong answers do not result in a penalty; 5 to 9 wrong answers cancel one correct answer; 10 to 14 wrong answers cancel two correct answers; and so on)

Name: _____ **ID number:** _____

Unless otherwise specified, assume that:

$$V_T = 25 \text{ mV}$$

$$n = 1$$

$$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$J_p = -qD_p \frac{dp}{dx} \quad J_n = qD_n \frac{dn}{dx}$$

$$J_d = (qp\mu_p + qn\mu_n)E$$

$$I = J \times A$$

1. An amplifier operating from ± 15 V power supplies provides a 5 V rms sine-wave signal to a 1 k Ω load and draws negligible current from the signal source. The amplifier draws a current of 3 mA from each of its two power supplies. Find the power dissipated (lost) in the amplifier (in mW).

- a) 9 b) 26 c) 41 d) 65 e) 54

2. An amplifier has a linear transfer characteristic passing through (0, 0) and with output saturation at 10 V and -10 V. The amplifier gain is 100 V/V. The input voltage consists of a sine-wave component superimposed over a 30 mV DC component. What is the amplitude (in V) of the largest undistorted sine-wave that can appear at the output?


- a) 5 b) 8 c) 7 d) 6 e) 9

3. An amplifier has the transfer characteristic $v_o = e^{3(v_i-1)}$ for $v_i \geq 1$ V and $v_o \leq 20$ V. Both voltages are expressed in V. If the output voltage at the operating point is 10 V, find the voltage gain (in dB).


- a) 29.5 b) 31.1 c) 32.5 d) 25.1 e) 27.6

4. The diodes in the circuit shown below are ideal. Find the forward current in diode D_2 (in mA) if $V_{CC} = 6$ V.

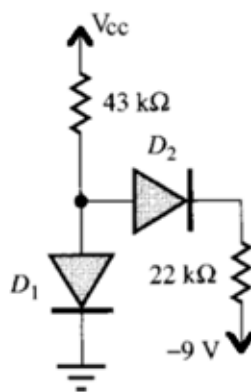- a) 0.26 b) 0.29 c) 0.32 d) 0.35 e) 0.23



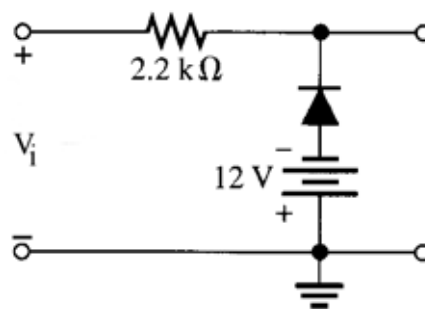
In the circuit shown below, the sine-wave input V_i has a *peak-to-peak* value of 48 V. The diode is modeled by a fixed 0.8 V drop when conducting, and by an open circuit when OFF. Refer to this circuit for questions 5 and 6.



5. Find the peak inverse voltage (PIV) of the diode (in V).
 a) 30 b) 32 c) 34 d) **36** e) 38
6. Find the peak value of the diode current (in mA).
 a) 6.0 b) 2.4 c) 3.3 d) 4.2 e) **5.1**

7. The diode in the circuit shown below is modeled by a fixed 0.8 V drop when conducting, and by an open circuit when OFF. The square-wave input voltage V_i is -6 V for 50% of the time, and $+6$ V for 50% of the time. Find the average (DC) value of the output voltage V_o (in V).

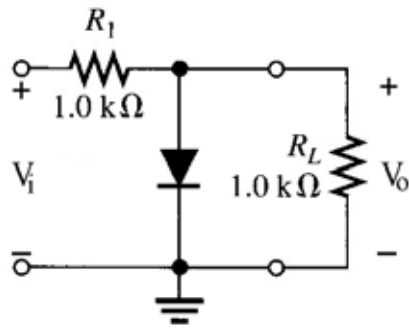- a) **-1.1** b) -1.6 c) -2.1 d) -2.6 e) -3.1



8. A diode conducts 0.1 mA at 0.8 V and its voltage changes by 0.060 V for every decade change in current. Find its reverse saturation current I_s (in A).

- a) **4.64×10^{-18}** b) 3.73×10^{-16} c) 1.75×10^{-14} d) 1.29×10^{-13} e) 5.34×10^{-12}

9. The average (DC) value of the output voltage of a full-wave bridge rectifier is 14 V. If the diodes are ideal and the load is purely resistive, find the RMS value of the sinusoidal supply voltage (in V rms) at the transformer secondary.

- a) **15.5** b) 13.3 c) 14.4 d) 11.1 e) 12.2

10. A half-wave peak rectifier is fed with a sinusoidal voltage source $v_I = V_p \times \sin(2\pi ft)$ V. The diode is ideal, the capacitance $C = 100 \mu\text{F}$, and the load resistance $R = 10 \text{ k}\Omega$. If the output ripple voltage should not exceed $0.01 \times V_p$, find the minimum supply frequency f (in Hz).

- a) 20 b) 100 c) 50 d) 33.3 e) 25


11. The load resistor in a full-wave bridge rectifier with capacitor filter is 100Ω . The source is sinusoidal, with 8 V rms, and 50 Hz frequency. Find the ripple voltage (in V) if the capacitance value is 2 mF. Assume that each diode drops 0.65 V when conducting.

- a) 0.36 b) 0.50 c) 0.64 d) 0.78 e) 0.92

12. The total voltage across a diode is $v_D = 0.7 + 0.005 \times \sin(\omega t)$ V when the total diode current is $i_D = I_D + 0.05 \times \sin(\omega t)$ mA. The diode has $n = 1.8$ and negligible reverse saturation current. Find the DC value of the diode current (I_D) in mA.

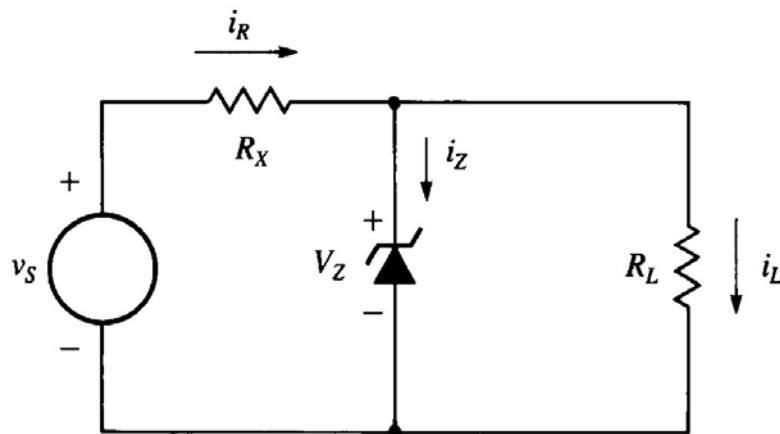- a) 0.35 b) 0.40 c) 0.45 d) 0.50 e) 0.3

The circuit shown below must be designed to provide a stabilized voltage for load currents i_L less than or equal to 9 mA when $v_S = 11$ V. The Zener diode has a nominal Zener voltage of 6.2 V at a test current $I_{ZT} = 20$ mA, a resistance $r_Z = 10 \Omega$, and should conduct a current of at least 1 mA to ensure operation in the breakdown region. Refer to this circuit for questions 13 and 14.



13. What is the maximum value of R_X (in Ω) for which the Zener diode remains in the breakdown region?

- a) 499 b) 599 c) 399 d) 199 e) 299

14. Assume that $R_X = 190 \Omega$. At no-load (R_L is disconnected), find the change in the Zener voltage (in V) if the supply voltage v_S changes by 3 V.


- a) 0.15 b) 0.20 c) 0.25 d) 0.05 e) 0.10
-

15. A circuit consists of a 5 V DC source, a 1 k Ω resistor, and a forward-biased diode. The diode has $I_S = 10^{-12}$ A. Starting with an initial guess for the diode current of 5 mA, the value of the diode current after completing one iteration is found to be 4.1067 mA. Find the value of n for this diode.

- a) 1.8 b) 1.2 c) 1.4 d) 1.6 e) 1.0
-

16. Find the power dissipated in device X (in mW) when R is 1 k Ω . The load line is shown on the plot below.

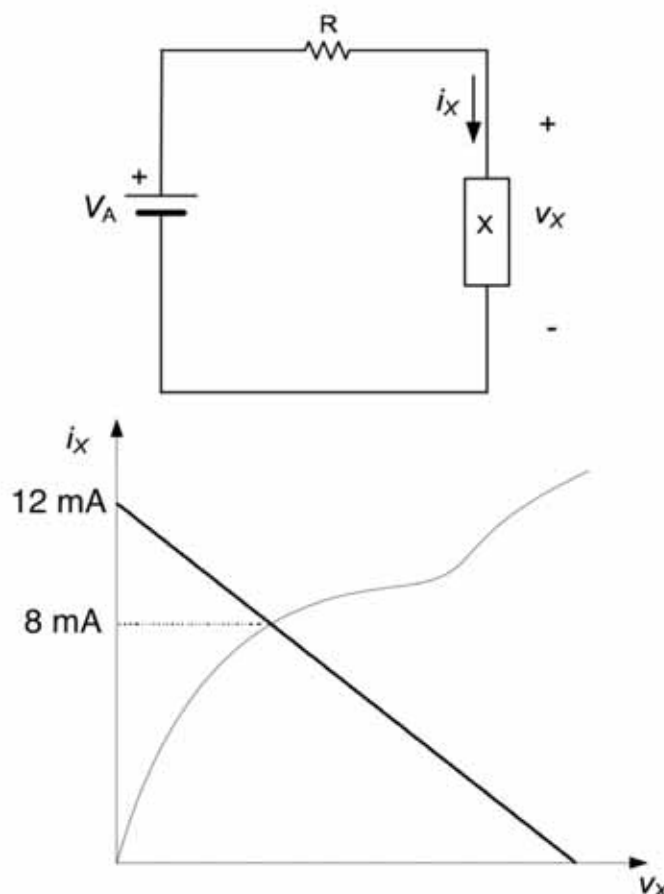- a) 70.4 b) 38.4 c) 48.0 d) 57.6 e) 32.0



17. A piece of semiconductor material is doped with donor atoms with a density $N_D = 1.1 \times 10^{17} \text{ cm}^{-3}$. Estimate the resulting hole density (in cm^{-3}).

- a) 1607 b) 1500 c) 2045 d) 1875 e) 1731


18. Estimate the conductivity (in S/cm) in the previous problem. The electron mobility is $1800 \text{ cm}^2/\text{V}\cdot\text{s}$ and is three times that of holes.

- a) 31.7 b) 34.6 c) 37.4 d) 40.3 e) 43.2

19. The diffusion current density for electrons in a piece of semiconductor is J_1 at $x = 0.1 \text{ cm}$ but becomes $0.85 \times J_1$ at $x = 0.3 \text{ cm}$. The electron density function is given by $n(x) = a + 3x + bx^3$, where x is in cm, and n is in cm^{-3} . Find the value of b (in cm^{-6}).

- a) -1.84 b) -6.43 c) -5.33 d) -4.19 e) -3.03

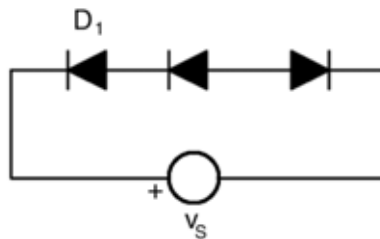20. In the circuit shown below, the three diodes are identical and have $I_S = 10^{-12} \text{ A}$, and $n = 2$. Find the PIV for diode D_1 when $v_S = 8.5 + 10 \sin(\omega t) \text{ V}$.



- a) 9.783 b) 10.083 c) 7.983 d) 8.483 e) 9.233