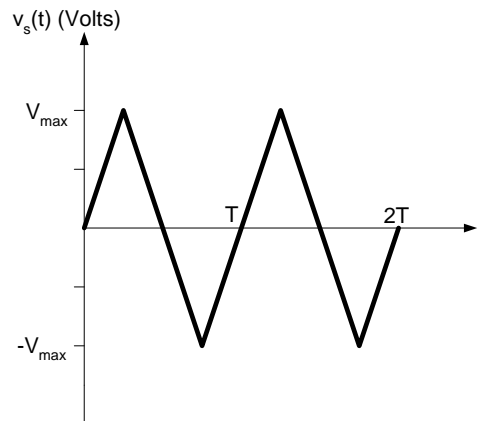


Homework 3

1. Consider the waveform shown below.




The waveform is superimposed on a 9 V DC source, and applied to a circuit consisting of a 1 K Ω resistor and a (conducting) diode. Find the value of V_{\max} for which small-signal analysis is applicable, if the variation in the diode voltage is limited to ± 10 mV. Assume that the diode drops a voltage of 0.7 V when conducting, and that $n = 1.7$. Provide a plot of the *total* diode current, as derived from DC and small-signal analyses.

2. Repeat Problem 2, parts (a) and (b) in Homework 2 using the following model for the conducting diodes: $V_{D0} = 0.68$ V, $r_D = 30$ Ω .

3. Design a Zener voltage regulator to provide a regulated voltage of around 9 V. The available 9.1 V, $\frac{1}{2}$ W Zener is specified to have a drop of 9.1 V at a test current of 16 mA. At this value of current r_Z is specified to be 6.25 Ω . The value of I_{ZK} for the Zener diode is 3 mA. The unregulated supply varies between 12 V and 15 V. The regulator is required to supply a load that dissipates 10 to 300 mW at 9 V.

- a. Find V_{Z0} for the Zener diode.
- b. Calculate the range of values for the resistor R in the circuit.
- c. Using a value of R that is close, to the nearest *standard resistor value*, to the upper range:
 - i. Find the change in load voltage that corresponds to the 12-to-15 V variation in the unregulated supply voltage. Assume that the load current is constant.
 - ii. Find the change in load voltage that corresponds to the full change in load current. Assume that the supply voltage is fixed.
 - iii. What is the maximum current that the Zener diode should be able to conduct? What is the Zener power dissipation under this condition?


I

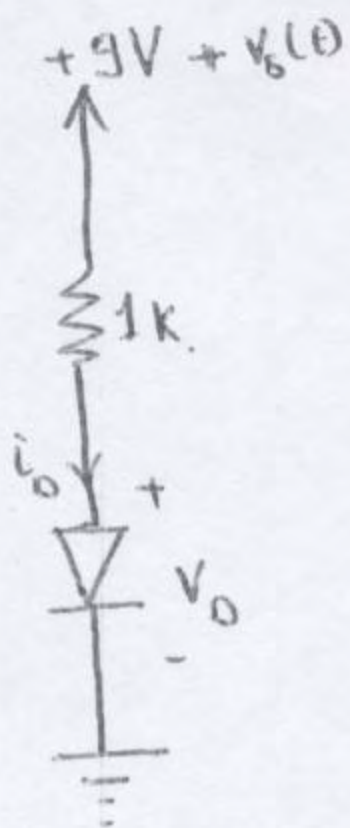

• DC analysis: $9 - R I_D - V_D = 0 \Rightarrow I_D = \frac{9 - 0.7}{1K} = 8.3 \text{ mA}$

• Small signal analysis for $n=1.7$ and $\pm 10 \text{ mV}$
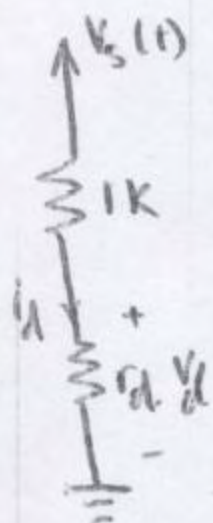
$$r_d = \frac{n V_T}{I_D} = \frac{1.7 (25 \text{ mV})}{8.3 \text{ mA}} = 5.12 \Omega$$



$$V_d = V_s \cdot \frac{r_d}{R + r_d}$$

max. $\Delta V_d = 20 \text{ mV}$

$$\Rightarrow \text{max } \Delta V_s = \Delta V_d \frac{(R + r_d)}{r_d}$$

$$\Rightarrow \text{max } \Delta V_s = 20 \left(\frac{1000 + 5.12}{5.12} \right)$$

$$= 3.926 \text{ V}$$

OR

$$V_{d \text{ peak}} = 10 \text{ mV}$$

$$\Rightarrow V_{s \text{ peak}} = V_{d \text{ peak}} \cdot \frac{R + r_d}{r_d}$$

$$\Rightarrow V_{s \text{ peak}} = 10 \left(\frac{1000 + 5.12}{5.12} \right)$$

$$= 1.963 \text{ V}$$

OR

$$V_{s \text{ max}} = \frac{\Delta V_s \text{ max}}{2} = V_{s \text{ peak}} = 1.963 \text{ V}$$

(1)

$$i_D(t) = I_D + i_d(t)$$

$$I_D = 8.3 \text{ mA}$$


$$i_d(t) = \frac{V_d(t)}{r_d} = \frac{V_d(t)}{5.12} = \frac{V_o(t)}{R+r_d}$$

$$V_o = 0.7 \pm 10 \text{ mV}$$

$$i_D = 8.3 \pm 1.95 \text{ mA}$$


$V_o(t)$ triangular wave $\Rightarrow i_d(t)$ triangular wave.
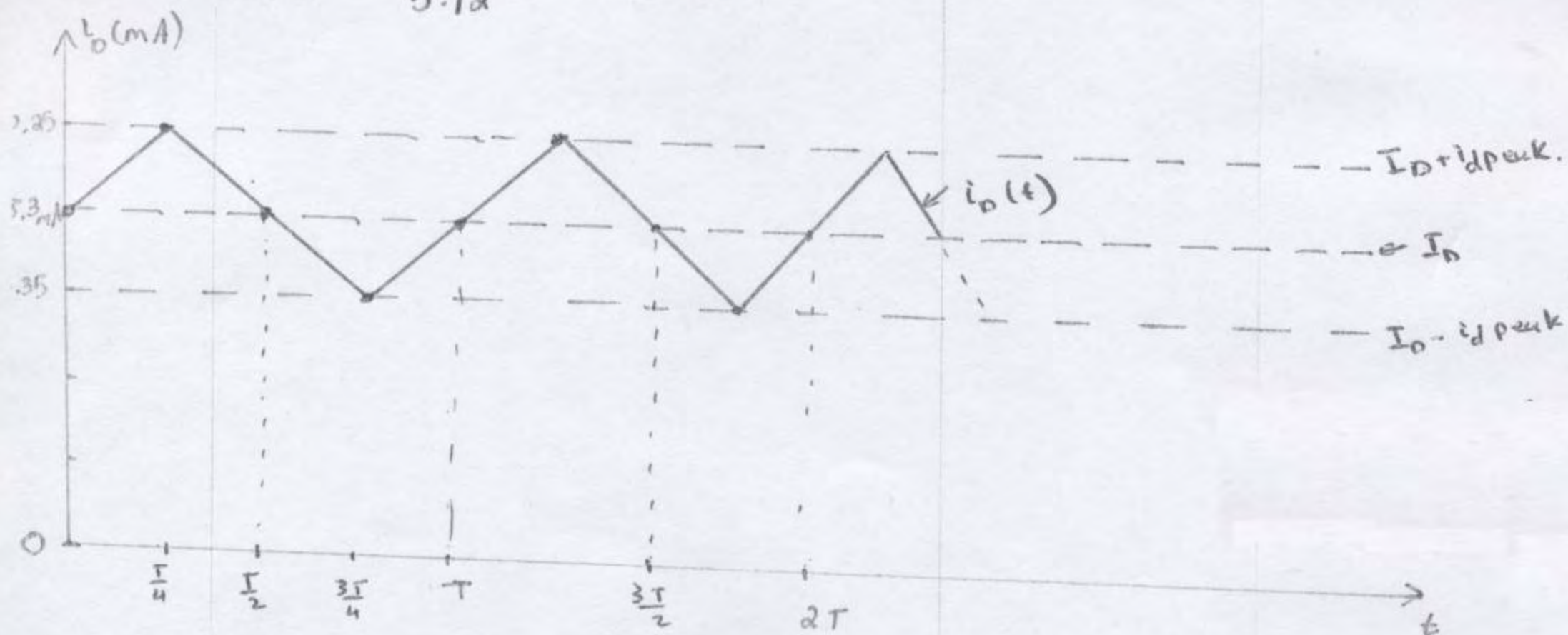
$$i_d(t)_{\text{peak}} = \frac{V_d \text{ peak}}{5.12} = \frac{10 \text{ mV}}{5.12} = 1.95 \text{ mA}$$



II

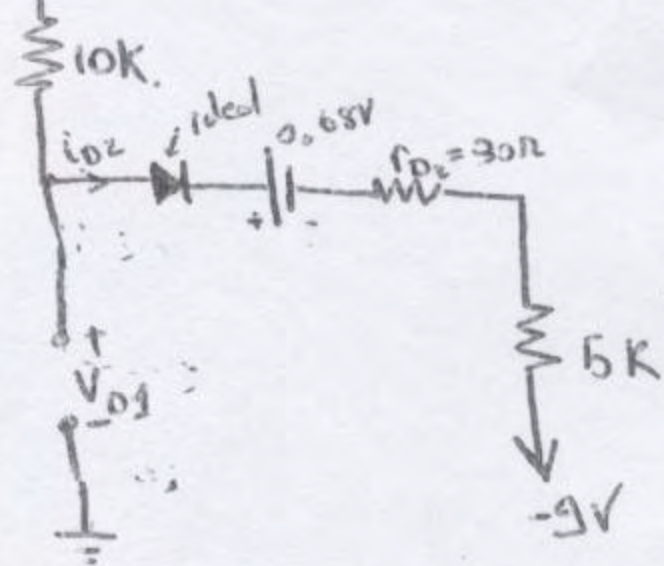a) 6V. Assume D_2 is conducting & D_1 is not conducting



$$\Rightarrow 6 - (-9) = 10(i_{D2}) + 0.68 + 0.03 i_{D2} + 5 i_{D2}$$

$$\Rightarrow i_{D2} = \frac{14.32}{15.03} = 0.953 \text{ mA}$$

$$V_{D2} = 0.68 + 0.03 \times i_{D2} = 0.708 \text{ V}$$

$$i_{D1} = 0 \text{ mA}$$


$$V_{D1} = 0.68 + 0.03 i_{D2} + 5 i_{D2} - 9 = -3.52 \text{ V}$$

D_1 (0 mA, -3.52V)

D_2 (0.953 mA, 0.708V)

(2)

b) Assume D_1 & D_2 conduct.

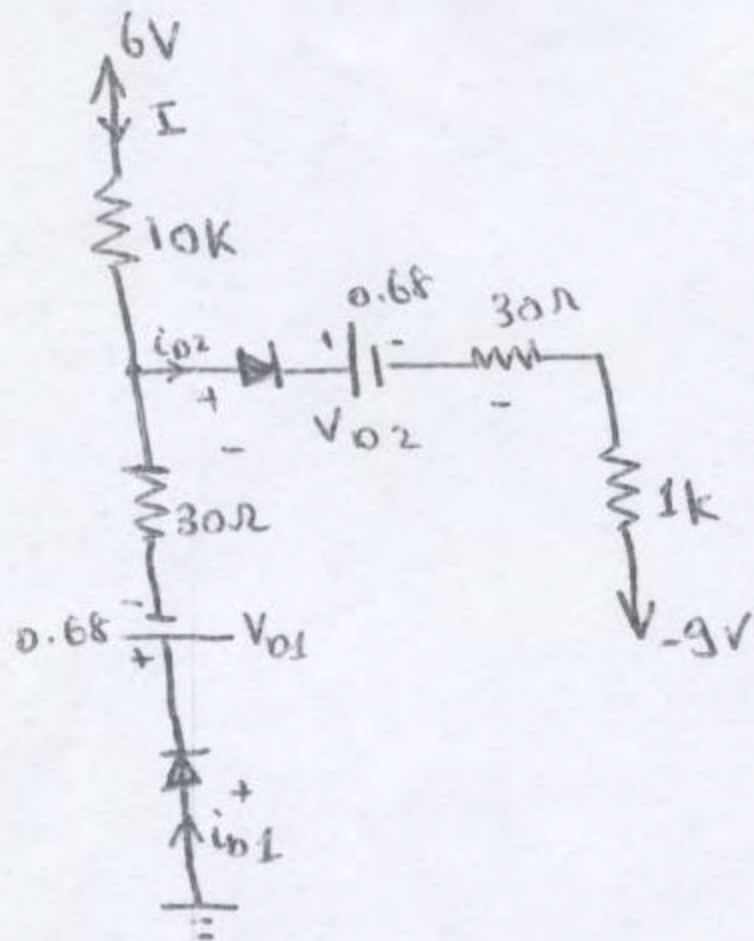

$$\begin{cases} 6 - (-9) = 10I + 0.68 + 0.03 i_{D2} + i_{D2} \\ 6 = 10I - 0.03 i_{D1} - 0.68 \\ I = i_{D2} - i_{D1} \end{cases}$$

$$\Rightarrow 14.32 = 11.03 i_{D2} - 10 i_{D1}$$

$$6.68 = 10 i_{D2} - 10.03 i_{D1}$$

$$\Rightarrow i_{D1} = 6.54 \text{ mA}$$

$$i_{D2} = 7.23 \text{ mA}$$


$$V_{D1} = 0.68 + 0.03 i_{D1} = 0.8762 \text{ V}$$

$$V_{D2} = 0.68 + 0.03 i_{D2} = 0.897 \text{ V}$$

D_1 (6.54 mA, 0.8762 V)

D_2 (7.23 mA, 0.897 V)

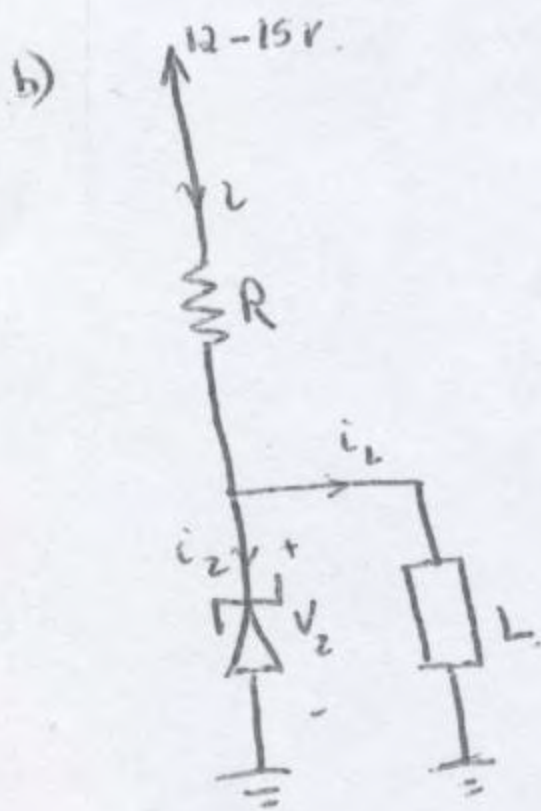III a) $V_z = V_{z0} + r_z I_z \Rightarrow 9.1 = V_{z0} + 6.25 (16 \text{ mA}) \Rightarrow V_{z0} = 9 \text{ V}$



$$* R = \frac{V_{\text{source}} - V_z}{i_z + i_L}$$

• for $P_L = 10 \text{ mW} \Rightarrow i_{L \text{ min}} = \frac{10 \text{ mW}}{9.1} = 1.09 \text{ mA}$

• for $P_L = 300 \text{ mW} \Rightarrow i_{L \text{ max}} = \frac{300 \text{ mW}}{9.1} = 32.96 \text{ mA}$

• $i_{z \text{ min}} = i_{z \text{ R}} = 3 \text{ mA}$

• $i_{z \text{ max}} = i_z \text{ at maximum power} = \frac{\frac{1}{2} \text{ W}}{V_z} = \frac{0.5}{9.1} = 54.9 \text{ mA}$

$$R = \frac{V_{\text{source}} - V_{z0} - r_z i_z}{i_z + i_L}$$

$$R_{\text{max}} = \frac{V_{\text{source max}} - V_{z0} - r_z i_{z \text{ max}}}{i_{z \text{ max}} + i_{L \text{ min}}} = \frac{15 - 9 - 6.25 (54.9 \times 10^{-3})}{54.9 \times 10^{-3} + 1.09 \times 10^{-3}} = 101 \Omega$$

$$R_{\min} = \frac{V_{\text{source min}} - V_{z0} - r_z I_{zK}}{i_{zK} + i_{L\text{max}}} = \frac{12 - 9 - 6.25(3 \times 10^{-3})}{3 \times 10^{-3} + 32.96 \times 10^{-3}} = 82.9 \Omega$$

$$82.9 \Omega \leq R \leq 101 \Omega$$

c) Using $R = 100 \Omega$.

i) $i_L = \text{constant}$

$$V_{\text{source}} - V_{\text{load}} - Ri = 0$$

$$V_{\text{load}} = V_z = 9 + 6.25(i_z)$$

$$V_{\text{source}} - 9 - 6.25i_z - 100i_z - 100i_L = 0$$

$$\Delta V_{\text{source}} - 106.25 \Delta i_z - 100 \Delta i_L = 0$$

$$\Rightarrow \Delta i_z = \frac{\Delta V_{\text{source}}}{106.25} = 28.2 \text{ mA}$$

$$\Delta V_z = \Delta V_{\text{load}} = 6.25 \Delta i_z = 176.5 \text{ mV} \Rightarrow V_{\text{load}} \text{ varies by } \pm 88.2 \text{ mV}$$

ii) $V_{\text{source}} = \text{constant}$

$$V_{\text{source}} - V_{\text{load}} - R(i_z + i_L) = 0$$

$$V_{\text{load}} = 9 + 6.25i_z$$

$$\Delta V_{\text{source}} - \Delta V_{\text{load}} - R \Delta i_z - R \Delta i_L = 0$$

$$\text{and } \Delta V_{\text{load}} = 6.25 \Delta i_z$$

$$\Rightarrow -\Delta V_{\text{load}} - \frac{R}{6.25} \Delta V_{\text{load}} - R \Delta i_L = 0$$

$$\Rightarrow \Delta V_{\text{load}} = \frac{-R}{\left(1 + \frac{R}{6.25}\right)} \Delta i_L = \frac{-100}{\left(1 + \frac{100}{6.25}\right)} (32.96 \text{ mA} - 1.09 \text{ mA}) = 187.5 \text{ mV}$$

$$\Rightarrow V_{\text{load}} \text{ varies by } \pm 93.7 \text{ mV}$$

$$\begin{aligned}
 \text{iii) } V_{\text{load max}} &= 9.1 + \frac{\Delta V_{\text{load}}}{2} \text{ due to } i_L + \frac{\Delta V_{\text{load}}}{2} \text{ due to } V_{\text{source}} \\
 &= 9.1 + 88.2 \times 10^{-3} + 93.7 \times 10^{-3} \\
 &= 9.282 \text{ V}
 \end{aligned}$$

$$i_z = \frac{V_{\text{load}} - V_{z0}}{r_z}$$

$$i_{z\text{max}} = \frac{V_{\text{load max}} - 9}{6.25} = 45.1 \text{ mA}$$

Power dissipation at $i_{z\text{max}}$ = $P = i_{z\text{max}} \cdot V_{z\text{max}} = 45.1 \times 10^{-3} \times 9.282 = 0.41 \text{ W} < 0.5$