

Homework 4

1. Consider the waveform shown in Figure 1.

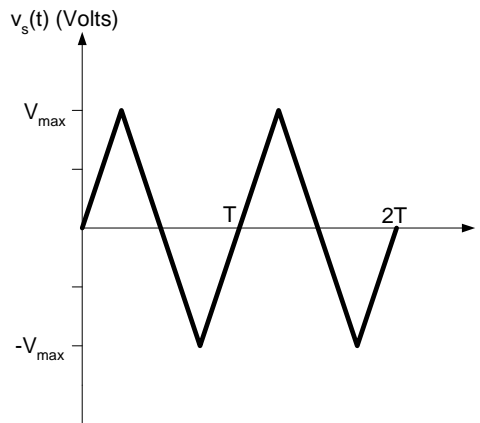


Figure 1


Assume that $V_{\max} = 12 \text{ V}$, and $T = 1/50 \text{ sec}$. This voltage is the input to a half-wave rectifier with a capacitor filter. The diode drops 0.8 V when conducting, and the load is a 1000Ω resistor.

- a. Calculate the value of the capacitor if the ripple voltage is at most 1 V .
- b. For what fraction of the cycle does the diode conduct?
- c. Find the average diode current.
- d. Find the peak diode current.
- e. Find the PIV for the diode.

2. Repeat Problem 1 for the case in which the rectifier is a full-wave rectifier using a 4-diode bridge.

3.

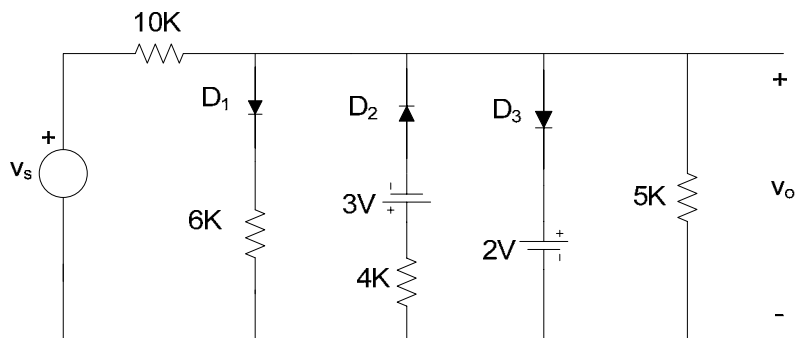a. Find and plot the transfer characteristics of the circuit shown below. Assume that when conducting in the forward direction, diodes drop 1 V .




b. Plot the output voltage when the source v_s is as given in Figure 1, with $V_{\max} = 15 \text{ V}$.

$$1) a) V_r = \frac{V_{max} V_o}{RCf} = \frac{12 - 0.8}{RC} \cdot T \Rightarrow C = \frac{11.2}{50(1)(1000)} = 224 \mu E$$

$V_o = V_{\text{across capacitor}}$.

b)

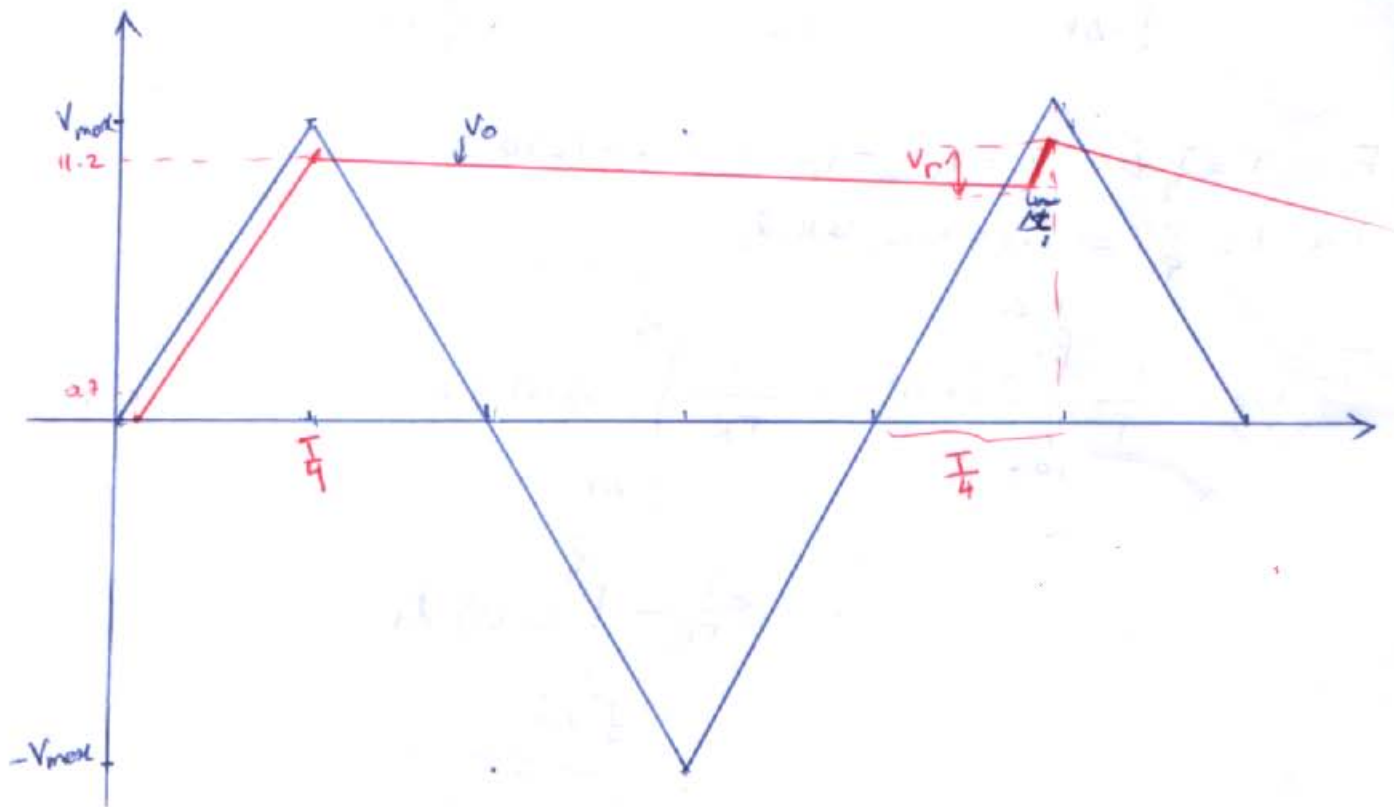

Using the slopes of the graph. with $\Delta t_1 =$ conducting time.

$$\frac{V_{max}}{\frac{T}{4}} = \frac{V_r}{\Delta t_1} \Rightarrow \Delta t_1 = \frac{\frac{T}{4} V_r}{V_{max}} = \frac{1}{12} = 0.0833 \text{ ms}$$

$$\text{fraction of time during which diode conducts} = \frac{\Delta t_1}{T} = \frac{\frac{T}{4} V_r}{T V_{max}} = \frac{1}{48} = 0.02083$$

$$\Rightarrow 2.083\%$$

$$c) i_0(t) = i_c + i_r = \frac{C dv_0}{dt} + \frac{v_0(t)}{R}$$

$$I_{0 \text{ avg}} = \frac{1}{T} \int_0^T i_0(t) dt \quad \text{but } i_0(t) = 0 \text{ for } t \notin [T/4 - \Delta t, T/4]$$

$$= \frac{1}{T} \int_{T/4 - \Delta t}^{T/4} i_0(t) dt = \frac{1}{T} \int_{T/4 - \Delta t}^{T/4} C \frac{dv_0}{dt} dt + \frac{1}{T} \int_{T/4 - \Delta t}^{T/4} \frac{v_0(t)}{R} dt$$

$$\text{For } t = T/4 - \Delta t \Rightarrow v_0 = v_{\text{max}} - v_r = 11.2 - 1 = 10.2$$

$$\text{For } t = T/4 \Rightarrow v_0 = v_{\text{max}} = 11.2$$

$$\therefore I_{0 \text{ avg}} = \frac{1}{T} \int_{10.2}^{11.2} C dv_0(t) + \frac{1}{TR} \int_{T/4 - \Delta t}^{T/4} v_0(t) dt$$

$$= \frac{1}{50} \cdot C (11.2 - 10.2) + \frac{1}{TR} \int_{T/4 - \Delta t}^{T/4} v_0(t) dt$$

Area under the curve.

$$\text{Area under the curve} = (v_{\text{max}} - v_r) \Delta t + \frac{v_r \Delta t}{2} = \left(v_{\text{max}} - \frac{v_r}{2} \right) \Delta t$$

$$\therefore I_{0 \text{ avg}} = 50 (224 \mu\text{F}) (1) + \frac{50}{1000} \left(v_{\text{max}} - \frac{v_r}{2} \right) \Delta t$$

$$= 11.2 \text{ mA} + \frac{50}{1000} \left(11.2 - \frac{1}{2} \right) 0.4167 \text{ ms}$$

$$= 11.423 \text{ mA}$$

$$d) \text{ Since } I_{D \text{ avg}} = \frac{\text{Area under the curve}}{\text{period}} = \frac{I_{D \text{ peak}} \times \text{conducting time}}{2} \cdot \frac{1}{T}$$




$$\Rightarrow I_{D \text{ peak}} = \frac{I_{D \text{ avg}} \cdot 2T}{\Delta t} = \frac{11.423 \times 2 \times 50}{0.4167 \text{ms}} = 1.0965 \text{A}$$

c) PIV :

$$V_s = V_D + V_o \Rightarrow V_D = V_s - V_o$$

$$\text{PIV} = |-V_{s \text{ max}} - V_{o \text{ max}}| = |-12 - 11.21| = 23.21 \text{V}$$

2)

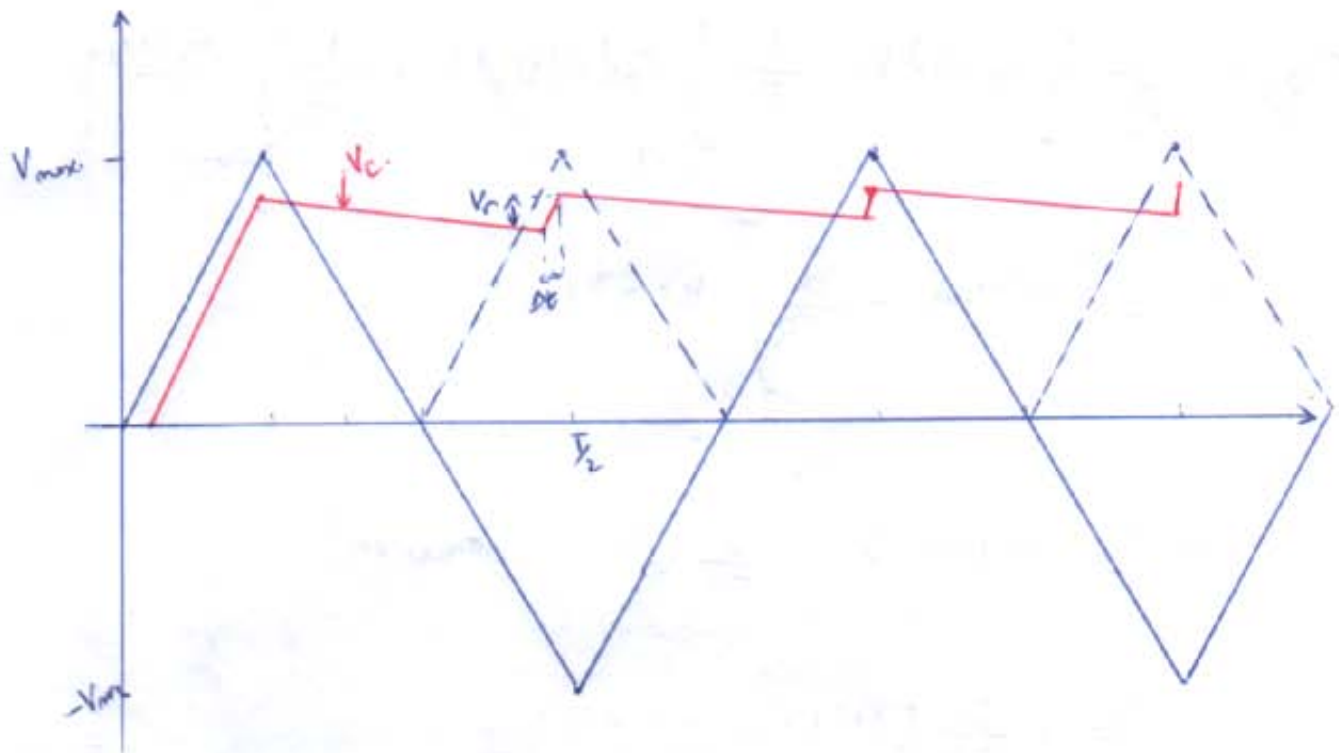

$$a) V_{c \text{ max}} = V_{s \text{ max}} - V_{o1} - V_{o2} \quad (\text{by KVL})$$

$$= 12 - 1.6 = 10.4 \text{V}$$

$$V_r = \frac{V_{c \text{ max}}}{RCf'} \quad ; f' = 2f \text{ since the period is divided by 2. It needs less time}$$

$$\Rightarrow C = \frac{V_{c \text{ max}}}{V_r R \frac{2}{T}} = \frac{10.4}{1(1000) 2 \times 50} = 104 \mu\text{F}$$

(3)

$$b) \frac{V_{smax}}{\frac{T}{4}} = \frac{V_r}{\Delta t} \Rightarrow \Delta t = \frac{1}{12} \times \frac{T}{4} = 0.4167 \text{ ms.}$$

Full wave rectifier \Rightarrow diodes conduct twice during period. T .

$$\Rightarrow \text{fraction of time during which diodes conduct} = \frac{2\Delta t}{T} = 0.0467 \\ \Rightarrow 4.16\%$$

$$c) i_o = i_c + i_R.$$

$$= C \frac{dV_o(t)}{dt} + \frac{V_o(t)}{R}$$

$$I_{Davg} = \frac{1}{\frac{T}{2}} \int_0^{\frac{T}{2}} i_o(t) dt = \frac{1}{\frac{T}{2}} \int_{\frac{T}{2}-\Delta t}^{\frac{T}{2}} C \frac{dV_o(t)}{dt} dt + \frac{1}{\frac{T}{2}} \int_{\frac{T}{2}-\Delta t}^{\frac{T}{2}} \frac{V_o(t)}{R} dt$$

$$= \frac{2}{T} \int_{9.4}^{10.4} C dV_o(t) + \frac{2}{TR} \int_{\frac{T}{2}-\Delta t}^{\frac{T}{2}} V_o(t) dt$$

$$= \frac{2C}{T} (10.4 - 9.4) + \frac{2}{TR} (\text{Area under the curve})$$

$$= \frac{2C}{T} + \frac{2}{TR} (\Delta t) (V_{max} - V_r + \frac{V_r}{2})$$

$$= \frac{2C}{T} + \frac{2}{TR} \Delta t (V_{max} - \frac{V_r}{2})$$

$$= 100 (104 \times 10^{-6}) + \frac{100}{1000} \cdot (0.4167 \times 10^{-3}) (10.4 - \frac{1}{2})$$

$$= 10.8 \text{ mA.}$$

d) $I_{Oavg} = \frac{\text{Area under the curve}}{\text{period}} = \frac{2I_{Dpeak} \times \Delta t}{2T}$

$\Rightarrow I_{Dpeak} = \frac{I_{Oavg} T}{\Delta t} = 518.36 \text{ mA}$


e) PIVs

$V_c + V_{D2} + V_{D3} = V_s$


$\Rightarrow V_D = \frac{V_s - V_c}{2}$

$PIV = \left| \frac{-V_{smax} - V_{cmex}}{2} \right| = \left| \frac{-12 - 10.4}{2} \right| = 11.2 \text{ V}$

3)

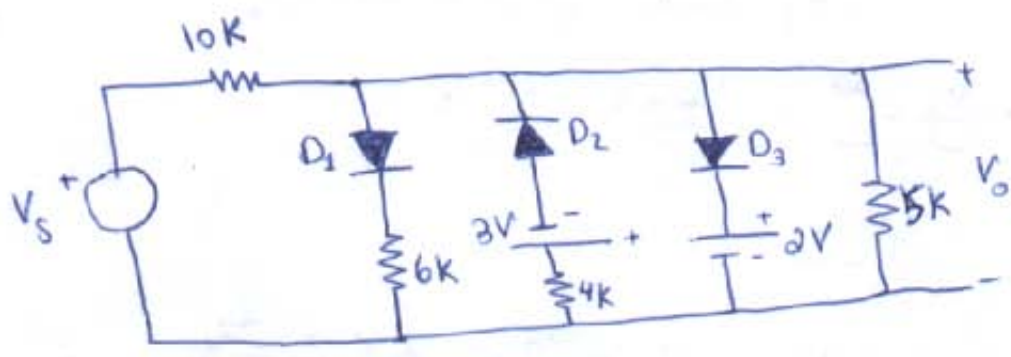

V_{th}

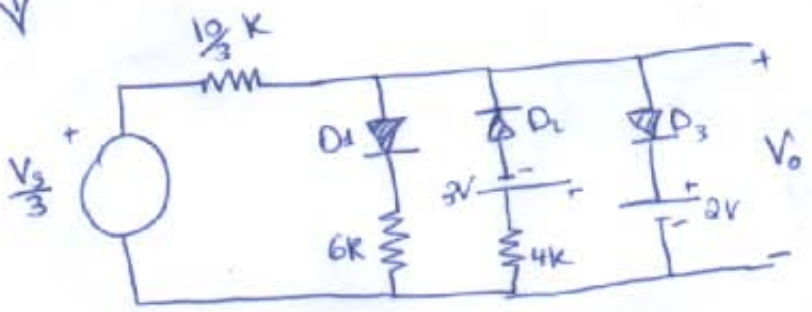

There are 8 possible cases but some are impossible for all values of V_s

	D_1	D_2	D_3
1	ON	ON	ON
2	ON	ON	OFF
3	ON	OFF	ON
4	OFF	ON	OFF
5	ON	OFF	OFF
6	OFF	ON	OFF
7	OFF	OFF	ON
8	OFF	OFF	OFF

(5)

Case 1: D1: ON ; D2: ON ; D3: ON.

$$\text{KVL} \Rightarrow V_{D1} + 6I_1 = V_{D3} + 2 \Rightarrow I_1 = \frac{1}{3} \text{ mA.}$$

$$V_{D1} + 6I_1 = -V_{D2} - 3V - 4I_2 \Rightarrow 7 = -4I_2 \Rightarrow I_2 < 0 \Rightarrow D2 \text{ off.}$$

∴ This case is impossible.

Case 2: D1: ON ; D2: ON ; D3: OFF

$$V_{D1} + 6I_1 = -V_{D2} - 3V - 4I_2 \Rightarrow 6I_1 + 4I_2 = -5$$

$$\Rightarrow I_1 + I_2 < 0 \Rightarrow I_1 < 0 \text{ or } I_2 < 0 \Rightarrow D1 \text{ or } D2 \text{ is off.}$$

∴ This case is impossible.

Case 3: D1: ON ; D2: OFF ; D3: ON.

$$V_{D1} + 6I_1 = V_{D3} + 2 \Rightarrow I_1 = \frac{1}{3} \text{ mA. ; } V_0 = V_{D3} + 2 = 3V.$$

$$I_{\text{in } \frac{10}{3} \text{ k}} = I = \frac{V_s - 10}{\frac{10}{3}} = \frac{V_s - 3}{\frac{10}{3}} = \frac{V_s - 9}{10}$$

$$I_3 = I - I_1 = \frac{V_s - 9}{10} - \frac{1}{3}$$

$$I_3 > 0 \Rightarrow \frac{V_s - 9}{10} > \frac{1}{3} \Rightarrow V_s > \frac{10}{3} + 9 \Rightarrow V_s > \frac{37}{3}$$

$$V_{D2} + 3 + V_{D3} + 2 = 0 \Rightarrow V_{D2} = -6 < 0 \Rightarrow \text{correct.}$$

∴ D1: ON ; D2: OFF ; D3: ON.

$$\text{For } V_s > \frac{37}{3} \text{ V ; } V_0 = 3V.$$

Case 4: D1: OFF ; D2: ON ; D3: ON

$$V_{D2} + 3 + 4I_2 = -V_{D3} - 2 \Rightarrow I_2 = \frac{-7}{4} < 0 \Rightarrow D2: \text{OFF}$$

∴ This case is impossible.

Case 5: D1: ON; D2: OFF; D3: OFF

$$\circ \circ \frac{V_3}{3} = \frac{10}{3} K I_1 + V_{01} + 6 I_1 \Rightarrow \frac{V_3}{3} - 1 = \left(\frac{10}{3} + 6\right) I_1 \Rightarrow I_1 = \frac{V_3}{28} - \frac{3}{28}$$

$$I_1 > 0 \Rightarrow \frac{V_3}{3} - 1 > 0 \Rightarrow V_3 > 3$$

$$V_0 = V_{01} + 6 I_1 = 1 + 6 \left(\frac{V_3}{28} - \frac{3}{28}\right) = 1 + \frac{6}{28} V_3 - \frac{18}{28} = \frac{6}{28} V_3 + \frac{10}{28} = \frac{3}{14} V_3 + \frac{5}{14}$$

$$\frac{V_3}{3} = \frac{10}{3} I_1 - V_{02} - 3 \Rightarrow V_{02} = \frac{10}{3} I_1 - \frac{V_3}{3} - 3$$

$$\Rightarrow V_{02} = \frac{10}{3} \left(\frac{1}{28} V_3 - \frac{3}{28}\right) - \frac{V_3}{3} - 3 = \frac{5}{3 \times 14} V_3 - \frac{5}{14} - \frac{V_3}{3} - 3 = -\frac{3V_3}{14} - \frac{47}{14}$$

$$V_{02} < 1 \Rightarrow -\frac{3V_3}{14} - \frac{47}{14} < 1 \Rightarrow -\frac{3V_3}{14} < \frac{61}{14} \Rightarrow V_3 > -\frac{61}{3}$$

which is true $V_3 > 3$

$$V_{03} = -V_{02} - 3 - 2 = \frac{3V_3}{14} + \frac{47}{14} - 5 = \frac{3V_3}{14} + \frac{23}{14}$$

$$V_{03} < 1 \Rightarrow \frac{3V_3}{14} + \frac{23}{14} < 1 \Rightarrow \frac{3V_3}{14} < \frac{37}{14} \Rightarrow V_3 < \frac{37}{3}$$

$\circ \circ$ D1: ON; D2: OFF; D3: OFF

$$3 < V_3 < \frac{37}{3}; \quad V_0 = \frac{3V_3}{14} + \frac{5}{14}$$

Case 6: D1: OFF; D2: ON; D3: OFF

$$\frac{V_3}{3} = \frac{10}{3} I_2 - V_{02} - 3 - 4(I_2) \Rightarrow \frac{V_3}{3} = \left(-\frac{10}{3} - 4\right) I_2 - 4$$

$$\Rightarrow I_2 = \frac{1}{-\left(\frac{10}{3} + 4\right)} \cdot \left(\frac{V_3}{3} + 4\right)$$

$$I_2 > 0 \Rightarrow -\left(\frac{V_3}{3} + 4\right) > 0 \Rightarrow -\frac{V_3}{3} > -4 \Rightarrow V_3 < -12V$$

$$V_{01} = \frac{10}{3} I_2 + \frac{V_3}{3} = \frac{-10}{\frac{10}{3} + 4} \left(\frac{V_3}{3} + 4\right) \frac{V_3}{3} - \frac{5}{11} \left(\frac{V_3}{3} + 4\right) + \frac{V_3}{3}$$

$$= \frac{2}{11} V_3 - \frac{20}{11}$$

$$V_{01} < 1 \Rightarrow 2V_3 - 20 < 11 \Rightarrow V_3 < \frac{31}{2} \text{ but } V_3 < -12V$$

$$V_{03} = V_{01} - 2 = \frac{2}{11} V_3 - \frac{42}{11}$$

$$V_{03} < 1 \Rightarrow V_3 < \frac{53}{2} \text{ but } V_3 < -12$$

(7)

$$\circ \circ \quad V_o = \frac{10}{3} I_2 + \frac{V_s}{3} = \frac{2}{11} V_s - \frac{20}{11}$$

$\circ \circ$ D1: OFF; D2: ON; D3: OFF.

$$V_s < -12V; \quad V_o = \frac{2}{11} V_s - \frac{20}{11}$$

Case 7: D1: OFF; D2: OFF; D3: ON

$$V_{D1} + 6(0) = V_{D3} + 2 = 3$$

$$\Rightarrow V_{D1} > 1 \Rightarrow D1 \text{ ON.}$$

$\circ \circ$ This case is impossible.

Case 8: All are off.

$$\frac{V_s}{3} = V_{D3} + 2V \Rightarrow V_{D3} = \frac{V_s}{3} - 2; \quad V_{D3} < 1 \Rightarrow V_s < 9$$

$$\frac{V_s}{3} = V_{D1} + 6(0) \Rightarrow V_{D1} < 1 \Rightarrow V_s < 3$$

$$\frac{V_s}{3} = -V_{D2} - 3 \Rightarrow V_{D2} < 1 \Rightarrow \frac{V_s}{3} + 3 > 1 \Rightarrow V_s > -12$$

$$V_o = \frac{V_s}{3}$$

$\circ \circ$ All Diode off


$$\text{for } -12 \leq V_s \leq 3; \quad V_o = \frac{V_s}{3}$$

$$\circ \circ \text{ For } V_s \leq -12V; \quad V_o = \frac{2}{11} V_s - \frac{20}{11}$$


$$-12 \leq V_s \leq 3V; \quad V_o = \frac{V_s}{3}$$

$$3V \leq V_s \leq \frac{37}{3}V; \quad V_o = \frac{3}{14} V_s + \frac{5}{14}$$
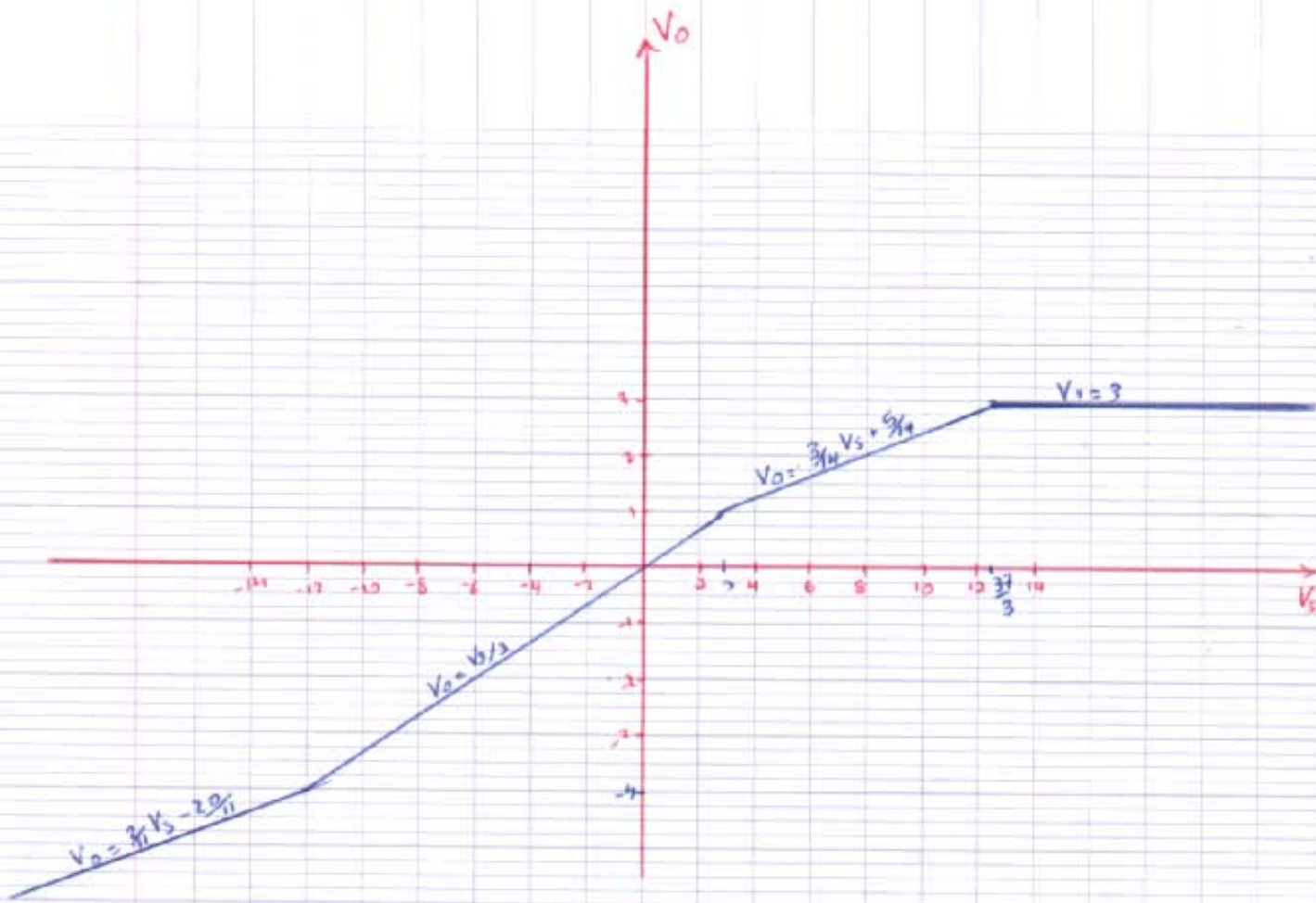
$$V_s \geq \frac{37}{3}V; \quad V_o = 3V.$$



b)

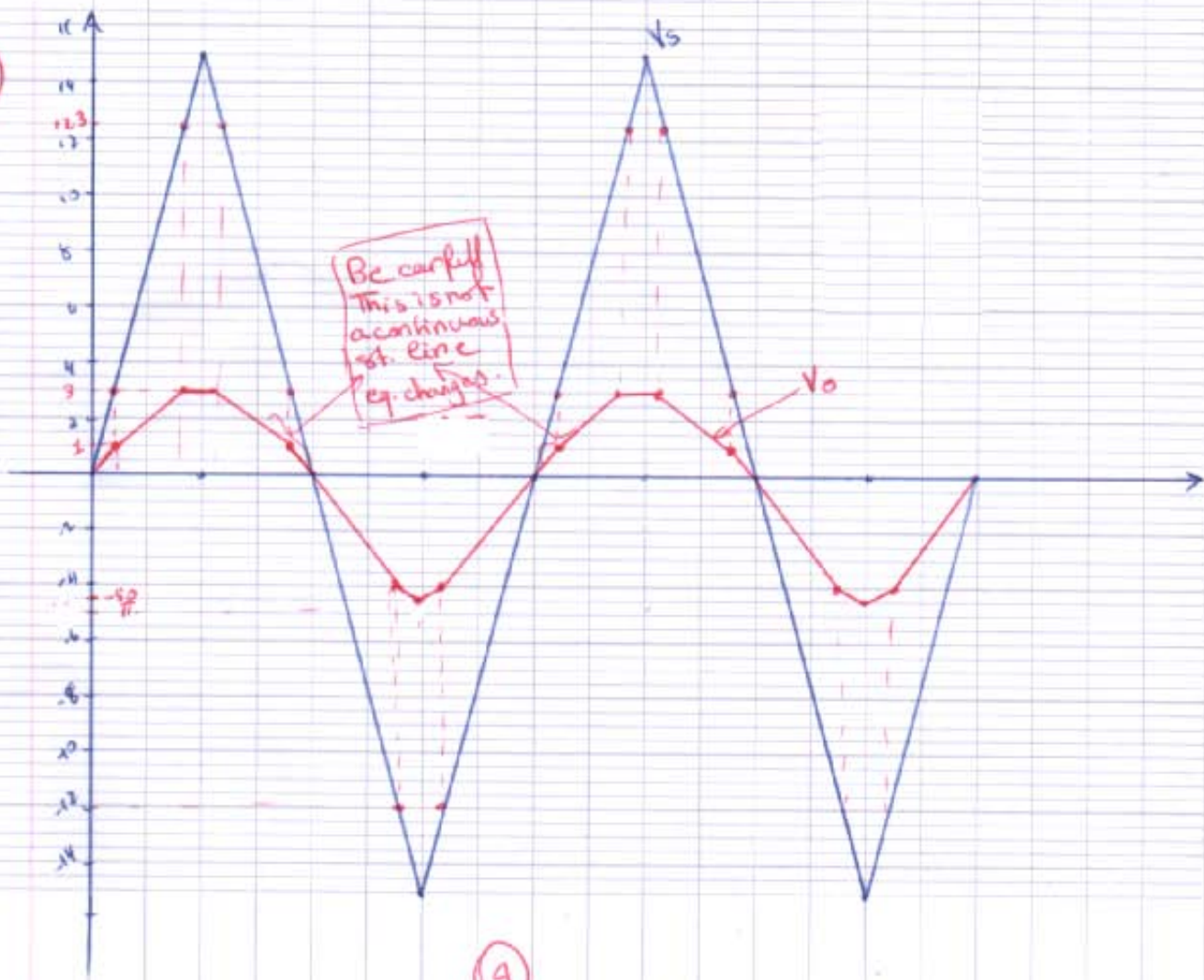

(9)