

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics

Fall 2007 – 2008

Homework 6


Problem 1.

- a) The mobility of electrons in the channel of an NMOS device is $1100 \text{ cm}^2/\text{V}\cdot\text{sec}$. Find the transconductance parameter k'_n for this MOSFET if its oxide thickness is 40 nm . The doping level in the channel is $N_A = 10^{16} \text{ cm}^{-3}$. The relative permittivity of the oxide (SiO_2) is 3.9 , and that of Silicon is 11.7 .
- b) The threshold voltage V_{t0} for this NMOS transistor is 0.8 V . Find the required dimensions of the gate of the NMOS transistor (W and L) to get a drain current of 0.1 mA when the MOSFET is biased at ($V_{GS} = 2.5 \text{ V}$, $V_{DS} = 2.5 \text{ V}$, $V_{BS} = 2 \text{ V}$). The minimum dimension is $0.25 \mu\text{m}$.
- c) The drain current of the NMOS transistor is I_{D1} at ($V_{GS} = 2.5 \text{ V}$, $V_{DS} = 2.5 \text{ V}$). When V_{DS} becomes 2 V , the current decreases by 10% to $0.9 I_{D1}$. Find the channel length modulation parameter λ of this transistor.

Problem 2.

The circuit shown below is a voltage-controlled attenuator. Assume $V_{GG} = 2.5 \text{ V}$, $R = 3.3 \text{ K}\Omega$, and for the MOSFET: $V_t = 0.8 \text{ V}$, $k'(W/L) = 0.12 \text{ mA/V}^2$.

- a) For what range of output voltages does the MOSFET behave as a (voltage-controlled) resistor? Assume that the square term is negligible when it is less than 5% of the linear term in the MOSFET current equation.
- b) Find the value of V_{OV} for the MOSFET and the value of its resistance r_{DS} when v_o satisfies the condition of part (a).
- c) Plot the attenuation factor (v_o/v_s) as a function of V_{GG} .

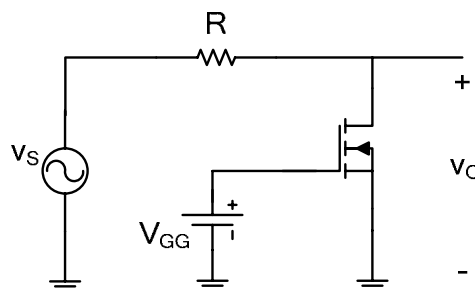


Problem 3.

Two identical enhancement MOSFETs with $k'_n(W/L) = 200 \mu\text{A}/\text{V}^2$, $V_t = 0.75 \text{ V}$, and $\lambda = 0.12 \text{ V}^{-1}$ are connected as shown below. The MOSFET drain current is 0.25 mA .

Assume that $V_{DD} = 5 \text{ V}$.

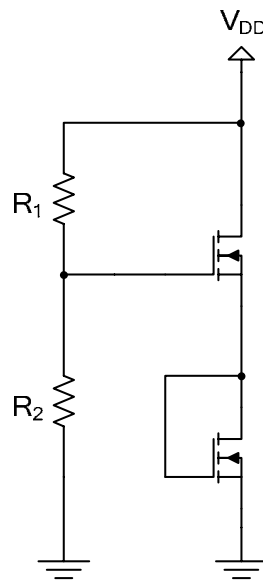- Find the value of V_{GS} for the lower MOSFET. In what region is this MOSFET operating?
- Find the voltage at the gate of the upper MOSFET. In what region is this MOSFET operating?
- Find the resistance R_1 when $R_2 = 820 \text{ K}\Omega$.



$$a) K'_n = \mu_n C_{ox} = \mu_n \frac{\epsilon_{ox}}{t_{ox}} = 1100 \times 10^{-4} \cdot \frac{3.9 \times 8.85 \times 10^{-12}}{40 \times 10^{-9}} = 34.9 \mu A/V^2$$

$$b) V_t = V_{t0} + \gamma (\sqrt{2\phi_F + V_{BS}} - \sqrt{2\phi_F})$$

$$\gamma = \frac{\sqrt{2q\epsilon_s N_A}}{C_{ox}} = \frac{\sqrt{2 \times 1.6 \times 10^{-19} \times 11.7 \times 8.85 \times 10^{-12} \times 10^{16} \times 10^6}}{3.9 \times 8.85 \times 10^{-12} / 40 \times 10^{-9}} = 0.667 V^{1/2}$$

$$V_t = 0.8 + 0.667 (\sqrt{0.6 + 2} - \sqrt{0.6}) = 1.36V$$

$$V_{GS} = 2.5 > V_t \Rightarrow \text{MOSFET is ON.}$$

$$V_{GS} - V_t = 1.14 \quad ; \quad V_{DS} > V_{GS} - V_t \Rightarrow \text{MOSFET is in saturation.}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$\frac{W}{L} = \frac{2I_D}{K'_n (V_{GS} - V_t)^2} = \frac{2 \times 0.1 \times 10^{-3}}{34.9 \times 10^{-6} (1.14)^2} = 1.62$$

$W > L$ and minimum dimension is $0.25 \mu m$

$$\therefore L_{\min} = 0.25 \mu m \quad \text{with} \quad \frac{W}{L} = 1.62.$$

$$W_{\min} = 0.405 \mu m$$

$$c) V_{DS2} = 2V > V_{GS} - V_t \Rightarrow \text{The MOSFET is still in saturation.}$$

$$I_{D1} = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS1})$$

$$I_{D2} = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS2})$$

$$\frac{I_{D2}}{I_{D1}} = \frac{0.9 I_{D1}}{I_{D1}} = \frac{\frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS2})}{\frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS1})} = \frac{1 + 2\lambda}{1 + 2.5\lambda} = 0.9$$

$$\Rightarrow 1 + 2\lambda = 0.9 + 2.25\lambda \Rightarrow 0.25\lambda = 0.1 \Rightarrow \lambda = 0.4 V^{-1}$$

$$\lambda = 0.4 V^{-1}$$

$$a) V_{DS} = V_o ; V_{GS} = V_{GG} = 2.5$$

For MOSFET to act as a voltage controlled resistor, It must be in the linear region and for small values of V_{DS}

$$\therefore V_{DS} < V_{GS} - V_t \Rightarrow V_{DS} < 2.5 - 0.8 \Rightarrow V_{DS} < 1.7V$$

$$I_D = \frac{1}{2} K_n' \frac{W}{L} (2(V_{GS} - V_t)V_{DS} - V_{DS}^2)$$

If V_{DS} is small enough \Rightarrow we can neglect V_{DS}^2 and $I_D = K_n' \frac{W}{L} (V_{GS} - V_t)V_{DS}$

Square term $< 5\%$ linear term.

$$V_{DS}^2 < 0.05 \times 2(V_{GS} - V_t)V_{DS}$$

$$\Rightarrow V_{DS}^2 < 0.17V_{DS} \Rightarrow V_{DS}(V_{DS} - 0.17) < 0.$$

$$\Rightarrow 0 < V_{DS} < 0.17 < 1.7V.$$

\therefore Range of V_o for the MOSFET to act as a resistor:

$$0 < V_o < 0.17V$$

$$b) V_{OV} = V_{GS} - V_t = 1.7V$$

$$r_{DS} = \frac{V_{DS}}{I_D} = \frac{1}{K_n' \frac{W}{L} V_{OV}} = \frac{1}{0.004m} = 4.9 K\Omega.$$

c) For $V_{GS} < V_t \Rightarrow V_{GG} < 0.8 \Rightarrow$ Mosfet is off

$$\Rightarrow V_o = V_s \Rightarrow \frac{V_o}{V_s} = 1$$

Note: In the saturation region, I_D becomes independent of $V_{DS} \Rightarrow V_s = R I_D + V_o$
 $\Rightarrow \frac{V_o}{V_s}$ will be a function of V_s .

In the linear region where $V_{DS}^2 < 0.05 \times 2(V_{GS} - V_t)V_{DS}$

\Rightarrow For: $0 < V_o < 0.1(V_{GG} - 0.8)$ The Mosfet acts as a resistor.

$$\text{with } r_{DS} = \frac{1}{K_n' \frac{W}{L} V_{OV}} = \frac{25K}{3(V_{GG} - 0.8)}$$

by voltage division: $V_o = \frac{r_{DS}}{r_{DS} + R} V_s$


⇒ Attenuation Factor $\frac{V_o}{V_s} = \frac{r_{DS}}{r_{DS} + R} = \frac{25}{\frac{25}{3(V_{CC} - 0.8)} + 3.3} = \frac{1}{1 + \frac{9.9}{25}(V_{CC} - 0.8)}$

$\frac{V_o}{V_s} = \frac{1}{0.6832 + 0.396V_{CC}}$

As long as $V_{CC} > 0.8$ and $0 < V_o < 0.1(V_{CC} - 0.8)$

$\frac{V_o}{V_s} = \frac{25}{17.08 + 9.9V_{CC}}$

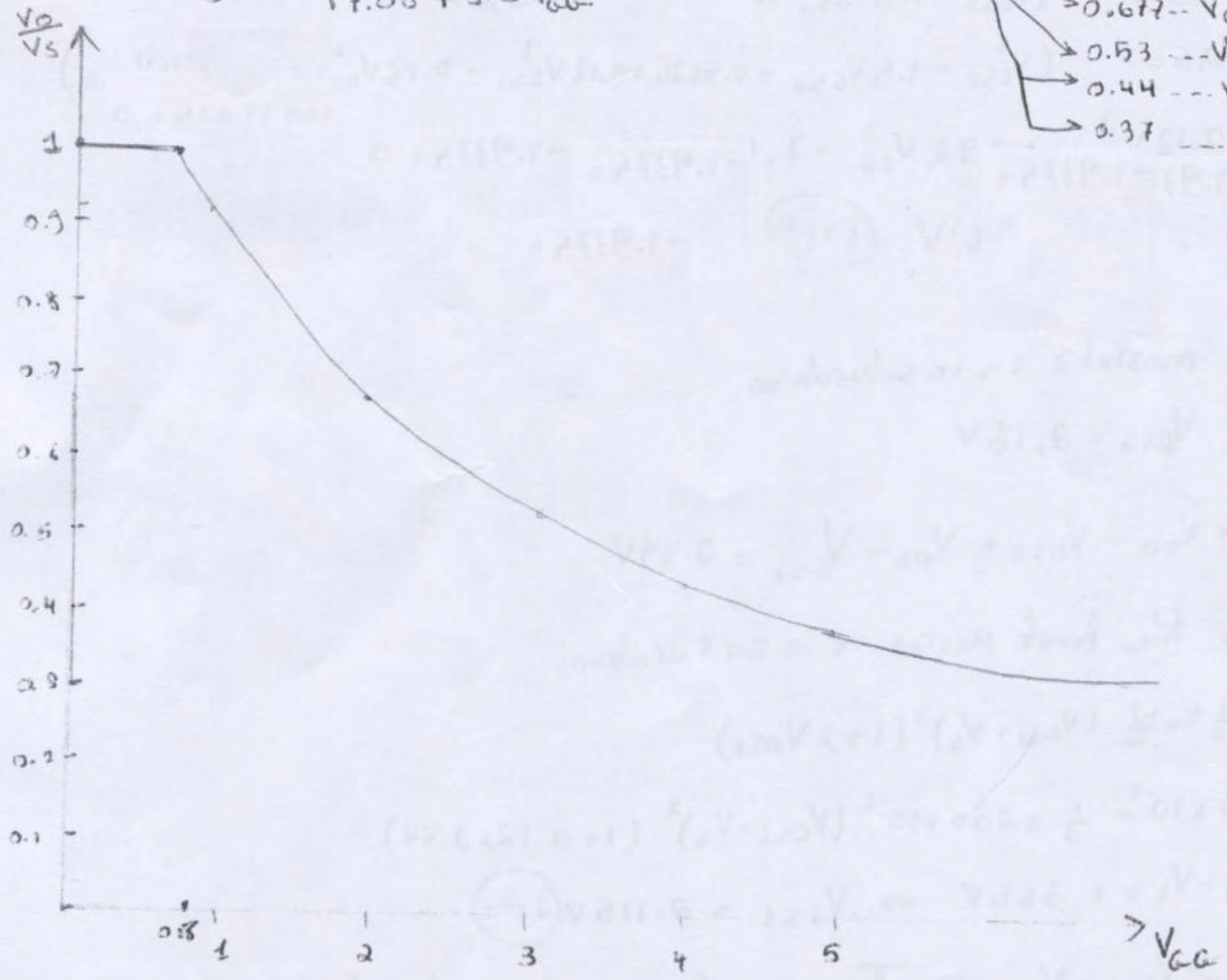- ↳ $V_{CC} = 0.8$
- ↳ $0.926 - V_{CC} = 1$
- ↳ $0.677 - V_{CC} = 2$
- ↳ $0.53 - V_{CC} = 3$
- ↳ $0.44 - V_{CC} = 4$
- ↳ $0.37 - V_{CC} = 5$



III

$$a) V_{DD} = V_{DS1} + V_{DS2}, \quad I_{D1} = I_{D2} = \text{mA since } I_C = 0$$

$$V_{D2} = V_{S1} = V_{G2}$$

$$\Rightarrow V_{DS2} = V_{GS2}$$

$$\Rightarrow V_{DS2} > V_{GS2} - V_t \Rightarrow \text{MOSFET 2 is in saturation}$$

$$\Rightarrow I_{D2} = \frac{1}{2} K_n \frac{W}{L} (V_{GS2} - V_t)^2 (1 + \lambda V_{DS2})$$

$$\Rightarrow 0.25 \times 10^{-3} = \frac{1}{2} \times 200 \times 10^{-6} (V_{GS2} - 0.75)^2 (1 + 0.12 V_{GS2})$$

$$\Rightarrow 2.5 = (V_{GS2}^2 - 1.5 V_{GS2} + 0.5625) (1 + 0.12 V_{GS2})$$

$$\Rightarrow 2.5 = (V_{GS2}^2 - 1.5 V_{GS2} + 0.5625 + 0.12 V_{GS2}^3 - 0.18 V_{GS2}^2 + 0.0675 V_{GS2})$$

$$\Rightarrow 0.12 V_{GS2}^3 + 0.82 V_{GS2}^2 - 1.4325 V_{GS2} - 1.9375 = 0$$

$$\Rightarrow V_{GS2} = 2.16 \text{ V}$$

∴ MOSFET 2 is in saturation

$$V_{GS2} = 2.16 \text{ V}$$

$$b) V_{DS1} = V_{DD} - V_{DS2} = V_{DD} - V_{GS2} = 2.84 \text{ V}$$

Assume the first MOSFET is in saturation:

$$\Rightarrow I_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1})$$

$$\Rightarrow 0.25 \times 10^{-3} = \frac{1}{2} \times 200 \times 10^{-6} (V_{GS1} - V_t)^2 (1 + 0.12 \times 2.84)$$

$$\Rightarrow V_{GS1} - V_t = 1.365 \text{ V} \Rightarrow V_{GS1} = 2.115 \text{ V}$$

$V_{DS1} > V_{GS1} - V_t \Rightarrow$ The assumption is correct and the MOSFET is in Saturation

$$\therefore V_{S1} = V_{D2} = V_{G2} = V_{GS2} = 2.16$$

$$\Rightarrow V_{G1} - V_{S1} = 2.115 \Rightarrow V_{G1} = 4.275 \text{ V}$$

\Rightarrow Voltage at the gate of the first MOSFET is 4.275 V

and it is in saturation

$$c) V_{G2} = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{820}{R_1 + 820} \times 5$$

$$\Rightarrow R_1 + 820 = \frac{820 \times 5}{V_{G2}} \Rightarrow R_1 = 139 \text{ K}\Omega$$