

Home work 7:

a) Under DC conditions: (Capacitors are open circuit)
The MOSFET is used as an Amplifier, so it is biased to operate in the saturation region.

$$I_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$\Rightarrow 0.25 \times 10^{-3} = \frac{1}{2} \times 10^{-3} V_{OV}^2 (1 + 0.025 \times 2.5)$$

$$\Rightarrow 0.5 = V_{OV}^2 (1.0625) \Rightarrow V_{OV} = 0.686V$$

$$r_o = \frac{V_{DS} + \frac{1}{\lambda}}{I_D} = \frac{2.5 + \frac{1}{0.025}}{0.25 \times 10^{-3}} = \frac{42.5}{0.25 \times 10^{-3}} = 170 K\Omega$$

$$-A_v = -\frac{\partial I_D}{\partial V_{OV}} (R_D \parallel R_L \parallel r_o)$$

$$-9 = -\frac{0.5 \times 10^{-3}}{0.686} (R_D \parallel R_L \parallel r_o) \Rightarrow R_D \parallel R_L \parallel r_o = 9 \times 0.686 \times 2 K\Omega = 12.348 K\Omega$$

$$\Rightarrow \frac{1}{R_D} + \frac{1}{R_L} + \frac{1}{r_o} = \frac{1}{12.348 K} \Rightarrow \frac{1}{R_D} = \frac{1}{12.348 K} - \frac{1}{170 K} - \frac{1}{33 K}$$

$$\Rightarrow R_D = 22.32 K\Omega$$

$$-V_{DD} = R_D I_D + V_{DS} + R_S I_D \Rightarrow 9 = 0.25 \times 22.32 + 2.5 + R_S \times 0.25 \times 10^{-3}$$

$$\Rightarrow R_S = 3.68 K\Omega$$

$$-V_{GS} - V_t = 0.686 \Rightarrow V_G - V_S - V_t = 0.686 \Rightarrow V_G = 0.686 + 0.9 + R_S I_D = 2.505V$$

$$R_{in} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 1 M\Omega$$

$$V_G = V_{DD} \cdot \frac{R_2}{R_1 + R_2} \Rightarrow \frac{R_2}{R_1 + R_2} = 0.2784$$

$$\therefore R_1 (0.2784) = 1 M\Omega \Rightarrow R_1 = 3.6 M\Omega$$

$$\frac{R_2}{3.6 + R_2} = 0.2784 \Rightarrow R_2 = 1.385 M\Omega$$

Design: C: very large.

$$R_D = 22.32 K\Omega$$

$$R_S = 3.68 K\Omega$$

$$R_1 = 3.6 M\Omega$$

$$R_2 = 1.385 M\Omega$$

b)

Under AC or high frequency conditions: Capacitors act as short circuit.

$$V_{GS} = V_{GS} + v_{gs}$$

$$\text{MOSFET in cutoff if } V_{GS} \leq V_t \Rightarrow V_{GS} + v_{gs} \leq V_t$$

$$\Rightarrow v_{gs} \leq -V_{ov} \Rightarrow v_{gs} \leq -0.686$$

$$\text{but } C_s \text{ is short circuit} \Rightarrow V_s = 0 \Rightarrow v_{gs} = v_i$$

$$\text{MOSFET in cutoff if } v_i \leq -0.686$$

$$\Rightarrow \text{if } |v_i|_{\text{peak}} \geq 0.686V \Rightarrow \text{MOSFET will enter cutoff.}$$

$$\Rightarrow |v_i| \leq 0.686V \Rightarrow \text{MOSFET will not enter cutoff.}$$

For largest value of v_i so that MOSFET enters cutoff v_i is 0.686V.

2) As long as $V_{GS} \geq V_{GS} - V_t \Rightarrow$ MOSFET in saturation.

$$\Rightarrow V_{GS} + v_{gs} \geq V_{GS} + v_{gs} - V_t \Rightarrow 2.5 + v_{gs} \geq v_{gs} + V_{ov}$$

$$v_{gs} = v_i \quad ; \quad v_{ds} = v_o \quad (V_s = 0)$$

$$\Rightarrow 2.5 + v_o \geq v_i + V_{ov}$$

$$\text{but } v_o = A_v v_i$$

$$\Rightarrow 2.5 + A_v v_i \geq v_i + V_{ov}$$

$$\Rightarrow v_i(1 - A_v) \leq -V_{ov} + 2.5 \Rightarrow v_i \leq \frac{2.5 - V_{ov}}{1 - (-9)} \Rightarrow v_i \leq \frac{2.5 - V_{ov}}{10}$$

$$\Rightarrow v_i \leq 0.1814V$$

The largest possible input that results in MOSFET entering linear region is 0.1814V

3) $v_{gs \text{ peak}} = v_i \text{ peak}$

$v_i \text{ peak} \leq 0.0343V_{ov} \Rightarrow$ largest value of v_i that results in distortion is 0.0343V.

$$|v_i| \leq 0.686V \Rightarrow \text{avoid cutoff}$$

$$|v_i| \leq 0.1814V \Rightarrow \text{avoid linear region}$$

$$|v_i| \leq 0.0343V \Rightarrow \text{avoid distortion}$$

$$\Rightarrow |v_i| \leq 0.0343V \text{ to avoid all above conditions}$$