

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics

Fall 2007 – 2008

Homework 9

Consider a CMOS inverter with the following circuit parameters:


The N-channel MOSFET has $L = 0.5 \mu\text{m}$, $W = 2 \mu\text{m}$, $V_t = 0.7 \text{ V}$, and $k' = 200 \mu\text{A}/\text{V}^2$.

The P-channel MOSFET has $L = 0.5 \mu\text{m}$, $W = 5 \mu\text{m}$, $V_t = -0.8 \text{ V}$, and $k' = 120 \mu\text{A}/\text{V}^2$.


The supply voltage is $V_{DD} = 2.5 \text{ V}$.

- a) Find the values of V_{OL} and V_{OH} for this inverter.
- b) Find the value of V_{OL} when a $1 \text{ K}\Omega$ resistor is connected from the output to V_{DD} . The input is at V_{DD} . What is the total circuit power dissipation?
- c) Find the value of V_{OH} when a $1 \text{ K}\Omega$ resistor is connected from the output to ground. The input is at 0 V . What is the total circuit power dissipation?
- d) Find the values of V_{IL} and V_{IH} . Calculate the noise margins.
- e) Find the values of V_{IL} and V_{IH} when channel length modulation is *not* negligible. Assume in this part that $\lambda_n = 0.2 \text{ V}^{-1}$ and $|\lambda_p| = 0.15 \text{ V}^{-1}$.
- f) A 0.1 pF capacitor is now connected from output to ground.
 1. The input switches from 0 to V_{DD} at $t = 0$. Find the time instant at which the output reaches $0.2V_{DD}$.
 2. The input switches back to 0 at $t = 1 \mu\text{sec}$. Find the time instant at which the output reaches $0.8V_{DD}$.

Home work 3

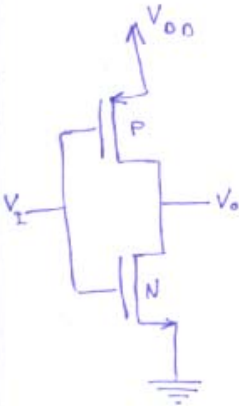
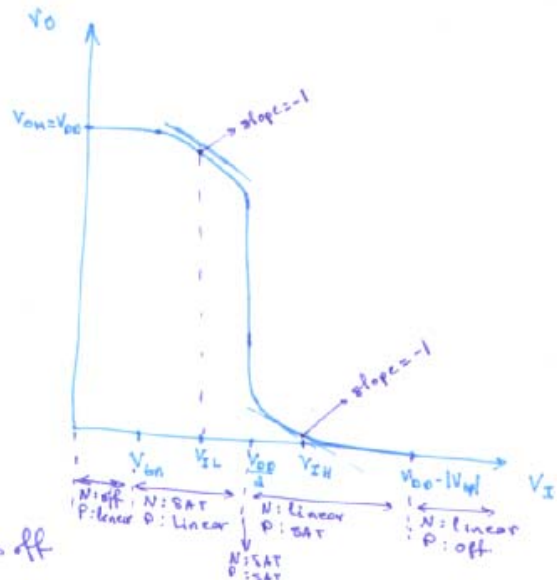
$$\begin{aligned} V_{GS_P} &= V_I - V_{DD} \\ V_{DS_P} &= V_O - V_{DD} \\ V_{GS_N} &= V_I \\ V_{DS_N} &= V_O \end{aligned}$$



a) For $V_I < V_{th}$ $\Rightarrow I_{D_P} = I_{D_N} = 0 \text{mA}$ and Nmos is off

$$I_{D_P} = 0 \text{mA} \Rightarrow Pmos \text{ in linear region} \Rightarrow 0 = \frac{1}{2} K_P \left(\frac{W}{L}\right)_P (2(V_{GS_P} - V_{th_P})V_{DS_P} - V_{DS_P}^2)$$

$$\Rightarrow V_{DS_P} = 0 \text{V} \Rightarrow V_O - V_{DD} = 0 \Rightarrow V_O = V_{DD} = 3 \text{V}$$


$$\therefore V_{OH} = V_{DD} = 2.5 \text{V}$$

For $V_I = V_{DD} \Rightarrow V_{GS_P} = 0 \text{V} \Rightarrow V_{GS_P} > V_{th_P} \Rightarrow Pmos \text{ is off} \Rightarrow I_{D_P} = I_{D_N} = 0 \text{mA}$

$$I_{D_N} = 0 \text{mA} \Rightarrow Nmos \text{ in linear region} \Rightarrow 0 = \frac{1}{2} K_N \left(\frac{W}{L}\right)_N (2(V_{GS_N} - V_{th_N})V_{DS_N} - V_{DS_N}^2)$$

$$\Rightarrow V_{DS_N} = 0 \text{V} \Rightarrow V_O = 0 \text{V}$$

$$\therefore V_{OL} = 0 \text{V}$$

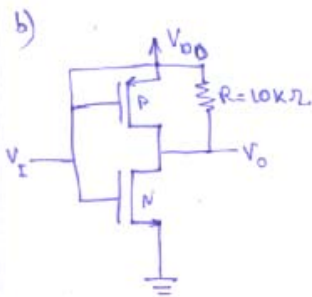


For $V_I = V_{DD} \Rightarrow V_{GS_P} = 0 \text{V} \Rightarrow Pmos \text{ is off} \Rightarrow I_{D_P} = 0 \text{mA}$

$I_{D_N} = \frac{V_{DD} - V_{OL}}{1 \text{ k}\Omega}$; $V_{GS_N} = 2.5 \text{V}$; $V_{OL} \ll 2.5 \text{V} \Rightarrow Nmos \text{ in linear region}$

$$\frac{1}{2} K_N \left(\frac{W}{L}\right)_N (2(V_{GS_N} - V_{th_N})V_{DS_N} - V_{DS_N}^2) = \frac{V_{DD} - V_{OL}}{1 \text{ k}\Omega} \Rightarrow \frac{1}{2} \times 200 \mu \times \frac{2}{0.5} (2(2.5 - 0.7)V_{OL} - V_{OL}^2) = 2.5 \text{m} - \frac{V_{OL}}{1 \text{ k}\Omega}$$

$$\Rightarrow 0.4 \times 2 \times (1.5)V_{OL} - 0.4V_{OL}^2 = 2.5 - V_{OL} \Rightarrow 0.4V_{OL}^2 - 2.4V_{OL} + 2.5 = 0 \Rightarrow V_{OL} = 1.3 \text{V}$$

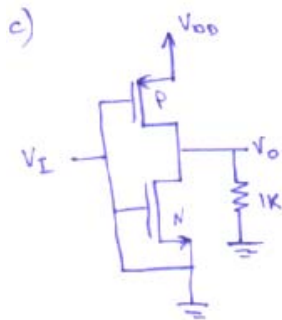Total power dissipation = $V_{DD} \times \text{current in } V_{DD} = V_{DD} \times (I_{in} + I_{Dp} + I_{Dn}) = V_{DD} \times I_{Dn}$
 in the circuit.
 $= V_{DD} \left(\frac{V_{DD} - V_{OL}}{1K} \right) = \frac{V_{DD} (2.5 - 1.3)}{1K} = 3 \text{ mW}$



For $V_I = 0 \Rightarrow V_{GSn} < V_{tn} \Rightarrow \text{NMOS is off} \Rightarrow I_{Dn} = 0 \text{ mA}$; PMOS in linear region

$$I_{Dp} = \frac{V_{OH}}{1K}$$

$$\frac{1}{2} K_p \left(\frac{W}{L} \right)_p (2(V_{GSp} - V_{tp})(V_{OH} - 2.5) - (V_{OH} - 2.5)^2) = \frac{V_{OH}}{1K}$$

$$\frac{1}{2} 120\mu \frac{5}{0.5} (2(-2.5 + 0.8)(V_{OH} - 2.5) - (V_{OH} - 2.5)^2) = \frac{V_{OH}}{1K}$$

$$1.2(-1.7)(V_{OH} - 2.5) - 0.6(V_{OH} - 2.5)^2 = V_{OH}$$

$$-2.04V_{OH} + 5.1 - 0.6V_{OH}^2 + 3V_{OH} - 3.75 = V_{OH}$$

$$\Rightarrow 0.6V_{OH}^2 + 0.04V_{OH} - 1.35 = 0$$

$$\Rightarrow V_{OH} = 1.47V$$

Total power dissipated in the circuit = Power in DC source = $V_{DD} \times I = V_{DD} \times I_{Dp}$
 supplied
 $= 2.5 \times \frac{1.47}{1K} = 3.675 \text{ mW}$

d) For V_{IL} : PMOS is in linear region and NMOS in SAT.

$$\Rightarrow \frac{1}{2} K_n \left(\frac{W}{L} \right)_n (V_{GSn} - V_{tn})^2 = \frac{1}{2} K_p \left(\frac{W}{L} \right)_p (2(V_{GSp} - V_{tp})(V_{OH}) - V_{OH}^2)$$

$$\Rightarrow 200 \times 2 (V_{IL} - 0.7)^2 = 120 \times 5 (2(V_{IL} - 2.5 + 0.8)(V_O - 2.5) - (V_O - 2.5)^2)$$

$$\Rightarrow 2(V_{IL} - 0.7)^2 = 3(2(V_{IL} - 1.7)(V_O - 2.5) - (V_O - 2.5)^2) \quad \text{--- (1)}$$

For V_{IL} : $\left. \frac{dV_O}{dV_I} \right|_{V_I = V_{IL}} = -1 \right\} \text{take derivative with respect to } \delta V_I$

$$\Rightarrow 4(V_{IL} - 0.7) = 6(V_O - 2.5) + 6(V_{IL} - 1.7) \left(\frac{dV_O}{dV_I} \right) - 6 \frac{dV_O}{dV_I} (V_O - 2.5)$$

$$\Rightarrow 4V_{IL} - 2.8 = 6V_O - 15 - 6V_{IL} + 10.2 - 6V_O + 15$$

$$\Rightarrow 10V_{IL} = 12V_O - 17 \Rightarrow V_O = \frac{10}{12} V_{IL} + \frac{17}{12} \quad \text{--- (2)}$$

Replace equation 2 in 1

$$\Rightarrow 2(V_{IL}-0.7)^2 = 6(V_{IL}-1.7)\left(\frac{5}{6}V_{IL} + \frac{17}{12} - 2.5\right) - 3\left(\frac{5}{6}V_{IL} + \frac{17}{12} - 2.5\right)^2$$

$$\Rightarrow \frac{11}{12}V_{IL}^2 - \frac{407}{60}V_{IL} + \frac{7859}{1200} = 0$$

$$\Rightarrow V_{IL} = 1.14V$$

$$NML = V_{IL} - V_{OL} = 1.24V$$

For $V_{IH} \Rightarrow$ PMOS in SAT and NMOS in linear region

$$\Rightarrow \frac{1}{2}K_n\left(\frac{W}{L}\right)_n (2(V_{DSn}-V_{tn})(V_{DSn}) - V_{DSn}^2) = \frac{1}{2}K_p\left(\frac{W}{L}\right)_p (V_{DSp}-V_{tp})^2$$

$$\Rightarrow 200 \times 2 (2(V_{IH}-0.7)(V_o) - V_o^2) = 120 \times 5 (V_{IH}-2.5+0.8)^2$$

$$\Rightarrow 4(V_{IH}-0.7)(V_o) - 2V_o^2 = 3(V_{IH}-1.7)^2 \text{ ----- (1)}$$

$$\left. \frac{dV_o}{dV_I} \right|_{V_I=V_{IH}} = -1$$

$$\Rightarrow 4V_o + 4(V_{IH}-0.7)\frac{dV_o}{dV_I} - 4\frac{dV_o}{dV_I}V_o = 6(V_{IH}-1.7)$$

$$\Rightarrow 4V_o - 4V_{IH} + 2.8 + 4V_o = 6V_{IH} - 10.2$$

$$\Rightarrow 8V_o = 10V_{IH} - 13 \text{ --}$$

$$\Rightarrow V_o = \frac{5}{4}V_{IH} - \frac{13}{8} \text{ --- (2)}$$

Replace equation 2 in 1

$$\Rightarrow 4(V_{IH}-0.7)\left(\frac{5}{4}V_{IH}-\frac{13}{8}\right) - 2\left(\frac{5}{4}V_{IH}-\frac{13}{8}\right)^2 = 3(V_{IH}-1.7)^2$$

$$\Rightarrow \frac{4}{8}V_{IH}^2 - \frac{333}{40}V_{IH} + \frac{7521}{800} = 0$$

$$\Rightarrow V_{IH} = 1.39V$$

$$NMH = V_{OH} - V_{IH} = 1.11V$$

c) For V_{IL} : PMOS in linear region, NMOS in SAT

$$\Rightarrow \frac{1}{2}K_n\left(\frac{W}{L}\right)_n (V_{DSn}-V_{tn})^2 (1 + \lambda_n V_{DSn}) = \frac{1}{2}K_p\left(\frac{W}{L}\right)_p (2(V_{DSp}-V_{tp})V_{DSp} - V_{DSp}^2)$$

$$\Rightarrow 2(V_{IL}-0.7)^2 (1 + 0.2V_o) = 3(2(V_{IL}-2.5+0.8)(V_o-2.5) - (V_o-2.5)^2)$$

$$\Rightarrow 2(V_{IL}-0.7)^2 (1 + 0.2V_o) = 6(V_{IL}-1.7)(V_o-2.5) - 3(V_o-2.5)^2 \text{ ----- (1)}$$

$$\left. \frac{dV_o}{dV_I} \right|_{V_I=V_{IL}} = -1$$

$$\Rightarrow 4(V_{IL}-0.7)(1+0.2V_o) + 2(V_{IL}-0.7)^2 \left(0.2\frac{dV_o}{dV_I}\right) = 6(V_o-2.5) + 6(V_{IL}-1.7)\frac{dV_o}{dV_I} - 6\frac{dV_o}{dV_I}(V_o-2.5)$$

$$\Rightarrow 4(V_{IL}-0.7) + 0.8V_0(V_{IL}-0.7) - 0.4(V_{IL}-0.7)^2 = 6V_0 - 15 - 6(V_{IL}-1.7) + 6V_0 - 15$$

$$\Rightarrow 4(V_{IL}-0.7)(1 + 0.1(V_{IL}-0.7)) + 30 + 6(V_{IL}-1.7) = (12 + 0.8(V_{IL}-0.7))V_0$$

$$\Rightarrow 4V_{IL} - 2.8 - 0.4V_{IL}^2 + 0.56V_{IL} - 0.196 + 6V_{IL} - 10.2 + 30 = (0.8V_{IL} + 11.44)V_0$$

$$\Rightarrow \frac{-0.4V_{IL}^2 + 10.56V_{IL} + 16.804}{0.8V_{IL} + 11.44} = V_0 \quad \text{--- (2)}$$

Replace (2) in (1):

$$2(V_{IL}-0.7)^2 \left(1 + 0.2 \cdot \frac{-0.4V_{IL}^2 + 10.56V_{IL} + 16.804}{0.8V_{IL} + 11.44}\right) = 6(V_{IL}-1.7) \left(\frac{-0.4V_{IL}^2 + 10.56V_{IL} + 16.804}{0.8V_{IL} + 11.44} - 2.5\right) - 3 \left(\frac{-0.4V_{IL}^2 + 10.56V_{IL} + 16.804}{0.8V_{IL} + 11.44} - 2.5\right)^2$$

$$\Rightarrow 20V_{IL}^5 - 845V_{IL}^4 - 7632V_{IL}^3 + 7192.9V_{IL}^2 - 105715.69V_{IL} + 123918.7611 = 0$$

$$V_{IL} = 1.1404V$$

For V_{IH} : Pmos in SAT, Nmos in linear

$$\frac{1}{2} K_n \left(\frac{W}{L}\right)_n^2 (V_{GSn} - V_{tn}) (V_{GSn} - V_{DSn}) = \frac{1}{2} K_p \left(\frac{W}{L}\right)_p (V_{GSp} - V_{tp})^2 (1 + \lambda_p V_{DSp})$$

$$4(V_{IH}-0.7)V_0 - 2V_0^2 = 3(V_{IH}-1.7)^2 (1.375 - 0.15V_0) \quad \text{--- (1)}$$

$$\left. \frac{dV_0}{dV_{IH}} \right|_{V_{IH}=V_{IH}} = -1$$

$$4V_0 + 4(V_{IH}-0.7) \frac{dV_0}{dV_{IH}} - 4V_0 \frac{dV_0}{dV_{IH}} = 6(V_{IH}-1.7)(1.375 - 0.15V_0) + 3(V_{IH}-1.7)^2 (-0.15 \frac{dV_0}{dV_{IH}})$$

$$\Rightarrow 4V_0 - 4V_{IH} + 2.8 + 4V_0 = 8.25V_{IH} - 14.025 - 0.9(V_{IH}-1.7)V_0 + 0.45(V_{IH}-1.7)^2$$

$$\Rightarrow V_0 (8 + 0.9(V_{IH}-1.7)) = 4V_{IH} + 8.25V_{IH} - 1.53V_{IH} + 0.45V_{IH}^2 - 16.825 + 1.3005$$

$$\Rightarrow V_0 = \frac{0.45V_{IH}^2 + 10.72V_{IH} - 15.5245}{0.9V_{IH} + 6.47} \quad \text{--- (2)}$$

Replace (2) in (1)

$$4(V_{IH}-0.7) \left(\frac{0.45V_{IH}^2 + 10.72V_{IH} - 15.5245}{0.9V_{IH} + 6.47}\right) - 2 \left(\frac{0.45V_{IH}^2 + 10.72V_{IH} - 15.5245}{0.9V_{IH} + 6.47}\right)^2 = 3(V_{IH}-1.7)^2 (1.375 - 0.15V_0)$$

$$\Rightarrow 729V_{IH}^5 + 11623.5V_{IH}^4 - 2547.9V_{IH}^3 - 592472.97V_{IH}^2 + 3131229.9645V_{IH} - 3321757.61553 = 0$$

$$\Rightarrow V_{IH} = 1.436V$$

f) 1- V_I switches from 0 to V_{DD}

\Rightarrow now $V_I = V_{DD} \Rightarrow P_{mos}$ is off $\Rightarrow i_{DP} = 0 \Rightarrow i_{DN} = -i_C \Rightarrow i_{DN} = -C \frac{dv_o}{dt}$

$$V_{GSN} = V_I = 2.5$$

$$V_{DSN} = V_o$$

\Rightarrow For $V_o > 2.5 - 0.7 \Rightarrow N_{mos}$ in SAT

For $V_o < 2.5 - 0.7 \Rightarrow N_{mos}$ in linear region

$$i_{DN} = -C \frac{dv_o}{dt} \Rightarrow dt = -\frac{C dv_o}{i_{DN}} \Rightarrow \Delta t = -C \int \frac{dv_o}{i_{DN}} ; \Delta t = t_1 - t = t_1 - 0 = t_1$$

$$\Rightarrow t_1 = \int_{V_{DD}}^{0.2V_{DD}} \frac{-C dv_o}{i_{DN}} = \int_{V_{DD}}^{V_{DD}-0.7} \frac{-C dv_o}{i_{DN_{SAT}}} + \int_{V_{DD}-0.7}^{0.2V_{DD}} \frac{-C dv_o}{i_{DN_{linear}}}$$

$$= \int_{2.5}^{1.8} \frac{-C dv_o}{\frac{1}{2} k_n \left(\frac{W}{L}\right)_n (V_{GSN} - V_{th})^2} + \int_{1.8}^{0.5} \frac{-C dv_o}{\frac{1}{2} k_n \left(\frac{W}{L}\right)_n (2(V_{GSN} - V_{th})V_o - V_o^2)}$$

$$= \frac{C}{\frac{1}{2} k_n \left(\frac{W}{L}\right)_n} \left[\int_{1.8}^{2.5} \frac{dv_o}{(1.8)^2} + \int_{0.5}^{1.8} \frac{dv_o}{3.6V_o - V_o^2} \right]$$

$$= \frac{0.1 \times 10^{-12}}{100 \times 10^{-4} \times \frac{2}{0.5}} \left[\frac{(2.5-1.8)}{(1.8)^2} + \frac{5}{18} \ln\left(\frac{V_o}{5V_o-18}\right) \right]_{0.5}^{1.8}$$

$$= 2.5 \times 10^{-10} \left[\frac{0.7}{1.8^2} + \frac{5}{18} \ln(0.2) - \frac{5}{18} \ln\left(\frac{1}{31}\right) \right]$$

$$= 0.18 \text{ nsec.}$$

2- $V_I = 0 \Rightarrow N_{mos}$ become off $\Rightarrow i_{DN} = 0 \Rightarrow i_{DP} = i_C \Rightarrow i_{DP} = C \frac{dv_o}{dt}$

$$V_{GSP} = V_{DD} + V_I - V_I - V_{DD}$$

$$V_{GSP} = V_o - V_{DD}$$

For $V_o - V_{DD} < V_I - V_{DD} - V_{th} \Rightarrow V_o < 0.8 \Rightarrow P_{mos}$ in SAT

For $V_o - V_{DD} > V_I - V_{DD} - V_{th} \Rightarrow V_o > 0.8 \Rightarrow P_{mos}$ in linear region

$$i_{DP} = +C \frac{dv_o}{dt} \Rightarrow dt = \frac{C dv_o}{i_{DP}} \Rightarrow \Delta t = C \int \frac{dv_o}{i_{DP}} ; \Delta t = t_2 - t_1 \Rightarrow t_2 = \Delta t + 1 \mu\text{sec.}$$

$$\Delta t = C \int_0^{0.8} \frac{dv_o}{i_{DP_{SAT}}} + C \int_{0.8}^{0.8V_{DD}} \frac{dv_o}{i_{DP_{linear}}} = C \int_0^{0.8} \frac{dv_o}{\frac{1}{2} k_p \left(\frac{W}{L}\right)_p (V_{GSP} - V_{th})^2} + C \int_{0.8}^{2} \frac{dv_o}{\frac{1}{2} k_p \left(\frac{W}{L}\right)_p (2(V_{GSP} - V_{th})V_{GSP} - V_{GSP}^2)}$$

$$\Delta t = \frac{C}{\frac{1}{2} k \left(\frac{W}{L} \right)_f} \left[\int_0^{0.8} \frac{dv_0}{(-1.7)^4} + \int_{0.8}^2 \frac{dv_0}{-3.4(v_0 - 2.5) - (v_0 - 2.5)^2} \right]$$

$$= \frac{0.1 \times 10^{-12}}{\frac{1}{2} \times 120 \times 10^6 \times \frac{5}{0.5}} \left[\frac{0.8}{1.7^2} + \int_{0.8}^2 \frac{-dv_0}{(v_0 - 2.5)(v_0 + 0.9)} \right]$$

$$= \frac{10^{-9}}{6} \left[\frac{0.8}{1.7^2} + \frac{5}{17} \ln \left(\left| \frac{10v_0 + 9}{2v_0 - 5} \right| \right) \right]_{0.8}^2$$

$$= \frac{10^{-9}}{6} \left[\frac{0.8}{1.7^2} + \frac{5}{17} \ln 29 - \frac{5}{17} \ln(5) \right] = 0.1323 \text{ nsec.}$$

$$\Rightarrow t_2 = \Delta t + 1 \mu\text{sec} = 1000.1323 \text{ nsec} \approx 1 \mu\text{sec}$$