

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics

Fall 2011 – 2012

Homework 1

Due Wednesday October 5, 2011 at 9:00 am

Problem 1. [50 points]

An amplifier has the transfer characteristic: $v_O = 12 - 10 (v_I - 3)^2$ V.

where v_O and v_I are in volts. This transfer characteristic applies for $3 < v_I < v_O + 3$ V, and v_O positive.

At the limits of this region, the amplifier saturates.

- a) [15 points] Sketch and clearly label the transfer characteristic. What are the saturation levels $L+$ and $L-$ and the corresponding values of v_I ?
- b) [10 points] Bias the amplifier to obtain a DC output voltage of 6 V. What value of input DC voltage V_I is required?
- c) [10 points] Calculate the value of the voltage gain (in V/V and in dB) at the bias point.
- d) [15 points] If a sinusoidal input signal is superimposed on the DC bias voltage V_I , that is: $v_I = V_I + V_i \cos(\omega t)$, find the resulting v_O . Express v_O as the sum of a DC component, a signal component at ω with amplitude A_1 and another component at 2ω , with amplitude A_2 . The component at 2ω is **undesirable** and is the result of the nonlinear transfer characteristic of the amplifier. If it is required to limit the ratio $\left| \frac{A_2}{A_1} \right|$ to 1%, what is the corresponding upper limit on V_i ?

Problem 2. [50 points]

An amplifier operating from ± 12.7 V power supplies has a linear transfer characteristic except for output saturation at ± 11 V.

- a) [12 points] The *peak-to-peak* value of the largest sinusoidal wave that can be applied at the amplifier input without output distortion is 0.5 V. Find the amplifier voltage gain in V/V and in dB.
- b) [8 points] What is the corresponding output power for an 32Ω load?
- c) [20 points] What is the power gain, in W/W and in dB, if the input power is 10 mW? What is the current gain of the amplifier, in A/A and in dB?
- d) [10 points] What is the amplifier efficiency (in %) if the DC current drawn from each power supply is 200 mA?