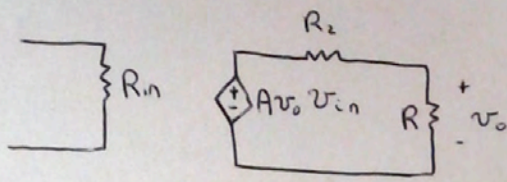


# HW 8

Nadim Hachem  
201100705

## Problem 1:



a) b)

\* For  $R = 33 \text{ k}\Omega$

$$v_o = \frac{33}{33 + R_2} A v_o v_{in}$$

$$\frac{v_o}{v_{in}} = \frac{33}{33 + R_2} A v_o = 99$$

\* For  $R = 39 \text{ k}\Omega$ ,

$$\frac{v_o}{v_{in}} = \frac{39}{39 + R_2} A v_o = 108$$

$$\begin{cases} 33 A v_o = 99 (33 + R_2) \\ 39 A v_o = 108 (39 + R_2) \end{cases}$$

Solving these 2 equations with 2 unknowns we get:

$$A v_o = 216 \text{ V/V}$$

$$R_2 = 39 \text{ k}\Omega$$

c) with  $47 \text{ k}\Omega$  resistance,

$$v_{in} = \frac{R_{in}}{R_{in} + 47} v_{sig} = 0.76 v_{sig}$$


$$\Rightarrow R_{in} = 0.76 (R_{in} + 47)$$

$$R_{in} (1 - 0.76) = 47 \times 0.76$$

$$R_{in} = 148.83 \text{ k}\Omega$$

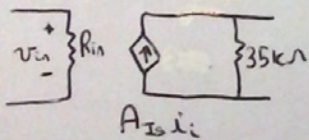
## Problem 2:

$$R_{in} = 150 \text{ k}\Omega \quad A_{is} = 200 \text{ A/V}$$




$$A v_o = G_m R_{out} = \frac{A_{is}}{R_{in}} \times R_{out} = 46.67 \text{ V/V}$$

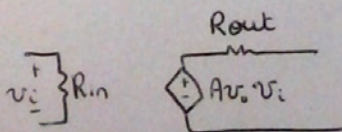
$$G_m = \frac{A v_o}{R_o} = \frac{46.67}{35} = 1.33 \text{ mA/V}$$



$$A v_o = 46.67 \text{ V/V}$$

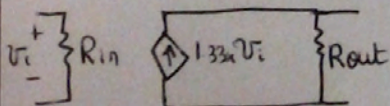

$$G_m = 1.33 \text{ mA/V}$$

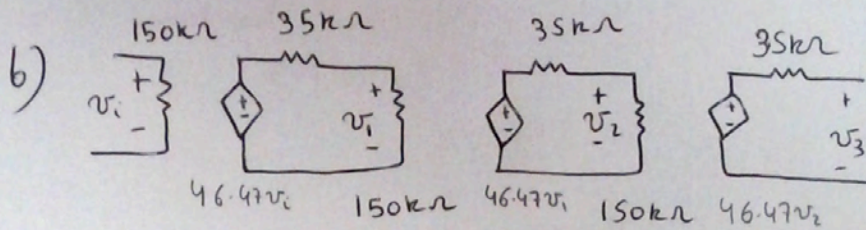

$$R_{in} = \frac{v_i}{i_i} = 150 \text{ k}\Omega$$

$$R_{out} = \frac{v_x}{i_x} \Big|_{v_{in}=0} = 35 \text{ k}\Omega \quad (v_x \text{ and } i_x \text{ are test voltage and current})$$

$$v_1 = \frac{150}{150+35} \times 46.47 v_i \Rightarrow A v_1 = \frac{v_1}{v_{in}} = 36.68 \text{ V/V}$$

$$v_2 = \frac{150}{150+35} \times 46.47 v_1 \Rightarrow A v_2 = 36.68 \text{ V/V}$$

$$v_3 = 46.47 v_2 \Rightarrow A v_3 = 46.47$$

$$A v_o = \frac{v_{out}}{v_{in}} = \frac{v_3}{v_i} = \frac{v_3}{v_2} \times \frac{v_2}{v_1} \times \frac{v_1}{v_i} = A v_3 \times A v_2 \times A v_1 = 65971 \text{ V/V}$$

$$A_{is} = \frac{R_{in}}{R_{out}} A v_o = 282732 \text{ A/A}$$

$$G_m = \frac{A v_o}{R_{out}} = 1.88 \text{ A/V}$$



$$c) v_o = v_L = \frac{56}{56+35} \times v_3 = 28.6 v_2$$

$$v_i = \frac{150}{150+200} v_{sig} = 0.428 v_{sig}$$

$$\frac{v_{out}}{v_i} = \frac{v_{out}}{v_3} \times \frac{v_3}{v_2} \times \frac{v_2}{v_1} \times \frac{v_1}{v_i} = 0.614 A v_o = 40597 \text{ V/V}$$

$$\frac{v_{out}}{v_{sig}} = \frac{v_{out}}{v_i} \times \frac{v_i}{v_{sig}} = 17399 \text{ V/V}$$

$$\text{in dB, } \frac{v_{out}}{v_{sig}} = 84.8 \text{ dB}$$

$$\frac{i_{out}}{i_{sig}} = \frac{v_{out} / R_L}{v_{sig} / (R_{in} + R_{sig})} = \frac{v_{out}}{v_{sig}} \times \frac{150 + 200}{56} = 108743 \text{ A/A}$$

$$\text{in dB, } A_i = 20 \log(A_{i(\text{norm})}) = 100 \text{ dB}$$

$$A_p = \frac{v_{out}}{v_{sig}} \times \frac{i_{out}}{i_{sig}} = 1.89 \times 10^9 \text{ W/W}$$

$$\text{in dB, } A_p = 20 \log A_{p(\text{W/W})} = 92.77 \text{ dB}$$
