

**American University of Beirut**  
 Department of Electrical and Computer Engineering  
**EECE 310 – Electronics I**  
**Fall 2004 – 2005**  
**Quiz 2 – December 22, 2004**  
**Closed Book – 90 minutes**

**P1 /16**  
**P2 /12**  
**P3 /20**  
**P4 /10**  
**P5 /12**  
**P6 /10**  
**P7 /20**

**Grade /100**

**NAME:** \_\_\_\_\_ **ID Number:** \_\_\_\_\_


*I have neither given nor received aid on this exam*

**SIGNATURE**

**Problem 1 [16 points]**



The drain current  $I_D$  of an enhancement n-channel MOSFET is measured at different values of  $V_{GS}$ ,  $V_{DS}$ , and  $V_{BS}$ . The results are shown in the table below. For this transistor, find the values of  $V_{t0}$ ,  $k'(W/L)$ ,  $\lambda$ , and  $\gamma$ . Assume that  $2|\phi_f| = 0.6$  V.


$V_{GS}$ (V)	$V_{DS}$ (V)	$V_{BS}$ (V)	$I_D$ ( $\mu$ A)
2	2	0	101.25
3	3	0	340.20
2	3	0	105.00
2	3	-2	63.69

 

 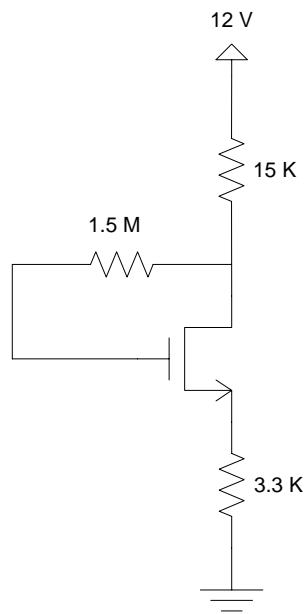**Problem 2 [12 points]**


For the MOSFET shown in the circuit below, find  $V_{GS}$ ,  $V_{DS}$ , and  $I_D$ . In what region is the transistor operating? The MOSFET parameters are  $V_t = 1\text{ V}$  and  $k'(W/L) = 0.1\text{ mA/V}^2$ .



 


**Problem 3 [20 points]**

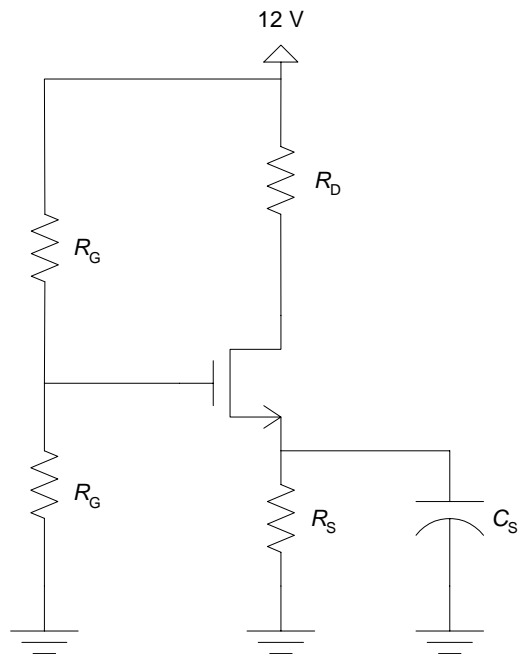a) The MOSFET shown in the circuit below is to be biased in the saturation region at  $V_{DS} = 5\text{ V}$ ,  $I_D = 0.5\text{ mA}$ . Find the required values of  $R_D$  and  $R_S$ , and calculate the values of the DC voltages  $V_G$ ,  $V_S$ , and  $V_D$ . The MOSFET parameters are  $V_t = 0.8\text{ V}$ ,  $k'(W/L) = 0.06\text{ mA/V}^2$ , and  $\lambda = 0.03\text{ V}^{-1}$ .






 b) The circuit is used as an amplifier with input at the gate, and output taken at the drain. What is the voltage gain of this amplifier at midband?




c) What is the maximum sinusoidal voltage swing at the drain (with input signal applied at the gate) for the MOSFET to remain in saturation? Express the swing as a DC value, a maximum value, and a minimum value.

 


**Problem 4. [10 points]**

 a) A MOSFET is biased at  $V_{DS} = 10\text{ V}$ ,  $V_{GS} = 5\text{ V}$ , and the resulting drain current is  $I_D = 1\text{ mA}$ . Show the small-signal T-model of this MOSFET at the bias point (with all component values). The MOSFET parameters are  $V_t = 1\text{ V}$ , and  $\lambda = 0.01\text{ V}^{-1}$ .




b) How would you modify the T-model if body-effect is present with a signal voltage  $v_{bs}$  appearing between body and source? Show the resulting circuit.

 



**Problem 5. [12 points]**

 a) Three identical amplifier stages are cascaded. For each of the amplifier stages, the input resistance is  $100\text{ K}\Omega$ , the output resistance is  $20\text{ K}\Omega$ , and the open-circuit voltage gain is 30. Show the model of the resulting (single) voltage amplifier, with values of  $R_i$ ,  $R_o$ , and  $A_{vo}$ .





b) Show the equivalent model, with component values, for a (single) transconductance amplifier.




**Problem 6. [10 points]**

Find the input resistance, voltage gain ( $v_{out}/v_{sig}$ ), and output resistance of the MOSFET amplifier shown. The MOSFET small-signal parameters are  $g_m$  and  $r_o$ .

 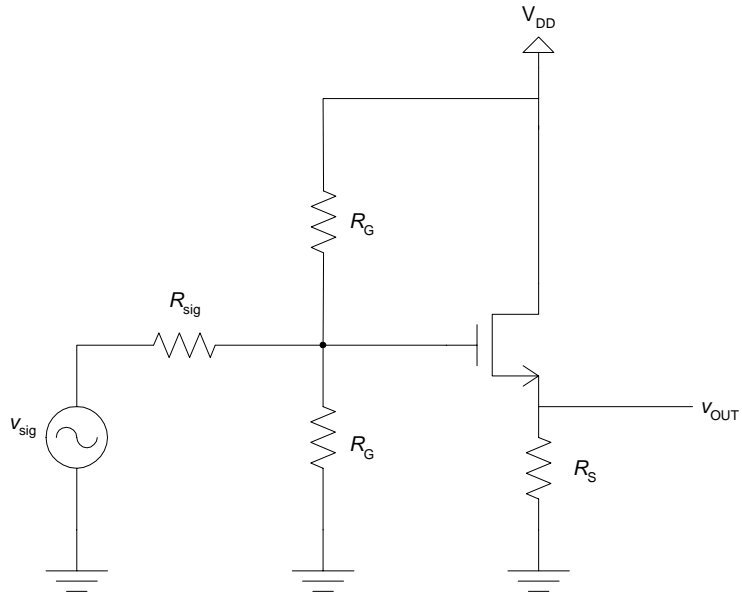


**Problem 7. [20 points]**

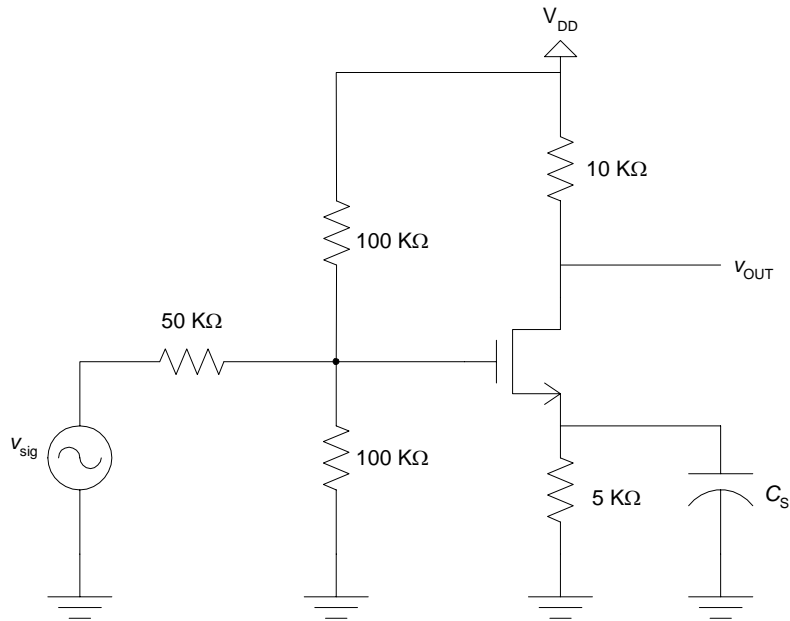a) Find the midband gain  $v_{out}/v_{sig}$  of the amplifier shown in the circuit below. The MOSFET is biased such that its small-signal transconductance is  $g_m = 1 \text{ mA/V}$ . Express the gain in dB.




 ~~b) What is the upper 3 dB frequency (in Hz) of this amplifier if  $C_{gs} = C_{gd} = 1 \text{ pF}$ ? Use the Miller approximation. What is the bandwidth of this amplifier if its lower 3 dB frequency is 100 Hz?~~





 ~~c) Show the magnitude Bode plot for the amplifier transfer function  $V_{out}/V_{sig}$ . Use a range of frequencies from 1 Hz to 1 MHz.~~



d) Find the value of the bypass capacitor  $C_S$  to get a lower 3 dB frequency of 100 Hz. Hint: Use the T-model to find  $V_{out}(s)/V_{sig}(s)$  at low frequency, then use the definition of the lower 3 dB frequency to solve  $\frac{|V_{out}(j\omega_L)|}{|V_{sig}(j\omega_L)|} = \frac{|midband\ gain|}{\sqrt{2}}$ .