

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics I
 Quiz 2 – December 16, 2006
 Closed Book – No Programmable Calculators
 120 minutes
Penalty is 5 to 1

Name: _____ ID number: _____

Use

$$n_i \approx 1.25 \times 10^{10} / \text{cm}^3$$

$$D_p = 12 \text{ cm}^2/\text{s}, D_n = 34 \text{ cm}^2/\text{s}$$

$$\mu_p = 480 \text{ cm}^2/\text{V.s.}, \mu_n = 1350 \text{ cm}^2/\text{V.s.}$$

$$q = 1.6 \times 10^{-19} \text{ C}, V_T \approx 25 \text{ mV}, \epsilon_{\text{Si}} = 1.04 \times 10^{-12} \text{ F/cm}$$

$$1 \mu\text{m} = 10^{-4} \text{ cm}$$

$$1 \text{ fF} = 10^{-15} \text{ F}$$

Neglect body effect

1- A MOSFET is biased in the saturation region at a fixed V_{DS} , and at $I_D = 2 \text{ mA}$, and $V_{OV} = 1 \text{ V}$. Find the increase in the drain current (in mA) when the gate-to-source voltage increases by 10 mV.

- a) 0.08 b) 0.07 **c) 0.04** d) 0.05 e) 0.06

2- A MOSFET with $k'_n(W/L) = 1 \text{ mA/V}^2$, $V_t = 1.3 \text{ V}$, and $\lambda = 0.04 \text{ V}^{-1}$, is biased at $V_{GS} = 2 \text{ V}$, $V_{DS} = 4 \text{ V}$. Find the value of r_o (in $\text{K}\Omega$) for this MOSFET.

- a) 88.9 **b) 102.0** c) 61.7 d) 69.2 e) 78.1

Consider the two-stage amplifier shown in Figure 1. Assume $G = 2 \text{ mA/V}$.

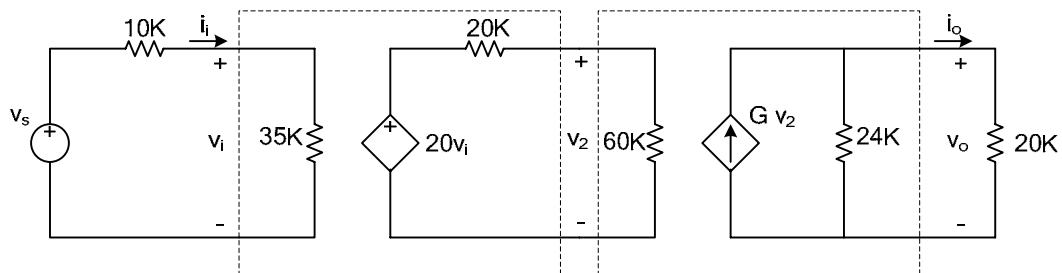


Figure 1

3- Find the value of the input resistance (in $K\Omega$).

- a) 30 **b) 35** c) 40 d) 45 e) 50

4- Find the value of the output resistance (in $K\Omega$).

- a) 15 b) 27 **c) 24** d) 21 e) 18

5- Find the voltage gain of the amplifier (v_o/v_i).

- a) 257.1 b) 307.3 c) 284.2 d) 344.7 **e) 327.3**

6- Find the current gain (i_o/i_i).

- a) 517.0 **b) 572.7** c) 614.6 d) 639.5 e) 642.9

Consider the amplifier shown in Figure 2. The capacitors are very large.

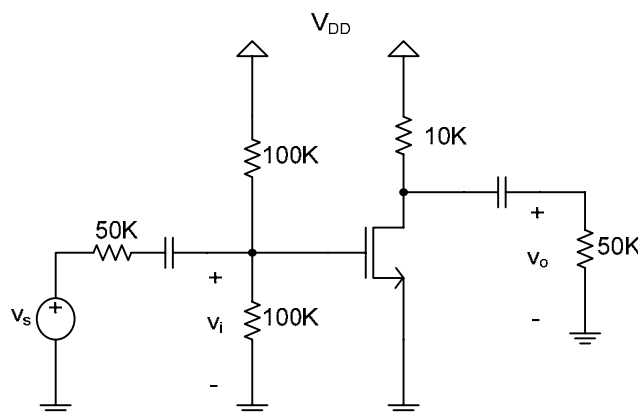


Figure 2

7- The MOSFET is biased such that $g_m = 1.2 \text{ mA/V}$ and $r_o = 55 \text{ K}\Omega$. Find the small-signal voltage gain of the amplifier (v_o/v_s).

- a) -2.7 b) -3.1 c) -3.5 d) -3.9 **e) -4.3**

8- Assume that the gain from gate to drain v_o/v_i is -6 . The drain of the MOSFET is biased at a DC voltage of 5 V. What should be the DC voltage at the gate (in V) in order to have a signal swing of $\pm 2.0 \text{ V}$ at the drain, while keeping the MOSFET in saturation? The transistor has $V_t = 1 \text{ V}$.

- a) 3.67** b) 3.90 c) 4.60 d) 4.37 e) 4.13

Consider the common-source MOSFET amplifier shown in Figure 3. Neglect channel-length modulation.


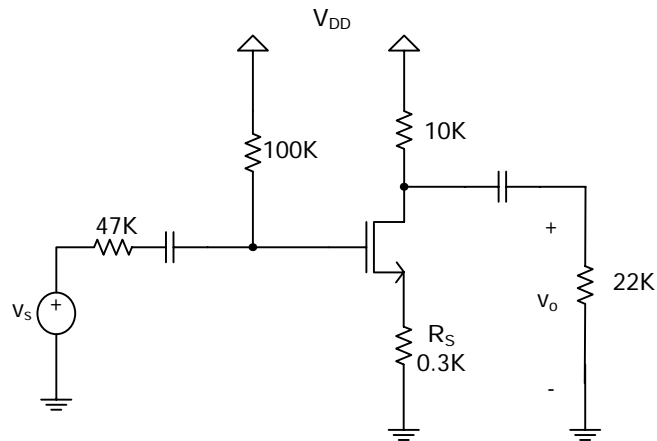


Figure 3

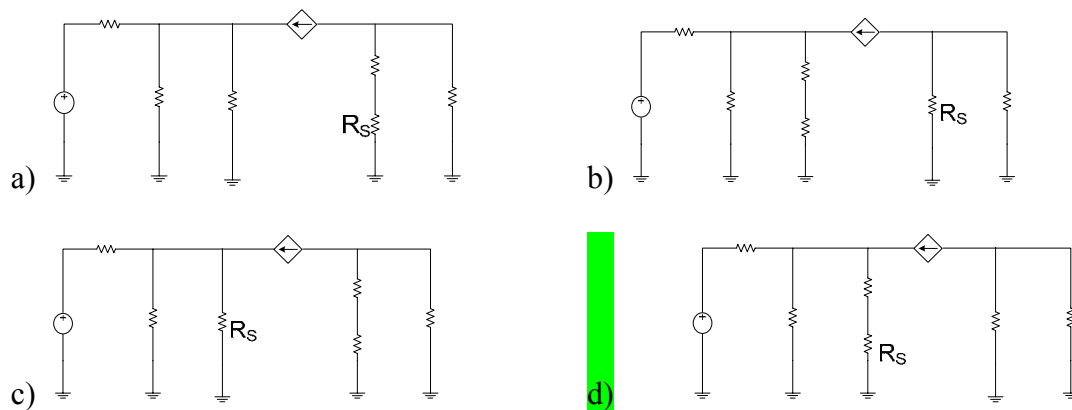9- Which of the following circuits corresponds to its small-signal equivalent?



10- Find the voltage gain v_o/v_s for the amplifier. The MOSFET small-signal transconductance is $g_m = 1.8 \text{ mA/V}$.

- a) -5.5 b) -4.8 c) -2.6 d) -3.8 e) -3.2

11- A voltage of magnitude 8 V is applied across the ends of a bar of intrinsic Silicon having a cross-sectional area of 0.25 cm^2 . How long should the bar be (in cm) in order to have a current of $12 \mu\text{A}$ flowing through it?

- a) 0.76 b) 0.69 c) 0.61 d) 0.46 e) 0.53

For a particular PN junction, the acceptor concentration is $5 \times 10^{16} / \text{cm}^3$, and the donor concentration is $3 \times 10^{12} / \text{cm}^3$.

12- Find the junction potential (in V) if no external bias is applied.

- a) 0.46 b) 0.69 c) 0.63 d) 0.57 **e) 0.52**

13- Find the concentration of holes (in cm^{-3}) in the n-type material.

- a) 5.2×10^6 b) 5.2×10^8 **c) 5.2×10^7** d) 5.2×10^4 e) 5.2×10^5

14- Find the depletion capacitance (in fF) when an 8 V reverse-bias is applied across this diode. The junction cross-sectional area is $500 \mu\text{m}^2$. The width of the depletion region is given by

$$W = \sqrt{\frac{2\epsilon_{\text{Si}}}{|q|} (V_o + V_R) \left(\frac{1}{N_A} + \frac{1}{N_D} \right)}$$

- a) 26 b) 8.5 c) 2.7 **d) 0.86** e) 0.27

15- The hole concentration in the n-type material of a PN junction diode under forward bias is described by:

$$p(x) = 10^5 + 10^{17} e^{-x/L_p} \quad \text{holes/cm}^3$$

with $L_p = 3 \mu\text{m}$. Given that the cross-sectional area of the junction is $240 \mu\text{m}^2$, find the hole diffusion current (in mA) that flows in the n-material at $x = 2 \mu\text{m}$.

- a) 0.26 b) 0.39 c) 0.53 d) 0.66 **e) 0.79**

To analyze the circuit shown in Figure 4, we use the MOSFET characteristics shown in Figure 5.

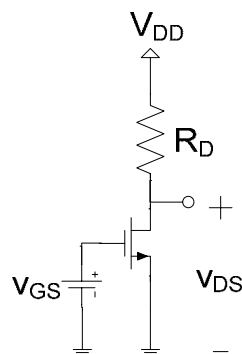


Figure 4

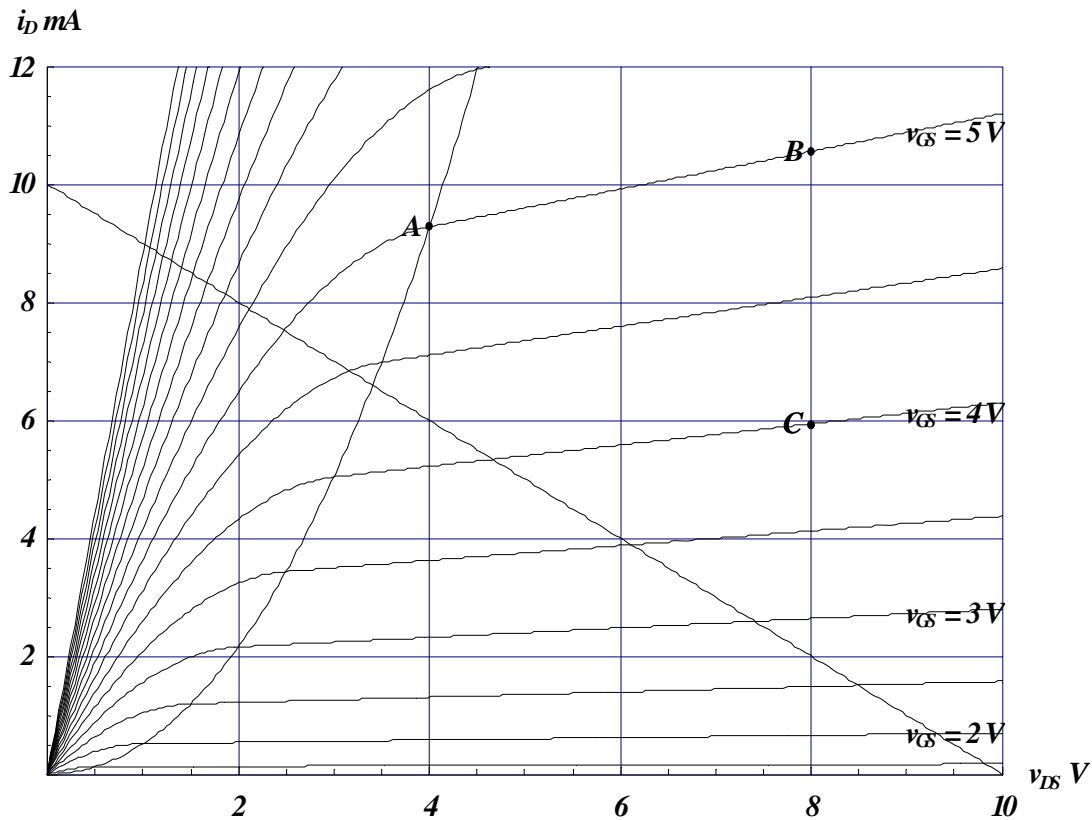


Figure 5

Figure 5 shows the characteristics for an NMOS transistor for a set of values of V_{GS} . The lowest value of V_{GS} is 1.5 V, the highest value is 10 V, with a step size of 0.5 V. Also a load line for the resistor R_D in the drain branch is shown in the figure. The values for i_D at the three points **A**, **B**, and **C** shown on the graph are:

$$i_{D(A)} = 9.28 \text{ mA}$$

$$i_{D(B)} = 10.56 \text{ mA}$$

$$i_{D(C)} = 5.94 \text{ mA}$$

16- What is the value of the resistor R_D in Ω ?

- a) 1000 b) 800 c) 750 d) 1100 e) 1200

17- What is the value of V_A in V? Use points **A** and **B** on the graph. *Hint*: Use the MOSFET current equation in saturation.

- a) 10 b) 25 c) 30 d) 20 e) 15

18- What is the value of V_t in V? Use points **B** and **C** on the graph. *Hint*: Use the MOSFET current equation in saturation.

- a) 1.0 b) 0.9 c) 0.8 d) 0.7 e) 0.6

19- In the circuit, V_{GS} is set at 2.5 V. Construct a second load line for the case when the supply voltage V_{DD} is *reduced by 2 V*. Find the value of V_{DS} (in V) at the new quiescent point Q .

- a) 4.3 b) 3.4 **c) 6.6** d) 7.3 e) 5.7

Consider the circuit shown in Figure 6. For the MOSFET, $k'_n(W/L) = 1 \text{ mA/V}^2$, $V_t = 0.7 \text{ V}$, and $\lambda = 0$. Assume $R = 1400 \ \Omega$.

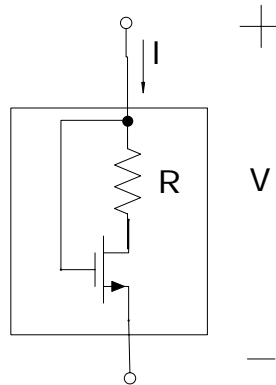


Figure 6

20- The condition for operation of the MOSFET in the saturation region, rather than in the triode (linear) region, is:

- a) **$I \leq 0.5 \text{ mA}$**
 b) $I \geq 0.5 \text{ mA}$
 c) $V \leq 1.4 \text{ V}$
 d) $V \geq 0.7 \text{ V}$

21- For $I = 0.5 \text{ mA}$, what is the value of V (in V)?

- a) 1.60 b) 2.41 c) 2.58 d) 2.21 **e) 1.70**

In the circuit shown in Figure 7, the NMOS transistor is characterized by $k'_n(W/L) = 1 \text{ mA/V}^2$, $V_t = 1 \text{ V}$ and $\lambda = 0$. The PMOS transistor is characterized by $k'_p(W/L) = 0.25 \text{ mA/V}^2$, $|V_t| = 1 \text{ V}$ and $\lambda = 0$.

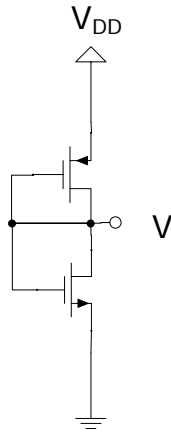


Figure 7

22- Given that $V = 5\text{ V}$, what is the value of I_D in mA?

- a) 12.5 **b) 8.0** c) 4.5 d) 0.5 e) 2.0

23- If $V_{DD} = 8\text{ V}$, what is the voltage V (in V) at the connected gates?

- a) 3.67 b) 2.33 c) 2.67 **d) 3.00** e) 3.33

The NMOS transistor in the circuit of Figure 8 is characterized by $k'_n(W/L) = 0.5\text{ mA/V}^2$, $V_t = 1\text{ V}$, and $\lambda = 0$. The MOSFET is biased at $I_D = 0.5\text{ mA}$. Assume $V_{DD} = 8\text{ V}$.

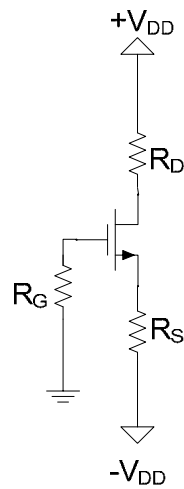


Figure 8

24- Assuming operation in the saturation region, find R_D (in $\text{K}\Omega$) if the drain voltage to ground $V_D = 2\text{ V}$.

- a) 14 **b) 12** c) 6 d) 8 e) 10

25- Find R_S (in $\text{K}\Omega$).

- a) 5.17 b) 7.17 c) 9.17 **d) 11.17** e) 13.17