

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics
 Quiz 2 – December 7, 2007
 Closed Book – *No Programmable Calculators*
 90 minutes
Penalty is 5 to 1

Name: _____ ID number: _____

Use

$$n_i \approx 1.25 \times 10^{10} / \text{cm}^3$$

$$D_p = 12 \text{ cm}^2/\text{s}, D_n = 34 \text{ cm}^2/\text{s}$$

$$\mu_p = 470 \text{ cm}^2/\text{V.s.}, \mu_n = 1333 \text{ cm}^2/\text{V.s.}$$


$$q = 1.6 \times 10^{-19} \text{ C}$$

$$k = 1.38 \times 10^{-23} \text{ J/K}$$

$$1 \text{ } \mu\text{m} = 10^{-4} \text{ cm}$$

$$V_T \approx 25 \text{ mV (when } T \text{ is not specified)}$$

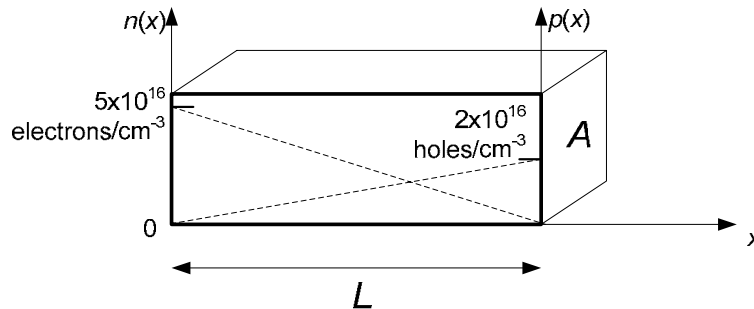1. The electron and hole concentrations in a semiconductor material are as shown in the figure below.



The direction of current flow is in the:

- a) negative x direction for holes, positive x direction for electrons
- b) positive x direction for holes, positive x direction for electrons
- c) **negative x direction for holes, negative x direction for electrons**
- d) positive x direction for holes, negative x direction for electrons
- e) none of the above

2. In Problem 1, the magnitude of the total current (in μA) when $L = 2.5 \text{ } \mu\text{m}$ and $A = 1 \text{ } \mu\text{m}^2$ is:

- a) 10.3 b) 31 c) 20.7 d) 15.5 e) **12.4**

3. A PN junction diode is formed by doping the P type at a density $N_A = 4 \times 10^{16} \text{ cm}^{-3}$ and the N type at a density $N_D = 5 \times 10^{17} \text{ cm}^{-3}$. Find the minority concentration in the N-type material (in cm^{-3}).

- a) 390.6 b) 260.4 c) 520.8 d) 223.2 e) **312.5**

4. Find the potential barrier (in V) at $T = 273 \text{ K}$, when the doping density of acceptors is increased to $7 \times 10^{16} \text{ cm}^{-3}$.

- a) 0.758 b) 0.769 c) **0.778** d) 0.785 e) 0.792

5. An N-channel MOSFET with $k' = 100 \mu\text{A}/\text{V}^2$ is biased in the triode (linear) region. The drain current is 1 mA at an overdrive voltage of 0.6 V. When V_{OV} increases to 0.8 V, with constant V_{DS} , the drain current increases to 1.9 mA.

Find the value of V_{DS} (in V).

- a) 0.89 b) 0.84 c) 0.63 d) **0.76** e) 0.4

6. Find the value of (W/L) for the MOSFET in the previous problem.

- a) 72.8 b) 62.5 c) 55.7 d) **59.6** e) 65.8

7. A P-channel MOSFET is biased at $V_{GS} = -3$, $V_{DS} = -1$, and has a threshold voltage $V_t = -1 \text{ V}$. Find its region of operation.

- a) Saturation
 b) Not enough data to decide
 c) **Triode (linear)**
 d) Cut-off
 e) None of the above

8. In the circuit shown in Figure A, find the value of V_{DD} (in V) that will place the MOSFET at the *edge* of saturation (i.e. at the intersection between triode and saturation). Assume $R_D = 6 \text{ K}\Omega$, and for the MOSFET: $k'(W/L) = 0.5 \text{ mA}/\text{V}^2$ and $V_t = 0.7 \text{ V}$.

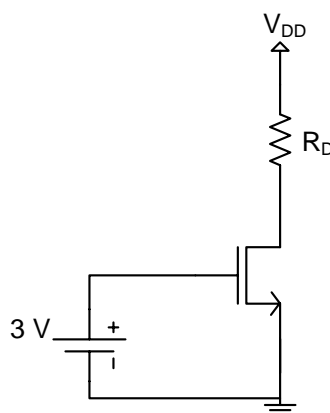


Figure A

- a) **10.2** b) 11.6 c) 8.91 d) 6.27 e) 7.59

9. In the circuit shown in Figure A, assume $V_{DD} = 12$ and $R_D = 5 \text{ K}\Omega$. For the MOSFET: $k'(W/L) = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, and $\lambda = 0.03 \text{ V}^{-1}$. Find the value of V_{DS} (in V) for the MOSFET.

- a) 3.89 b) 2.81 c) 6.25 d) **5.04** e) 7.55


10. Find the value of g_m (in mA/V) for the MOSFET in Problem 9.

- a) 1.67 b) 1.47 c) 0.81 d) 1.04 e) **1.26**

11. Find the value of r_o (in $\text{K}\Omega$) for the MOSFET in Problem 9.

- a) 45.9 b) 34.4 c) **27.5** d) 22.9 e) 19.7

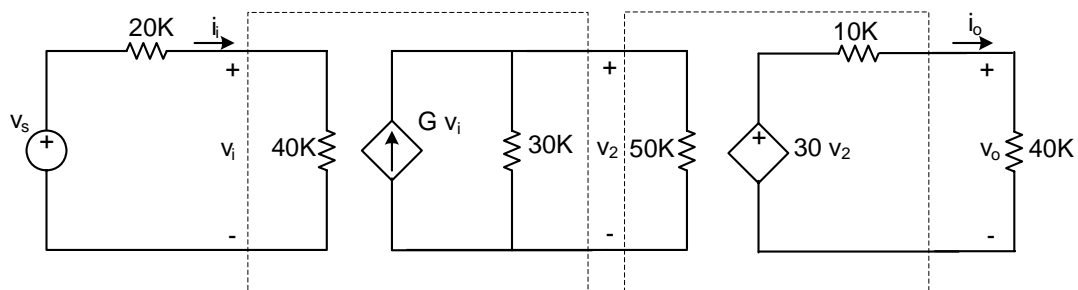12. Consider the two-stage amplifier shown below. What should be the value of G (in mA/V) to get an overall voltage gain v_o/v_s of 750?



- a) 2 b) **2.5** c) 3 d) 1 e) 1.5

13. Find the overall current gain, in the circuit of Problem 12, i_o/i_i , when the 40K load is replaced by a short circuit. Assume that $G = 7 \text{ mA/V}$.

- a) 20250 b) **15750** c) 11250 d) 13500 e) 18000

Consider the MOSFET amplifier shown in Figure B. The capacitors are very large.

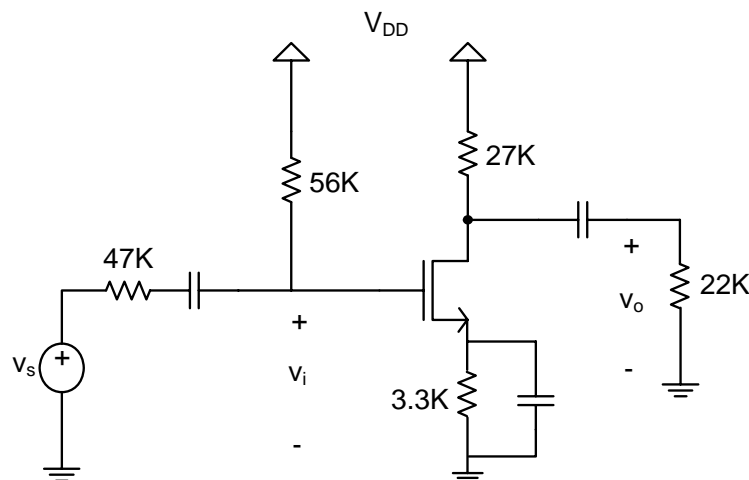


Figure B

14. The MOSFET is biased such that $g_m = 0.85 \text{ mA/V}$ and $r_o = 100 \text{ K}\Omega$. Find the small-signal voltage gain of the amplifier (v_o/v_i).

- a) -9.7 b) -7.6 c) -8.1 d) -8.6 e) -9.2

15. Assume that the gain from gate to drain v_o/v_i is -10. What should be the DC voltage at the drain (in V) in order to have a signal swing of $\pm 2 \text{ V}$ at the drain, while keeping the MOSFET in saturation? The transistor is biased at $V_{OV} = 0.7 \text{ V}$. Neglect signal distortion.

- a) 3.1 b) 3.3 c) 2.7 d) 2.9 e) 2.5


16. Find the input resistance (in $\text{K}\Omega$) of the amplifier shown in Figure B.

- a) 56 b) 68 c) 82 d) 39 e) 47

To analyze the circuit shown below, we use the MOSFET characteristics shown in Figure C. The $i_D - v_{DS}$ curves correspond to the following values of V_{GS} : 1.2, 1.7, 2.2, 2.7, and 3.2 V.

The three points shown on the plot have the following coordinates (3.3 V , 3.26 mA), (3.3 V , 5.10 mA), and (4.5 V , 5.36 mA)

Assume that V_{DD} is 5 V and $R_D = 1 \text{ K}\Omega$.

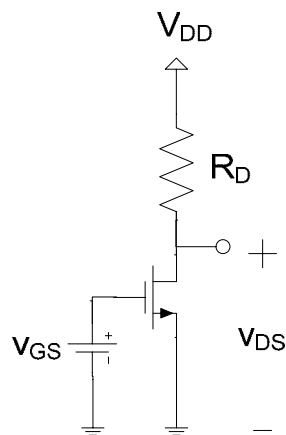

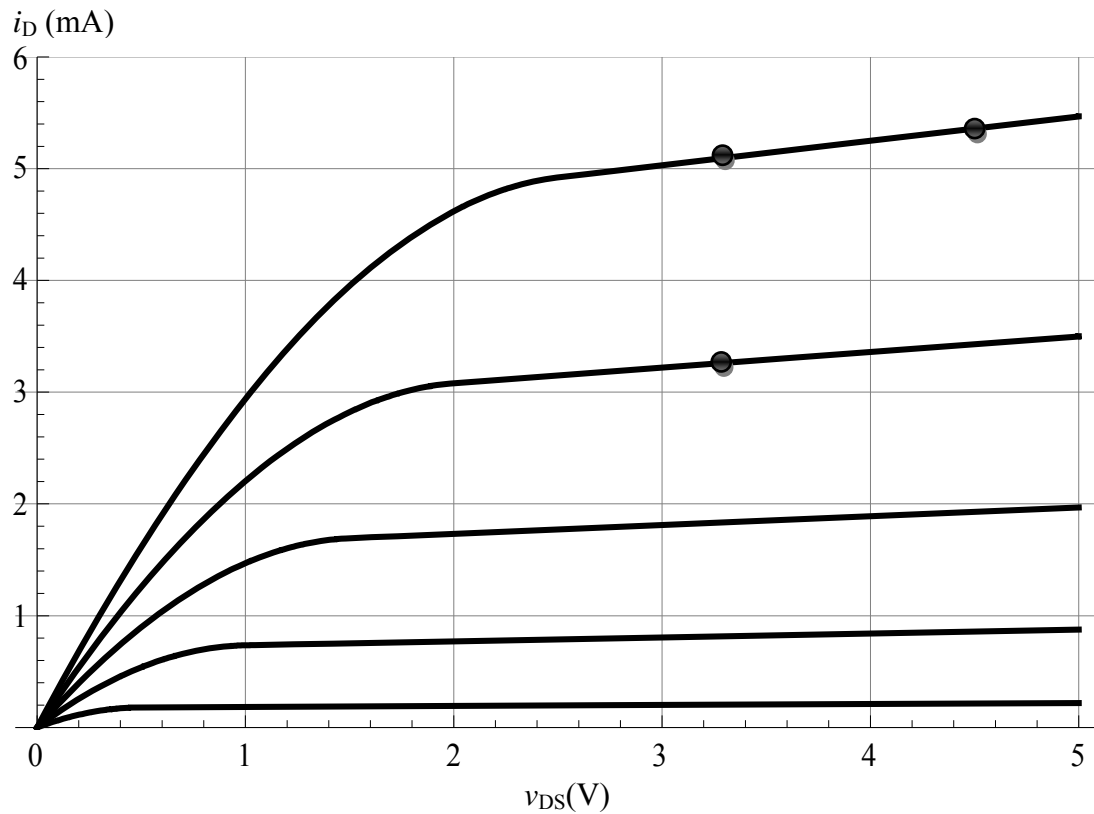


Figure C

17. Find the drain current (in mA) at the operating (Q) point of the MOSFET when $V_{GS} = 2.2$ V.

- a) 1.8 b) 3.1 c) 3.6 d) 0.8 e) 0.3

18. Determine the value of λ (in V^{-1}) for the MOSFET.

- a) 0.05 b) 0.07 c) 0.03 d) 0.02 e) 0.01


19. Determine the value of V_t (in V) for the MOSFET.

- a) 1.3 b) 1.1 c) 0.7 d) 0.9 e) 0.5

20. What is the region of operation of the MOSFET if V_{GS} is raised to 3.2 V?

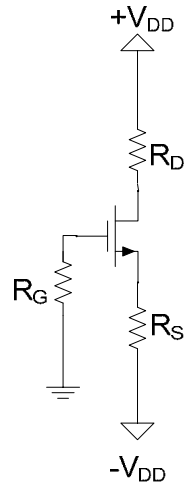- a) Linear b) Saturation c) Cut-off d) Not enough data to decide

In the circuit shown below, V_{DD} is 9 V. The resistor values are $R_D = 3.3$ K Ω , $R_S = 2.2$ K Ω , and $R_G = 470$ K Ω .




21. Find the voltage at the gate of the MOSFET.
 a) $V_{DD}/2$ **b) 0** c) V_{DD} d) $-V_{DD}$ e) none of the above

22. Find V_{DS} (in V) if $I_D = 1$ mA.
 a) 4.5 b) 6.5 c) 8.5 d) 10.5 e) **12.5**

23. Find I_D (in mA) when the MOSFET parameters are $k'(W/L) = 1$ mA/V² and $V_t = 1.2$ V.
 a) 1.78 b) **2.52** c) 1.06 d) 1.42 e) 2.15

24. The threshold voltage of an N-channel MOSFET increases from 0.8 to 1.1 V when the source-to-body voltage (V_{SB}) increases from 0 to 3 V. Find the value of γ (in V^{1/2}) for this transistor. Assume that $2\phi_F = 0.6$ V.
 a) 0.445 b) 0.623 c) 0.356 d) **0.267** e) 0.534

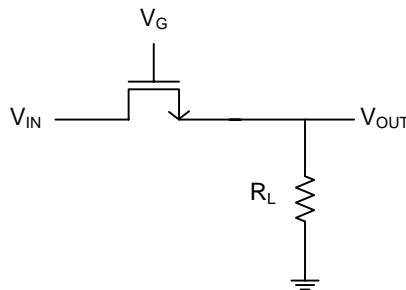25. In the circuit shown below, V_{IN} is a *very small* voltage. Find the minimum V_G (in V) such that the circuit attenuates V_{IN} by not more than 5%. Assume $R_L = 150$ Ω . For the MOSFET: $k'(W/L) = 1$ mA/V² and $V_t = 0.8$ V.



a) 1.22 b) 1.85 c) **1.15** d) 1.33 e) 1.50