

American University of Beirut
Department of Electrical and Computer Engineering

EECE 310 – Electronics

Quiz 2 – December 19, 2009

Closed Book – *No Programmable Calculators*

90 minutes

Penalty is 5 to 1

(1 to 4 wrong answers do not result in a penalty; 5 to 9 wrong answers cancel one correct answer; 10 to 14 wrong answers cancel two correct answers; and so on)

Name: _____ ID number: _____

Two voltage amplifiers are cascaded to amplify the voltage signal of a source v_i and deliver it to a load $R_L = 50 \text{ k}\Omega$.

The first amplifier is modeled by an input resistance $R_i = 160 \text{ k}\Omega$, output resistance $R_o = 10 \text{ k}\Omega$, and open-circuit voltage gain $A_{vo} = 100 \text{ V/V}$.

The second amplifier is modeled by $R_i = 20 \text{ k}\Omega$, output resistance $R_o = 40 \text{ k}\Omega$, and $A_{vo} = 30 \text{ V/V}$.

1. Find the voltage gain v_o/v_i (in V/V), where v_o is the voltage across R_L .

- a) 1000 b) 1667 c) 1429 d) 1250 e) 1111

2. Considering the two cascaded amplifiers as one equivalent amplifier, what is the input resistance (in $\text{k}\Omega$) of this equivalent amplifier?

- a) 100 b) 120 c) 140 d) 160 e) 180

3. Considering the two cascaded amplifiers as one equivalent amplifier, what is the output resistance (in $\text{k}\Omega$) of this equivalent amplifier?


- a) 40 b) 50 c) 10 d) 20 e) 30

4. In the circuit shown below, V_H is a small voltage not exceeding a few millivolts.

The MOSFET parameters are $V_{t0} = 0.8 \text{ V}$ and $k' W/L = 0.5 \text{ mA/V}^2$.

Find the ratio V_{DS}/V_H when $V_{GG} = 6.3 \text{ V}$.

- a) 0.15 b) 0.17 c) 0.23 d) 0.21 e) 0.19

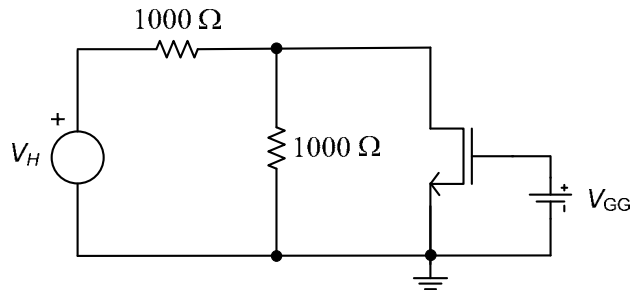

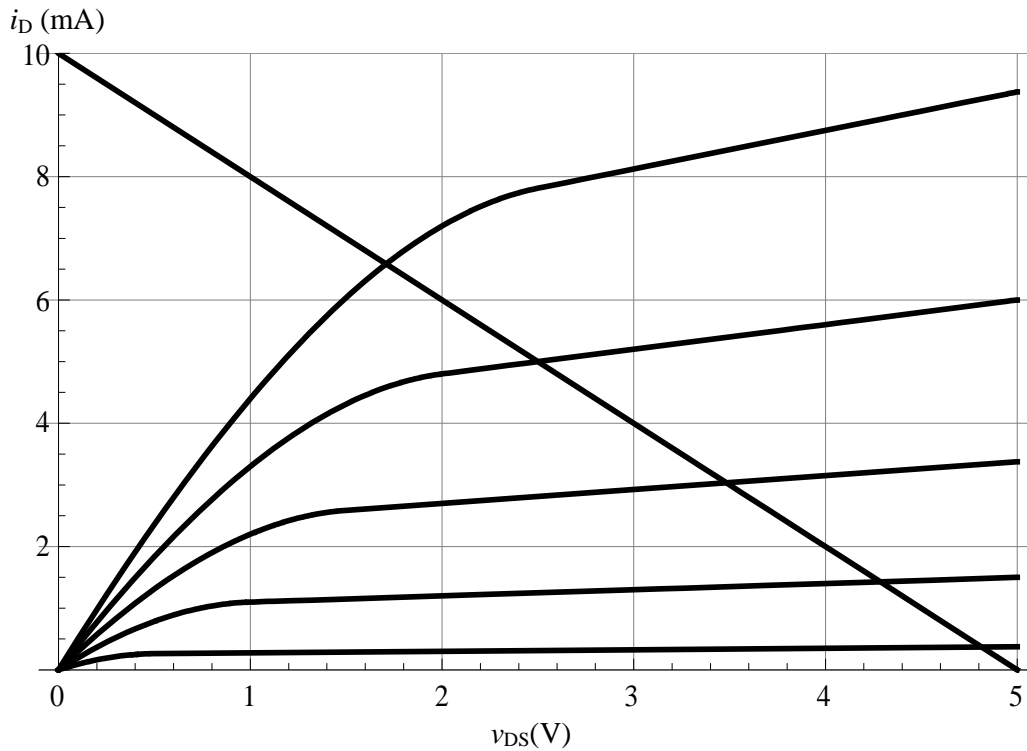


Figure A

The MOSFET whose $i_D - v_{DS}$ characteristics are shown in Figure A is to be biased at $V_{DS} = 3$ V, $I_D = 4$ mA. The curves correspond to the following values of V_{GS} : 1.5, 2, 2.5, 3, and 3.5 V. The load line is also shown in the figure.

5. Estimate the value of V_{GS} (in V) at the bias point.

- a) 3.15 b) 1.75 c) 2.25 d) 3.25 e) 2.75

6. Find the peak-to-peak variation in drain current (in mA) if the peak-to-peak variation in v_{DS} is 1 V.

- a) 2 b) 1 c) 0.5 d) 4 e) 3

7. Estimate the value of the drain-to-source resistance r_{DS} (in Ohms) for small v_{DS} in the triode region, when V_{GS} is 3.5 V.

- a) 800 b) 1000 c) 200 d) 400 e) 600

The drain current of an enhancement N-channel MOSFET is measured at several values of V_{GS} , V_{DS} , and V_{SB} , as shown in the table below.

For this MOSFET, $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\gamma = 0.4 \text{ V}^{1/2}$, and $2\phi_f = 0.6 \text{ V}$.

V_{GS} (V)	V_{DS} (V)	V_{SB} (V)	I_D (μA)
2	5	0	158.4
3	5	0	532.4
3	6	0	542.08
3	5	3	I_X
3	0.5	0	I_Y

8. Find the value of V_{t0} (in V).

- a) 0.80 b) 0.60 c) 1.2 d) 1.4 e) 1.6

9. Find the output resistance r_o in saturation (in $\text{k}\Omega$) corresponding to $V_{GS} = 3 \text{ V}$ and $V_{SB} = 0$.

- a) 85.03 b) 78.12 c) 123.46 d) 173.61 e) 103.31

10. Find the aspect ratio W/L .

- a) 2 b) 5 c) 10 d) 12 e) 4

11. Find I_X (in μA).

- a) 364.2 b) 298.4 c) 250.9 d) 337.2 e) 209.3

12. Find I_Y (in μA).


- a) 345 b) 195 c) 107.5 d) 337.5 e) 193.7

13. An enhancement PMOS transistor has $k'_p (W/L) = 100 \mu\text{A}/\text{V}^2$, $V_t = -1 \text{ V}$, and $\lambda = -0.02 \text{ V}^{-1}$. The gate is connected to ground, and the source to +3 V. Find the drain current (in μA) for $V_D = -3 \text{ V}$.

- a) 960 b) 1550 c) 2304 d) 224 e) 522


14. Find the value of the resistor R_D (in $k\Omega$) in the circuit shown below if the MOSFET is biased at a drain current of 1 mA.
 The MOSFET parameters are $V_{t0} = 0.75$ V, $k'(W/L) = 0.2$ mA/V², and $V_A = 5$ V.
 Assume $V_{GS} = 3$ V and $V_{DD} = 7$ V.

- a) 1.1 **b) 2.1** c) 3.1 d) 4.1 e) 5.1

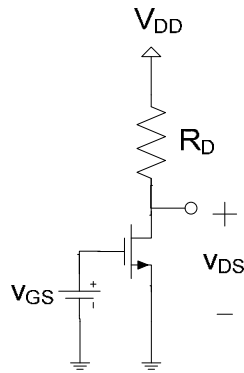

15. Find the voltage V_{DS} (in V) for the MOSFET in the circuit shown below. The MOSFET parameters are $V_{t0} = 1$ V and $k'(W/L) = 0.5$ mA/V². Assume $R_S = 1000$ Ω .

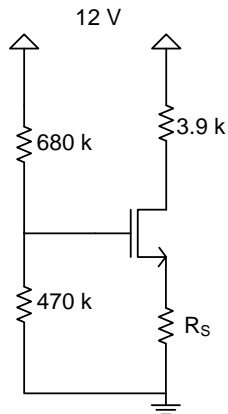- a) 5.21 b) 4.26 **c) 4.77** d) 3.23 e) 3.76



16. In the previous problem, what value of R_S (in Ohms) places the MOSFET *at the edge* of the saturation region?

- a) 422 b) 357 c) 281 **d) 493** e) 196

Consider the MOSFET amplifier shown in Figure B. The MOSFET is biased in the saturation region such that $V_{OV} = V_{GS} - V_t = 1\text{ V}$ and $I_D = 0.7\text{ mA}$. The capacitors are very large and $R_A = R_B = 200\text{ k}\Omega$, $R_D = 15\text{ k}\Omega$, $R_L = 20\text{ k}\Omega$, $R_{sig} = 10\text{ k}\Omega$. Neglect channel-length modulation.

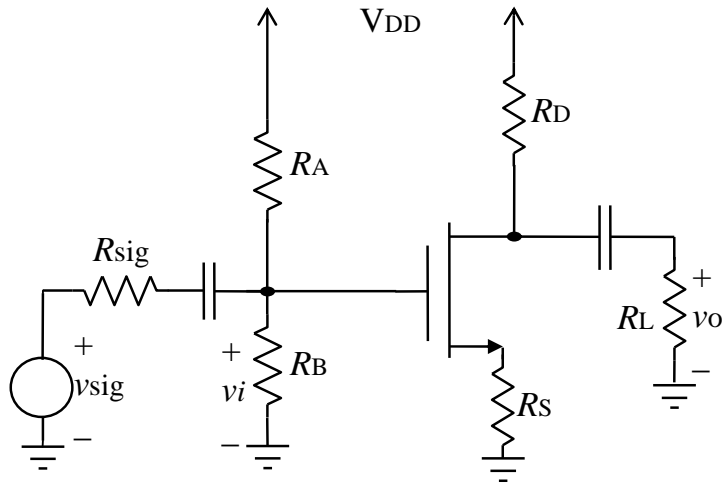


Figure B


17. Find g_m (in mA/V).

- a) 1.8 b) 1.6 c) 1.0 d) 1.2 e) 1.4

18. Assume g_m for the MOSFET is 1.4 mA/V. Find the small-signal voltage gain v_o/v_i (in V/V) if R_S is replaced by a short circuit.

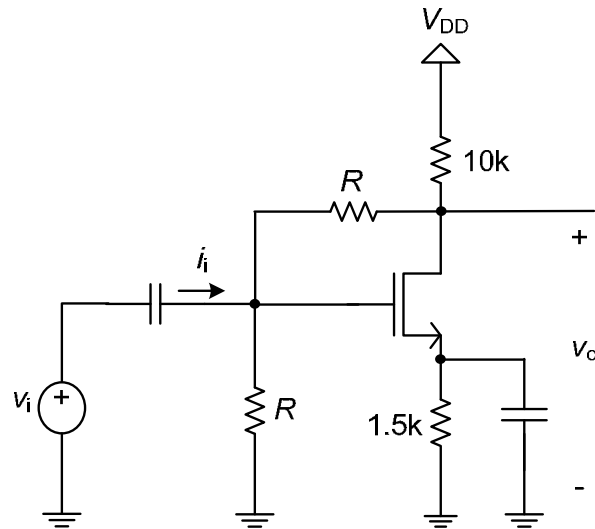- a) -15.4 b) -13.7 c) -12.0 d) -10.3 e) -8.6

In the circuit shown below, the MOSFET is biased in the saturation region such that $g_m = 1 \text{ mA/V}$ and $r_o = 50 \text{ k}\Omega$. Assume that all capacitors are very large, and that $R = 470 \text{ k}\Omega$.



19. Find the small-signal voltage gain v_o/v_i .

- a) **-8.2** b) -9.0 c) -5.7 d) -6.5 e) -7.3

20. Find the input resistance v_i/i_i in $\text{k}\Omega$.

- a) 61 b) 55 c) 50 **d) 46** e) 43

21. Assume that the gain from gate to drain v_o/v_i is *very large*. What is the maximum signal swing (in V) at the drain that keeps the MOSFET in saturation?

The transistor is biased at $V_{OV} = V_{GS} - V_t = 1 \text{ V}$, $V_{DS} = 3 \text{ V}$. V_{DD} is very large.

- a) +/- 3 b) +/- 4 c) +/- 3.5 **d) +/- 2** e) +/- 2.5