

American University of Beirut
 Department of Electrical and Computer Engineering
EECE 310 – Electronics I
Fall 2004 – 2005
Quiz 1 – November 5, 2004
Closed Book – 90 minutes

P1	/16
P2	/12
P3	/12
P4	/12
P5	/6
P6	/12
P7	/10
P8	/10
P9	/10
Grade	/100

NAME: _____ **ID Number:** _____

I have neither given nor received aid on this exam

SIGNATURE


ASSUME $V_T = 25 \text{ mV}$, UNLESS OTHERWISE SPECIFIED

Problem 1 [16 points]

An amplifier is characterized by the following relationships between its output voltage and its input voltage:

$$\begin{array}{ll}
 v_O = 1 \text{ V} & \text{for } v_I < 2 \text{ V} \\
 v_O \text{ (in V)} = 3 v_I - 5 & \text{for } 2 \text{ V} \leq v_I \leq 3 \text{ V} \\
 v_O = 4 \text{ V} & \text{for } v_I > 3 \text{ V}
 \end{array}$$

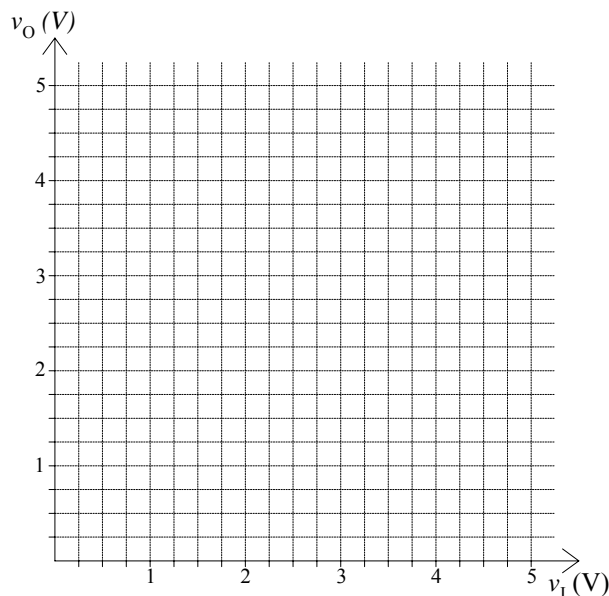a) Plot the amplifier transfer characteristics (v_O versus v_I) for $0 \text{ V} \leq v_I \leq 5 \text{ V}$. [3 points]




b) In the amplification region, what is the gain of the amplifier (in V/V)? What is the gain of the amplifier in dB? [3 points]

c) What is the maximum peak-to-peak undistorted variation in the output voltage? What is the corresponding peak-to-peak variation in the input voltage? [3 points]

d) Where should the bias point (V_L , V_O) of this amplifier be in order to get the maximum undistorted output? [3 points]

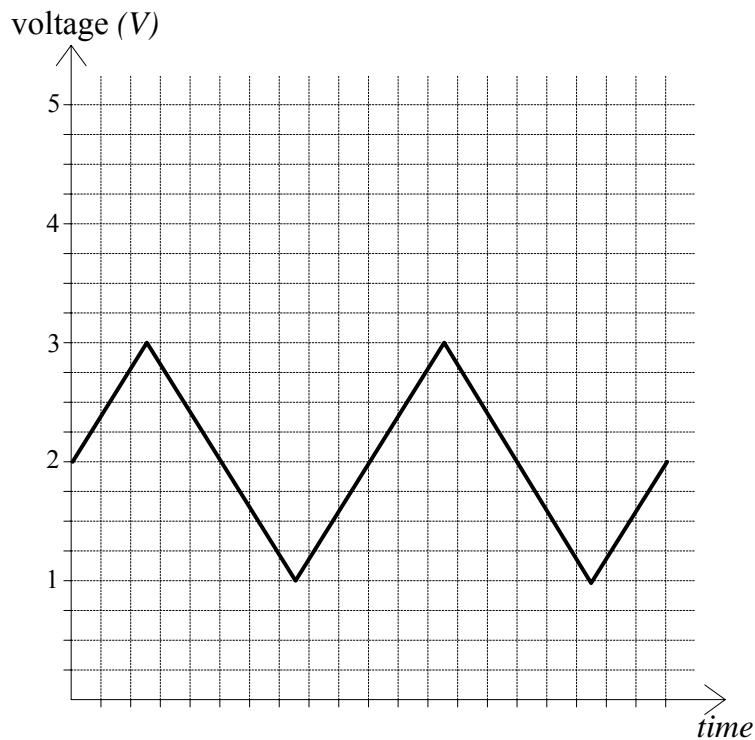e) For the input waveform shown below, plot and label, on the same graph, the output waveform. [4 points]



Problem 2 [12 points]

Measurements on a Si diode were taken at $v_D = 0.35 \text{ V}$, 0.45 V , 0.55 V , and 0.65 V . The natural logarithm of the diode current in Amps, $\ln(i_D)$, is plotted on the y-axis versus v_D in Volts, on the x-axis. The resulting *straight-line* has a slope of 32, and a y-axis intercept of -30 .


a) For this diode, find the values of n and I_S . [8 points]

b) What is the diode current when $v_D = 0.7 \text{ V}$? [4 points]

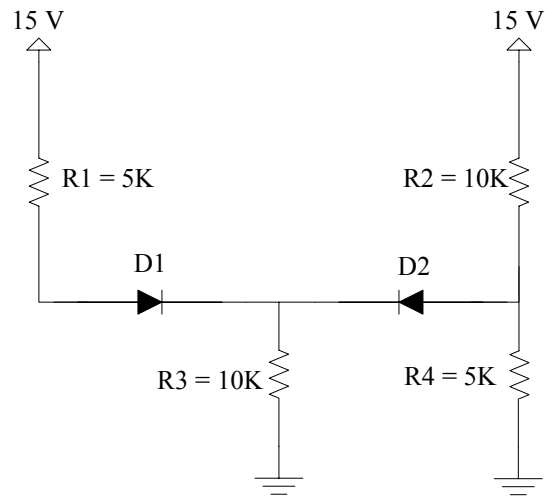Problem 3 [12 points]

The diodes in the circuit shown drop 0.7 V when conducting.

Calculate the current in D2 and the voltage across R3. Verify all your assumptions.




Blank area for student solution.

Problem 4 [12 points]

A certain device X is described by the following I-V characteristic:


$$i_X = \frac{v_X}{4} + \sqrt{v_X} \quad i_X \text{ is in mA and } v_X \text{ is in Volts}$$

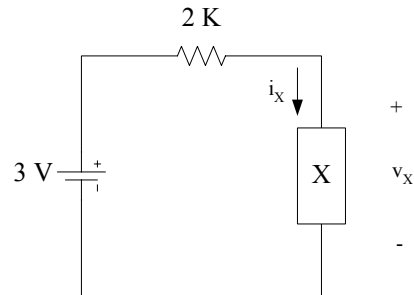This device is connected in series with a $2 \text{ K}\Omega$ resistor and a 3 V battery as shown below.



- a) Using numerical iterations, and starting with $v_X = 0.8 \text{ V}$, find the values of v_X and i_X for the device in this circuit. Show all steps in the calculation, and stop the iterations when consecutive values of v_X do not differ by more than 2 mV in absolute value. [6 points]

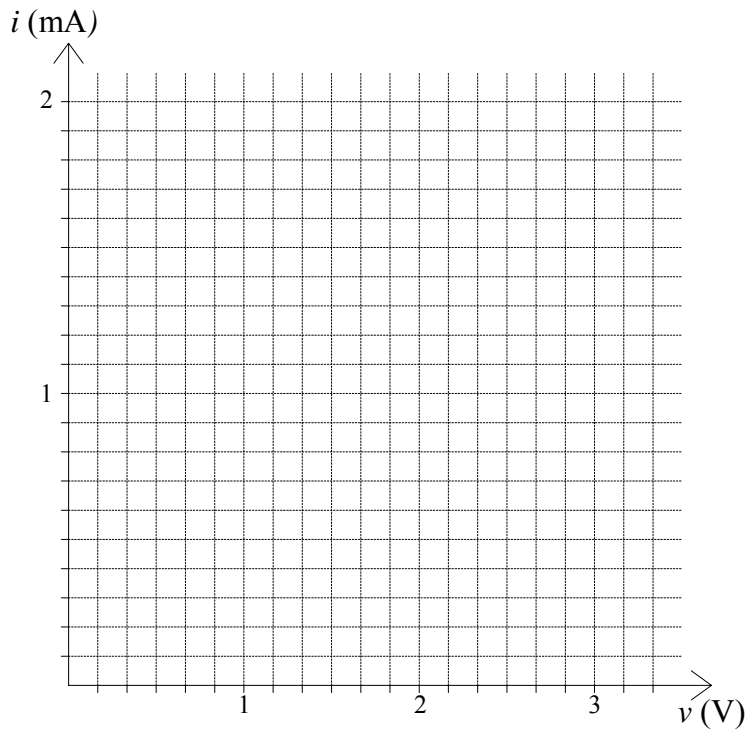b) Plot the I-V characteristic for the device on the graph below at values of $v_X = 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1.0,$ and 1.1 V. Then, use the load line method to *graphically* determine i_X and v_X . [6 points]



Problem 5 [6 points]

A Si diode is biased at a DC current of 5 mA. What is the peak-to-peak *signal current* that can appear in the diode without exceeding the small-signal approximation limit?

Problem 6 [12 points]


A full-wave rectifier with a center-tap transformer uses two diodes that are assumed ideal. The average value of the output voltage is 10 V, across a 100 Ω load resistor.

a) Find the maximum value of the sinusoidal voltage at the secondary of the transformer (from the center tap to one of the transformer terminals on the secondary.)
[4 points]


b) Find the average diode current. [4 points]

c) Find the diode PIV. [4 points]

Problem 7 [10 points]


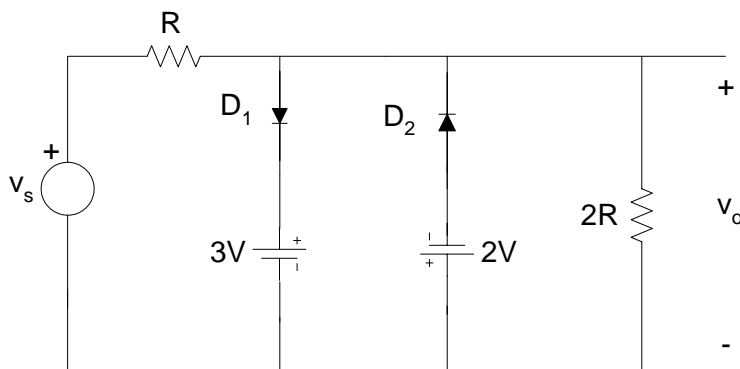


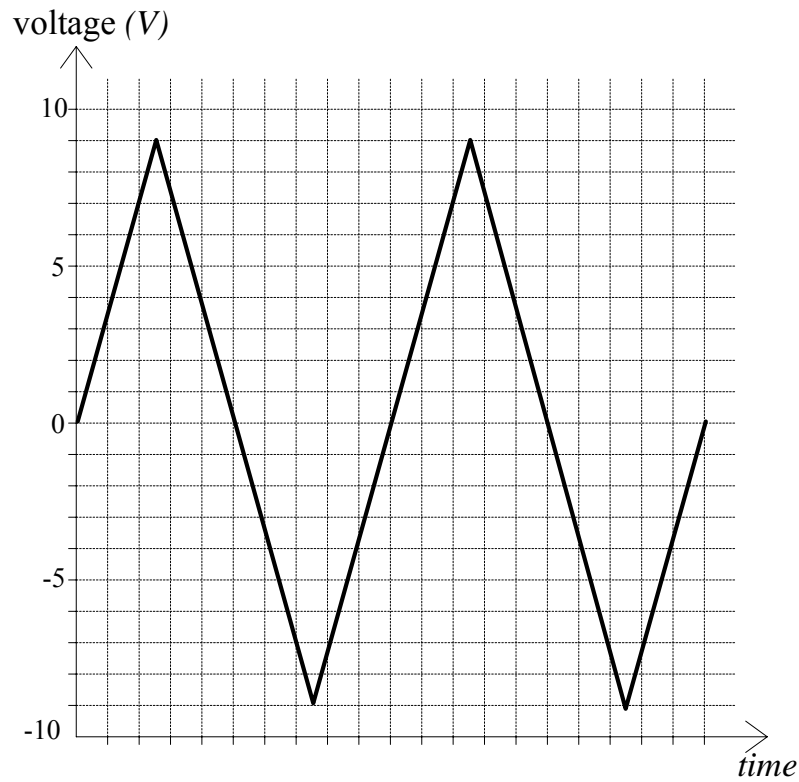For the v_s waveform shown below, plot and label, on the same graph, the output waveform that is produced by the circuit shown above.



 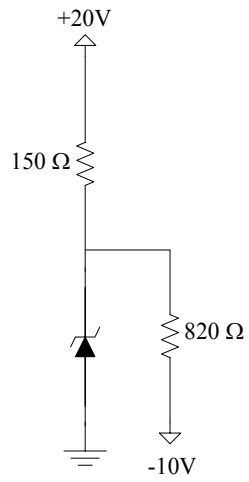Problem 8 [10 points]

The Zener diode shown in the circuit below is rated at $V_Z = 12\text{ V}$ for a test current of 25 mA . The value of the incremental Zener resistance r_Z is $10\ \Omega$. The Zener knee current I_{ZK} is 5 mA . Find the Zener current and the Zener voltage in the circuit shown. Verify all assumptions.



Problem 9 [10 points]

The density of donor atoms in a semiconductor is $5 \times 10^{16} \text{ cm}^{-3}$. The mobility of electrons in the semiconductor is $1300 \text{ cm}^2/\text{V}\cdot\text{sec}$ and that of holes is $500 \text{ cm}^2/\text{V}\cdot\text{sec}$. The intrinsic density is $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$. The magnitude of electron charge is $1.6 \times 10^{-19} \text{ C}$.

a) Is the semiconductor N-type or P-type? Why? [2 points]

b) Find the hole concentration. Does the hole concentration increase, decrease, or remain unchanged when temperature increases? [2 points]

c) Find the concentration of free electrons. Does the free electron concentration increase, decrease, or remain unchanged when temperature increases? [2 points]

d) Calculate the conductivity of the semiconductor. [2 points]

e) Find the drift current density due to holes if an electric field of 10^4 V/cm is applied. [2 points]