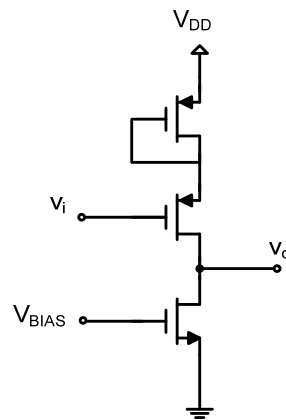


NAME: \_\_\_\_\_ ID Number: \_\_\_\_\_

**Problem 1. [14 points]**


Find the gain  $v_o/v_i$  and output resistance  $R_o$  of the amplifier shown below. The PMOS transistors are long and have negligible  $\lambda$ , while for the NMOS transistor  $r_o = 35 \text{ k}\Omega$ . The transconductances  $g_m$  of the MOSFETs are all equal to  $1 \text{ mA/V}$ .

$V_{BIAS}$  is a DC voltage. All transistors are internal to the amplifier.



**Problem 2. [8 points]**

The source follower shown below is used as an audio amplifier. The MOSFET is biased such that its  $g_m = 1 \text{ mA/V}$  and  $r_o = 90 \text{ k}\Omega$ . The current source has an output resistance of  $60 \text{ k}\Omega$ . Determine the maximum  $C_L$  to have an upper 3-dB frequency of  $20 \text{ kHz}$ .

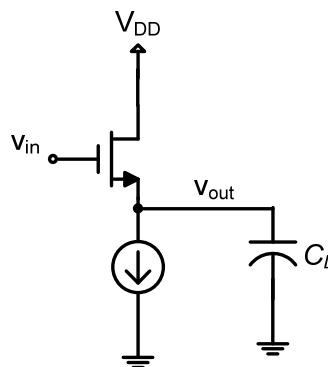

**Problem 3. [5 points]**

An operational amplifier has a differential gain of  $10^5$  and a CMRR of  $78 \text{ dB}$ . Find the common-mode gain.

**Problem 4. [33 points]**

a) Consider the current source shown in Figure 1.

Assume  $V_{DD} = 2.5$  V and  $I_{REF} = 75$   $\mu$ A.

Find the value of  $R$  if the MOSFETs have  $W = 3$   $\mu$ m,  $L = 1$   $\mu$ m,  $V_t = 0.6$  V, and  $k'_n = 200$   $\mu$ A/V<sup>2</sup>.

Assume that  $V'_A = 10$  V/ $\mu$ m.

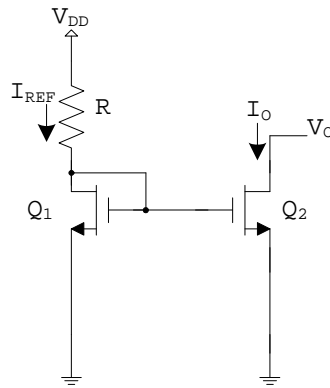


Figure 1

b) What is the lowest possible value of  $V_O$ ?

c) The two MOSFETs are matched. Find the change in the output current that corresponds to a change in the output voltage from 1 V to 2.5 V.

d) Repeat part (c) if  $Q_1$  has  $W/L = 3$   $\mu$ m / 1  $\mu$ m but  $Q_2$  has  $W/L = 15$   $\mu$ m / 5  $\mu$ m.

e) What should be the value of a resistance that is inserted between the source of  $Q_2$  and ground to reduce the output current to 10  $\mu$ A? The two MOSFETs are matched with  $W/L = 3$   $\mu$ m / 1  $\mu$ m.

f) With the resistance of part (e) inserted between the source and  $Q_2$  and ground, find the change in the output current that corresponds to a change in the output voltage from 1 V to 2.5 V.

**Problem 5. [40 points]**

The CMOS common-source amplifier shown in Figure 2 is biased using  $I_{REF} = 75 \mu\text{A}$ , and has  $W/L = 6 \mu\text{m}/0.25 \mu\text{m}$  for all transistors,  $k'_n = 250 \mu\text{A}/\text{V}^2$ ,  $k'_p = 100 \mu\text{A}/\text{V}^2$ ,  $V'_{An} = 10 \text{ V}/\mu\text{m}$ ,  $|V'_{Ap}| = 5 \text{ V}/\mu\text{m}$ ,  $V_{in} = -V_{tp} = 0.6 \text{ V}$ .

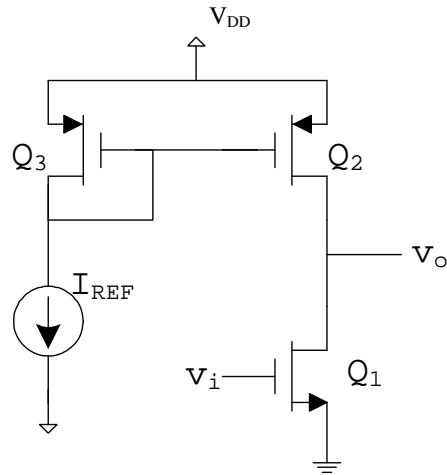


Figure 2

a) Neglecting channel-length modulation in the DC analysis, find:  $V_{OV1}$ ,  $g_{m1}$ ,  $r_{o1}$ ,  $r_{o2}$ , and the voltage gain  $v_o/v_i$ .

Assume now that for all MOSFETs in the circuit,  $C_{gs} = 12 \text{ fF}$ ,  $C_{gd} = 10 \text{ fF}$ ,  $C_{db} = 25 \text{ fF}$ , and  $C_{sb} = 25 \text{ fF}$ . The signal source (not shown in the figure) has a source resistance  $R_{SIG}$  of  $47 \text{ k}\Omega$ .

b) Using Miller's theorem, and assuming that the input circuit determines the upper 3-dB frequency  $f_H$ , find the value of  $f_H$ .

c) Based on the complete amplifier transfer function  $V_o(s)/V_{sig}(s)$ , show *and label* the Bode plots for magnitude and phase.

d) Using the open-circuit time constant methods, find the resistance seen by each capacitor, and estimate the value of  $f_H$ . Show all work.