

**American University of Beirut**  
Faculty of Engineering and Architecture  
Department of Electrical and Computer Engineering  
EE 042 - Analog Electronics  
Instructors: L. Chaar and A. Kayssi  
Quiz 1  
Saturday November 14, 1998

Closed Book  
Programmable Calculators Are Not Allowed.

**Time: 1.5 hours**

VERSION A

Name: \_\_\_\_\_ ID#: \_\_\_\_\_

- ☐ Provide your answer on the *computer card only*.
- ☐ Return the computer card attached to the question sheet.
- ☐ Use a pencil for marking your answers and ID number on the computer card.
- ☐ When using an eraser, make sure you erased well.
- ☐ On this sheet, write with a pen your name followed by your ID number.
- ☐ All questions are graded equally.

1. What is the version of your question sheet? (This question is not graded.)
  - a) Version A
  - b) Version B
  - c) Version C
  - d) Version D
  - e) Version E

**Assume in all problems that:  $V_{BE} = 0.7\text{ V}$ ,  $V_T = 25\text{ mV}$ , and that all capacitors are large**

**All problems are equally graded**

2. Calculate the input resistance  $R_i$  of the amplifier shown in Figure 1. For the BJTs,  $\beta = 100$ ,  $V_A = 70\text{V}$ . Neglect base current during DC analysis.

- a)  $112.5\text{ K}\Omega$
- b)  $85.6\text{ K}\Omega$
- c)  $73.5\text{ K}\Omega$
- d)  $211.9\text{ K}\Omega$
- e)  $180\text{ K}\Omega$

3. Calculate the output resistance  $R_o$  of the amplifier shown in Figure 1. For the BJTs,  $\beta = 100$ ,  $V_A = 70\text{V}$ . Neglect base current during DC analysis.

- a)  $18.7\text{ K}\Omega$
- b)  $20\text{ K}\Omega$
- c)  $100\text{ K}\Omega$
- d)  $16.67\text{ K}\Omega$
- e)  $39.2\text{ K}\Omega$

4. Calculate the voltage gain  $v_o/v_s$  for the amplifier shown in Figure 1. For the BJTs,  $\beta = 100$ . Neglect base current during DC analysis. Also, neglect  $r_o$  for the two transistors.

- a) 623.4
- b) 586.2
- c) 478.7
- d) 345.9
- e) none of the above

5. In the circuit of Figure 2, what should be the values of  $R_E$  and  $R_L$  to get a voltage gain  $v_o/v_s = -10$ , and an input resistance  $R_i = 500\text{ K}\Omega$ ? Assume  $\beta = 75$  and  $r_e \ll R_E$ .

- a)  $R_E = 4.22\text{ K}\Omega$ ,  $R_L = 100\text{ K}\Omega$
- b)  $R_E = 5.39\text{ K}\Omega$ ,  $R_L = 33.33\text{ K}\Omega$
- c)  $R_E = 8.01\text{ K}\Omega$ ,  $R_L = 220.2\text{ K}\Omega$
- d)  $R_E = 6.58\text{ K}\Omega$ ,  $R_L = 66.68\text{ K}\Omega$
- e)  $R_E = 2.33\text{ K}\Omega$ ,  $R_L = 51.42\text{ K}\Omega$

6. In the circuit of Figure 3, find the voltage gain  $v_{o1}/v_s$ . Assume  $\beta = 100$ . Neglect base current in the DC analysis.

- a) -0.984
- b) -2.65
- c) -18.3
- d) 9.64
- e) -322.5

7. In the circuit of Figure 3, find the voltage gain  $v_{o2}/v_s$ . Assume  $\beta = 100$ . Neglect base current in the DC analysis.

- a) 1
- b) 0.923
- c) 0.867
- d) 0.954
- e) 0.994

8. A differential amplifier employing  $10\text{ K}\Omega$  collector resistors, and for which the emitter bias current source is  $400\text{ }\mu\text{A}$ , uses BJTs for which  $\beta = 200$ . It is driven differentially by signal sources ( $+v_d/2$  and  $-v_d/2$ ) whose source resistances are  $10\text{ K}\Omega$  each. The emitter current source has an output resistance of  $500\text{ K}\Omega$ . For an output taken single-endedly, find the magnitude of the voltage gain  $v_o/v_d$  and the CMRR.

- a)  $|v_o/v_d| = 28.5$ , CMRR = 69.1 dB
- b)  $|v_o/v_d| = 20.2$ , CMRR = 78.2 dB
- c)  $|v_o/v_d| = 33.5$ , CMRR = 82.3 dB
- d)  $|v_o/v_d| = 45.1$ , CMRR = 45.6 dB
- e) none of the above

9. Find the voltage gain  $v_o/v_d$  and the CMRR for the circuit of Problem 8 when two emitter resistors  $R_E = 9\text{ r}_e$  are added to the circuit.

- a)  $|v_o/v_d| = 13.4$ , CMRR = 80.5 dB
- b)  $|v_o/v_d| = 3.83$ , CMRR = 51.7 dB
- c)  $|v_o/v_d| = 12.6$ , CMRR = 122.4 dB
- d)  $|v_o/v_d| = 6.63$ , CMRR = 44.9 dB
- e) none of the above

10. For the differential amplifier shown in Figure 4, find the magnitude of the differential gain  $v_o/v_d$  when  $v_{B1} = +v_d/2$  and  $v_{B2} = -v_d/2$ .

- a) 23.6
- b) 82.5
- c) 94.1
- d) 17.4
- e) 41.2

11. For the circuit shown in Figure 4, calculate the CMRR.

- a) 67.2 dB
- b) 82.9 dB
- c) 75.6 dB
- d) 56.9 dB
- e) 49.1 dB

12. When the inputs to a differential amplifier are  $\sin(t) - \cos(t)\text{ mV}$  and  $\sin(t) + \cos(t)\text{ mV}$ , the output is  $20000\cos(t) - \sin(t)\text{ mV}$ . Find the CMRR.

- a) 20 dB
- b) 40 dB
- c) 80 dB
- d) 100 dB
- e) 60 dB

13. A source follower amplifier uses MOSFETs for which  $V_t = 1\text{ V}$ ,  $V_A$  is very large and body effect is negligible. If the MOSFET is biased at  $I_D = 1\text{ mA}$ ,  $V_{GS} = 2\text{ V}$ , what is the range of load resistances for which the voltage gain of the follower is greater than 0.9?

- a)  $> 500\text{ }\Omega$
- b)  $> 4500\text{ }\Omega$
- c)  $< 4500\text{ }\Omega$
- d)  $< 450\text{ }\Omega$
- e)  $> 450\text{ }\Omega$

14. The common source amplifier shown in Figure 5 uses MOSFETs for which  $k'(W/L) = 20 \mu\text{A}/\text{V}^2$  and  $V_A = 100 \text{ V}$ . How does the voltage gain  $v_o/v_s$  change when  $I_{\text{REF}}$  is reduced from  $100 \mu\text{A}$  to  $1 \mu\text{A}$ ?

- a) The magnitude of the gain decreases from 316.2 to 31.6
- b) The magnitude of the gain decreases from 632 to 63.2
- c) The magnitude of the gain increases from 63.2 to 632
- d) The magnitude of the gain increases from 31.6 to 316.2
- e) There is not enough data to solve this problem.

15. Which of the following statements is true?

- I. The voltage gain of an emitter-follower is much larger than 1
- II. The input resistance of a common-base is very small
- III. The output resistance of a common-drain is very large
- IV. The current gain of common-emitter is always close to 1

- a) only I is true
- b) only II is true
- c) only III is true
- d) only IV is true
- e) all are false

