

**American University of Beirut**

Department of Electrical and Computer Engineering

EECE 311 – Electronic Circuits

Spring 2009

Midterm – April 15, 2009

Open Book – 120 minutes

NAME: \_\_\_\_\_ ID Number: \_\_\_\_\_


- ❖ All questions are equally graded
- ❖ PENALTY is **four-to-one** (four wrong answers cancel one correct answer, one to three wrong answers have no effect)
- ❖ Grading is based on the answers marked on the SCANTRON sheet only.

Assume that:

The DC drain current of a MOSFET in SAT is given by  $I_D = \frac{1}{2}k' \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$ .

The DC collector current of a BJT in ACTIVE is given by  $I_C = I_S \exp \left( \frac{V_{BE}}{V_T} \right)$ , and  $V_T = 25$  mV.


The common-source amplifier shown is loaded by a PMOS current source *with a source resistor*  $R_S$ . The inclusion of  $R_S$  must raise the output resistance of the PMOS current source to ten times  $r_{oN}$  (i.e.  $R_{OP} = 10r_{oN}$ ). Assume that the MOSFETs are biased at a drain current of 0.5 mA.  $V_B$  is a DC source. The MOSFET parameters are:  
 $k_n' = 0.2 \text{ mA/V}^2$ ,  $V_{in} = 0.5 \text{ V}$ ,  $\lambda_n = 0.1 \text{ V}^{-1}$ ,  $k_p' = 0.1 \text{ mA/V}^2$ ,  $V_{tp} = -0.6 \text{ V}$ ,  $\lambda_p = 0.1 \text{ V}^{-1}$ .

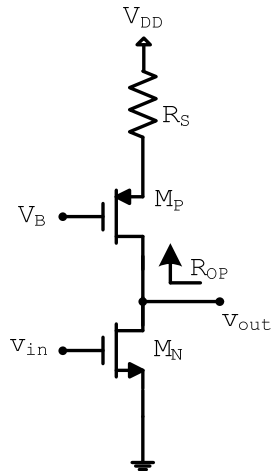

1. Find the value of  $R_S$  (in  $\text{K}\Omega$ ) if  $(W/L)_P = 150$ .  
 (a) 1.82      (b) 1.99      (c) 3.13      (d) 2.67      (e) **2.29**
2. Determine the value of  $(W/L)_N$  to obtain a voltage gain of  $-30$ .  
 (a) 9.45      (b) 6.05      (c) 24.2      (d) 18.5      (e) **13.6**
3. What is the output voltage swing (maximum – minimum, in V) to ensure saturation region operation for both MOSFETs? Assume  $V_{DD} = 3 \text{ V}$ .  
 (a) 0.63      (b) 0.84      (c) **1.0**      (d) 2.0      (e) 3.0


-----

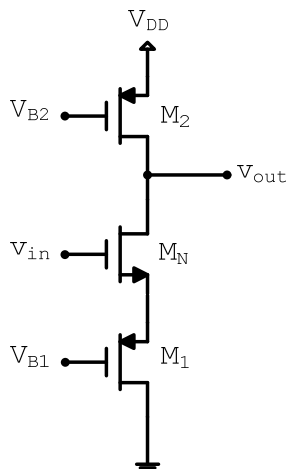4. Find the voltage gain  $v_{out}/v_{in}$  of the amplifier shown. Assume all MOSFETs have the same  $g_m$  and that transistor  $M_N$  has a *long channel* (i.e.  $\lambda = 0$ ), while  $r_{o1} = r_{o2} = 36/g_m$ .  $V_{B1}$  and  $V_{B2}$  are DC voltages.  
 (a)  $-16.1$       (b)  $-24.1$       (c)  $-22.1$       (d)  $-20.1$       (e)  **$-18.1$**



----

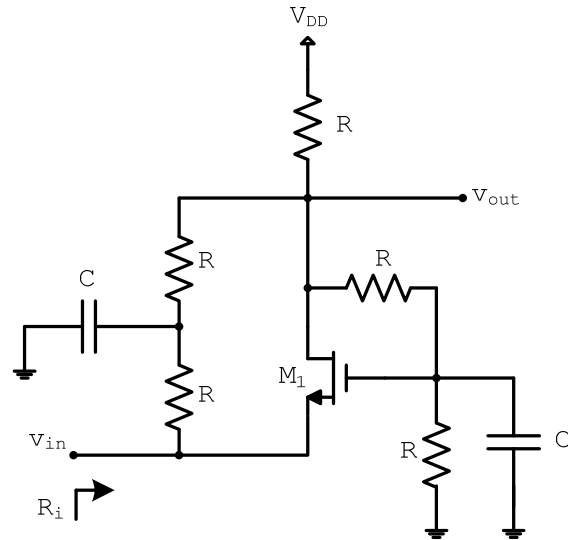
In the circuit shown below, the MOSFET has a long channel ( $\lambda = 0$ ) and is biased such that its transconductance  $g_m = 1 \text{ mA/V}$ . The resistors are all equal to  $21 \text{ K}\Omega$ . The capacitors are very large.



5. Identify the type of amplifier stage. It is common-  
 (a) follower (b) source (c) drain (d) **gate** (e) emitter
6. Find the voltage gain  $v_{out}/v_{in}$ .  
 (a) 4 (b) 5 (c) 6 (d) **7** (e) 8
7. Find the input resistance  $R_i$  in  $\text{K}\Omega$ .  
 (a) 15/16 (b) 18/19 (c) 24/25 (d) 12/13 (e) **21/22**

----

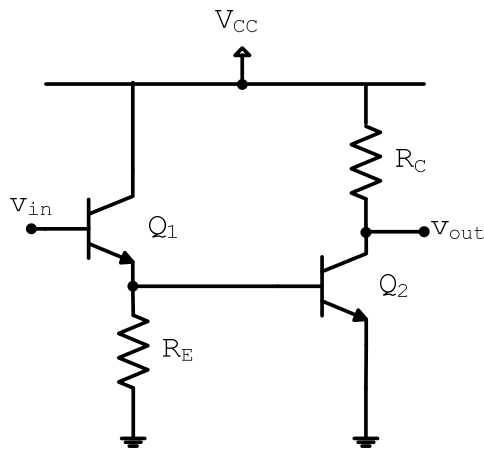8. Calculate the input resistance of the circuit shown below, in  $\text{K}\Omega$ . The BJTs are biased at a collector current of  $1 \text{ mA}$  and have  $\beta = 100$  and  $V_A = 50 \text{ V}$ . Assume  $R_C = 12 \text{ K}\Omega$  and  $R_E = 0.6 \text{ K}\Omega$ .  
 (a) 57.1 (b) **50.9** (c) 29.4 (d) 37.1 (e) 44.2



9. Calculate the output resistance of the circuit in  $\text{K}\Omega$ . All circuit elements are an internal part of the amplifier.

- (a) 8.33      (b) 9.68      (c) 10.9      (d) 6.89      (e) 5.36

10. Find the voltage gain  $v_{\text{out}}/v_{\text{in}}$ .

- (a) -367.9      (b) -314.3      (c) -195.9      (d) -418.2      (e) -257.1

11. Find the current gain of the amplifier when a  $10 \text{ K}\Omega$  load is connected at the output (from the collector of  $Q_2$  to ground). The output current is that flowing in the load resistor, while the input current comes from  $v_{\text{in}}$ .

- (a) -1141.2      (b) -951.7      (c) -758.4      (d) -375.2      (e) -564.3


----

The two BJTs in the circuit shown below are biased such that:

$r_{\pi 1} = 4 \text{ K}\Omega$ ,  $r_{o1} = 80 \text{ K}\Omega$ ,  $g_{m1} = g_{m2} = 30 \text{ mA/V}$ ,  $r_{\pi 2} = 3 \text{ K}\Omega$ , and  $r_{o2} = 12 \text{ K}\Omega$ .

Also assume that  $C_{\pi 1} = C_{\pi 2} = 0.2 \text{ pF}$  and  $C_{\mu 1} = C_{\mu 2} = 0.1 \text{ pF}$ .

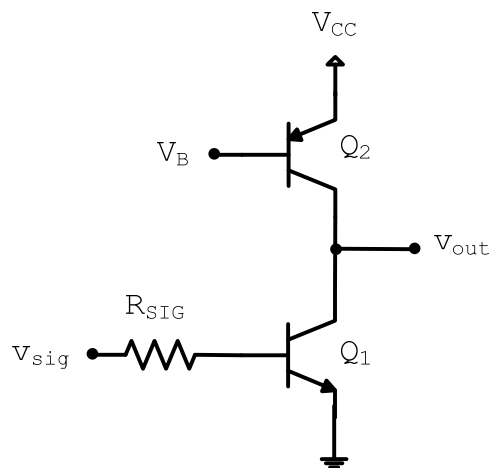The signal source resistance is  $R_{\text{SIG}} = 10 \text{ K}\Omega$ .



12. Using Miller's theorem, find the total equivalent capacitance (in pF) that appears between the base of  $Q_1$  and ground.

- (a) 57.4      (b) 27      (c) 31.6      (d) 38.2      (e) 44.4

13. Using Miller's theorem, find the total equivalent capacitance (in pF) that appears between the collector of  $Q_1$  and ground.

- (a) 0      (b) 0.3      (c) 0.4      (d) 0.2      (e) 0.1

14. Find the resistance seen by the capacitance of the previous question (in  $\text{K}\Omega$ ).

- (a) 8.89      (b) 10.4      (c) 12.6      (d) 14.7      (e) 19.0

15. Find the 3-dB frequency (in MHz) using OCTC, considering only the two capacitances obtained in questions 12 and 13.

- (a) 1.7      (b) 1.4      (c) 0.95      (d) 2.0      (e) 1.2

----

The transfer function of an amplifier is given by  $A(s) = \frac{1 + s / \omega_1}{(1 + s / \omega_2)(1 + s / \omega_3)}$ ,

where  $\omega_1 = 18,000$  rad/sec,  $\omega_2 = 6,000$  rad/sec, and  $\omega_3 = 30,000$  rad/sec.

16. Find the frequency (in Krad/sec) at which the gain drops by 8 dB from its DC value.

- (a) 11.9      (b) 14.3      (c) 17.0      (d) 20.2      (e) 23.9


17. The input to the amplifier is  $\sin(\omega_0 t)$  V, where  $\omega_0 = 6600$  rad/sec. Find the amplitude (in V) of the output waveform.

- (a) 0.4      (b) 0.8      (c) 0.7      (d) 0.6      (e) 0.5

----

18. Find the frequency  $f_x$  (x-axis intercept, in MHz) in the Bode plot shown below. The low-frequency gain  $A_0$  is 180 dB.

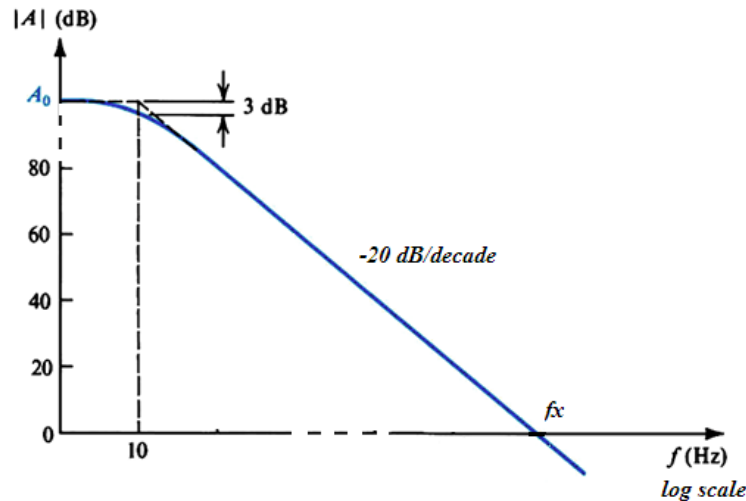- (a) 1      (b) 10      (c) 100      (d) 1000      (e) 10,000



----

19. What is the maximum frequency (in MHz) of a sinusoidal signal with a 1 V amplitude to be differentiated by an OP-AMP differentiator circuit *without slew-rate distortion*? The slew-rate specification of the OP-AMP is  $10 \text{ V}/\mu\text{s}$  and the differentiator time constant is  $8 \text{ ns}$ .

- (a) 4.2      (b) 3.8      (c) 7.1      (d) 5.6      (e) 5.0


----

Assume that the OP-AMP in the circuit shown below is ideal.

Assume also that the MOSFET is in saturation, with small-signal parameters

$g_m = 1 \text{ mA/V}$ ,  $r_o = 50 \text{ K}\Omega$ .

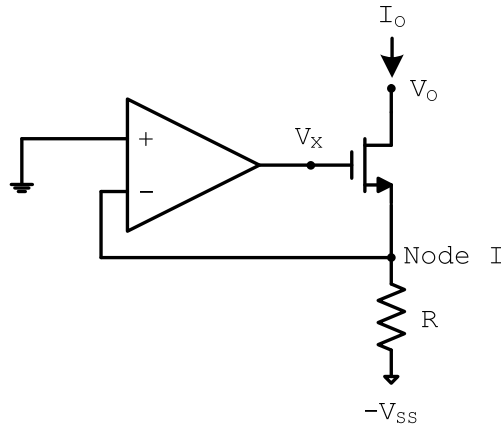The negative supply is  $-V_{SS} = -2 \text{ V}$  and  $R = 20 \text{ K}\Omega$ .



20. Find the output current  $I_O$  in  $\mu\text{A}$ .  
 (a) 100 (b) 50 (c) 400 (d) 300 (e) 200
21. Find the change in the output current (in  $\mu\text{A}$ ) when the output voltage increases by +1V.  
 (a) 50 (b) 0 (c) 20 (d) 0.93 (e) 1
22. A resistor  $R_X$  equal to  $10\text{ K}\Omega$  is now inserted between the source terminal of the MOSFET and Node I. Find the voltage  $V_X$  (in V) at the output of the OP-AMP if the MOSFET threshold voltage is 0.7 V.  
 (a) 1.3 (b) 1.9 (c) 3.1 (d) 5.5 (e) 4.3
23.  $R_X$  is now removed. Find the change in the output current (in nA) when the output voltage increases by +1V if the OP-AMP has a *finite open-loop gain* of 250.  
 (a) 4 (b) 9.9 (c) 6.6 (d) 5 (e) 3.3

----

Two amplifiers are cascaded. The first amplifier has an input resistance of  $10\text{ K}\Omega$ , an output resistance of  $10\text{ K}\Omega$ , and an *open-circuit* voltage gain function of  $\frac{90}{1+s/10^5}$ . The second amplifier has an input resistance of  $20\text{ K}\Omega$ , an output resistance of  $5\text{ K}\Omega$ , and an *open-circuit* voltage gain function of  $\frac{60}{1+s/3 \times 10^5}$ .


24. Find the overall low-frequency voltage gain of the cascade when a load resistor of  $10\text{ K}\Omega$  is connected at the output of the second stage.  
 (a) 1600 (b) 2000 (c) 3200 (d) 2800 (e) 2400
25. Find the overall upper 3 dB frequency  $f_H$  (in KHz).  
 (a) 14.5 (b) 13.3 (c) 15.9 (d) 47.7 (e) 31.8

----

In the cascode amplifier shown below, all MOSFETs have  $(W/L) = 100$  and are biased at a drain current of 0.3 mA.

The MOSFET parameters are:
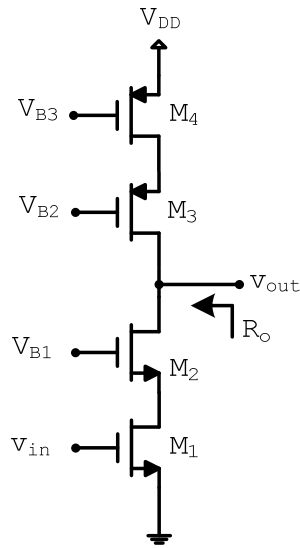
$$k_n' = 0.2\text{ mA/V}^2, V_{tn} = 0.5\text{ V}, \lambda_n = 0.1\text{ V}^{-1}, k_p' = 0.1\text{ mA/V}^2, V_{tp} = -0.6\text{ V}, \lambda_p = 0.2\text{ V}^{-1}.$$



26. Find the required DC bias level in  $v_{IN}$  (in V).

- (a) 0.765 (b) 0.673 (c) 0.700 (d) 0.724 (e) 0.745

27. Find the output resistance  $R_O$  (in  $K\Omega$ ).

- (a) 217.2 (b) 284.0 (c) 173.1 (d) 603.7 (e) 394.7


28. The high-frequency response of the amplifier is governed by a load capacitance, connected from the output node to ground. What is the maximum value of this load capacitance (in pF) to have an upper 3-dB frequency of 100 KHz?

- (a) 2.64 (b) 4.03 (c) 5.60 (d) 7.33 (e) 9.19

----

29. Assume that the OP-AMP is ideal in the circuit shown below. The resistors shown in the circuit are  $R_1 = 10 K\Omega$ ,  $R_2 = 50 K\Omega$ , and  $R_3 = 10 K\Omega$ . Find the voltage gain  $v_{out}/v_{in}$ .

- (a) 5 (b) 6 (c) 3 (d) 21 (e) 11

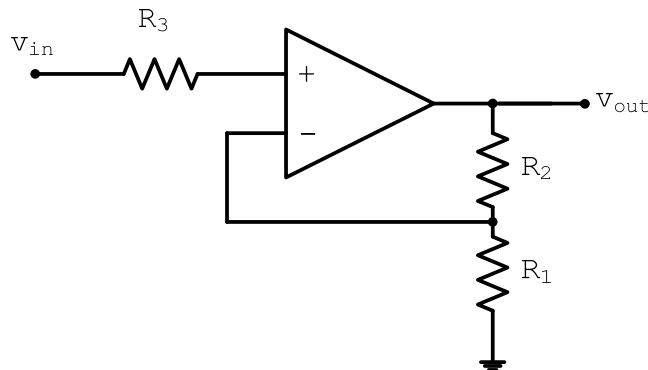

30. Assume now that the OP-AMP specifications show an input bias current of 150 nA, and that the input current flowing into the non-inverting input is two times larger than the current flowing into the inverting input. What DC output voltage (in mV) results due to the input bias current, only (the input  $v_{in}$  is zero in this case)?

- (a) -1 (b) -5 (c) -37 (d) -17 (e) -7

----