

**American University of Beirut**  
 Department of Electrical and Computer Engineering  
**EECE 311 – Electronic Circuits**  
**Summer 2008**  
**Midterm – July 22, 2008**  
**Open Book – 90 minutes**

NAME: \_\_\_\_\_ **Solution** \_\_\_\_\_ ID Number: \_\_\_\_\_

**Problem 1 [30 points]**

Consider the current mirror shown in Figure 1. The MOSFET parameters are  $k' = 220 \mu\text{A}/\text{V}^2$ ,  $V_t = 0.5 \text{ V}$ ,  $V_A' = 20 \text{ V}/\mu\text{m}$ , and  $(W/L)_1 = 10\mu\text{m} / 0.25\mu\text{m}$ . Assume that the DC drain current of a MOSFET in SAT is given by  $I_D \approx \frac{1}{2} k' \left(\frac{W}{L}\right) V_{ov}^2$ .

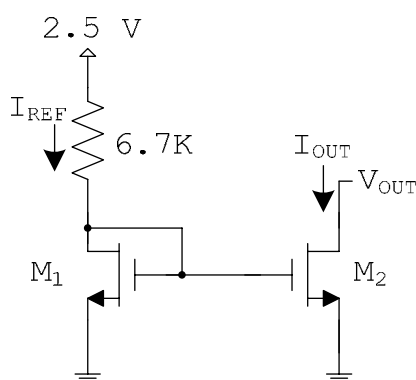


Figure 1

a) [6 points] Find the value of the reference current  $I_{REF}$ .

$$I_{REF} = (V_{DD} - V_{DS})/R = (V_{DD} - V_{GS})/R = (2.5 - x)/6.7\text{K} \quad \text{where } x = V_{GS}$$

$$\text{Also: } I_{REF} = \frac{1}{2} k' (W/L) (V_{GS} - V_t)^2 = \frac{1}{2} (220\text{e-}6) (10/0.25) (V_{GS} - 0.5)^2 \Rightarrow$$

$$0.5(220\text{e-}6)(10/0.25)(x - 0.5)^2 = (2.5 - x)/10\text{K}$$

$$\text{Solve to get: } x = V_{GS} = 0.744 \text{ V} \Rightarrow I_{REF} = 262 \mu\text{A}$$

b) The output current should nominally be equal to  $I_{REF}$ . It is also specified that the output current  $I_{OUT}$  should not change by more than +3% when the output voltage  $V_{OUT}$  changes by +1 V.

i) [6 points] What should be the output resistance of the current mirror?

$$I_{OUT} = 262 \mu\text{A}. \text{ A change of 3\% is therefore } \Delta I_{OUT} = 7.86 \mu\text{A} \text{ for } \Delta V_{OUT} = 1\text{V}.$$

$$\text{The output resistance is } \Delta V_{OUT}/\Delta I_{OUT} = 1/7.86 \mu\text{A} = 127.2 \text{ K}\Omega.$$

ii) [6 points] Determine the values of  $W$  and  $L$  for  $M_2$ .

$$R_{out} = r_{o2} = V_{A2}/I_{D2} = V_{A2}/262\mu\text{A} = 127.2 \text{ K} \Rightarrow V_{A2} = 33.33 \text{ V}.$$

$$L_2 = V_{A2}/V_A' = 33.33/20 = 1.666 \mu\text{m}.$$

$$W_2/L_2 = 10/0.25 \Rightarrow W_2 = 10/0.25 \times 1.666 = 66.65 \mu\text{m}.$$

c) A resistor  $R_P$  is now inserted between the source terminal of M2 and ground, in order to make the value of the output current  $I_{OUT} = I_{REF}/10$ .

i) [6 points] Find  $R_P$ .

$$I_{OUT} = 26.2 \mu\text{A} = I_{D2}.$$

$$V_{GS1} = 0.744 \text{ V}$$

$$I_{D2} = \frac{1}{2}(220\text{e-}6)(40)(V_{GS2} - 0.5)^2 \Rightarrow V_{GS2} = 0.5772 \text{ V}$$

$$V_{GS1} - V_{GS2} = I_{OUT} \times R_P \Rightarrow$$

$$R_P = (0.744 - 0.5772)/26.2\mu = 6.366 \text{ K}$$

ii) [6 points] Find the new change in  $I_O$  (as a *percentage*) when  $V_{OUT}$  changes by +1 V.

Output resistance is  $r_{o2} + R_P + g_{m2} r_{o2} R_P$

$$r_{o2} = V_{A2}/I_{OUT} = 33.33/26.2\mu = 1272.1 \text{ K}$$

$$g_{m2} = I_{OUT}/(0.5(V_{GS2} - V_t)) = 26.2\mu / (0.5(0.5772 - 0.5)) = 0.6788 \text{ mA/V}$$

Output resistance =  $r_{o2} + R_P + g_{m2} r_{o2} R_P =$

$$1272.1 \text{ K} + 6.366 \text{ K} + 0.6788 \text{ m} \times 6.366 \text{ K} \times 1272.1 \text{ K} = 6775.5 \text{ K}$$

$$\Delta I_{OUT} = \Delta V_{OUT}/R_{out} = 1/6775.5\text{K} = 0.1476 \mu\text{A}$$

As a percentage this is:  $0.1476/26.2 = 0.56\%$

## Problem 2 [30 points]

The BJT shown in the amplifier circuit of Figure 3 is biased such that  $g_m = 40 \text{ mA/V}$ ,  $r_\pi = 4 \text{ K}\Omega$ , and  $r_o = 15 \text{ K}\Omega$ . The resistance values are  $R_B = 10 \text{ K}\Omega$ ,  $R_C = 5 \text{ K}\Omega$ , and  $R_{sig} = 20 \text{ K}\Omega$ .

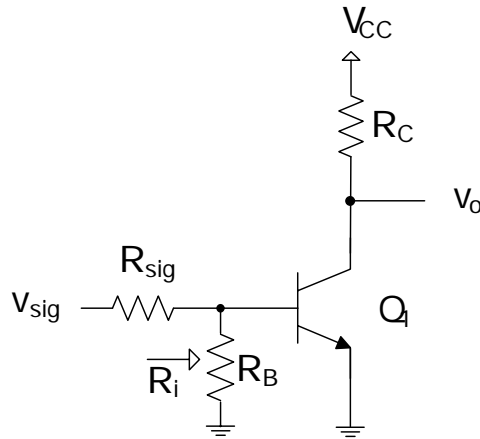


Figure 3

a) Find input resistance  $R_i$ , as shown in the figure.

$$R_i = R_B // r_\pi = 10 // 4 = 2.857 \text{ K}\Omega.$$

b) Find the output resistance. Assume that all elements of the circuit are an internal part of the amplifier.

$$R_o = R_C // r_o = 5 // 15 = 3.75 \text{ K}\Omega.$$

c) Find the voltage gain  $v_o/v_{sig}$ .

$$v_o/v_{sig} = (v_o/v_b) (v_b/v_{sig}) = -g_m R'_L (R_i/(R_i + R_{sig})) = -g_m (r_o // R_C) (R_i/(R_i + R_{sig}))$$

$$\Rightarrow v_o/v_{sig} = -40(3.75)(2.857/22.857) = -18.75 \text{ V/V}$$

Assume in the following that for the BJT,  $C_\pi = 20 \text{ fF}$ ,  $C_\mu = 10 \text{ fF}$ , and that a load capacitor  $C_L = 50 \text{ fF}$  is connected from the output node to ground.

d) Using Miller's theorem, and assuming that the input circuit determines the upper 3-dB frequency  $f_H$ , find the value of  $f_H$ .

$$\text{Miller's constant } K = -g_m R'_L = -g_m (r_o // R_C) = -40(3.75) = -150$$

$$C_{in} = C_\pi + (1 - K)C_\mu = 20 + (151)10 = 1530 \text{ fF}$$


$$R_{in} = R_B // r_\pi // R_{sig} = 10 // 4 // 20 = 2.5 \text{ K}$$

$$f_H = 1/(2\pi R_{in} C_{in}) = 1/(2\pi \times 2.5 \text{ K} \times 1530 \text{ fF}) = 41.6 \text{ MHz}$$

e) Based on the results of (c) and (d), show and *label* the Bode plot for the magnitude of the voltage gain ( $v_o/v_{sig}$ ).

$$G = 20 \log|A_M| = 20 \log(18.75) = 25.5 \text{ dB}$$

$$f_H = 41.6 \text{ MHz}$$

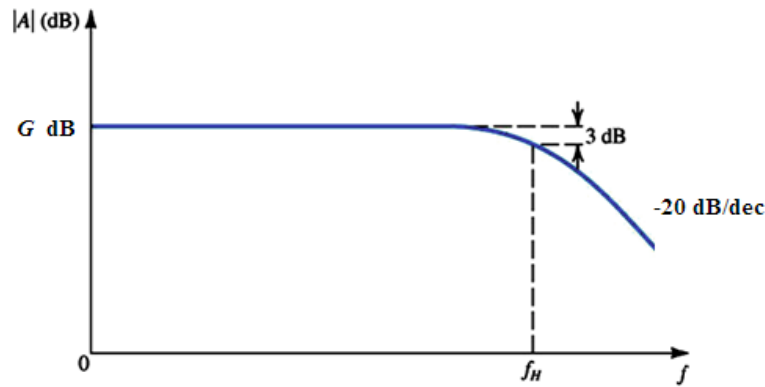

f) Using the open-circuit time constants methods, find the resistance seen by each capacitor, and estimate the value of  $f_H$ .

$$R_{\pi} = R_B // r_{\pi} // R_{sig} = 2.5 \text{ K}$$

$$R_{CL} = R_o = 3.75 \text{ K}$$

$$R_{\mu} = R_{\pi} + R_o + g_m R_{\pi} R_o = 381.25 \text{ K}$$

$$f_H = 1/(2\pi(C_{\pi} R_{\pi} + C_L R_{CL} + C_{\mu} R_{\mu})) = 39.3 \text{ MHz}$$

### Problem 3 [20 points]

a) [12 points] Design a non-inverting opamp amplifier for the following specifications:

Voltage gain = 5, gain error = 1%, bandwidth = 10 MHz.

Determine the *ratio* of the two resistors in the circuit, the opamp open-loop gain  $A_M$ , and the opamp unity-gain frequency  $f_t$ .

$$\text{Gain} = (1 + R_2/R_1)/(1 + (1 + R_2/R_1)/A_M)$$

$$\text{Nominal gain is } (1 + R_2/R_1) \Rightarrow R_2/R_1 = 4$$

$$\text{Error} = (1 + R_2/R_1)/A_M = 5/A_M = 0.01 \Rightarrow A_M = 500$$

Bandwidth is  $f_b$ . Gain-bandwidth product is approximately fixed

$$\Rightarrow 5 f_b = A_M f_t \Rightarrow f_t = 50 \text{ MHz} / 500 = 0.1 \text{ MHz}$$

b) [8 points] What is the largest peak-to-peak sinusoidal swing at the input of an opamp integrator with an integrator time constant of 16 nsec, that produces an output free from slewing? The slew rate of the opamp is 0.1 V/nsec.

Hint: find  $\left. \frac{dv_{out}}{dt} \right|_{\max}$  when the input is  $V_p \sin(\omega t)$ .

$$v_{out} = 1/(RC) \int v_i dt \Rightarrow v_{out} = V_p/\omega RC \cos(\omega t)$$

$$dv_{out}/dt = -V_p/RC \sin(\omega t)$$

the maximum value is  $V_p/RC$ ; this should be  $\leq$  slew\_rate

$$\text{Therefore } V_p = RC \times \text{slew\_rate} = 16 \text{ nsec} \times 0.1 \text{ V/nsec} = 1.6 \text{ V}$$

The maximum peak-to-peak input is therefore  $2 \times 1.6 = 3.2 \text{ V}$

#### Problem 4 [20 points]

Design the source follower of Figure 2 (determine  $R_S$  and  $W/L$ ) for a power budget of 1 mW and a voltage gain  $v_{out}/v_{in}$  of 0.9 when  $R_L = 10 \text{ K}$ .

The MOSFET parameters are  $k' = 220 \mu\text{A}/\text{V}^2$ ,  $V_t = 0.5 \text{ V}$ , and  $V_A = 5 \text{ V}$ .

Assume that the DC drain current of a MOSFET in SAT is given by  $I_D \approx \frac{1}{2} k' \left( \frac{W}{L} \right) V_{OV}^2$ , and that all capacitors are very large.

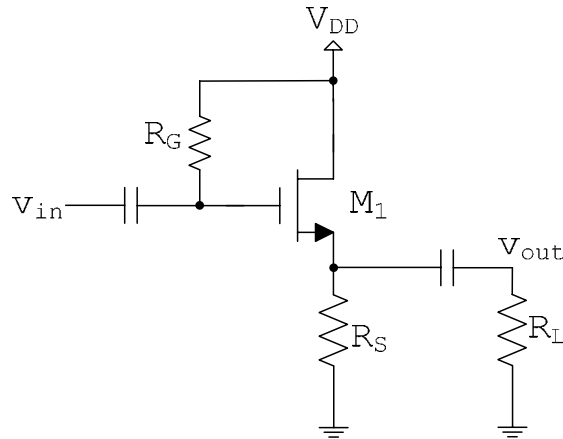


Figure 3

$$V_{DD} = 2.5 \text{ V}$$

$$I_D = 1 \text{ mW} / 2.5 \text{ V} = 0.4 \text{ mA}$$

$$r_o = V_A / I_D = 5 / 0.4 = 12.5 \text{ K}$$

$$2 I_D / V_{OV} = g_m \Rightarrow V_{OV} = 2 I_D / g_m$$

$$\text{Gain} = v_{out} / v_{in} = R' / (1/g_m + R') \quad \text{where} \quad R' = R_S // r_o // R_L$$

$$\Rightarrow 0.9 = R' / (1/g_m + R') \Rightarrow g_m = 9/R'$$

Solve by iterations with an initial guess of  $V_{OV} = 0.2 \text{ V}$ .

Find

$$V_{GS} = V_{OV} + V_t;$$

$$V_S = V_G - V_{GS} = V_{DD} - V_{GS};$$

$$R_S = V_S / I_D;$$

$$R' = R_S // r_o // R_L;$$

$$g_m = 9/R';$$

$$V_{OV} = 2 I_D / g_m;$$

Repeat above steps until convergence.

VOV	VGS	VS	RS	R'	gm
0.2000	0.7000	1.8000	4500.0000	2486.1878	0.00362
0.2210	0.7210	1.7790	4447.5138	2470.0828	0.00364
0.2196	0.7196	1.7804	4451.0927	2471.1864	0.00364
0.2197	0.7197	1.7803	4450.8475	2471.1108	0.00364

W/L is calculated from the current equation:

$$I_D = \frac{1}{2}k' (W/L)V_{OV}^2 \Rightarrow (W/L) = 2I_D / (k' V_{OV}^2) = 2 \times 0.4\text{e-}3 / (220\text{e-}6 \times 0.2197^2)$$

$$\Rightarrow (W/L) = 75.3$$