

## American University of Beirut

DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

EECE 311 – Electronic Circuits (Sections 1 & 2)


Spring 2008

### HOMEWORK 2

Due Wednesday March 12, 2008 at 1:00 PM
 
#### 1. Common Source Amplifier

The common-source stage shown below must provide a voltage gain of 10 and has a power budget of 1 mW.




The technology parameters are:  $k'_n = 300 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = 0.45 \text{ V}$ ,  $V_{An} = 5 \text{ V}$ ,  $k'_p = 100 \mu\text{A}/\text{V}^2$ ,  $V_{tp} = -0.5 \text{ V}$ , and  $|V_{Ap}| = 4 \text{ V}$ .

Assume in the following that for the DC quantities:  $I_D \approx \frac{1}{2} k' \left( \frac{W}{L} \right) V_{OV}^2$ .

- Find the value of  $(W/L)_1$
- Find the required value of  $V_{BIAS}$  if  $(W/L)_2$  is  $(20/0.18)$ .

 
#### 2. Common Gate Amplifier

Design the common-gate stage shown below for an input impedance of  $50 \Omega$  and voltage gain of 5. Assume a power budget of 2 mW. You should determine the aspect ratio  $(W/L)$  for the MOSFET, the value of  $R_D$  and the value of the current source  $I_1$ . The technology parameters are:  $k'_n = 300 \mu\text{A}/\text{V}^2$  and  $V_{tn} = 0.45 \text{ V}$ . Neglect channel-length modulation.


 
### 3. Emitter Follower


Design the emitter-follower circuit shown below for a power budget of 3 mW and an output impedance of 50  $\Omega$ . Neglect base width modulation, and assume that  $\beta \rightarrow \infty$ . Determine that value of  $I_{REF}$  and the value of the ratio  $A_{EI}/A_{E-REF}$ .


 
### 4. MOSFET Cascode

For the cascode circuit shown below, assume  $(W/L) = 10 \mu\text{m}/0.18 \mu\text{m}$  for all MOSFETs, and that  $V_{BIAS} = 0.9 \text{ V}$ . Use PSpice to plot the input-output characteristics ( $v_o$  versus  $v_i$ ). Note that the body terminals are connected to the supplies (ground for NMOS and  $V_{DD}$  for PMOS.) Determine from the plot the point at which the small-signal gain is maximum, in absolute value.


Now suppose the biasing circuitry that produces the above DC value of  $v_i$  incurs an error of  $\pm 20 \text{ mV}$ . Explain what happens to the voltage gain.



Use the SPICE models posted on Moodle.

 
### 5. Miller's Theorem

Use Miller's theorem to estimate the input and output poles of the circuit shown below. Neglect base-width modulation and the internal BJT capacitors.


 
## 6. Active Inductor

The circuit shown below is called an active inductor. Neglecting all other capacitances, and channel-length modulation, compute the input impedance  $Z_{in}$ . Use Bode's rules to plot the magnitude of  $Z_{in}$  and explain how it exhibits inductive behavior.



## 7. Cascode Frequency Response

We wish to design the cascode circuit shown below for an input pole frequency of 5 GHz and an output pole frequency of 10 GHz. Assume  $Q_1$  and  $Q_2$  are identical,  $I_D = 0.5$  mA,  $C_{GS} = \frac{2}{3} W \times L \times C_{ox}$ ,  $C_{ox} = 12$  fF/ $\mu\text{m}^2$ ,  $\mu_n C_{ox} = 100$   $\mu\text{A}/\text{V}^2$ ,  $\lambda = 0$ ,  $L = 0.18$   $\mu\text{m}$ ,  $C_{GD} = C_0 \times W$ , where  $C_0 = 0.2$  fF/ $\mu\text{m}$ . Determine the maximum allowable values of  $R_{sig}$  and  $R_D$ , and the voltage gain. Use Miller's approximation for  $C_{GD}$ . Assume an overdrive voltage of 200 mV for each MOSFET.

