

American University of Beirut

DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

EECE 311 – Electronic Circuits (Sections 1 & 2)


Spring 2008

HOMEWORK 4

Due Wednesday April 7, 2008 at 1:00 PM

Problem 1.


Calculate the differential voltage gain $v_{out}/(v_{in1}-v_{in2})$ in the circuit shown below. Assume perfect symmetry, but do *not* neglect channel length modulation. *Hint:* Use the half-circuit technique.

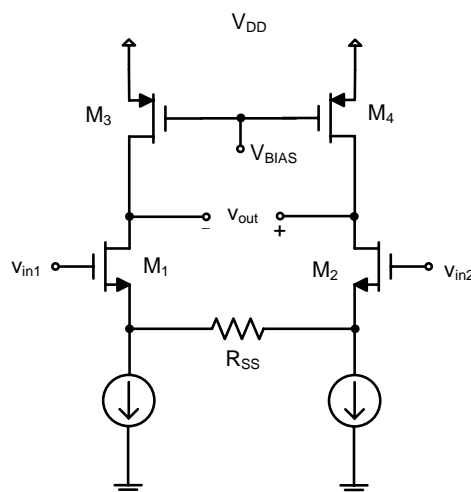

Problem 2.

The circuit shown below should provide a differential gain of 100 V/V at a power budget of 1 mW. Assume $V_{A,n} = 6$ V, $V_{CC} = 2.5$ V, and very large β .

- Find the bias current I_{EE} .
- Estimate g_{mN} and r_{oN} .
- Calculate r_{oP} and estimate $V_{A,p}$.
- Estimate the input bias current if β_N is 200.
- Estimate the input offset current if β_N is matched to within $\pm 2\%$.

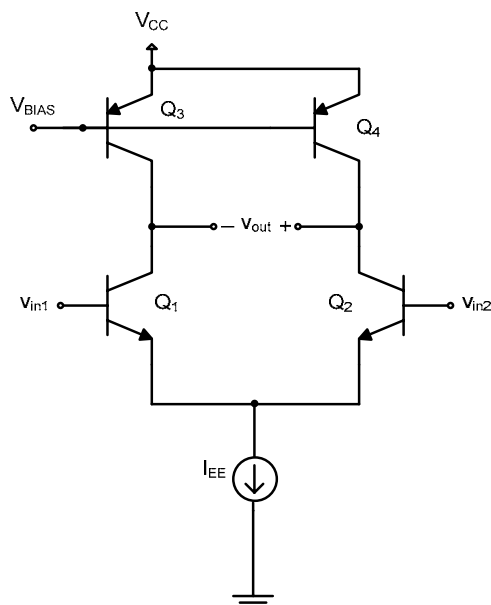

Problem 3.

Design the MOS differential amplifier shown in Figure 7.1 in the textbook for a differential voltage gain of 5 V/V and a power dissipation of 1 mW if the overdrive voltage must be at least 150 mV.

Assume $k'_n = 100 \mu\text{A}/\text{V}^2$ and $V_{DD} = 1.8 \text{ V}$. Neglect channel length modulation.


Find the values of I , R_D , and (W/L) for the MOSFETs.

Problem 4.

The differential amplifier shown below must provide a differential gain of 40 V/V. Assume that all transistors have the same overdrive voltage, and a circuit power budget of 2 mW. Also assume that

$V_{A,n} = 10 \text{ V}$, $V_{A,p} = 5 \text{ V}$, $k'_n = 100 \mu\text{A}/\text{V}^2$, $k'_p = 50 \mu\text{A}/\text{V}^2$, and $V_{DD} = 1.8 \text{ V}$.

- Design the circuit by calculating the current I_{SS} , the overdrive voltage, and the (W/L) ratios of all MOSFETs.
- Find the CMRR of the amplifier when the output is single-ended.

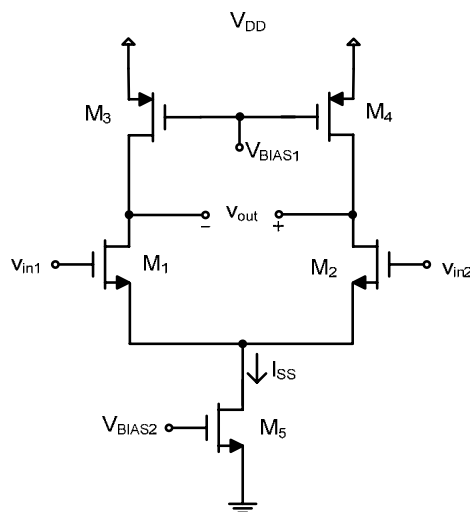

Problem 5.

Design the *telescopic* cascode amplifier shown below, for a differential voltage gain of 600 V/V with a power budget of 4 mW. Assume an overdrive voltage of 100 mV for the NMOS devices and 150 mV for the PMOS devices. Using $V_{A,n} = 10 \text{ V}$, $k'_n = 100 \mu\text{A}/\text{V}^2$, $k'_p = 50 \mu\text{A}/\text{V}^2$, and $V_{DD} = 1.8 \text{ V}$, determine the required value of $V_{A,p}$. Determine (W/L) for MOSFETs M_1 to M_8 . Assume that $M_1 - M_4$ are identical, and so are $M_5 - M_8$.

