

### Homework 3 Solution

#### Problem 1

a - Find the value of  $V_{SG}$  for  $Q_3$ .

$$I_{Ref} = \frac{1}{2} K_p' \left(\frac{W}{L}\right)_p (V_{SG} - V_{tp})^2 (1 + |V_A| V_A)$$

$$\Rightarrow 15 \mu A = \frac{1}{2} \times 100 \mu A \times 10 (V_{SG} - 0,5)^2 (1 + 0,35 V_{SG})$$

$$\Rightarrow 0,35 V_{SG}^3 + 0,65 V_{SG}^2 - 0,9125 V_{SG} + 0,22 = 0$$

$$\Rightarrow \boxed{V_{SG} = 0,656 V}$$

b - Find  $I_{D_2}$  when  $V_o = \frac{V_{DD}}{2}$

$$I_{D_2} = \frac{1}{2} K_p' \left(\frac{W}{L}\right)_p (V_{SG_2} - V_{tp})^2 (1 + 0,35 V_{SG_2})$$

$$V_o = \frac{V_{DD}}{2} = 0,9 V$$

$$V_{SG_2} = V_s - V_{D_2} = V_{DD} - V_o = 0,9 V$$

$$V_{SG_2} = V_{SG_3} = 0,656 V$$

$$I_{D_2} = \frac{1}{2} \times 100 \mu A \times 10 \times (0,656 - 0,5)^2 (1 + 0,35 \times 0,9)$$

$$\Rightarrow \boxed{I_{D_2} = 16 \mu A}$$

c -  $V_{Sig} = 0$  ;  $V_o = \frac{V_{DD}}{2} = 0,9 V$

$$I_{D_2} = 16 \mu A = I_{D_1}$$

$$I_{D_1} = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_n (V_{GS} - V_t)^2 (1 + 0,4 V_{DS})$$

$$V_{GS} = V_{Bias} - V_s$$

$$V_s = R_s \cdot I_{D_1} = 50 \times 16 \cdot 10^{-6} = 8 \cdot 10^{-4} V$$

$$V_{DS} = V_D - V_s = V_o - V_s = 0,9 - 8 \cdot 10^{-4} = 0,8992 V$$

$$16 \mu A = \frac{1}{2} \times 350 \mu A \times 2 \times (V_{GS} - 0,45)^2 (1 + 0,4 \times 0,8992)$$

$$\Rightarrow V_{GS} = 0,6334 V$$

$$V_{Bias} - V_s = V_{GS} = 0,6334 V$$

$$\Rightarrow V_{Bias} = 0,6334 + 8 \cdot 10^{-4} \Rightarrow \boxed{V_{Bias} = 0,6342 V}$$

d - Find the values of  $g_{m1}$ ,  $r_{o1}$ ,  $r_{o2}$ ,  $R_{in}$  and  $R_{out}$

$$g_{m1} = \frac{2ID_1}{V_{ov}} = \frac{2 \times 16 \mu}{V_{as} - V_t} = \frac{2 \times 16 \mu}{0,6334 - 0,45} = 1744 \text{ mA/V}$$

$$r_{o1} = \frac{V_A + V_{DS}}{I_{D1}} = \frac{1/2 + 0,8992}{16 \mu} = 212,45 \text{ k}\Omega$$

$$r_{o2} = \frac{V_A + V_{SD2}}{I_{D2}} = \frac{1/2 + 0,35 + 0,3}{16 \mu} = 234,82 \text{ k}\Omega$$

$$R_{in} = \frac{V_i}{i_i} = \frac{r_{o1} + R_L}{1 + (g_{m1} + g_{m2}) r_{o2}} = \frac{r_{o1} + r_{o2}}{1 + g_{m1} (1 + g_{m2}) r_{o2}}$$

$$\Rightarrow R_{in} = \frac{212,45 + 234,82}{1 + (0,174 + 0,2 \times 0,174) \times 212,45} = 9,882 \text{ k}\Omega$$

$$R_{out} = r_{o1} + (1 + g_{m1} (1 + g_{m2}) r_{o2}) \cdot R_S$$

$$R_{out} = 212,45 \left( 1 + (0,174 + 0,2 \times 0,174) \times 212,45 \right) \times 50 \cdot 10^{-3}$$

$$\boxed{R_{out} = 214,71 \text{ k}\Omega}$$

e - Find  $\frac{V_o}{V_{sig}}$

$$G_V = \frac{V_o}{V_{sig}} = (1 + g_{m2} (1 + g_{m1}) r_{o2}) \cdot \frac{r_{o2}}{r_{o1} + r_{o2}} \times \frac{R_{in}}{R_{in} + R_S} = 23,77 \text{ V/V}$$

f - Q<sub>2</sub> saturated if:  $V_{SDP} \geq V_{SGP} - |V_{tp}|$

$$V_{SDP} \geq 0,656 - 0,5$$

$$V_{SDP} \geq 0,156 \text{ V}$$

$$V_{DD} - V_{DP} \geq 0,156 \text{ V}$$

$$V_{DD} - V_o \geq 0,156$$

$$V_o \leq 1,8 - 0,156$$

$$V_o \leq 1,644 \text{ V}$$

Q<sub>2</sub> is saturated if:  $V_{DS} \geq V_{as} - V_{tn}$

$$V_{DS} \geq 0,6334 - 0,45$$

$$V_{DS} \geq 0,1834$$

$$V_o - V_s \geq 0,1834$$

$$V_o - 16 \mu \times 50 \geq 0,1835$$

$$V_o \geq 0,1843 \text{ V}$$

$$V_o \text{ peak-to-peak} = 1,644 - 0,1843 = 1,4597 \text{ V}$$

$$V_{sig} \text{ peak-to-peak} = V_{peak} - V_{peak} = 1,4597 / 23,64 = 61,747 \text{ mV}$$

g - Scan it from Rami Fatayri's Homework

$$h - f_{P1} = \frac{1}{2\pi(C_{gs} + C_{sb})(R_s \parallel \frac{1}{g_m + g_{mb}})}$$

$$f_{P1} = \frac{1}{2\pi(25+10) \cdot 10^{-15} (50 \parallel \frac{1}{0,174(1+0,2) \cdot 10^{-3}})} = 3,9 \cdot 10^{11} \text{ Hz} = 390 \text{ GHz}$$

$$f_{P2} = \frac{1}{2\pi(C_L + C_{gd} + C_{db})(R_L \parallel R_{out})} = \frac{1}{2\pi(50+5+10) \cdot 10^{-15} (234,82 \parallel 214,7)}$$

$$f_{P2} = 21,831 \text{ MHz}$$


$$f_H = \frac{1}{2\pi(R_2(C_{gs} + C_{sb}) + R_2(C_{gd} + C_{db} + C_L))}$$

$$R_2 = R_{in} \parallel R_s = 9,882 \parallel 0,05 = 49,74 \Omega$$


$$R_2 = R_{out} \parallel R_L = 234,82 \parallel 214,7 \text{ K} = 112,154 \text{ K} \cdot \Omega$$

$$\Rightarrow f_H = 21,326 \text{ MHz}$$

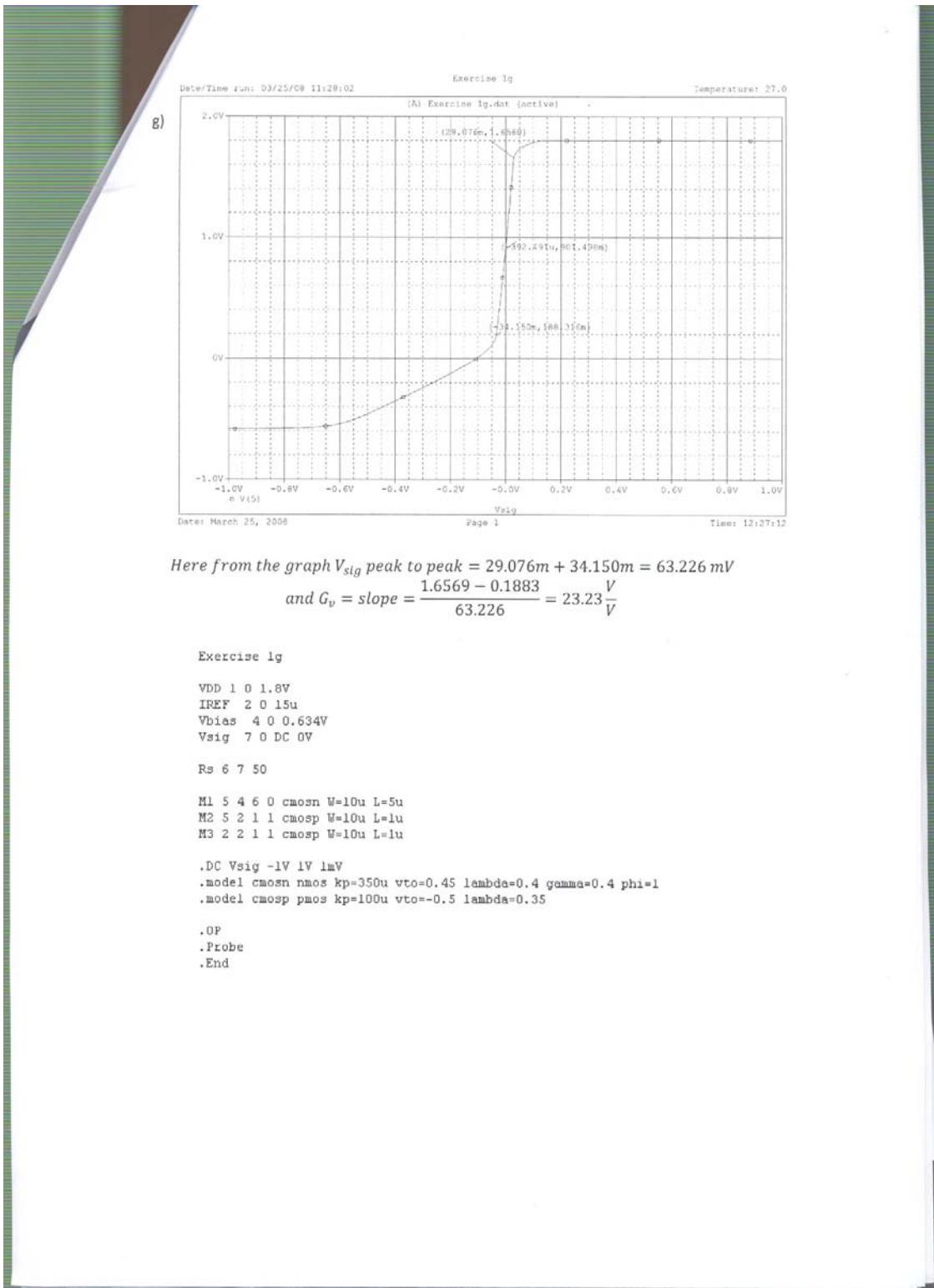i - Scan it from Rami Fatayri's Homework.



i)

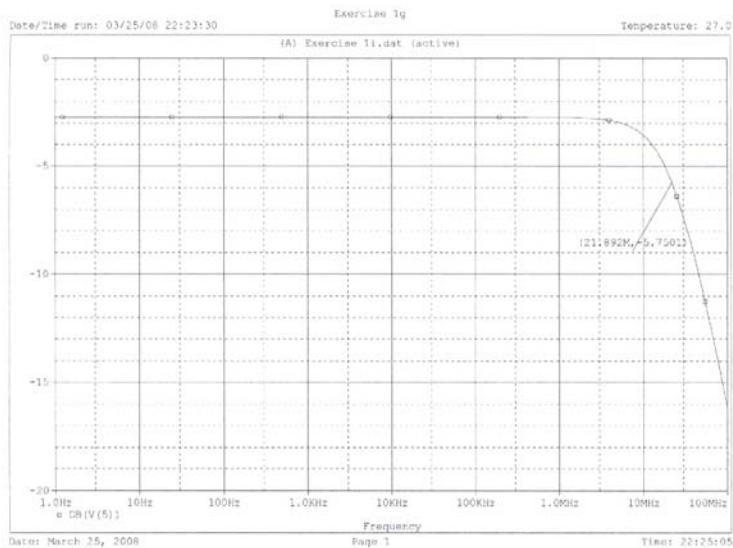

The 3db frequency from the bode plot is 21.892 MHz which is really close to the one we calculated which is 21.84 MHz.

#### Exercise 1i

```
VDD 1 0 1.8V
IREF 2 0 15u
Vbias 4 0 0.634V
Vsig 7 0 AC 30.71mV


Rs 6 7 50
Cgs 4 6 25f
Ugd 4 5 5f
Cdb 5 0 10f
Csb 6 0 10f
CL 5 0 50f

M1 5 4 6 0 cmosn W=10u L=5u
M2 5 2 1 1 cmosp W=10u L=lu
M3 2 2 1 1 cmosp W=10u L=lu

.AC DEC 10 1 1e8
.model cmosn nmos kp=350u vto=0.45 lambda=0.4 gamma=0.4 phi=1
.model cmosp pmos kp=100u vto=-0.5 lambda=0.35

.OP
.Probe
.End
```

Praktikum 2.

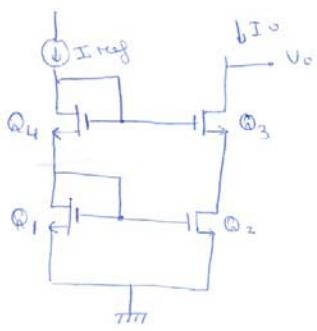

$$\begin{aligned}I_{REF} &= 10 \mu A \\V_o &= 2,5 V \\K_n^2 \frac{W}{L} &= 1 \text{ mA/V}^2 \\V_t &= 0,5 V \\V_A &= 10 V\end{aligned}$$

$$\begin{aligned}\Rightarrow I_{REF} &= I_{D4} = \frac{1}{2} K_n^2 \frac{W}{L} (V_{GS4} - V_t)^2 \left(1 + \frac{V_{GS4}}{V_A}\right) \\&\Rightarrow 10 \mu A = \frac{1}{2} \times 1 \text{ mA/V}^2 (V_{GS4} - 0,5 V)^2 \left(1 + \frac{V_{GS4}}{10}\right) \\&\Rightarrow 10^{-2} = \frac{1}{2} (V_{GS4} - 0,5)^2 \left(1 + \frac{V_{GS4}}{10}\right) \\&\Rightarrow \frac{V_{GS4}^3}{10} + \frac{9}{10} V_{GS4}^2 - 0,975 V_{GS4} + 0,23 = 0\end{aligned}$$

$$\Rightarrow V_{GS4} = 0,6371 V > V_t = 0,5 V \Rightarrow \text{accepted}$$

$$V_{GS4} = 0,361 V < V_t \Rightarrow \text{rejected}$$

$$V_{GS4} = -0,998 < V_t \Rightarrow \text{Rejected}$$

$$\Rightarrow \boxed{V_{GS4} = 0,6371 V}$$

$$\bullet I_{REF} = I_{D2} = I_{D3}$$

$$\Rightarrow \frac{1}{2} K_n^2 \frac{W}{L} (V_{GS2} - V_t)^2 \left(1 + \frac{V_{DS2}}{V_A}\right) = \frac{1}{2} K_n^2 \frac{W}{L} (V_{GS3} - V_t)^2 \left(1 + \frac{V_{DS3}}{V_A}\right)$$

$$V_{GS2} = V_{GS1} = V_{GS4} = 0,6371$$

$$V_{GS3} = V_0 - V_{S3} = V_{GS4} + V_{GS1} - V_{S3} = 2 \times 0,6371 - V_{DS2}$$

$$\Rightarrow V_{GS3} = 1,2742 - V_{DS2}$$

$$V_{GS3} = V_0 - V_{DS2} = 2,5 - V_{DS2}$$

Replacing

$$\gamma_2 \frac{W}{L} \left( V_{DS1} - V_t \right)^2 \left( 1 + \frac{V_{DS2}}{V_A} \right)$$

$$\Rightarrow -0,1 V_{DS2}^3 + 1,4084 V_{DS2}^2 - 1,997317 V_{DS2} + 0,730435 = 0$$

$$\Rightarrow V_{DS2} = 0,6492 \text{ V} \Rightarrow V_{DS3} = 0,625 > V_t \text{ (accepted)}$$

$$V_{DS2} = 0,8974 \text{ V} \Rightarrow V_{DS3} = 0,3768 < V_t \text{ (neglected)}$$

$$V_{DS2} = 1,537 \text{ V} \Rightarrow V_{DS3} = -1,962 < V_t \text{ (neglected)}$$

$$\Rightarrow \boxed{V_{DS2} = 0,6492}$$

$$I_o = \gamma_2 \frac{W}{L} \frac{w}{2} \left( V_{DS1} - V_t \right)^2 \left( 1 + \frac{V_{DS2}}{V_A} \right)$$

$$\Rightarrow \boxed{I_o = 10,0083 \mu\text{A}}$$

Output resistance

$$g_{m3} = \frac{\partial I_o}{\partial V_{out}} = \frac{\partial I_o}{\partial V_{DS3} - V_t} = 160,13 \mu\text{A/V}$$

$$R_{o3} = \frac{V_A + V_{DS3}}{I_o} = 1184 \text{ k}\Omega$$

$$R_{o2} = \frac{V_A + V_{DS2}}{I_o} = \frac{V_A}{I_o} = 1064 \text{ k}\Omega$$

$$R_o \approx g_{m3} R_{o3} R_{o2} = 201,56 \text{ M}\Omega$$

b) Minimum value of  $V_o$

Q3 saturates when  $V_{DS3} \geq V_{DS3} - V_t$

$$\Rightarrow V_{DS3 \min} = V_{DS3} - V_t$$

$$(V_o - V_{DS3})_{\min} = (V_o - V_{DS3})_{\min} - V_t$$

$$V_o \min = V_o \min - V_t$$

$$V_o \min = V_o = 1,2742 \text{ V}$$

$$\Rightarrow \boxed{V_o \ min = 0,7742 \text{ V}}$$

Problem 3

$$\text{a) } \frac{I_2}{I_0} = \frac{(\omega/L)_2}{(\omega/L)_0} = \frac{2,0}{5} = 4$$

$$I_2 = 4 I_0$$

$$\boxed{I_0 = \frac{1}{2} K_n' \left( \frac{\omega}{L} \right)_0 (V_{GS_3} - V_t)^2} \quad (1)$$

$$V_{GS_3} = 3 - 10 \cdot 10^{-3} \times 4 I_2$$

$$\boxed{V_{GS_3} = 3 - 4 \cdot 10^4 I_0} \quad (2)$$

$$\boxed{I_0 = \frac{1}{2} K_n' \left( \frac{\omega}{L} \right)_0 (V_{GS_1} - V_t)^2} \quad (3)$$

$$\frac{(1)}{(3)} \Rightarrow 1 = \frac{(\omega/L)_0 (V_{GS_3} - V_t)^2}{(\omega/L)_0 (V_{GS_1} - V_t)^2}$$

$$4 (V_{GS_3} - V_t)^2 = (V_{GS_1} - V_t)^2$$

$$V_{GS_2} = V_{S_3}$$

$$4 (V_{GS_3} - V_t)^2 = (V_{S_3} - V_t)^2$$

$$V_{S_3} - V_t = 2 (V_{GS_3} - V_t)$$

$$V_{S_3} - V_t = 2 V_{G_3} - 2 V_{S_3} - V_t$$

$$3 V_{S_3} = 2 V_{G_3} - V_t = 2 V_{G_3} - 0,4$$

$$\begin{aligned} I_0 &= \frac{1}{2} K_n' \left( \frac{\omega}{L} \right)_0 (V_{G_3} - \frac{2}{3} V_{G_3} + \frac{1}{3} \times 0,4 - 0,4)^2 \\ &= \frac{1}{2} \times 200 \cdot 10^{-6} \times 20 \left( \frac{V_{G_3}}{3} - \frac{2}{3} \times 0,4 \right)^2 = \frac{2}{9} \cdot 10^{-3} (V_{G_3} - 0,8)^2 \end{aligned}$$

Replacing  $V_{G_3}$ :

$$I_0 = \frac{2 \cdot 10^{-3}}{9} (3 - 4 \cdot 10^4 I_0 - 0,8)^2 = \frac{2}{9} \cdot 10^{-3} (2,2 - 4 \cdot 10^4 I_0)^2$$

$$I_0 = \frac{2 \cdot 10^{-3}}{9} (4,84 + 1,6 \cdot 10^9 I_0^2 - 1,76 \cdot 10^5 I_0)$$

$$\Rightarrow \frac{3,9}{9} \cdot 10^6 I_0^2 - \frac{361}{9} I_0 + \frac{968}{9} \cdot 10^{-3} = 0$$

$$\boxed{\begin{aligned} I_{0,1} &= 6,89 \cdot 10^{-5} \text{ A} \\ I_{0,2} &= 4,388 \cdot 10^{-5} \text{ A} \end{aligned}}$$

with  $I_o = 6,89 \cdot 10^{-5} A$ , we can calculate

$$V_{Q_3} = 3 - 4 \cdot 10^4 I_o = 0,244 V$$

$$V_{AS_1} = 0,77 V$$

inacceptable since  $V_{Q_3}$  must be greater than  $V_{AS_1}$ ,

$$I_o = 4,388 \cdot 10^{-5} A$$

$$I_o = \frac{1}{2} K_n' \left( \frac{W}{L} \right)_1 (V_{AS_1} - V_t)^2 \Rightarrow V_{AS_1} = V_{DS_1} = V_D = 0,696 V$$

balancing the drain voltages of  $Q_1$  and  $Q_2$ , we should

$$\text{make } V_{D_2} = V_D = 0,696 V$$

$$V_{DS_4} = V_{Q_4} = V_{Q_3} - V_{D_2} = (3 - 4 \cdot 10^4 I_o) - 0,696$$

$$V_{DS_4} = 1,2448 - 0,696 = 0,5488 V$$

$$V_{DS_4} = V_{AS_4} = 0,5488 V$$

$$V_{OV_4} = V_{AS_4} - V_t = 0,5488 - 0,4 = 0,1488 V$$

$$I_2 = \frac{1}{2} K_n' \left( \frac{W}{L} \right)_4 V_{DS_4}^2$$

$$\left( \frac{W}{L} \right)_4 = \frac{I_2}{\frac{1}{2} K_n' (V_{OV_4})^2} = \frac{4 \times 4,388 \cdot 10^{-5}}{0,5 \times 0,2 \cdot 10^{-3} \times 0,1488^2}$$

$$\boxed{\left( \frac{W}{L} \right)_4 = 79,272}$$

$$b) g_{m_3} = \frac{2 I_{D_3}}{(V_{CS_3} - V_t)} = 594 \cdot 10^{-6} A/V$$

$$r_{o2} = \frac{1}{\lambda \cdot I_{D_2}} = 151,86 \times 10^3 \Omega$$

$$r_{o3} = \frac{1}{\lambda \cdot I_{D_3}} = 151,86 \cdot 10^3 \Omega$$

$$\Rightarrow R_o = r_{o2} \cdot r_{o3} \cdot g_{m_3} = 13,7 \cdot 10^6 \Omega$$

$$\boxed{R_o = 13,7 \cdot 10^6 \Omega}$$

$$\begin{aligned}
 c - V_{\text{min}} &= V_{AS_3} + V_{AS_2} - V_t = 0,84 \text{ V} \\
 \Rightarrow \Delta V_o &= 3 - V_{\text{min}} = 3 - 0,844 = 2,156 \text{ V} \\
 \Rightarrow \Delta I_o &= \frac{\Delta V_o}{R_o} = \frac{2,156}{13,7 \cdot 10^6} = 0,16 \mu\text{A} \\
 \Rightarrow \% &= \frac{\Delta I_o}{I_o} \times 100\% = 0,36\%
 \end{aligned}$$

#### Problem 4

$$a - A_{2v} = \frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \left( \frac{1 + R_2/R_1}{A_{2v}} \right)} = \frac{-560/56}{1 + \left( \frac{1 + 150}{8000} \right)} = \boxed{-98,7 \text{ V/V}}$$

$$b - A_{2t} \omega = 2\pi f = 94,25 \text{ Krad/s}$$

$$\Rightarrow A = \frac{Av}{1 + \frac{i\omega}{\omega_p}} = 78,71 / 2,49 \text{ V/V}$$

$$\text{where } \omega_p = \frac{\omega_t}{1 + \frac{R_2}{R_1}} = 124,4 \text{ Krad/s}$$

$$\Rightarrow \boxed{V_o = 157,4 \cdot \sin(\omega t + 2,49)}$$

#### Problem 5

$$P = 10 \text{ W}$$

$$R_L = 8 \Omega$$

$$F = 20 \text{ kHz}$$

$$P = \frac{V_o^2}{R_L} \Rightarrow V_o^2 = R_L \cdot P = 8 \times 10 = 80$$

$$V_{\text{rms}} = \sqrt{80} \Rightarrow V_{\text{max}} = \sqrt{2} \cdot V_{\text{rms}} = \sqrt{2} \cdot \sqrt{80} = 12,64 \text{ V}$$

To avoid distortion:

$$SR = V_{\text{max}} \cdot \omega_t = 12,64 \times 20,10^3 \times 2\pi = 1588774 \text{ V/s}$$

$$\boxed{SR = 1,59 \text{ V/}\mu\text{s}}$$

Problem 6

$$v_o(t) = 2400 v_1(t) - 2391 v_2(t) \quad v_1(t) \rightarrow v_2(t) \text{ amplifier inputs}$$

$$\text{CHRR} = 20 \log \left| \frac{A_d}{A_{cm}} \right|$$

$$v_o(t) = A_d N_{id} + A_{cm} N_{icm}$$

$$\begin{cases} N_{id} = v_{i2} - v_{i1} \\ v_{icm} = V_L(v_{i1} + v_{i2}) \end{cases} \Rightarrow \begin{cases} v_{i1} = v_{icm} - \frac{v_{id}}{2} \\ v_{i2} = v_{icm} + \frac{v_{id}}{2} \end{cases}$$

$$\Rightarrow v_o(t) = 2400 v_1(t) - 2391 v_2(t)$$

$$= -4791 \left( \frac{v_{id}}{2} \right) + 9 v_{icm}$$

$$\Rightarrow A_d = \frac{-4791}{2} \quad A_{cm} = 9$$

$$\Rightarrow \text{CHRR} = 20 \log \frac{4791}{18} = 48,5 \text{ dB}$$