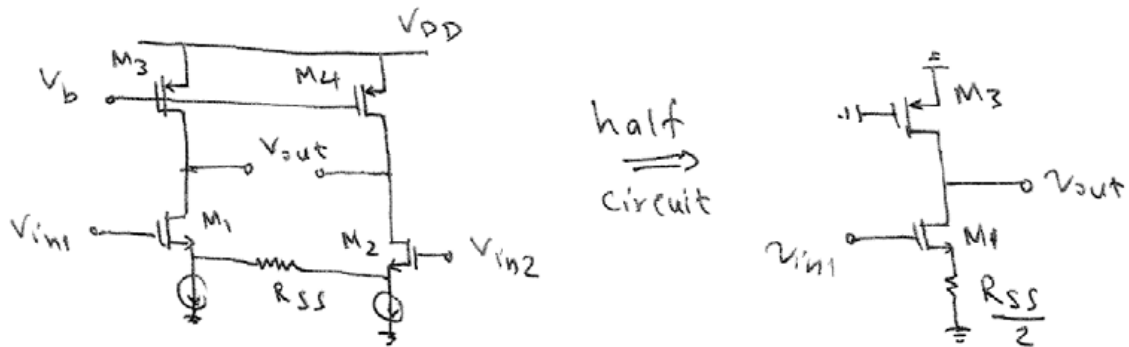


Homework 4 Solution

Problem 1



$$v_{out1}/v_{in1} = -g_{m1} r_{o1} r_{o3} / (r_{o3} + R_{out})$$

Equation 6.145 in textbook

$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) R_{SS}/2$$

Equation 6.142 in textbook

$$v_{out1}/v_{in1} = -g_{m1} r_{o1} r_{o3} / (r_{o1} + r_{o3} + (1 + g_{m1} r_{o1}) R_{SS}/2)$$


Similarly, and assuming symmetry

$$v_{out2}/v_{in2} = -g_{m1} r_{o1} r_{o3} / (r_{o1} + r_{o3} + (1 + g_{m1} r_{o1}) R_{SS}/2)$$

Therefore

$$(v_{out2} - v_{out1}) / (v_{in1} - v_{in2}) = g_{m1} r_{o1} r_{o3} / (r_{o1} + r_{o3} + (1 + g_{m1} r_{o1}) R_{SS}/2)$$

Problem 2

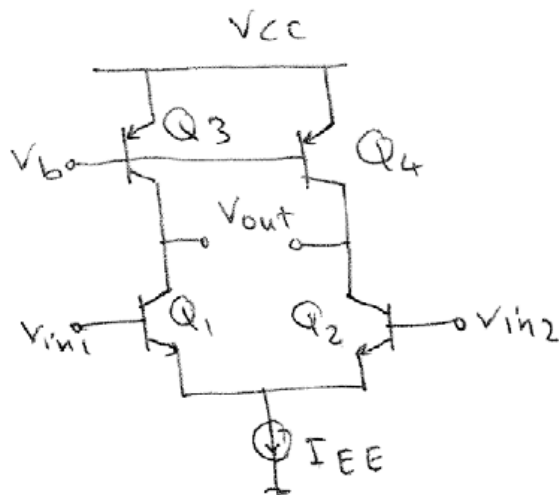

$$A_v = 100$$

$$P = 1 \text{ mW}$$

$$V_{A, \text{in}} = 6$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW} = I_{EE} V_{CC} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$r_{oN} = \frac{V_{A, \text{in}}}{I_{EE}/2} = \frac{6}{0.2 \times 10^{-3}} = 30 \text{ k}\Omega, \quad g_{mN} = \frac{I_{EE}/2}{V_T} = \frac{0.2}{26} \text{ S}$$

$$A_v = g_{mN} (r_{oN} \parallel r_{op}) \Rightarrow$$

$$100 = \frac{0.2}{26} (30 \times 10^3 \parallel r_{op}) \Rightarrow r_{op} = 22.94 \text{ k}\Omega$$

$$\Rightarrow V_{A, \text{p}} = r_{op} \frac{I_{EE}}{2} = 4.588 \text{ V}$$


Note: For $V_T = 25 \text{ mV}$, the answer is slightly different at 4.286 V .

Input bias current: $I_B = I_{EE}/2(\beta+1) = 0.995 \mu\text{A}$.

Input offset current: $I_{OS} = I_B \Delta\beta/\beta = 39.8 \text{ nA}$.

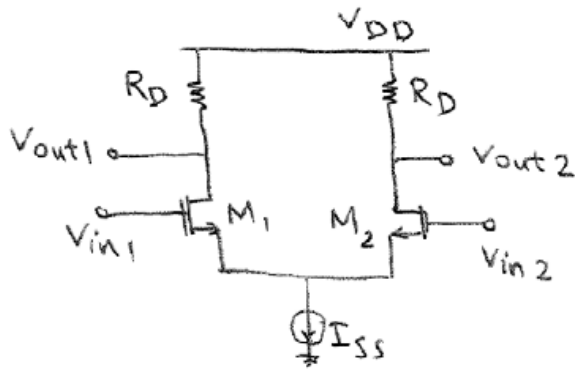Problem 3

Assuming $V_{SS} = 0$ in Figure 7.1. In the following $(V_{GS} - V_{TH})_{\text{equil}}$ is V_{OV}



$$A_v = 5$$

$$P = 1 \text{ mW}$$

$$(V_{GS} - V_{TH})_{\text{equil}} = 150 \text{ mV}$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$V_{DD} = 1.8 \text{ V}$$

$$P = 1 \text{ mW} = V_{DD} I_{SS} = 1.8 I_{SS} \Rightarrow I_{SS} = 0.556 \text{ mA}$$

$$g_{m1} = \frac{2 I_{D1}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{0.556 \times 10^{-3}}{0.15}$$

$$= 3.704 \text{ mS}$$

$$A_v = g_{m1} R_D \Rightarrow 5 = 3.704 \times 10^{-3} \times R_D \Rightarrow R_D = 1.35 \text{ k}\Omega$$


$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.15 = \sqrt{\frac{0.556 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 246.91$$

Solution for $V_{SS} = -1.8 \text{ V}$ is similar, and will be considered correct.

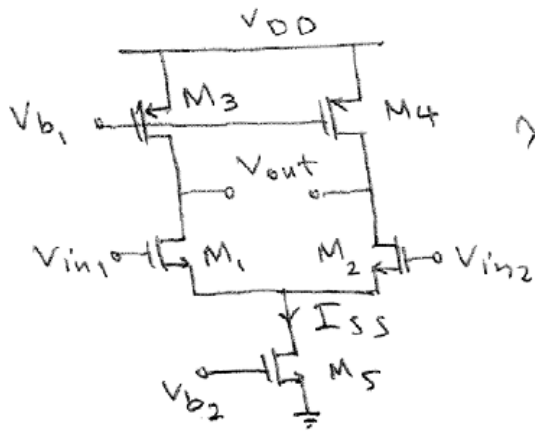Problem 4

In the following $(V_{GS} - V_{TH})_{equil}$ is the same as V_{OV}



$$\begin{aligned}
 A_V &= 40 \\
 (V_{GS} - V_{TH})_{equil} &=? \\
 \lambda_n &= 0.1 \text{ V}^{-1} \quad \lambda_p = 0.2 \text{ V}^{-1} \\
 \mu_n C_{ox} &= 100 \text{ } \mu\text{A/V}^2 \\
 \mu_p C_{ox} &= 50 \text{ } \mu\text{A/V}^2 \\
 V_{DD} &= 1.8 \\
 P &= 2 \text{ mW}
 \end{aligned}$$

$$A_V = -g_{m_N} (r_{o_p} \parallel r_{o_N}) = -\frac{I_{SS}}{(V_{GS_1} - V_{TH})_{equil}} \left(\frac{1}{\frac{I_{SS} \lambda_n}{2}} \parallel \frac{1}{\frac{I_{SS} \lambda_p}{2}} \right)$$

$$= -\frac{2}{(V_{GS_1} - V_{TH})_{equil}} \left(\frac{1}{\lambda_n} \parallel \frac{1}{\lambda_p} \right) \Rightarrow$$

$$\frac{2}{(V_{GS_1} - V_{TH})_{equil}} (10 \parallel 5) = 40 \Rightarrow (V_{GS_1} - V_{TH})_{equil} = 166.67 \text{ mV}$$

$$P = 2 \times 10^{-3} = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$\left(\frac{W}{L}\right)_{1,2} = \frac{I_{SS}}{\mu_n C_{ox} (V_{GS} - V_{TH})_{\text{equil}}^2} = \frac{1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 400$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{I_{SS}}{\mu_p C_{ox} (V_{GS} - V_{TH})_{\text{equil}}^2} = \frac{1.11 \times 10^{-3}}{0.5 \times 10^{-4} \times (0.16667)^2} = 800$$

$$\left(\frac{W}{L}\right)_5 = \frac{2 I_{SS}}{\mu_n C_{ox} (V_{GS} - V_{TH})_{\text{equil}}^2} = \frac{2 \times 1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 800$$

CMRR when output is single-ended

Common-mode gain is $g_{m1} r_{o1} r_{o3} / (r_{o1} + r_{o3} + (1 + g_{m1} r_{o1}) (2r_{o5}))$. This result is similar to Problem 1 with $R_{SS}/2$ replaced with $(2r_{o5})$.

$$r_{o3} = 9 \text{ K}\Omega$$

$$r_{o5} = 9 \text{ K}\Omega \quad (\text{current flowing in } M_5 \text{ is } I_{SS})$$

$$r_{o1} = 18 \text{ K}\Omega$$


$$g_{m1} = 6.667 \text{ mA/V}$$

$$A_{\text{cm}} = 0.49 \text{ V/V}$$

$$A_{\text{d[single-ended]}} = 40/2 = 20 \text{ V/V}$$

$$\text{CMRR} = 20 \log_{10}(20/0.49) = 32.2 \text{ dB}$$

Problem 5

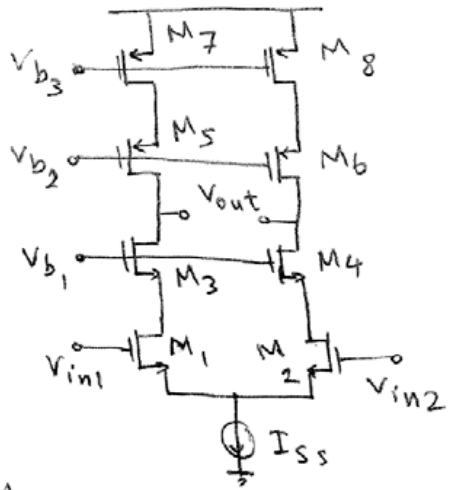

$$A_v = 600$$

$$P = 4 \text{ mW}$$

$$(V_{GS} - V_{TH})_{NMOS} = 100 \text{ mV}$$

$$(V_{GS} - V_{TH})_{PMOS} = 150 \text{ mV}$$

$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$

$$\mu_p C_{ox} = 50 \text{ } \mu\text{A/V}^2$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$A_v \approx g_{m1} [(g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7})] = 600$$

$$P = 4 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{4 \times 10^{-3}}{1.8} = 2.22 \text{ mA}$$

$$g_{m_{1-4}} = \frac{2I_{D1}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{2.22 \times 10^{-3}}{0.1} = 22.22 \text{ mS}$$

$$g_{m_{5-8}} = \frac{2I_{D5}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{2.22 \times 10^{-3}}{0.15} = 14.815 \text{ mS}$$

$$r_{o1-4} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \times \frac{2.22}{2} \times 10^{-3}} = 9 \text{ k}\Omega$$

$$r_{o5-8} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = \frac{1}{\lambda_p \times \frac{2.22}{2} \times 10^{-3}} = \frac{0.9 \times 10^3}{\lambda_p}$$

in Av
=> equation

$$22.22 \times 10^{-3} \left[(22.22 \times 10^{-3} \times 81 \times 10^6) \parallel (14.815 \times 10^{-3} \times \frac{0.81 \times 10^6}{\lambda_p^2}) \right] = 600 \Rightarrow$$

$$\lambda_p = 0.66 \text{ V}^{-1}$$

$$\left(\frac{W}{L}\right)_{NMOS} = I_{SS} / (\mu_n C_{ox} (V_{GS} - V_{TH})_{NMOS}^2) = 2222.2$$

$$\left(\frac{W}{L}\right)_{PMOS} = I_{SS} / (\mu_p C_{ox} (V_{GS} - V_{TH})_{PMOS}^2) = 1975.31$$

$$V_{Ap} = 1/\lambda_p = 1.5 \text{ V.}$$