

American University of Beirut
Faculty of Engineering and Architecture
Department of Electrical and Computer Engineering
EE 042 - Analog Electronics
Instructors: A. Kayssi and M. Krisht
Quiz 1
Saturday November 23, 1996

Closed Book
Programmable Calculators Are Not Allowed.

Time: 1.5 hours

VERSION A

The figures for this quiz are missing

Name: _____ ID#: _____

- Provide your answer on the *computer card only*.
- Return the computer card attached to the question sheet.
- Use a pencil for marking your answers and ID number on the computer card.
- When using an eraser, make sure you erased well.
- On this sheet, write with a pen your name followed by your ID number.
- All questions are graded equally.

1. What is the version of your question sheet? (This question is not graded.)
 - a) Version A
 - b) Version B
 - c) Version C
 - d) Version D
 - e) Version E

Unless otherwise specified, assume $V_T = 25\text{ mV}$, β is very large, and $|V_{BE}| = 0.7\text{ V}$

2. Determine R_C and R_E in the circuit of **Figure 8** to have $V_O = 0\text{ V}$ and $V_{CE} = 3\text{ V}$. Assume $\beta = 200$ (do not neglect I_B).
 - a) $R_C = 0.82\text{ k}\Omega$, $R_E = 1.65\text{ k}\Omega$
 - b) $R_C = 1.65\text{ k}\Omega$, $R_E = 0.82\text{ k}\Omega$
 - c) $R_C = 1.82\text{ k}\Omega$, $R_E = 0.65\text{ k}\Omega$
 - d) $R_C = 0.65\text{ k}\Omega$, $R_E = 1.82\text{ k}\Omega$
 - e) none of the above

3. Find the value of R required to satisfy the current relationships in the circuit of **Figure 7**.
 - a) $100\text{ k}\Omega$
 - b) $50\text{ k}\Omega$
 - c) $200\text{ k}\Omega$
 - d) $105\text{ k}\Omega$
 - e) none of the above

4. For the circuit shown in **Figure 13**, find the voltage gain V_O/V_i . Assume $\beta = 40$, and $r_\pi = 1\text{ k}\Omega$.
 - a) -33.7
 - b) -28.3
 - c) -14.6
 - d) -3.51
 - e) none of the above

5. Find the current gain I_O/I_i directly, as defined in the circuit of **Figure 12**. The JFET parameters are $I_{DSS} = 4\text{ mA}$ and $V_p = -2\text{ V}$ and is biased at $I_D = 1\text{ mA}$.
 - a) -340
 - b) -680
 - c) -170
 - d) -425
 - e) none of the above

6. A MOSFET source follower is biased at $I_D = 0.5\text{ mA}$. What is the value of V_{GS} if the small signal output resistance is 500Ω and $V_t = 1\text{ V}$.
 - a) 2.2 V
 - b) 2 V
 - c) 1.5 V
 - d) 1.2 V
 - e) none of the above

7. Find the differential gain $v_O/(v_1 - v_2)$ in the circuit of **Figure 4**.
 - a) -100
 - b) -200
 - c) 200
 - d) 100
 - e) none of the above

8. Find the common-mode rejection ratio (CMRR) for the circuit of **Figure 4**. Assume $V_A = 100V$.
- a) 73 dB
 - b) 82 dB
 - c) 66 dB
 - d) 78 dB
 - e) none of the above
9. Find the value of the emitter resistors, to be inserted between the emitters of Q_1 and Q_2 and node X in the circuit of **Figure 4**, to have a differential input resistance of $200K\Omega$. Assume $\beta = 99$.
- a) $1.5 k\Omega$
 - b) $5 k\Omega$
 - c) 150Ω
 - d) 35Ω
 - e) none of the above
10. Find the value of R in the circuit of **Figure 3** in order to have $V_O = 2V$.
- a) $7.17 k\Omega$
 - b) $9.5 k\Omega$
 - c) $14.3 k\Omega$
 - d) $19 k\Omega$
 - e) none of the above
11. All the BJTs in the circuit of **Figure 9** are biased at $I_C = 1mA$ and have $\beta = 100$. Find V_O/V_3 and V_3/V_2 . (*Hint*: Include the loading effect of the last stage on the second stage).
- a) $V_O/V_3 = -60, V_3/V_2 = 0.985$
 - b) $V_O/V_3 = -80, V_3/V_2 = 0.994$
 - c) $V_O/V_3 = -60, V_3/V_2 = 0.994$
 - d) $V_O/V_3 = -80, V_3/V_2 = 0.985$
 - e) none of the above
12. Find V_O/V_S in the circuit of **Figure 9**.
- a) 540.5
 - b) 187.4
 - c) 932.6
 - d) 349.1
 - e) none of the above
13. Find the range of values of I_O in the circuit of **Figure 2**, when β varies between 75 and 175.
- a) 0.918 to 0.925 mA
 - b) 0.459 to 0.462 mA
 - c) 0.468 to 0.471 mA
 - d) 0.926 to 0.931 mA
 - e) none of the above